

Signal Conditioning Piezoelectric Sensors

James Karki

Mixed Signal Products

ABSTRACT

Piezoelectric elements are used to construct transducers for a vast number of different applications. Piezoelectric materials generate an electrical charge in response to mechanical movement, or vice versa, produce mechanical movement in response to electrical input.

This report discusses the basic concepts of piezoelectric transducers used as sensors and two circuits commonly used for signal conditioning their output.

Contents

1	Introduction	1
2	Theory and Modeling	2
3	Signal Conditioning	2
3.1	Voltage Mode Amplifier	3
3.2	Charge Mode Amplifier	4
3.3	Signal Conditioning Made Easier	4
Appendix A		5

List of Figures

1	Sensor Models	2
2	Voltage Mode Amplifier Circuit	3
3	Charge Mode Amplifier Circuit	4

1 Introduction

The word piezo comes from the Greek word piezein, meaning to press or squeeze.

Piezoelectricity refers to the generation of electricity or of electric polarity in dielectric crystals when subjected to mechanical stress and conversely, the generation of stress in such crystals in response to an applied voltage. In 1880, the Curie brothers found that quartz changed its dimensions when subjected to an electrical field and generated electrical charge when pressure was applied. Since that time, researchers have found piezoelectric properties in hundreds of ceramic and plastic materials.

Many piezoelectric materials also show electrical effects due to temperature changes and radiation. This report is limited to piezoelectricity. More detailed information on particular sensors can be found by contacting the manufacturer.

2 Theory and Modeling

The basic theory behind piezoelectricity is based on the electrical dipole. At the molecular level, the structure of a piezoelectric material is typically an ionic bonded crystal. At rest, the dipoles formed by the positive and negative ions cancel each other due to the symmetry of the crystal structure, and an electric field is not observed. When stressed, the crystal deforms, symmetry is lost, and a net dipole moment is created. This dipole moment forms an electric field across the crystal.

In this manner, the materials generate an electrical charge that is proportional to the pressure applied. If a reciprocating force is applied, an ac voltage is seen across the terminals of the device. Piezoelectric sensors are not suited for static or dc applications because the electrical charge produced decays with time due to the internal impedance of the sensor and the input impedance of the signal conditioning circuits. However, they are well suited for dynamic or ac applications.

A piezoelectric sensor is modeled as a charge source with a shunt capacitor and resistor, or as a voltage source with a series capacitor and resistor. These models are shown in Figure 1 along with a typical schematic symbol. The charge produced depends on the piezoelectric constant of the device. The capacitance is determined by the area, the width, and the dielectric constant of the material. As previously mentioned, the resistance accounts for the dissipation of static charge.

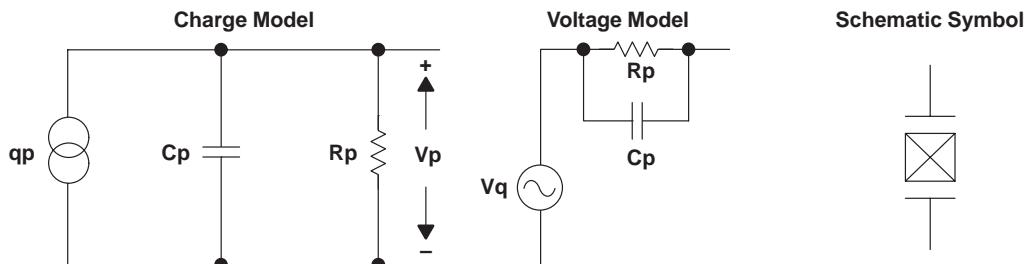


Figure 1. Sensor Models

3 Signal Conditioning

Normal output voltages from piezoelectric sensors can vary from microvolts to hundreds of volts, and signal conditioning circuitry requirements vary substantially. Key items to consider when designing the amplifier are:

- Frequency of operation
- Signal amplitude
- Input impedance
- Mode of operation

The following discussion assumes that the sensor output needs a moderate amount of amplification, and that the desired signal levels are in the 3-V to 5-V range for full scale.

Typically, the high impedance of the sensor requires an amplifier with high-input impedance. JFET or CMOS input op amps, like the TLV2771, are natural choices.

Two circuits are used for signal conditioning. Figure 2 shows a voltage mode amplifier circuit, and Figure 3 shows a charge mode amplifier circuit. Voltage mode amplification is used when the amplifier is very close to the sensor. Charge mode amplification is used when the amplifier is remote to the sensor.

3.1 Voltage Mode Amplifier

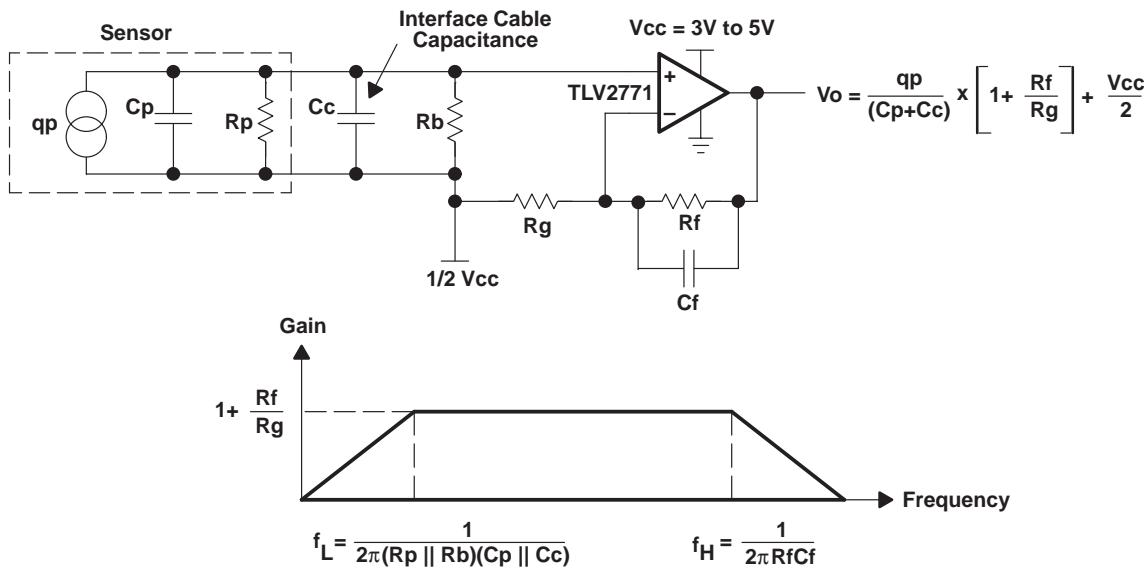


Figure 2. Voltage Mode Amplifier Circuit

In a voltage mode amplifier, the output depends on the amount of capacitance seen by the sensor. The capacitance associated with the interface cable will affect the output voltage. If the cable is moved or replaced, variations in C_c can cause problems.

Resistor R_b provides a dc bias path for the amplifier input stage.

Choice of R_f and C_f sets the upper cutoff frequency.

The lower cutoff frequency is calculated by: $f_L = \frac{1}{2\pi(R_p \parallel R_b)(C_p \parallel C_c)}$.

Resistor R_b should be chosen as high as possible and interface cabling reduced to a minimum. For the TLV2771 op amp, $R_b = 10 \text{ M}\Omega$ will result in a typical offset of $60 \mu\text{V}$ over the commercial temperature range.

The biasing shown will put the output voltage at $1/2 V_{cc}$ with no input. The output will swing above and below this dc level.

3.2 Charge Mode Amplifier

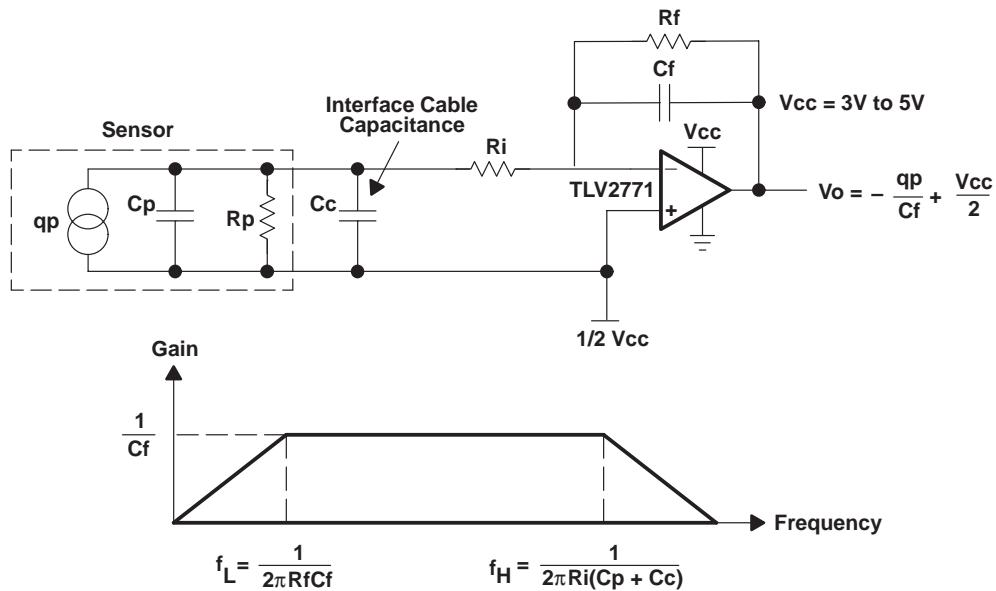


Figure 3. Charge Mode Amplifier Circuit

The charge mode amplifier will balance the charge injected into the negative input by charging feedback capacitor C_f . Resistor R_f bleeds the charge off capacitor C_f at a low rate to prevent the amplifier from drifting into saturation. Resistor R_f also provides a dc bias path for the negative input. The value of R_f and C_f set the low cutoff frequency of the amplifier.

The action of the amplifier maintains 0 V across its input terminals so that the stray capacitance associated with interface cabling does not present a problem. Resistor R_i provides ESD protection. Resistor R_i and capacitors C_p and C_{cc} combine to produce roll off at higher frequency.

The biasing shown will put the output voltage at $1/2 V_{cc}$ with no input. The output will swing around this dc level.

3.3 Signal Conditioning Made Easier

Some manufacturers have made signal conditioning of their piezoelectric sensors easier by integrating FET buffers into the sensor. Still, proper biasing is important and additional amplification may be desired. Refer to Application Note 3V Accelerometer Featuring TLV2772, literature number SLVA040 (http://www.ti.com/sc/docs/apps/analog/operational_amplifiers.html) for an example.

Appendix A Circuit Computation With q

Computation of node voltages can always be performed based on current or voltage sources and circuit impedance. Calculating circuit voltages based on a charge source may seem difficult at first, but it is actually simple.

Computing node voltage in a circuit with a charge source and a capacitor is a simple matter when using the definition of capacitance, $C = \frac{q}{v}$ (or $v = \frac{q}{C}$). But what if you have resistors or inductors?

Operational calculus in the form of the Laplace operator, s, is the cornerstone of circuit analysis. Using the impedance form of Ohm's Law, $V = I \times Z$, the technique replaces circuit elements with their s-domain impedance: $C \rightarrow \frac{1}{sC}$, $L \rightarrow sL$, and R remains R. These are based on the

relationships: $v = \frac{1}{C} \int i \, dt$, $v = L \frac{di}{dt}$, and $v = iR$. In short form: if the relationship is an integral, divide by s, if it is a differential, multiply by s, and if it is neither, do not do anything.

Since current is the time differential of charge, $i = \frac{dq}{dt}$ (or $\int i \, dt = q$), substituting for i in the

standard relationships: $v = \frac{q}{C}$, $v = L \frac{d^2q}{dt^2}$ and $v = R \frac{dq}{dt}$. The new s-domain replacements become: $C \rightarrow \frac{1}{sC}$, $L \rightarrow s^2L$, and $R \rightarrow sR$. In short form, multiply everything by s.

If this is too complicated, perform the circuit analysis as if the charge sources were current sources, multiply the answer by s, and change the i to q. The result is the same. For example, using the charge model for the piezoelectric sensor shown in Figure 1:

Substituting sR_P for R_P and $\frac{1}{sC_P}$ for C_P , the sensor output voltage is $v_p = q \left(\frac{sR_P}{1 + sR_P C_P} \right)$.

Or, assuming the charge source is a current source we find $v_p = i \left(\frac{R_P}{1 + sR_P C_P} \right)$. Then multiplying by s and substituting q for i, gives the same result.

IMPORTANT NOTICE

Texas Instruments and its subsidiaries (TI) reserve the right to make changes to their products or to discontinue any product or service without notice, and advise customers to obtain the latest version of relevant information to verify, before placing orders, that information being relied on is current and complete. All products are sold subject to the terms and conditions of sale supplied at the time of order acknowledgment, including those pertaining to warranty, patent infringement, and limitation of liability.

TI warrants performance of its semiconductor products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are utilized to the extent TI deems necessary to support this warranty. Specific testing of all parameters of each device is not necessarily performed, except those mandated by government requirements.

Customers are responsible for their applications using TI components.

In order to minimize risks associated with the customer's applications, adequate design and operating safeguards must be provided by the customer to minimize inherent or procedural hazards.

TI assumes no liability for applications assistance or customer product design. TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right of TI covering or relating to any combination, machine, or process in which such semiconductor products or services might be or are used. TI's publication of information regarding any third party's products or services does not constitute TI's approval, warranty or endorsement thereof.

Copyright © 2000, Texas Instruments Incorporated

SUNSTAR商斯达实业集团是集研发、生产、工程、销售、代理经销、技术咨询、信息服务等为一体的高科技企业，是专业高科技电子产品生产厂家，是具有 10 多年历史的专业电子元器件供应商，是中国最早和最大的仓储式连锁规模经营大型综合电子零部件代理分销商之一，是一家专业代理和分銷世界各大品牌IC芯片和電子元器件的连锁经营綜合性国际公司。在香港、北京、深圳、上海、西安、成都等全国主要电子市场设有直属分公司和产品展示展销窗口门市部专卖店及代理分销商，已在全国范围内建成强大统一的供货和代理分销网络。我们专业代理经销、开发生产电子元器件、集成电路、传感器、微波光电元器件、工控机/DOC/DOM电子盘、专用电路、单片机开发、MCU/DSP/ARM/FPGA软件硬件、二极管、三极管、模块等，是您可靠的一站式现货配套供应商、方案提供商、部件功能模块开发配套商。**专业以现代信息产业（计算机、通讯及传感器）三大支柱之一的传感器为主营业务，专业经营各类传感器的代理、销售生产、网络信息、科技图书资料及配套产品设计、工程开发。我们的专业网站——中国传感器科技信息网（全球传感器数据库）www.SENSOR-IC.COM 服务于全球高科技生产商及贸易商，为企业科技产品开发提供技术交流平台。欢迎各厂商互通有无、交换信息、交换链接、发布寻求代理信息。欢迎国外高科技传感器、变送器、执行器、自动控制产品厂商介绍产品到 中国，共同开拓市场。**本网站是关于各种传感器-变送器-仪器仪表及工业自动化大型专业网站，深入到工业控制、系统工程计 测计量、自动化、安防报警、消费电子等众多领域，把最新的传感器-变送器-仪器仪表买卖信息，最新技术供求，最新采购商，行业动态，发展方向，最新的技术应用和市场资讯及时的传递给广大科技开发、科学的研究、产品设计人员。本网站已成功为石油、化工、电力、医药、生物、航空、航天、国防、能源、冶金、电子、工业、农业、交通、汽车、矿山、煤炭、纺织、信息、通信、IT、安防、环保、印刷、科研、气象、仪器仪表等领域从事科学的研究、产品设计、开发、生产制造的科技人员、管理人员 和采购人员提供满意服务。**我公司专业开发生产、代理、经销、销售各种传感器、变送器 敏感元器件、开关、执行器、仪器仪表、自动化控制系统：**专门从事设计、生产、销售各种传感器、变送器、各种测控仪表、热工仪表、现场控制器、计算机控制系统、数据采集系统、各类环境监控系统、专用控制系统应用软件以及嵌入式系统开发及应用等工作。如热敏电阻、压敏电阻、温度传感器、温度变送器、湿度传感器、湿度变送器、气体传感器、气体变送器、压力传感器、压力变送、称重传感器、物（液）位传感器、物（液）位变送器、流量传感器、流量变送器、电流（压）传感器、溶氧传感器、霍尔传感器、图像传感器、超声波传感器、位移传感器、速度传感器、加速度传感器、扭距传感器、红外传感器、紫外传感器、火焰传感器、激光传感器、振动传感器、轴角传感器、光电传感器、接近传感器、干簧管传感器、继电器传感器、微型电泵、磁敏（阻）传感器、压力开关、接近开关、光电开关、色标传感器、光纤传感器、齿轮测速传感器、时间继电器、计数器、计米器、温控仪、固态继电器、调压模块、电磁铁、电压表、电流表等特殊传感器。同时承接传感器应用电路、产品设计和自动化工程项目。

更多产品请看本公司产品专用销售网站：

商斯达中国传感器科技信息网：<http://www.sensor-ic.com/>

商斯达工控安防网：<http://www.pc-ps.net/>

商斯达电子 元器件网：<http://www.sunstare.com/>

商斯达微波光电产品网:<HTTP://www.rfoe.net/>

商斯达消费电子产品网:<http://www.icasic.com/>

商斯达军工产品网:<http://www.junpinic.com/>

商斯达实业科技产品网:<http://www.sunstars.cn/>传感器销售热线：

地址：深圳市福田区福华路福庆街鸿图大厦 1602 室

电话：0755-83607652 83376489 83376549 83370250 83370251 82500323

传真：0755-83376182 (0) 13902971329 MSN: SUNS8888@hotmail.com

邮编：518033 E-mail:szss20@163.com QQ: 195847376

深圳赛格展销部：深圳华强北路赛格电子市场 2583 号 电话：0755-83665529 25059422

技术支持：0755-83394033 13501568376

欢迎索取免费详细资料、设计指南和光盘；产品凡多，未能尽录，欢迎来电查询。

北京分公司：北京海淀区知春路 132 号中发电子大厦 3097 号

TEL: 010-81159046 82615020 13501189838 FAX: 010-62543996

上海分公司：上海市北京东路 668 号上海赛格电子市场 D125 号

TEL: 021-28311762 56703037 13701955389 FAX: 021-56703037

西安分公司：西安高新区 20 所(中国电子科技集团导航技术研究所)

西安劳动南路 88 号电子商城二楼 D23 号

TEL: 029-81022619 13072977981 FAX:029-88789382