

## RELEVANT PRODUCTS

- AWT6146

## INTRODUCTION


This power amplifier module is designed to support dual, tri and quad band applications. The module includes an integrated power control scheme that facilitates fast and easy production calibration and reduces the number of external components required to complete a power control function. This integrated control loop reduces the development time associated with optimizing loop filters to meet time mask and switching transient requirements, as it is completely self-contained.

The module size is a competitive 7mm x 7mm and with the few external components required, it is well suited for a small form factor transmit front-end solution.
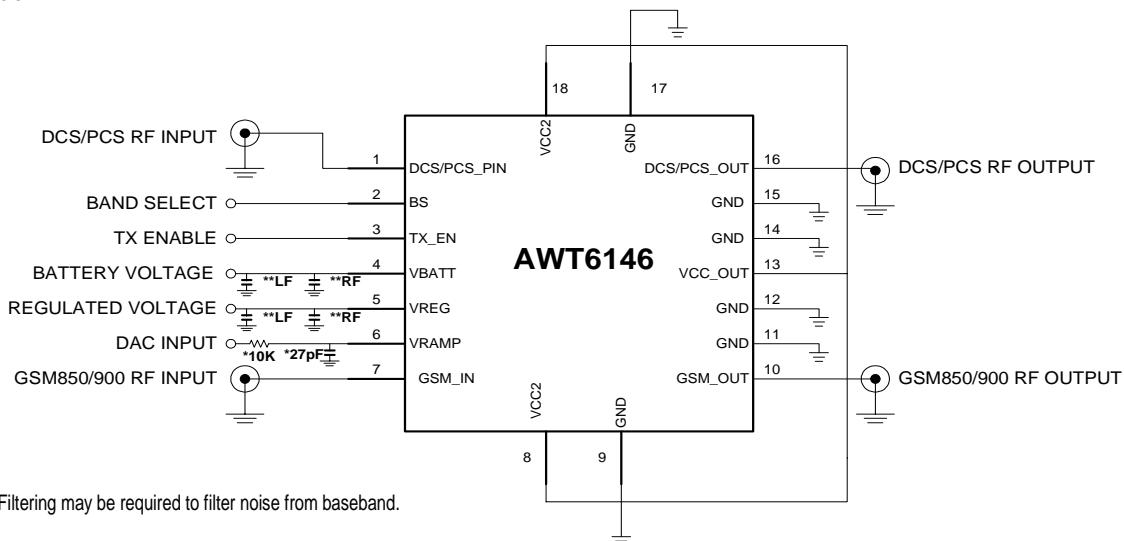
## GENERAL DESCRIPTION

The application circuit below shows the relative ease with which this amplifier can be designed into a GSM transmit front-end. All of the RF ports for this device are internally matched to  $50\Omega$ , with internal DC blocks provided at the RF ports.

The RF inputs can interface to transmit VCO's with the addition of simple attenuators. These can be used to set the input drive to the PA and is generally good practice to help minimise any possible load pulling effects at the VCO, PA interface. The RF outputs can interface directly to an antenna switch module to complete the front-end solution.



\* Filtering may be required to filter noise from baseband.

\*\*Provision for both RF and Low Frequency (LF) decoupling of supplies is recommended and consistent with good design practice. The values chosen depend on SRF of capacitors used, ground via inductance, capacitor location, and thus have layout dependency.

**Figure 1: Application Schematic**

SUNSTAR 商斯达实业集团是集研发、生产、工程、销售、代理经销、技术咨询、信息服务等为一体的高科技企业，是专业高科技电子产品生产厂家，是具有 10 多年历史的专业电子元器件供应商，是中国最早和最大的仓储式连锁规模经营大型综合电子零部件代理分销商之一，是一家专业代理和分销世界各大品牌 IC 芯片和电子元器件的连锁经营综合性国际公司，专业经营进口、国产名厂名牌电子元件，型号、种类齐全。在香港、北京、深圳、上海、西安、成都等全国主要电子市场设有直属分公司和产品展示展销窗口门市部专卖店及代理分销商，已在全国范围内建成强大统一的供货和代理分销网络。我们专业代理经销、开发生产电子元器件、集成电路、传感器、微波光电元器件、工控机/DOC/DOM 电子盘、专用电路、单片机开发、MCU/DSP/ARM/FPGA 软件硬件、二极管、三极管、模块等，是您可靠的一站式现货配套供应商、方案提供商、部件功能模块开发配套商。商斯达实业公司拥有庞大的资料库，有数位毕业于著名高校——有中国电子工业摇篮之称的西安电子科技大学（西军电）并长期从事国防尖端科技研究的高级工程师为您精挑细选、量身订做各种高科技电子元器件，并解决各种技术问题。

微波光电部专业代理经销高频、微波、光纤、光电元器件、组件、部件、模块、整机；电磁兼容元器件、材料、设备；微波 CAD、EDA 软件、开发测试仿真工具；微波、光纤仪器仪表。欢迎国外高科技微波、光纤厂商将优秀产品介绍到中国、共同开拓市场。长期大量现货专业批发高频、微波、卫星、光纤、电视、CATV 器件：晶振、VCO、连接器、PIN 开关、变容二极管、开关二极管、低噪晶体管、功率电阻及电容、放大器、功率管、MMIC、混频器、耦合器、功分器、振荡器、合成器、衰减器、滤波器、隔离器、环行器、移相器、调制解调器；光电子元器件和组件：红外发射管、红外接收管、光电开关、光敏管、发光二极管和发光二极管组件、半导体激光二极管和激光器组件、光电探测器和光接收组件、光发射接收模块、光纤激光器和光放大器、光调制器、光开关、DWDM 用光发射和接收器件、用户接入系统光光收发器件与模块、光纤连接器、光纤跳线/尾纤、光衰减器、光纤适配器、光隔离器、光耦合器、光环行器、光复用器/转换器；无线收发芯片和模组、蓝牙芯片和模组。

更多产品请看本公司产品专用销售网站：

商斯达中国传感器科技信息网：<http://www.sensor-ic.com/>

商斯达工控安防网：<http://www.pc-ps.net/>

商斯达电子元器件网：<http://www.sunstare.com/>

商斯达微波光电产品网：<HTTP://www.rfoe.net/>

商斯达消费电子产品网：<http://www.icasic.com/>

商斯达实业科技产品网：<http://www.sunstars.cn/> 微波元器件销售热线：

地址：深圳市福田区福华路福庆街鸿图大厦 1602 室

电话：0755-82884100 83397033 83396822 83398585

传真：0755-83376182 (0) 13823648918 MSN：[SUNS8888@hotmail.com](mailto:SUNS8888@hotmail.com)

邮编：518033 E-mail：[szss20@163.com](mailto:szss20@163.com) QQ：195847376

深圳赛格展销部：深圳华强北路赛格电子市场 2583 号 电话：0755-83665529 25059422

技术支持：0755-83394033 13501568376

欢迎索取免费详细资料、设计指南和光盘；产品凡多，未能尽录，欢迎来电查询。

北京分公司：北京海淀区知春路 132 号中发电子大厦 3097 号

TEL：010-81159046 82615020 13501189838 FAX：010-62543996

上海分公司：上海市北京东路 668 号上海赛格电子市场 D125 号

TEL：021-28311762 56703037 13701955389 FAX：021-56703037

西安分公司：西安高新区 20 所(中国电子科技集团导航技术研究所)

西安劳动南路 88 号电子商城二楼 D23 号

TEL：029-81022619 13072977981 FAX:029-88789382

## DESCRIPTION (Continued)

The logical control inputs, TX\_EN and BS, are both 1.8 V and 3 V logic compliant. The TX\_EN is used to enable the amplifier typically with the TX burst. The BS is used to select which amplifier is enabled.

## POWER CONTROL

The scheme used is a closed loop method that requires only the application of an analog voltage to the VRAMP pin to set the output power. This can be applied directly from a standard DAC output. The method used does not require any power or current sensing.

Setting the VRAMP voltage, in turn sets the collector voltages of the power amplifiers to a multiple of the VRAMP voltage using a pre-determined formula. This collector voltage is regulated in a voltage control loop as shown in Figure 2 below. The amplifier's bias is held constant while the collector voltage is adjusted to set the power. The relationship between the output power and collector voltage is represented by EQ 1.

$$P_{\text{OUT}} (\text{watts}) = \frac{(2V_{\text{CC}} - V_{\text{SAT}})^2}{(8 \cdot R_{\text{LOAD}})} \quad (\text{EQ 1})$$

where  $V_{\text{CC}}$ ,  $V_{\text{SAT}}$  are the collector voltage and saturation voltage of the transistor respectively. This expression shows how the power variation due to VBATT is limited due to voltage control loop.

Under extreme conditions, as the battery voltage degrades, it is important to maintain the control loop bandwidth, so the collector voltage quickly follows VRAMP. This is done by adjusting VRAMP, such that:

$$\text{VRAMP} \leq 0.39 * \text{VBATT} - 0.17 \leq 1.5\text{V} \quad (\text{EQ2})$$

The effect of the loop bandwidth slowing can be seen most clearly in the switching transients measurement.

This adjustment can be incorporated in the software of the final application, so that performance is enhanced under low voltage conditions.

Another advantage of this control scheme is the improved noise performance due to individual stages being held in compression, thus improving the overall receive band noise performance.

## HIGH FREQUENCY DECOUPLING

It is generally good practice to provide for high frequency bypassing on the supply lines of an RF module like the VBATT and VREG. Effective high frequency bypassing requires the component be placed as close as possible to the devices and provide as direct a path ground as possible with preferably a via connection to the board ground.

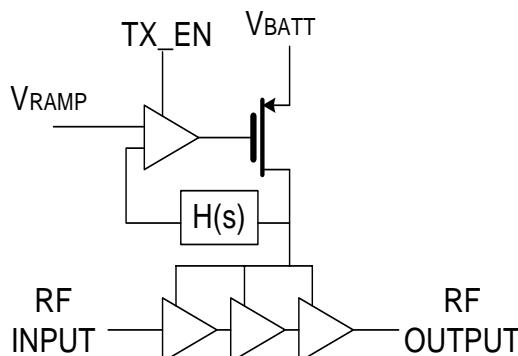


Figure 2: Voltage Control Loop

## TIMING

In order to meet the GSM power time template and switching transients, the sequence of events outlined in figure 5 is recommended. The timing between VREG and BS is not critical, they just need to be enabled and settled prior to TX\_EN going high (approx 2us).

The timing of the TX\_EN is critical to ensure the application has sufficient margin for meeting the burst timing requirement.

The PA "forward isolation 1" parameter and the T/R switch isolation ensure the template is met outside the burst. The PA "forward isolation 2" parameter ensures the time template is met during the burst with sufficient margin.

The ramp profile should be as close as possible to a raised cosine waveform to achieve the spectral efficiency needed for meeting switching transient requirements.

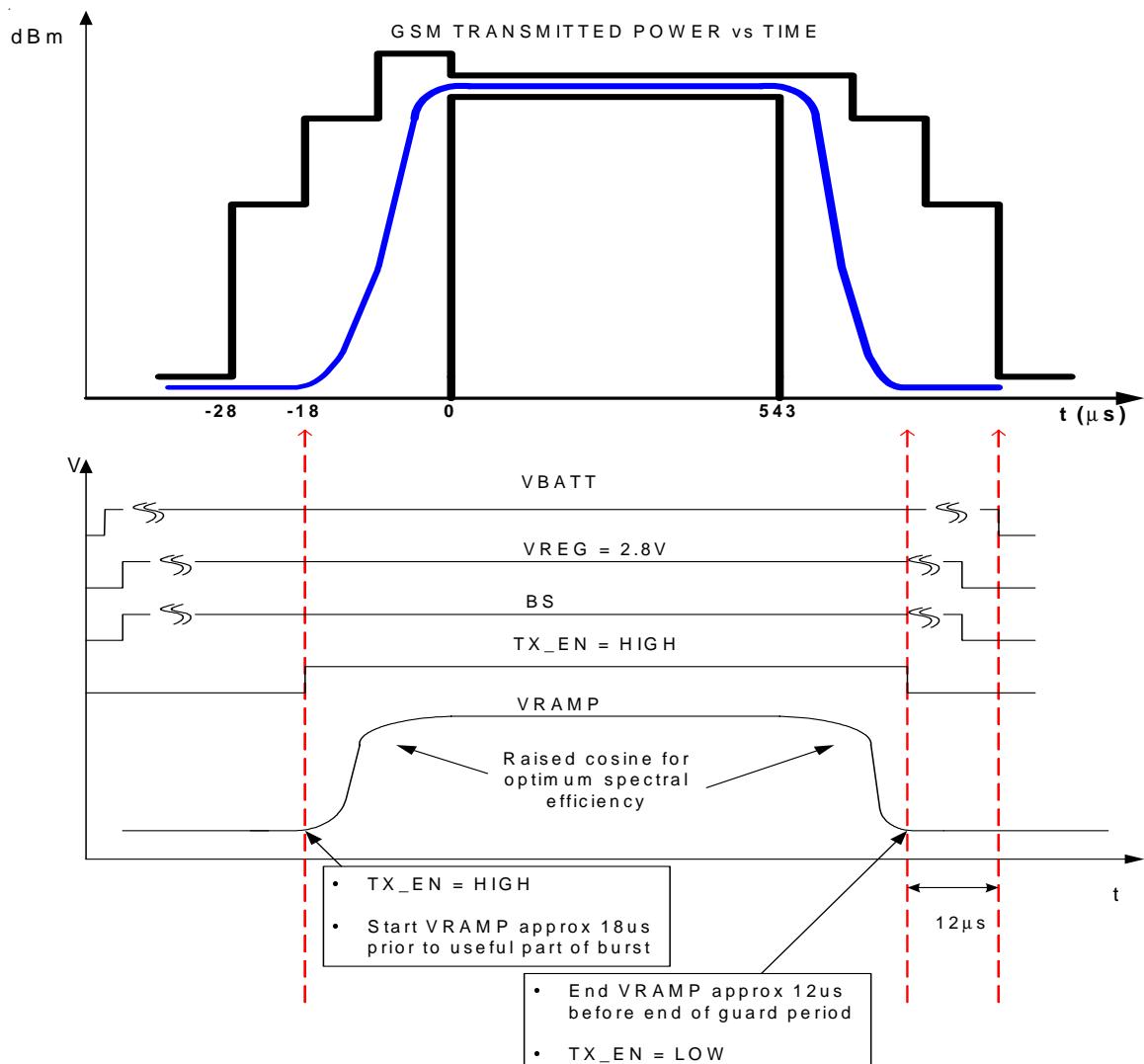


Figure 5: Timing recommendations

## EVALUATION BOARD

The evaluation board is a multilayer board using GETEK substrate which is similar to FR4 but has a more controlled dielectric constant. The board thickness is 1.57mm.

All the routing is on the top layer (1) of a 4 layer board with a distance of 0.36mm to the ground plane, which is on layer 2. All RF routing has been sized to present a  $50\Omega$  impedance.

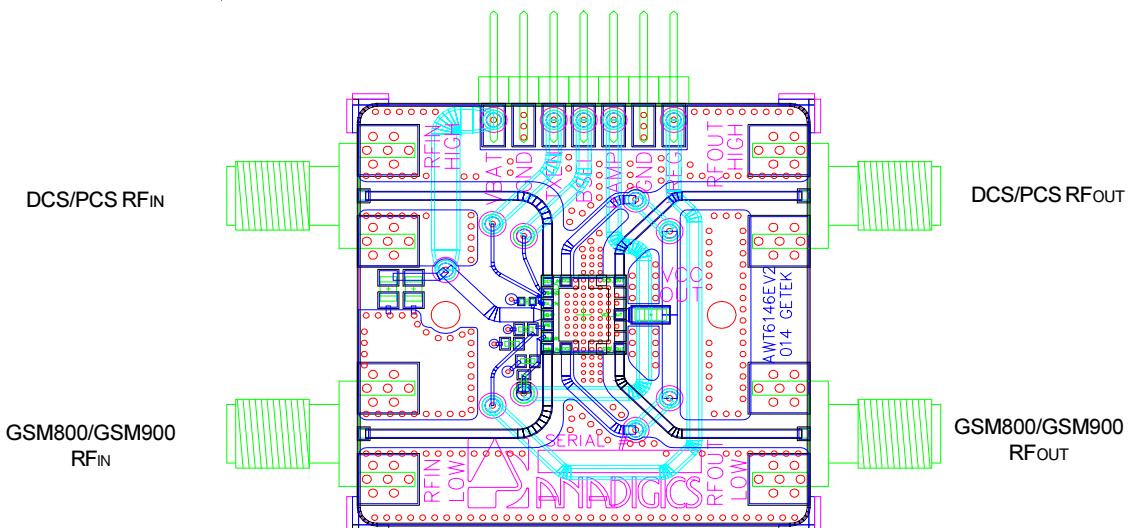


Figure 6: AWT6146 Evaluation Board



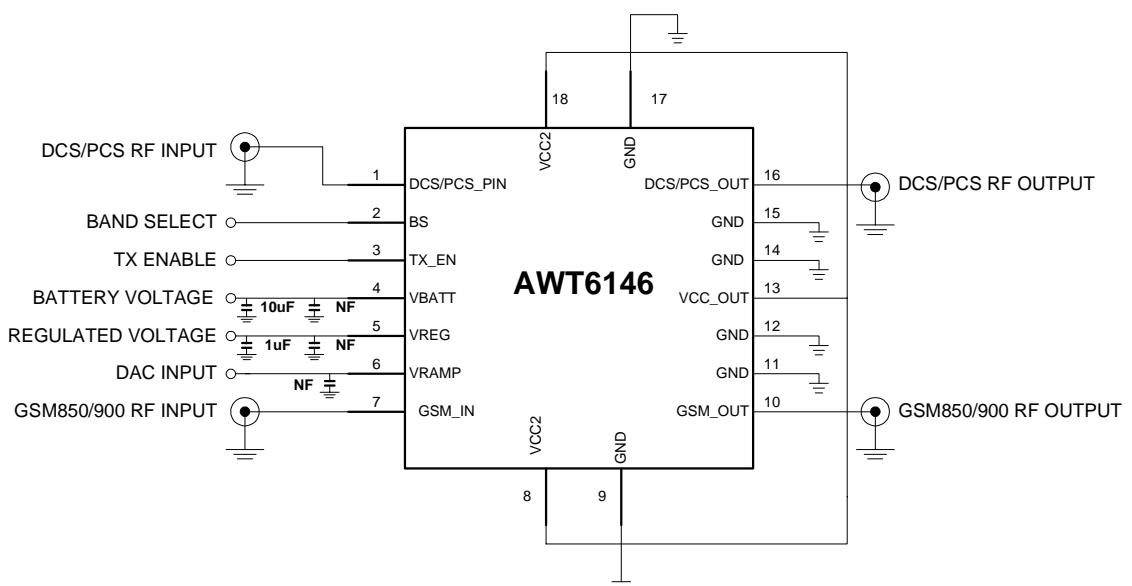



Figure 7: AWT6146 Evaluation Board Schematic

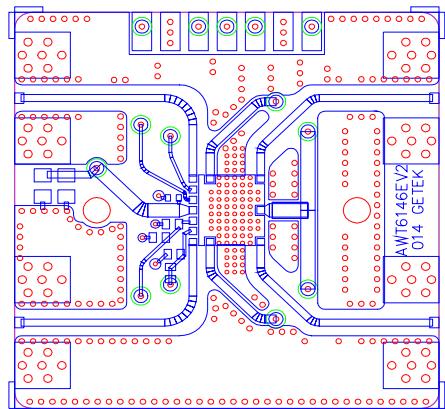


**Layer 1**

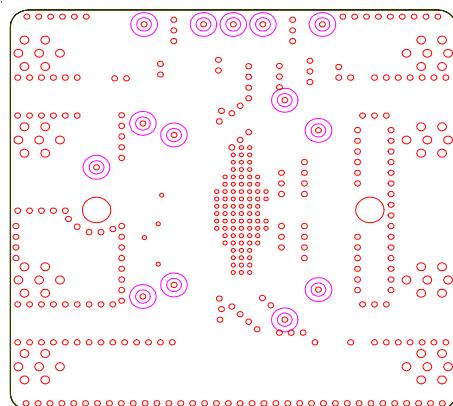


**Layer 2**

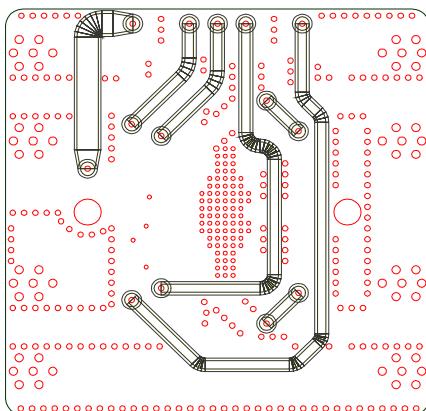

**Layer 3**

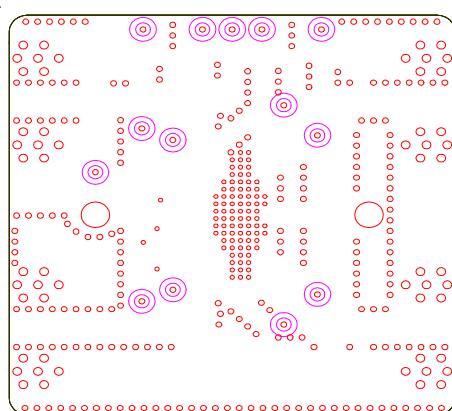

**Layer 4**

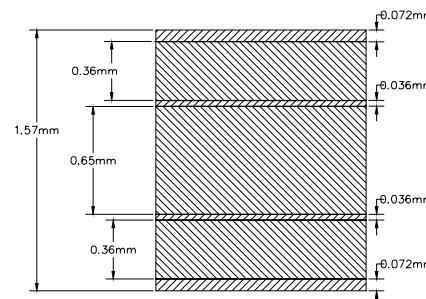

**LEGEND**

- ▨ CONDUCTOR LAYER
- ▨ DIELECTRIC LAYER

**Figure 8: Evaluation Board Layout and Structure**

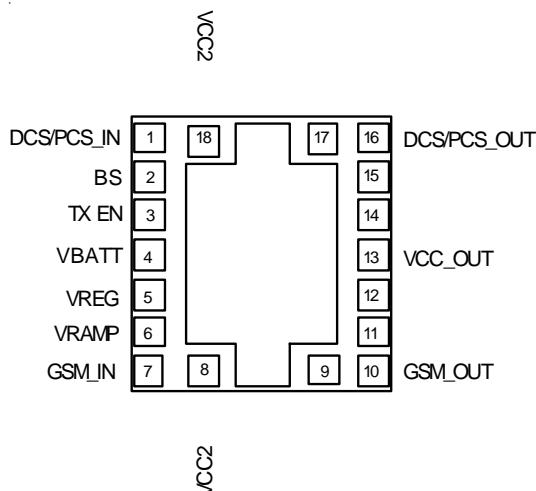


Figure 9: Pinout (X-Ray View)

PIN	NAME	DESCRIPTION	PIN	NAME	DESCRIPTION
1	DCS/PCS_IN	DCS/PCS RF Input	10	GSM_OUT	GSM850/900 RF Output
2	BS	Band Select Logic Input	11	GND	Ground
3	TX_EN	TX Enable Logic Input	12	GND	Ground
4	VBATT	Battery Supply Connection	13	VCC_OUT	Control Voltage Output which must be connected to VCC2, no decoupling
5	VREG	Regulated Supply Connection	14	GND	Ground
6	VRAMP	Analog Signal used to control the output power	15	GND	Ground
7	GSM_IN	GSM850/900 RF Input	16	DCS/PCS_OUT	DCS/PCS RF Output
8	VCC2	VCC Control Input for GSM850/900 Pre-amplifier	17	GND	Ground
9	GND	Ground	18	VCC2	VCC Control Input for DCS/PCS Pre-amplifier

Table 1: Pinout Description

## PACKAGE OUTLINE

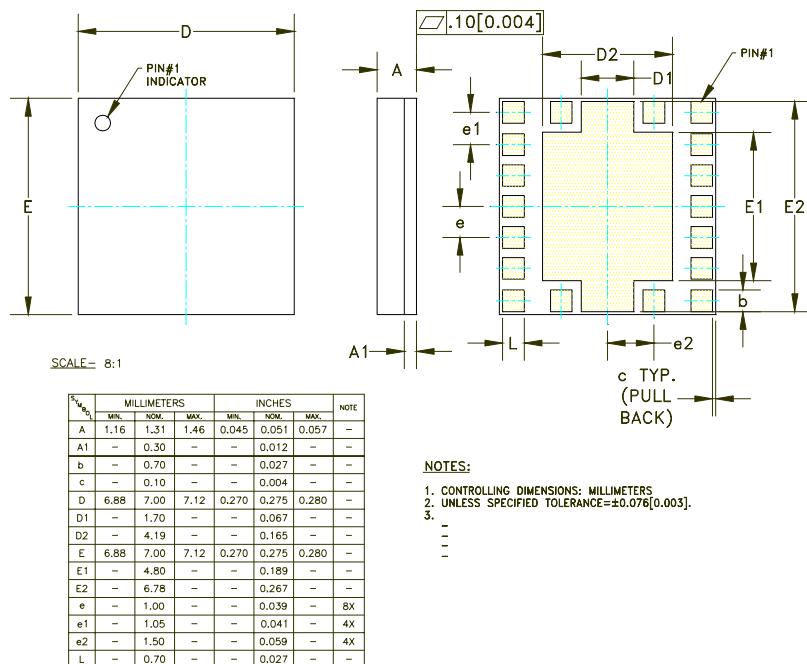


Figure 10: Package Outline

**NOTES**

**NOTES**

**NOTES**

**NOTES**



**ANADIGICS, Inc.**

141 Mount Bethel Road  
Warren, New Jersey 07059, U.S.A.  
Tel: +1 (908) 668-5000  
Fax: +1 (908) 668-5132

URL: <http://www.anadigics.com>  
E-mail: [Mktg@anadigics.com](mailto:Mktg@anadigics.com)

**IMPORTANT NOTICE**

ANADIGICS, Inc. reserves the right to make changes to its products or to discontinue any product at any time without notice. The product specifications contained in Advanced Product Information sheets and Preliminary Data Sheets are subject to change prior to a product's formal introduction. Information in Data Sheets have been carefully checked and are assumed to be reliable; however, ANADIGICS assumes no responsibilities for inaccuracies. ANADIGICS strongly urges customers to verify that the information they are using is current before placing orders.

**WARNING**

ANADIGICS products are not intended for use in life support appliances, devices or systems. Use of an ANADIGICS product in any such application without written consent is prohibited.

SUNSTAR 商斯达实业集团是集研发、生产、工程、销售、代理经销、技术咨询、信息服务等为一体的高科技企业，是专业高科技电子产品生产厂家，是具有 10 多年历史的专业电子元器件供应商，是中国最早和最大的仓储式连锁规模经营大型综合电子零部件代理分销商之一，是一家专业代理和分销世界各大品牌 IC 芯片和电子元器件的连锁经营综合性国际公司，专业经营进口、国产名厂名牌电子元件，型号、种类齐全。在香港、北京、深圳、上海、西安、成都等全国主要电子市场设有直属分公司和产品展示展销窗口门市部专卖店及代理分销商，已在全国范围内建成强大统一的供货和代理分销网络。我们专业代理经销、开发生产电子元器件、集成电路、传感器、微波光电元器件、工控机/DOC/DOM 电子盘、专用电路、单片机开发、MCU/DSP/ARM/FPGA 软件硬件、二极管、三极管、模块等，是您可靠的一站式现货配套供应商、方案提供商、部件功能模块开发配套商。商斯达实业公司拥有庞大的资料库，有数位毕业于著名高校——有中国电子工业摇篮之称的西安电子科技大学（西军电）并长期从事国防尖端科技研究的高级工程师为您精挑细选、量身订做各种高科技电子元器件，并解决各种技术问题。

微波光电部专业代理经销高频、微波、光纤、光电元器件、组件、部件、模块、整机；电磁兼容元器件、材料、设备；微波 CAD、EDA 软件、开发测试仿真工具；微波、光纤仪器仪表。欢迎国外高科技微波、光纤厂商将优秀产品介绍到中国、共同开拓市场。长期大量现货专业批发高频、微波、卫星、光纤、电视、CATV 器件：晶振、VCO、连接器、PIN 开关、变容二极管、开关二极管、低噪晶体管、功率电阻及电容、放大器、功率管、MMIC、混频器、耦合器、功分器、振荡器、合成器、衰减器、滤波器、隔离器、环行器、移相器、调制解调器；光电子元器件和组件：红外发射管、红外接收管、光电开关、光敏管、发光二极管和发光二极管组件、半导体激光二极管和激光器组件、光电探测器和光接收组件、光发射接收模块、光纤激光器和光放大器、光调制器、光开关、DWDM 用光发射和接收器件、用户接入系统光光收发器件与模块、光纤连接器、光纤跳线/尾纤、光衰减器、光纤适配器、光隔离器、光耦合器、光环行器、光复用器/转换器；无线收发芯片和模组、蓝牙芯片和模组。

更多产品请看本公司产品专用销售网站：

商斯达中国传感器科技信息网：<http://www.sensor-ic.com/>

商斯达工控安防网：<http://www.pc-ps.net/>

商斯达电子元器件网：<http://www.sunstare.com/>

商斯达微波光电产品网：<HTTP://www.rfoe.net/>

商斯达消费电子产品网：<http://www.icasic.com/>

商斯达实业科技产品网：<http://www.sunstars.cn/> 微波元器件销售热线：

地址：深圳市福田区福华路福庆街鸿图大厦 1602 室

电话：0755-82884100 83397033 83396822 83398585

传真：0755-83376182 (0) 13823648918 MSN：[SUNS8888@hotmail.com](mailto:SUNS8888@hotmail.com)

邮编：518033 E-mail：[szss20@163.com](mailto:szss20@163.com) QQ：195847376

深圳赛格展销部：深圳华强北路赛格电子市场 2583 号 电话：0755-83665529 25059422

技术支持：0755-83394033 13501568376

欢迎索取免费详细资料、设计指南和光盘；产品凡多，未能尽录，欢迎来电查询。

北京分公司：北京海淀区知春路 132 号中发电子大厦 3097 号

TEL：010-81159046 82615020 13501189838 FAX：010-62543996

上海分公司：上海市北京东路 668 号上海赛格电子市场 D125 号

TEL：021-28311762 56703037 13701955389 FAX：021-56703037

西安分公司：西安高新区 20 所(中国电子科技集团导航技术研究所)

西安劳动南路 88 号电子商城二楼 D23 号

TEL：029-81022619 13072977981 FAX:029-88789382