
Optical-based Analog Front End for Low-Speed Powerline Communications In The Home

White Paper

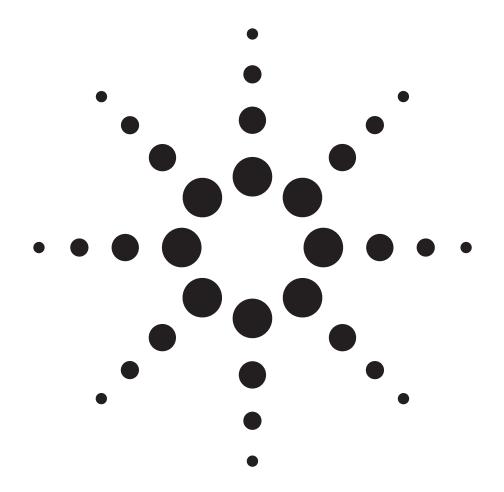

Agilent Technologies Semiconductor Products Group



The use of high-voltage power lines to carry voice signals has a history dating back to the early 1920s, with low-frequency amplitude-modulation systems operating over lines with voltages as high as 220,000 providing reliable voice links between power generating stations and dispatcher's offices. Later, the power utilities' carrier-current communications systems were refined to use single-sideband (SSB) multiplecarrier technology, and gradually expanded to include telemetry providing continual monitoring of load, voltage, and other power-system characteristics, as well as remote control of switching stations in remote locations.

Carrier-current systems that operate over the 120/240-volt AC electrical wiring in homes and commercial buildings have also been around for many years. Some examples include intercoms and baby monitors; remote controls for lights, switched AC outlets and appliances; and carrier-current AM radio transmitters using power wiring to broadcast programming within limited areas such as building and educational campuses. More recently low-speed digital communications systems for use over power wiring have been deployed. The common feature of all these systems is that they operate with low- to medium-frequency carriers and narrow transmitting bandwidths.

In Europe, the European Committee for Electrotechnical Standardization, CENELEC, produced EN50065, a standard covering the requirements for transmitting and receiving digital signals over 120/240-VAC wiring using carrier frequencies in the 3 kHz to 148.5 kHz range. The U.S. Federal Communications Commission has regulations for similar applications within the 45 kHz to 450 kHz frequency range, and in Japan PLC is permitted in the 10 kHz to 450 kHz range.

Today low-frequency powerline carrier modems can be used for many additional applications in homes and businesses, including:

- Home appliances
- Heating and ventilation control
- Lighting control
- Low-speed data communications networks
- Signs and information displays
- Fire and security alarm systems

These applications and frequencies are very different from the Broadband over Powerline (BPL) networking technologies, which are designed to provide networking and Internet access at DSL or cable modem speeds over electrical power wiring. "Home BPL" operates over the 120/240 VAC low-voltage distribution wires, while "Access BPL" operates over the medium-voltage (1 kV – 40 kV) power distribution network, to carry data over longer distrances. BPL carrier frequencies are in the 1 MHz to 80 MHz (megahertz), high frequency range.

Significance of the Analog Front End (AFE) to powerline modems

The use of digital signal processing techniques has significantly improved communication performance, but the troublesome problem of how to couple the analog-modulated signals from a powerline modem to and from electrical wiring has not seen any significant developments. The analog signal processing circuitry, together with other components required to couple the modulated signal on and off the power line is commonly given the collective name of analog front-end (AFE).

The AFE is called upon to provide voltage and current signal amplification, as well as providing galvanic isolation to protect the user and equipment being interfaced from both the nominal 120/240 volts and the transient voltages, which are common to power wiring. It is traditionally a complex circuit combining many discrete components with bulky isolation transformers.

This article introduces a new approach to the AFE, which uses optical coupling technology to provide significant improvements in the areas of power efficiency, system robustness and overall solution cost.

Figure 1 shows a block diagram of a typical powerline communication modem for use in home automation applications. The modulated signal is generated with a digital look-up table and a digital-to-analog converter (DAC). Demodulation is also carried out digitally, by first converting the received analog signal into the digital domain with an analog-to-digital converter (ADC), and then by applying subsequent digital processing. These two functions are typically integrated into a single modulator/ demodulator (modem) IC fabricated using a lowvoltage CMOS process.

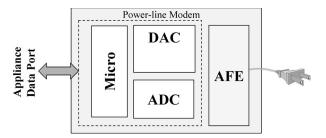


Figure 1: Typical frequency-shift keying (FSK) powerline communication modem (PLM) for use in home automation applications.

The use of CMOS IC processes allows the optimization of the die size, cost and power dissipation. However it makes the integration of analog circuitry problematic, which means that some, if not all, of the analog signal processing circuitry must be provided externally.

Although the modulator/demodulator topology used in the digital IC has a significant impact on overall communication performance, it is fair to say that in many cases the performance of the AFE has an equal, if not greater influence on the overall performance of the powerline modem.

AFE Requirements

The power line communication medium is a difficult environment compared to dedicated STP (shielded twisted pair) or coaxial cables. It places additional constraints and requirements on the AFE, particularly in the areas of:

- Insulation for voltage safety
- Surge voltage immunity
- Line attenuation
- Electromagnetic interference (EMI)
- Electromagnetic compatibility (EMC)

The 120 or 240 volts on home power wiring are potentially dangerous to the user. International safety norms and equipment regulations require the use of appropriate insulation barriers to protect the end user from the risk of electric shock. The traditional method used in powerline modems to provide safe insulation is an appropriately constructed and certified isolation transformer for coupling the modulated signal to and from the power line.

High voltage transient surges are a frequent occurrence on the power line and are considered to be normal and inevitable. However without sufficient protection all electrical circuitry is at risk from surge voltage-related damage. In particular semiconductor devices are vulnerable, since they can suffer either immediate catastrophic failure or accumulated damage resulting in shortened lifetimes.

In most power line-operated electronic equipment the only coupling mechanism between a power line voltage transient and the sensitive low-voltage circuitry is through the power supply. The low voltage circuits are normally very well protected from power line transients by the inherent low-pass filter characteristics of the power supply itself. Consequently the risk to the low voltage circuits is normally considered insignificant. The powerline modem, though, necessitates a higher-frequency communication path between the power line and the low voltage circuitry. Unfortunately this path not only enables data communications but also opens up the possibility of the transfer of power line surges into the sensitive low voltage circuitry.

To minimize this risk, it is common practice to incorporate supplementary over-voltage protection in the form of clamp diodes, silicon avalanche diodes and MOVs (metal oxide varistor). All of these protection devices have a significant amount of parasitic capacitance, which has the propensity of attenuating received signals. This means that the highest level of protection could also severely attenuate the desired communications.

Electromagnetic Compatibility

The operation of powerline modems can potentially create objectionable interference to radiofrequency appliances such as radios and televisions, either by interference conducted through the power wiring or radiated over the air from the power wiring. With respect to conducted interference, manufactures of powerline modems must ensure that the frequencies and amplitudes of the modulated signals meet applicable international conducted emission profiles, and guard against inadvertently transmitting out of band harmonics.

Electromagnetic emissions are similarly regulated. In the case of powerline modems electromagnetic interference (EMI) is of particular concern because most wiring is not shielded in any effective way. Unshielded communication cables subjected to common-mode currents have a very high propensity to propagate electromagnetic interference. Electromagnetic emissions can be minimized by either reducing the common-mode voltage or by increasing the commonmode impedance by minimizing the parasitic capacitance of the coupling device.

Attenuation

Communication signals on the power line are subjected to various degrees of attenuation, which vary with time and frequency.

One of the worst culprits for attenuating PLM signals are the capacitors installed to filter out the switching harmonics of switched-mode power supplies and lamp ballasts. On the one hand, implementers of PLM are grateful that these filter capacitors are installed, because they attenuate conducted noise transients. The downside is that the same capacitors can result in a very low power line impedance at the carrier frequencies used by home PLMs. Consequently the first measure taken to minimize attenuation of the transmitted signal is the use of a low impedance coupling circuit and a transmitter output stage with a high output current capability. This ensures minimum attenuation at the signal injection point. To counter inevitable attenuation of the transmitted signal the AFE receiver circuit amplifies the received signal before demodulating.

Immunity to Electromagnetic Interference

Electromagnetic interference immunity is the ability of the receiver to reject the interference generated by intentional and unintentional conducted and electromagnetic radiation. The EMI immunity performance of the PLM can be optimized in several ways. The first method is to maximize the signal-to-noise ratio (SNR) by minimizing the noise observed at the receiver. The second is to use noise-tolerant communication methods such as forward error correction (FEC) coding. The third method involves the use of multiple carrier frequencies. In practice, using a combination of these methods provides satisfactory EMI immunity. With respect to the AFE, reducing the amount of noise reaching the receiver enhances EMI immunity.

Noise propagates into the PLM receiver circuit in two ways: differential mode and common mode.

With differential noise, the noise is injected from the noise source as a voltage between the live and neutral wires of the power wiring. This differential noise signal is subject to the same attenuation effects as the transmitted modem signal. Consequently the amount of differential noise at the receiver will be dependent on the position of the noise injection point relative to the location of the receiving point.

In the case of common-mode noise, unshielded cables act as good antennas for picking up electromagnetic signals from both intentional emitters such as radio stations and unintentional emitters such as universal motors and lamp ballasts. The power line is no exception: since the live and neutral conductors run in close proximity to each other, electromagnetic noise is equally coupled onto both.

The amplitude of the common-mode noise coupled onto the power line will depend on the length of the conductors, and their position relatively to the devices radiating the electromagnetic noise. The power line impedance loads do not attenuate the common-mode noise voltage in the same way as they do to differential-mode noise. The consequence is that the commonmode noise becomes more significant in the case of heavily attenuated communications signals.

The amount of common-mode noise reaching the receiver is dependent on the leakage capacitance of the signal coupling transformer and the noise frequency. Ultimately the receiver circuit is not directly affected by common-mode noise, but is affected by common-mode noise converted to differential-mode noise by unavoidable asymmetry in the cable, transformer and receiver circuitry itself.

To reduce the influence of both differential and common-mode noise, a passive or active filter is used at the front end of the receiver. In this manner noise frequencies outside the communication band can be very effectively removed.


SUNSTAR微波光电 http://www.rfoe.net/ TEL:0755-83396822 FAX:0755-83376182 E-MAIL:szss20@163.com

More difficult to filter out are noise sources close to the transmitted carrier frequencies. It is these noise sources and the in band noise frequencies which ultimately cause the residual EMI immunity limitations for PLMs.

Optically Coupled AFEs

A transformer can inherently propagate signals in either direction while optical coupling methods use a unidirectional combination of optical emitter and detector, and can only propagate signals in one direction. To achieve bi-directional Communication in an optical AFE, one transformer has to be replaced with two optical channels. Fortunately optical packaging platforms allow multiple optical channels to be integrated into standard SMD type packages.

Figure 2 illustrates the construction of an integrated optical PLM AFE. Packaged inside the optical AFE are four discrete semiconductor elements: two LEDs (LED1 and LED2) and two BICMOS integrated circuits (IC1 and IC2). IC1 is ground referenced to the low voltage circuitry and IC2 is ground referenced to the power line.

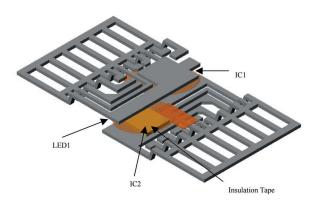

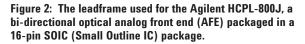


Figure 3 is the block diagram of the AFE. With respect to the transmit optical path, IC1 includes a transconductance amplifier, which drives LED1 with a forward current equal to the sum of a DC biasing current and a current which is directly proportional to the analog input signal. The type of LED used has a very linear currentto-light transfer characteristic to minimize harmonic distortion resulting from the electricalto-optical conversion.

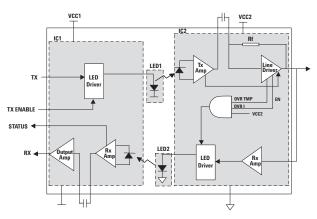


Figure 3: Block diagram showing the two CMOS ICs and the LED emitters used in the optical AFE.

On the power line side of the isolation boundary, a photodiode and photodetector amplifier are integrated into IC2, with circuit converting captured photons to an output voltage which is linearly related to the light emission of LED1.

The output of the photodetector amplifier is coupled to the output stage via an external AC coupling circuit. The primary function of the coupling circuit is to remove residual DC offset voltage from the output of the photodetector amplifier. This coupling circuit may also include filtering or frequency shaping to remove out-ofband harmonics generated in the modulator or optical channel.

The operation of the receiver optical path is very similar to that of the transmitter path with the optical emitter and detector functions integrated in IC2 and IC1, respectively.

In addition to the basic function of coupling transmitted and received signals other important features are integrated into the optical AFE. The first is the implementation of a highly linear line driver circuit, which is capable of delivering up to 1.0 A peak-to-peak. This high current capability ensures that an adequate transmit signal level is coupled onto the power line even in the case of very low power line impedance. The low distortion specification ensures that the generation of out-of-band harmonics is minimized.

SUNSTAR微波光电 http://www.rfoe.net/ TEL:0755-83396822 FAX:0755-83376182 E-MAIL:szss20@163.com

The optical AFE also includes an additional gain stage in the receive function, which may be used to amplify attenuated signals ensuring optimal link integrity even in worst-case signaling environments.

The optical AFE incorporates integrated control functions. To ensure that the line driver does not unnecessarily attenuate received signals, it is important that the line driver be switched to a high impedance state while the PLM is receiving signals. Normally this would require the use of an additional isolated communication channel to couple the transmit-enable signal from the modulator control circuit to the line driver. To minimize packaging complexities the optical AFE allows digital control signals to be simultaneously multiplexed with the analog signals, allowing a single optical channel to simultaneously transmit analog and digital control signals. One of these digital signals is the transmit-enable signal.

Since the output stage of the PLM is totally isolated from the appliance, in some cases the appliance's control circuitry would have no way of determining whether or not the V_{cc2} power supply voltage is present and correct. To prevent such a scenario an under-voltage detection circuit is included on IC2, which monitors V_{cc2} and transmits an indicator signal across the isolation boundary manner similar to that used for the transmit-enable signal.

Protection Features

To ensure maximum robustness of the modem the line driver circuit includes over-temperature and over-current protection. The over-current signal works in two ways: First it clamps the peak output current to a safe sustainable level; second it transmits an over-current signal back across the isolation boundary. Normally the peak output current is limited by the combined influence of the coupling impedance and the power line load.

Since the worst-case power line load can be very small, in some cases as low as 1Ω , the resulting peak current levels can potentially reach very high levels. To meet a realistic peak current limit, the coupling impedance has to be sufficiently large. Such high coupling impedance unfortunately will result in some attenuation of the transmit signal at nominal load conditions.

The provision of the isolated overcurrent signal facilitates an alternate peak current limiting strategy. That is to use the over-current signal to signal the microcontroller to progressively reduce the transmit signal amplitude until the over-current flag is disabled. Such a control strategy allows the use of a very small coupling impedance maximizing coupling efficiency under all load conditions.

Conclusion

One of the first and most obvious advantages of an optical solution is the ability to construct a low profile SMD component that contains not only the isolated coupling mechanism but also much of the analog signal processing components. This results in a large reduction in the number of components required, which in turn reduces the complexity and cost of a PLM. Figure 4 shows a complete powerline modem using an optical AFE.

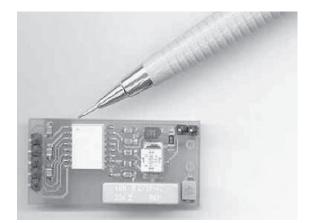


Figure 4: A complete powerline modem using the optical analog front-end.

In addition to these benefits an optical solution offers performance advantages, particularly in the areas of EMC, EMI and surge immunity. With respect to EMC and EMI optimization, reducing the parasitic capacitance of the isolation component increases the common mode impedance, which in turn reduces electromagnetic emissions and sensitivity to common mode noise transients.

The leakage capacitance of an optical signalcoupling device is directly related to the separation distance and coupling area between the optical emitter and detector. Unlike magnetic transformers, the optical signal coupling devices do not require close physical coupling to achieve

SUNSTAR微波光电 http://www.rfoe.net/ TEL:0755-83396822 FAX:0755-83376182 E-MAIL:szss20@163.com

satisfactory performance. Theoretically, optically coupled signal paths can operate through an optical fiber at distances of hundreds of kilometers, making the common-mode impedance infinitely high. In practical terms, optically integrated devices in standard SMD packages typically exhibit coupling capacitance on the order of 1.3 pF. This is a very significant improvement over magnetic transformers, which typically exhibit parasitic capacitances in the range of 30 to 100 pF.

Magnetic signal transformers are capable of not just transmitting and receiving communication signals; they are also capable of coupling high voltage surge transients. Conversely optical coupling devices are only inherently capable of coupling low-power optical signals. Transient voltage surges are very effectively blocked from reaching the low voltage appliance circuitry. From a practical point of view this means that the overall robustness of an electrical appliance need not be degraded by the inclusion of a PLM.

References

- Making Precompliance Conducted and Radiated Emissions Measurements with EMC Analysers. Agilent Application Note AN 1328.
- [2] Olaf G. Hooijen, "A Channel Model for the Residential Power Circuit Used as a Digital Communications Medium." *IEEE Transactions on Electromagnetic Compatibility*, vol. 40, no. 4, November 1998.
- [3] Harald Dalichau and Wolfgang Taeger, Description of the Technology and Comparisons of the Performance of two different Approaches for a Powerline Modem in the CENELEC-Band. Polytrax Information Technology AG.
- [4] R.M Vines, M.J. Trussel, L.J. Gales and J.B. O'Neal, Jr., "Noise on Residential Power Distribution Circuits." *IEEE Transactions on Electromagnetic Compatibility*, vol. 26, November 1984.

www.agilent.com/semiconductors

For product information and a complete list of distributors, please go to our web site. For technical assistance call: Americas/Canada: +1 (800) 235-0312 or (916) 788-6763 Europe: +49 (0) 6441 92460 China: 10800 650 0017 Hong Kong: (65) 6756 2394 India, Australia, New Zealand: (65) 6755 1939 Japan: (+81 3) 3335-8152(Domestic/International), or 0120-61-1280(Domestic Only) Korea: (65) 6755 1989

Singapore, Malaysia, Vietnam, Thailand, Philippines, Indonesia: (65) 6755 2044

Taiwan: (65) 6755 1843

Data subject to change. Copyright © 2003 Agilent Technologies, Inc. December 19, 2003 5989-0515EN

Agilent Technologies

SUNSTAR 商斯达实业集团是集研发、生产、工程、销售、代理经销、技术咨询、信息服务等为一体的高科技企业,是专业高科技电子产品生产厂家,是具有10多年历史的专业电子元器件供应商,是中国最早和最大的仓储式连锁规模经营大型综合电子零部件代理分销商之一,是一家专业代理和分銷世界各大品牌IC芯片和電子元器件的连锁经营综合性国际公司,专业经营进口、国产名厂名牌电子元件,型号、种类齐全。在香港、北京、深圳、上海、西安、成都等全国主要电子市场设有直属分公司和产品展示展销窗口门市部专卖店及代理分销商,已在全国范围内建成强大统一的供货和代理分销网络。我们专业代理经销、开发生产电子元器件、集成电路、传感器、微波光电元器件、工控机/DOC/DOM电子盘、专用电路、单片机开发、MCU/DSP/ARM/FPGA软件硬件、二极管、三极管、模块等,是您可靠的一站式现货配套供应商、方案提供商、部件功能模块开发配套商。商斯达实业公司拥有庞大的资料库,有数位毕业于著名高校——有中国电子工业摇篮之称的西安电子科技大学(西军电)并长期从事国防尖端科技研究的高级工程师为您精挑细选、量身订做各种高科技电子元器件,并解决各种技术问题。

微波光电部专业代理经销高频、微波、光纤、光电元器件、组件、部件、模块、整机;电 磁兼容元器件、材料、设备;微波 CAD、EDA 软件、开发测试仿真工具;微波、光纤仪器仪表。 欢迎国外高科技微波、光纤厂商将优秀产品介绍到中国、共同开拓市场。长期大量现货专业批发 高频、微波、卫星、光纤、电视、CATV 器件: 晶振、VCO、连接器、PIN 开关、变容二极管、开 关二极管、低噪晶体管、功率电阻及电容、放大器、功率管、MMIC、混频器、耦合器、功分器、 振荡器、合成器、衰减器、滤波器、隔离器、环行器、移相器、调制解调器;光电子元器件和组 件:红外发射管、红外接收管、光电开关、光敏管、发光二极管和发光二极管组件、半导体激光 二极管和激光器组件、光电探测器和光接收组件、光发射接收模块、光纤激光器和光放大器、光 调制器、光开关、DWDM 用光发射和接收器件、用户接入系统光光收发器件与模块、光纤连接器、 光纤跳线/尾纤、光衰减器、光纤适 配器、光隔离器、光耦合器、光环行器、光复用器/转换器; 无线收发芯片和模组、蓝牙芯片和模组。

更多产品请看本公司产品专用销售网站:

商斯达微波光电产品网:HTTP://www.rfoe.net/

商斯达中国传感器科技信息网: http://www.sensor-ic.com/

商斯达工控安防网: http://www.pc-ps.net/

商斯达电子元器件网: http://www.sunstare.com/

商斯达消费电子产品网://www.icasic.com/

商斯达实业科技产品网://www.sunstars.cn/ 射频微波光电元器件销售热线:

地址:深圳市福田区福华路福庆街鸿图大厦1602室

电话: 0755-83396822 83397033 83398585 82884100

传真: 0755-83376182 (0) 13823648918 MSN: SUNS8888@hotmail.com

邮编: 518033 E-mail:szss20@163.com QQ: 195847376

深圳赛格展销部: 深圳华强北路赛格电子市场 2583 号 电话: 0755-83665529 25059422 技术支持: 0755-83394033 13501568376

欢迎索取免费详细资料、设计指南和光盘;产品凡多,未能尽录,欢迎来电查询。

北京分公司:北京海淀区知春路 132 号中发电子大厦 3097 号

TEL: 010-81159046 82615020 13501189838 FAX: 010-62543996 上海分公司:上海市北京东路 668 号上海賽格电子市场 D125 号

TEL: 021-28311762 56703037 13701955389 FAX: 021-56703037

西安分公司:西安高新开发区 20 所(中国电子科技集团导航技术研究所)

西安劳动南路 88 号电子商城二楼 D23 号

TEL: 029-81022619 13072977981 FAX:029-88789382