

Loop Filter

Second and Third-Order Loops

Choosing the optimum loop filter for a design encompasses many tradeoffs. A general rule of thumb for choosing the loop filter bandwidth is 10 percent of the step size. A second-order loop (C_3 , R_3 , C_6 and R_6 omitted from Figure 1) will provide the least number of components and the fastest lock times. Widening the loop filter will improve lock time, although stability will suffer and lock time will actually degrade if it is made too wide. If lock time is not an important parameter, a narrower second-order filter will minimize residual FM without requiring additional components.

Third-order loop filters (as shown in Figure 1) provide a good compromise between lock time and residual FM. Using a third-order loop with 20 dB of rejection at the step size will halve the Residual FM as compared to a similar second-order loop, with minimum effect on lock time.

Maximum Loop Filter Bandwidth

The PE329x series PLLs contain capacitors to ground, internal to the charge pump circuitry. PLL1 contains a 50 pF capacitor and PLL2 contains a 100 pF capacitor. These capacitors are relatively transparent for narrow-band loop filters. As the loop bandwidth increases, however, the internal capacitor becomes dominant and limits loop bandwidth. For most applications this is not a concern. For example, a PLL1 application that uses a step size of 80 kHz can operate with an 8 kHz loop bandwidth.

Digital Control Lines

Control Line Noise

Frequency jitter can occur during programming if a low impedance (such as a capacitor to ground) is placed on any control line pin (clock, data, and load enable). The use of a 51k ohm resistor in series with the control line will eliminate the problem with no effect on programming time.

Enable Line Voltage

The PE329x series PLLs use a level-sensitive load enable. The digital controller must therefore provide an active low to the part at all times except when the data is to be loaded into the shift register. If the PLL controller does not hold the voltage low, a high value resistor to ground should be added to the enable line to ensure stable operation.

5 Volt Operation:

The PE329x series PLLs are not capable of accepting control voltages greater than 3.6 volts. Interfacing with 5 volt controllers requires the addition of resistive dividers to comply with the 3.6 volt maximum operating voltage.

Using the PE329x Series Fractional-N PLL s

Features

- Industry-leading fractional spur compensation: no adjusting required, stable over temperature
- Ultra-Low Power via FlexiPower variable supply voltages
- Modulo-32 fractional-N main counters

Sales Offices

United States

Peregrine Semiconductor Corp.

6175 Nancy Ridge Drive
San Diego, CA 92121
Tel 1-858-455-0660
Fax 1-858-455-0770

Japan

Peregrine Semiconductor K.K.

5A-5, 5F Imperial Tower
1-1-1 Uchisaiwaicho, Chiyoda-ku
Tokyo 100-0011 Japan
Tel: 03-3507-5755
Fax: 03-3507-5601

Europe

Peregrine Semiconductor Europe

Bâtiment Maine
13-15 rue des Quatre Vents
F- 92380 Garches
Tel 33-1-47-41-91-73
Fax 33-1-47-41-91-73

Australia

Peregrine Semiconductor Australia

8 Herb Elliot Ave.
Homebush, NSW 2140
Australia
Tel: 011-61-2-9763-4111
Fax: 011-61-2-9746-1501

For a list of representatives in your area, please refer to our Web site at: <http://www.peregrine-semi.com>

Application Note Identification

No patent rights or licenses to any circuits described in this application note are implied or granted to any third party.

Peregrine's products are not designed or intended for use in devices or systems intended for surgical implant, or in other applications intended to support or sustain life, or in any application in which the failure of the Peregrine product could create a situation in which personal injury or death might occur. Peregrine assumes no liability for damages, including consequential or incidental damages, arising out of the use of its products in such applications.

Peregrine products are protected under one or more of the following U.S. patents: 6,090,648; 6,057,555; 5,973,382; 5,973,363; 5,930,638; 5,920,233; 5,895,957; 5,883,396; 5,864,162; 5,863,823; 5,861,336; 5,663,570; 5,610,790; 5,600,169; 5,596,205; 5,572,040; 5,492,857; 5,416,043. Other patents may be pending or applied for.

*Peregrine, the Peregrine logotype, Peregrine Semiconductor Corp., and UTSi are registered trademarks of Peregrine Semiconductor Corporation.
Copyright © 2003 Peregrine Semiconductor Corp. All rights reserved.*