



PHILIPS

Philips Semiconductors B.V.

Gerstweg 2, 6534 AE Nijmegen, The Netherlands

Reportnr. : RNR-T45-97-B-0686
Author : T. Buss
Date : 22 Aug1997
Department : P.G. Transistors & Diodes, Development

900MHz DRIVER-AMPLIFIER WITH THE BFG425W

Abstract:

This application note contains an example of a Driver-Amplifier with the new BFG425W Double Poly RF-transistor. The driver is designed for a frequency $f=900\text{MHz}$.

Performance at $f=900\text{MHz}$, $T=25^\circ\text{C}$: Power Gain $>12\text{dB}$, Noise Figure $\text{NF}<2\text{dB}$.

Appendix I: Schematic of the circuit

Appendix II: Results of simulations and measurements

Appendix III: Printlayout and list of used components & materials



PHILIPS

Philips Semiconductors B.V.

Introduction:

With the new Philips silicon bipolar double poly BFG400W series, it is possible to design driver-amplifiers for high frequency applications with a low current and a low supply voltage. These amplifiers are well suited for the new generation low voltage high frequency wireless applications. In this note an example of such an amplifier will be given. This driver-amplifier is designed for a working frequency of 900MHz.

Designing the circuit:

The circuit is designed to show the following performance (target):

transistor: BFG425W

$V_{SUP}=3V$, $I_{SUP} \sim 10mA$

freq=900MHz

PowerGain: >12dB

VSWRi<1:2

VSWRo<1:2

The in- and outputmatching is realised with aRC-combination. Also extra emitter-inductance on both emitter-leads (μ -strips) are used to improve the matching. This emitter inductance is not necessary. The place of the via-holes is not critical.

Designing the layout:

A lay-out has been designed with HP-MDS. Appendix III contains the printlayout.

Measurements:

Measurements of the total circuit (epoxy PCB) are done (Appendix I).

Philips Semiconductors B.V.

Appendix I: Schematic of the circuit

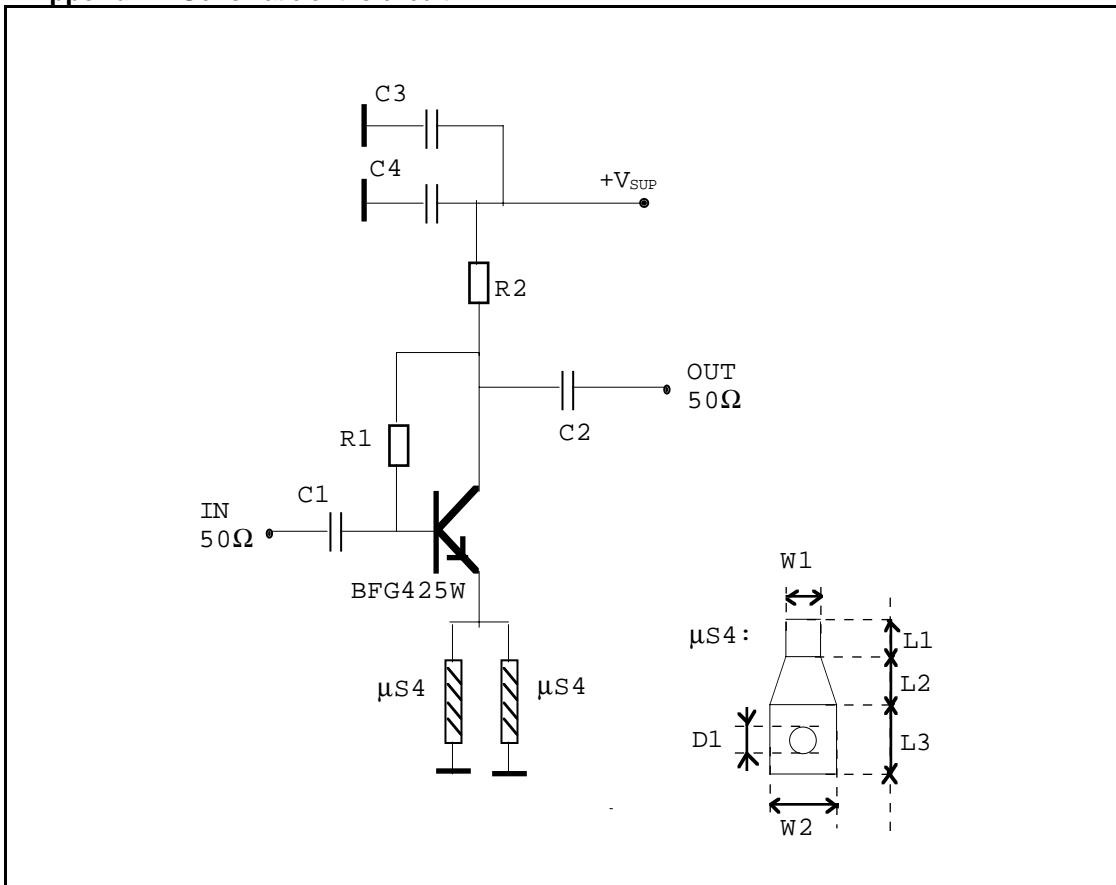


Figure 1: Driver circuit

900MHz Driver Component list:

Component:	Value:	Comment:
R1	3.3 kΩ	Bias.
R2	150 Ω	
C1	150 pF	Input match.
C2	150 pF	Output match.
C3	27 pF	900MHz short.
C4	1 nF	RF Decoupling
μs4	(nexttable)	Emitter induction: μ-stripline + via



PHILIPS

Philips Semiconductors B.V.

μ S4 Emitter induction (μ -stripline + via):

Name	Dimension	Description
L1	1.0mm	length μ -stripline; $Z_0 \sim 48\Omega$ (PCB: $\epsilon_r \sim 4.6$, H=0.5mm)
L2	1.0mm	length interconnect stripline and via-hole area
L3	1.0mm	length via-hole area
W1	0.5mm	width μ -stripline
W2	1.0mm	width via-hole area
D1	0.4mm	diameter of via-hole

Appendix II: Results of simulations and measurements:

BFG425W, $V_{SUP}=3.0V$, $I_{SUP} \sim 10.0mA$ @ $T=25^\circ C$


	Measurements PCB:	Comment:
f=900MHz		
$ S_{21} ^2$ [dB]	17	$P_{IN}=-30dBm$, $T=25^\circ C$
G_P [dB]	14	$P_{IN}=-10dBm$, $T=25^\circ C$
G_P [dB]	~10	$P_{IN}=-10dBm$, $T << 0^\circ C$ (Freeze spray)
VSWRi	1.8	$P_{IN}=-30dBm$, $T=25^\circ C$
VSWRo	1.5	$P_{IN}=-30dBm$, $T=25^\circ C$
Noise Figure [dB]	<2.0	$P_{IN}=-30dBm$, $T=25^\circ C$
IP3 [dBm] (output)	-	not measured



PHILIPS

Philips Semiconductors B.V.

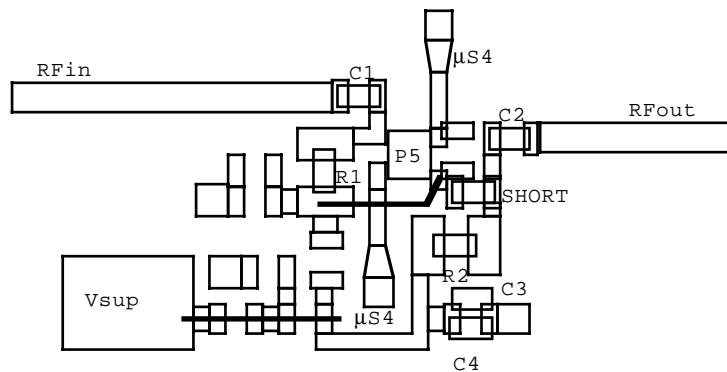Appendix III: Printlayout and list of used components & materials



900MHz Driver Amplifier
BFG425W

Figure 2: Printlayout

900MHz Driver Component list:

Component:	Value:	size:
R1	3.3 kΩ	0603 Philips
R2	150 Ω	0603 Philips
C1	150 pF	0603 Philips
C2	150 pF	0603 Philips
C3	27 pF	0603 Philips
C4	1 nF	0603 Philips
P5	BFG425W	SOT343R Philips
PCB	$\epsilon_r \sim 4.6, H=0.5\text{mm}$	FR4

note 1: The used PCB was designed for Low Noise Amplifier applications. Shorts and wires are used to adapt the PCB for this driver application.

SUNSTAR 商斯达实业集团是集研发、生产、工程、销售、代理经销、技术咨询、信息服务等为一体的高科技企业，是专业高科技电子产品生产厂家，是具有 10 多年历史的专业电子元器件供应商，是中国最早和最大的仓储式连锁规模经营大型综合电子零部件代理分销商之一，是一家专业代理和分销世界各大品牌 IC 芯片和电子元器件的连锁经营综合性国际公司，专业经营进口、国产名厂名牌电子元件，型号、种类齐全。在香港、北京、深圳、上海、西安、成都等全国主要电子市场设有直属分公司和产品展示展销窗口门市部专卖店及代理分销商，已在全国范围内建成强大统一的供货和代理分销网络。我们专业代理经销、开发生产电子元器件、集成电路、传感器、微波光电元器件、工控机/DOC/DOM 电子盘、专用电路、单片机开发、MCU/DSP/ARM/FPGA 软件硬件、二极管、三极管、模块等，是您可靠的一站式现货配套供应商、方案提供商、部件功能模块开发配套商。商斯达实业公司拥有庞大的资料库，有数位毕业于著名高校——有中国电子工业摇篮之称的西安电子科技大学（西军电）并长期从事国防尖端科技研究的高级工程师为您精挑细选、量身订做各种高科技电子元器件，并解决各种技术问题。

微波光电部专业代理经销高频、微波、光纤、光电元器件、组件、部件、模块、整机；电磁兼容元器件、材料、设备；微波 CAD、EDA 软件、开发测试仿真工具；微波、光纤仪器仪表。欢迎国外高科技微波、光纤厂商将优秀产品介绍到中国、共同开拓市场。长期大量现货专业批发高频、微波、卫星、光纤、电视、CATV 器件：晶振、VCO、连接器、PIN 开关、变容二极管、开关二极管、低噪晶体管、功率电阻及电容、放大器、功率管、MMIC、混频器、耦合器、功分器、振荡器、合成器、衰减器、滤波器、隔离器、环行器、移相器、调制解调器；光电子元器件和组件：红外发射管、红外接收管、光电开关、光敏管、发光二极管和发光二极管组件、半导体激光二极管和激光器组件、光电探测器和光接收组件、光发射接收模块、光纤激光器和光放大器、光调制器、光开关、DWDM 用光发射和接收器件、用户接入系统光光收发器件与模块、光纤连接器、光纤跳线/尾纤、光衰减器、光纤适配器、光隔离器、光耦合器、光环行器、光复用器/转换器；无线收发芯片和模组、蓝牙芯片和模组。

更多产品请看本公司产品专用销售网站：

商斯达中国传感器科技信息网：<http://www.sensor-ic.com/>

商斯达工控安防网：<http://www.pc-ps.net/>

商斯达电子元器件网：<http://www.sunstare.com/>

商斯达微波光电产品网：<HTTP://www.rfoe.net/>

商斯达消费电子产品网：<http://www.icasic.com/>

商斯达实业科技产品网：<http://www.sunstars.cn/> 微波元器件销售热线：

地址：深圳市福田区福华路福庆街鸿图大厦 1602 室

电话：0755-82884100 83397033 83396822 83398585

传真：0755-83376182 (0) 13823648918 MSN：SUNS8888@hotmail.com

邮编：518033 E-mail：szss20@163.com QQ：195847376

深圳赛格展销部：深圳华强北路赛格电子市场 2583 号 电话：0755-83665529 25059422

技术支持：0755-83394033 13501568376

欢迎索取免费详细资料、设计指南和光盘；产品凡多，未能尽录，欢迎来电查询。

北京分公司：北京海淀区知春路 132 号中发电子大厦 3097 号

TEL：010-81159046 82615020 13501189838 FAX：010-62543996

上海分公司：上海市北京东路 668 号上海赛格电子市场 D125 号

TEL：021-28311762 56703037 13701955389 FAX：021-56703037

西安分公司：西安高新区 20 所(中国电子科技集团导航技术研究所)

西安劳动南路 88 号电子商城二楼 D23 号

TEL：029-81022619 13072977981 FAX:029-88789382