

APPLICATION NOTE

**100 – 450 MHz 250 W Power
Amplifier with the BLF548
MOSFET**

AN98021

**100 – 450 MHz 250 W Power Amplifier
with the BLF548 MOSFET**

**Application Note
AN98021**

CONTENTS

1	INTRODUCTION
2	DESIGN CONSIDERATIONS
3	AMPLIFIER CONCEPT
4	INPUT CIRCUITRY
5	ADJUSTMENT OF THE AMPLIFIER
5.1	Tuning the outputnetwork
5.2	Testing the unit under RF conditions
5.3	Tuning the unit's inputnetwork
5.4	Combining the units
6	CONCLUSIONS
7	REFERENCES
8	APPENDIX A
9	APPENDIX B
10	APPENDIX C

100 – 450 MHz 250 W Power Amplifier with the BLF548 MOSFET

Application Note AN98021

1 INTRODUCTION

In this report the design procedures and measurement results are given of a two octave wideband amplifier (covering both the civil and military airbands between 100 and 450 MHz), equipped with two MOSFET devices, which is capable of generating 250 W of output power.

In order to achieve a good broadband capability one has to use devices with the output capacitance reduced to the utmost minimum. While applying PHILIPS' BLF548 MOSFETs it was possible to obtain a respectable powergain of more than 10 dB, throughout the whole band.

The BLF548 is a balanced N-channel enhancement mode vertical D-MOS transistor in a SOT262 package, especially designed for use in wideband amplifiers up to 500 MHz. The transistor is capable to deliver 150 W nominal outputpower at a supply voltage of 28 Volts. Due to the low output capacitance the attainable bandwidth will exceed 300 MHz.

2 DESIGN CONSIDERATIONS

While designing broadband amplifiers, one has to take several things into account:

- To select the right manufacturer, able to supply the products with a good reliability, gives a good support and offers a complete range of transistors e.g. for driverstages.
- To select the right active components, capable to fulfill the desired wishes, such as; high reliability, high powergain, high efficiency, excellent mismatch capabilities, right loadpower, good long-life properties and last but not least; good broadband capability.
- To terminate the transistor with the right load impedance, with other words, to determinate the right output matching network.
- To eliminate the 6 dB/octave gain slope throughout the band of operation, in order to achieve an acceptable gainflatness.
- To find the right input matching network; the input VSWR has to be low in order to achieve a good termination for the driverstage.
- To design the matching networks in such a way that they are capable to handle the, at some points very high, R.F. currents.

A balanced transistor was chosen in order to reduce the second harmonic (due to the push-pull effect) and to reduce the number of required components.

The criteria for chosen MOSFETs over bipolar transistors are; high powergain, high load mismatch capabilities, low noise and easy biasing.

Nowadays three major MOSFET suppliers are involved when $P_I = 150$ W is needed at $f = 500$ MHz and $V_{ds} = 28$ V. Available are; BLF548, industry type A and industry type B. Table 1 gives an overview of the characteristics of these 3 types.

Table 1

	BLF548	TYPE A	TYPE B	UNIT
f	500	400	500	MHz
Gp	>10	>10	>8	dB
η_d	>50	>50	>55	%
Ciss	105	180	140	pF
Coss	90	200	100	pF
Crss	25	20	32	pF
BW	300	133	266	MHz

100 – 450 MHz 250 W Power Amplifier with the BLF548 MOSFET

Application Note
AN98021

With: $BW = 1/(2\pi * R_{load} * C_o)$; $R_{load} = V_{ds}^2/(2 * P_I)$ and $C_o = 1.15 * C_{oss}$.

BW = bandwidth, R_{load} = loadresistance, C_o = outputcapacitance.

In order to achieve the best possible broadband results, the BLF548 is a very good choice.

Other Philips MOSFETs in the 500 MHz series are, followed by nominal loadpower:

12.5 Volts – single ended

BLF521	2 W
BLF522	5 W

28 Volts – single ended

BLF542	5 W
BLF543	10 W
BLF544	20 W

28 Volts – push-pull


BLF544B	20 W
BLF545	40 W
BLF546	80 W
BLF547	100 W
BLF548	150 W

3 AMPLIFIER CONCEPT

The amplifier concept described in this paper is based upon two identical modular units, each containing one BLF548 MOSFET. Both units are combined by means of two 3 dB – 90° hybrid couplers, which is shown in Fig.1. The main advantage is that the input VSWR will be very good; since it is independent of the mismatch introduced by the units, the 50 Ω termination will cause a good load for the driver stage, e.g. equipped with BLF544.

100 – 450 MHz 250 W Power Amplifier with the BLF548 MOSFET

Application Note AN98021

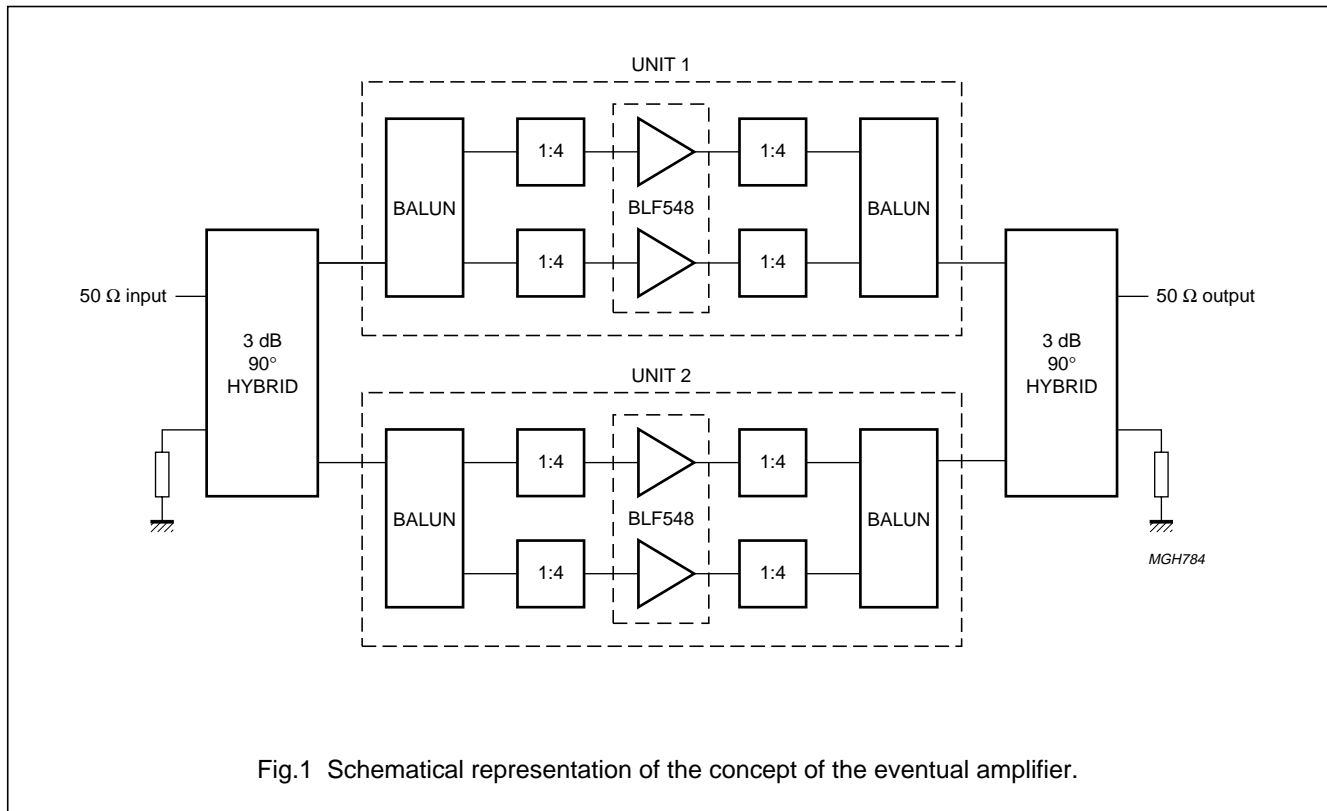

The following seven steps have been followed in order to develop a first prototype of one unit.

1. Determine the BLF548's 150 W output power load impedance between 100 and 500 MHz (50 MHz interval steps) by measurement techniques or simulations. At the moment of writing it was not possible to perform full automatic measurements at frequencies lower than 500 MHz with transistors build in a balanced SOT262 header. Therefore the load impedances have been calculated by means of the electrical equivalent diagram shown in Fig.2.
2. Find the correct output matching network which transforms the 50 Ω termination to the required load impedance for the frequency range 100-500 MHz.
3. Optimize the output matching network of step 2 with help of linear simulation software, such as Touchstone (EESOF).
4. Since the matching network will not have an ideal behaviour, it is necessary to determine the actual load impedance of the selected output matching network, again in 50 MHz steps between 100-500 MHz.
5. Calculate (or even better, determine by means of load-pull measurements) both the power gain and input impedance of the transistor by presenting the load impedances, found at step 4, to it. This is very important to investigate the behaviour of the transistor while terminating it with the selected output matching network.
6. Choose the right input matching network which has a minimum return loss (RI) at the highest frequency (450 MHz) and a declining RI for lower frequencies in a way that the gain increase effect for lower frequencies is equalized. Other possibilities, as feedback or frequency dependent damping at the gate side (by means of low R_g s), can be taken into consideration.
7. Optimize the input network for gain flatness by means of linear simulation software (Touchstone, EESOF). Remember the input VSWR throughout the band is taken care of by the use of 90° hybrids, which combine the two modular units.

100 – 450 MHz 250 W Power Amplifier
with the BLF548 MOSFET

Application Note
AN98021

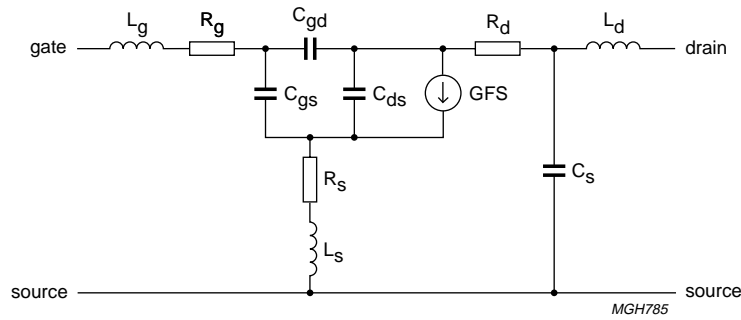


Fig.2 RF Power MOSFET equivalent diagram (one BLF548 section).

At the following pages the design steps are presented which were followed at PHILIPS' laboratories in order to design a 150 W unit. Using the diagram shown in Fig.2, powergain and impedances have been calculated first, using the data given in Table 2.

Table 2

Lg	0.58 nH	
Ls	0.11 nH	
Ld	0.50 nH	
Rg	0.09 Ω	
Rs	0.08 Ω	
Rd	0.19 Ω	
Cgd	29 pF	1.15 × Crss
Cgs	120 pF	1.5 × (Ciss-Crss)
Cds	72 pF	1.15 × (Coss-Crss-Cs)
Cs	2.4 pF	2.4 pF
Gfs'	1.6 S	0.5 × Gfs (for Class B)

Rg, Rd, Rs are derived from Rdson measurements, Gfs and Cs are measured, Cgs, Cds, Cgd derived from measured Ciss, Coss, Crss respectively. Lg, Ls and Ld are calculated.

Some of the assumptions are based on empirical rules and have proven to be correct in the past.

Gp and Zin can now be calculated:

100 – 450 MHz 250 W Power Amplifier with the BLF548 MOSFET

Application Note AN98021

$$Z_{in} = R_i + jX_i$$

$$G_p = 10 \cdot 10 \log (G_{fs}' \times R_{load} / \omega^2 \times L_s \times C_i)$$

with;

$$X_i = \omega \times L_i - 1 / (\omega \times C_i)$$

$$R_i = (G_{fs}' \times L_s) / C_i$$

$$L_i = L_q + (L_s \times C_{gs}) / C_i$$

$$C_i = C_{gs} + C_{gd} (1 + G_{fs}' \times R_{load})$$

$$\omega = 2 \pi f$$

Zload is chosen for maximum broadband capability.

Table 3 Calculated powergain, Zin and required Zload (series components)

F (MHz)	PL (W)	Gp (dB)	ZIN (Ω)	ZLOAD (Ω)
100	78.8	26.7	0.43 – j4.1	4.7 + j1.5
150	78.8	23.3	0.43 – j2.5	4.0 + j1.0
200	78.8	20.8	0.42 – j1.7	3.4 + j2.0
250	78.8	18.4	0.43 – j1.1	2.8 + j1.9
300	78.8	17.2	0.43 – j0.7	2.3 + j1.7
350	78.8	15.8	0.43 – j0.3	1.9 + j1.4
400	78.8	14.5	0.44 – j0.0	1.6 + j1.1
450	78.8	13.4	0.44 + j0.2	1.3 + j0.7
500	78.8	12.4	0.45 + j0.5	1.1 + j0.4

The data is also given in datahandbook “*RF power MOS transistors*” – Philips Components. It can be noticed that without any gaincompensation the powergain difference between 100 and 500 MHz will exceed 10 dB.

To terminate the transistor with the required loadimpedance, with respect to the broadband capability, the unbalanced 50 Ω load has to be transformed as close as possible to the loadimpedance as shown in Table 3. (Note: the impedances shown are based on one section, since the transistor is of a balanced type, Zin and Zload are related to virtual ground).

To reduce the number of components which would be needed in case of a lumped element solution, a coaxial semi-rigid balun is used to transform the unbalanced 50 Ω load into two 25 Ω sections that are 180° apart in phase and 90° away from virtual ground. This is followed by a coaxial 4 : 1 transformer, with a characteristic impedance of 25 Ω .

The result of this is: $R_p = (\sqrt{25 \times 25})/4 = 6.2 \Omega$, which is close to the required Rload of the transistor.

In order to give a good description of the outputnetwork, it will be described as a 3-port: one port terminated with 50 Ω unbalanced, the other two terminated with the transistor’s outputimpedance (the complex conjugate of loadimpedance). A computer listing of the outputnetwork is given in “Appendix A”. After optimizing the network to minimum returnloss (S11), while checking S13, the optimized return loss (in dB) of this network has been determined, see Fig.3. As a next step now the difference between the required and the network related loadimpedance can be (re-) calculated. The result on powergain (Gp) and imputimpedance (Zin) is given in Table 4.

100 – 450 MHz 250 W Power Amplifier with the BLF548 MOSFET

Application Note AN98021

Table 4 Result on Zin and Gp as a result of the presented outputmatching network

F (MHz)	PL (W)	Gp (dB)	ZIN (Ω)	ZLOAD (Ω)
100	78.6	32.7	$0.11 - j4.1$	$4.3 + j1.0$
150	78.8	19.7	$1.04 - j2.9$	$4.1 + j0.2$
200	78.8	17.3	$1.02 - j2.2$	$3.3 + j0.1$
250	78.8	16.0	$0.87 - j1.5$	$2.9 + j0.1$
300	78.8	14.9	$0.79 - j0.9$	$2.8 + j0.3$
350	78.8	13.5	$0.80 - j0.4$	$2.8 + j0.4$
400	78.8	12.4	$0.79 - j0.1$	$2.5 + j0.2$
450	78.8	12.0	$0.67 + j0.1$	$1.9 + j0.1$
500	72.0	12.4	$0.43 + j0.5$	$1.1 + j0.6$

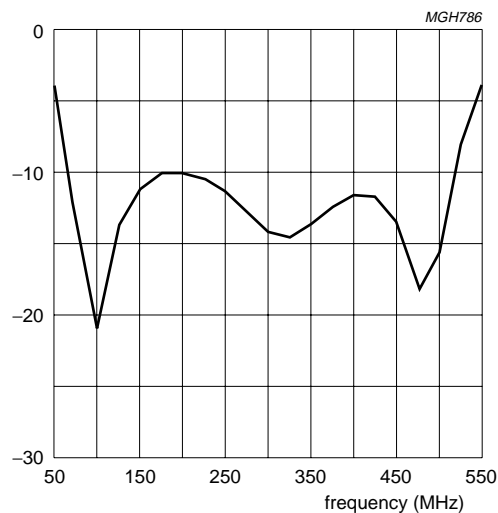


Fig.3 Simulated network response (output side).

4 INPUT CIRCUITRY

Since Zin and Gp are now determined in a accurate way, the inputcircuitry can be determined. Special attention is given to the flatness of the gain as a function of frequency. The input network also consists of a coaxial balun, followed by a 1 : 4 coaxial transformer, both made of semi-rigid coaxial cable. Since Zin is rather low the characteristic impedance of the 1 : 4 transformer was chosen to be 10 Ω .

The result of this is: $R_p = (\sqrt{25 \times 10})/4 = 3.9 \Omega$.

100 – 450 MHz 250 W Power Amplifier with the BLF548 MOSFET

Application Note AN98021

In order to compensate for the 6 dB/octave slope, matching to Z_{in} is achieved at 450 MHz. At lower frequencies a mismatch is created, resulting in a decrease of powergain inversely proportional to the increase of the gain related to the transistor's 6 dB/octave slope.

The network listing of the input circuitry, again presented as a 3-port, is given in "Appendix B". The network response (both input returnloss and predicted powergain) is given in Fig.4. Finally the schematic diagram and list of components are given in Fig.5. The unit's layout is given in Fig.6. Note: two toroidal cores around T2 and T3 are used to prevent oscillations.

5 ADJUSTMENT OF THE AMPLIFIER

5.1 Tuning the outputnetwork

In order to terminate the transistor with the proper load impedance, first the output network has to be tuned.

The transistor was replaced by a dummyload, representing the transistors output impedance under full power conditions. The dummyload was realized after fitting the data of Table 3. To the dummyload model (roughly R_{load} in parallel with C_{oss} , in series with draininductance L_d). Later the model was compensated for parasitics of both SOT262 header and network components.


Initial settings for each side of the dummyload are:

$$R_{load} = V_{ds}^2 / 2 \times P_I = 5.2 \Omega$$

$$C = 1.15 \times C_{oss} = 104 \text{ pF}$$

$$L = L_d = 0.5 \text{ nH}$$

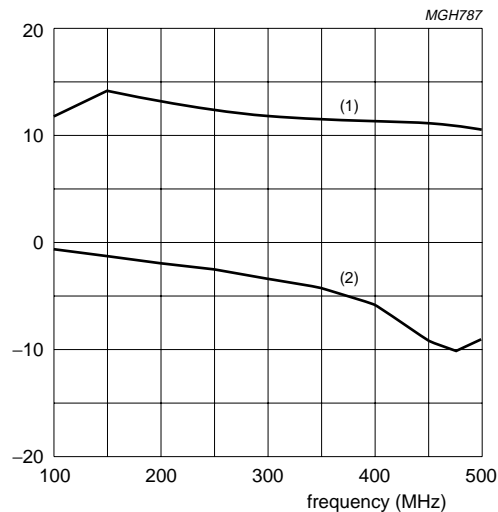The network listing is given in "Appendix C". The final result, the dummyload lay-out, is given in Fig.7.



(1) DB [S12].

(2) DB [S22].

Fig.4 Simulated network response of inputside (predicted $G_p = f(f)$).

100 – 450 MHz 250 W Power Amplifier
with the BLF548 MOSFET

Application Note
AN98021

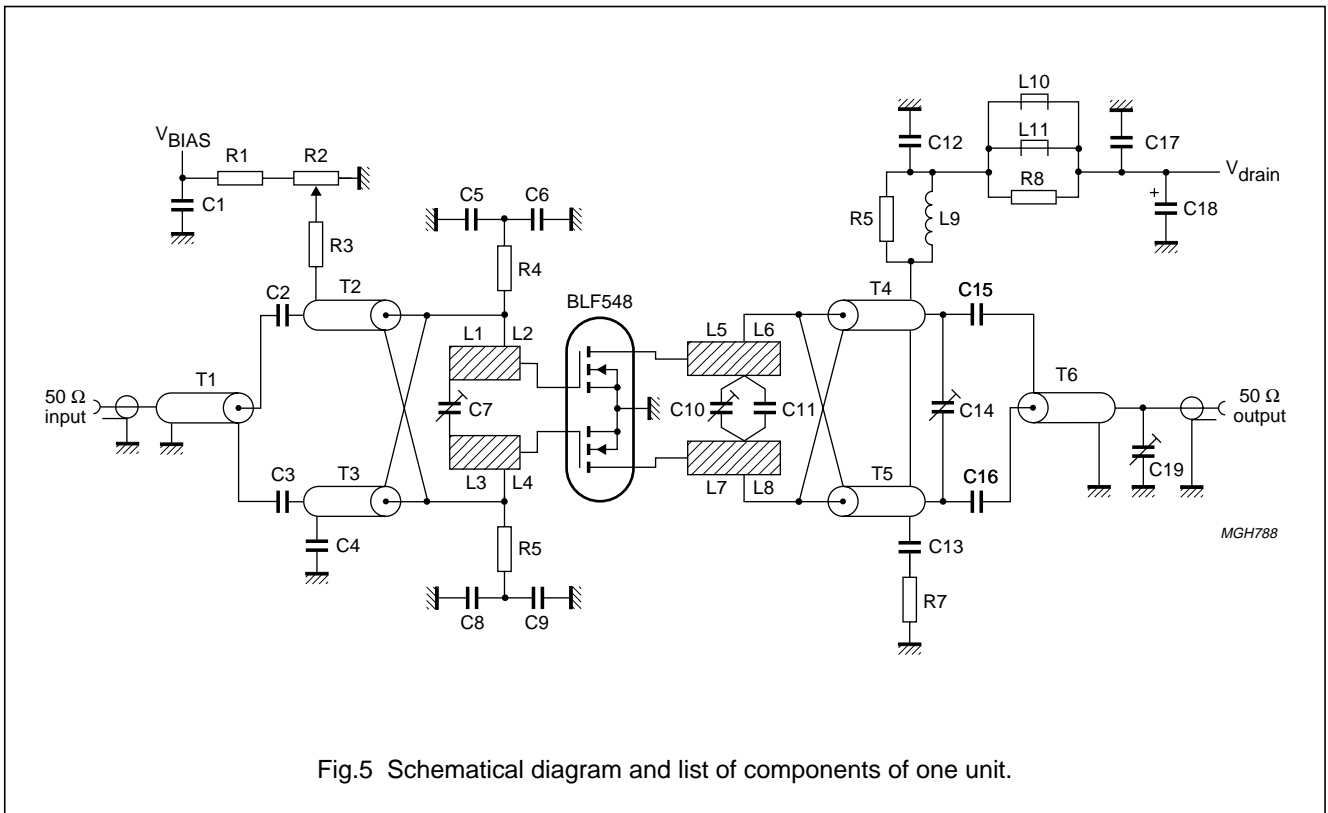


Fig.5 Schematical diagram and list of components of one unit.

100 – 450 MHz 250 W Power Amplifier with the BLF548 MOSFET



Application Note AN98021

List of components

DESIGNATION	DESCRIPTION	VALUE	DIMENSIONS	CATALOGUE NO.
C1, C17	multilayer ceramic chip capacitor	100 nF		2222 852 47104
C2, C3	multilayer ceramic chip capacitor (note 1)	47 pF		
C4, C5, C8	multilayer ceramic chip capacitor (note 1)	820 pF		
C6, C9	multilayer ceramic chip capacitor (note 1)	300 pF		
C7	film dielectric trimmer	2-18 pF		2222 809 09006
C10, C14	film dielectric trimmer	2-9 pF		2222 809 09005
C11	multilayer ceramic chip capacitor (note 2)	39 pF		
C12	capacitor	22 nF		
C13	capacitor	100 nF		
C15, C16	multilayer ceramic chip capacitor (note 1)	120 pF		
C18	63 V electrolytic capacitor	1 μ F		2222 685 78108
C19	film dielectric trimmer	1-5 pF		222 808 09004
L1, L3	stripline (note 3)	20 Ω	5 \times 8 mm	
L2, L4	stripline (note 3)	20 Ω	2.5 \times 8 mm	
L5, L7	stripline (note 3)	20 Ω	11.5 \times 8 mm	
L6, L8	stripline (note 3)	20 Ω	4 \times 8 mm	
L9	5 turns enamelled Cu wire on R6		1.4 mm	
L10, L11	grade 3B Ferroxcube wideband RF choke			4330 030 36642
T1	semi-rigid coax (note 4)	50 Ω	length 54 mm	
T2, T3	semi-rigid coax (note 4)	10 Ω	length 44 mm	
T4, T5	semi-rigid coax	25 Ω	length 53 mm	
T6	semi-rigid coax	50 Ω	length 74 mm	
R1	0.4 W metal film resistor	19.6 k Ω		2322 151 11963
R2	10 turn potentiometer	5 k Ω		2122 362 00725
R3, R4, R5	0.4 W metal film resistor	2.05 k Ω		2322 151 12052
R6, R7, R8	1.0 W metal film resistor	10 Ω		2322 153 71009

Notes

1. American Technical Ceramics type 100B or capacitor of same quality.
2. American Technical Ceramics type 175B or capacitor of same quality.
3. The striplines are on a double copper-clad PCB with P.T.F.E. fibre-glass dielectric ($\epsilon_r = 2.2$); thickness 1/32 inch.
4. T2 and T3 are equipped with a Toroidal core, grade 4C6 (cat.no. 4322 020 97171).

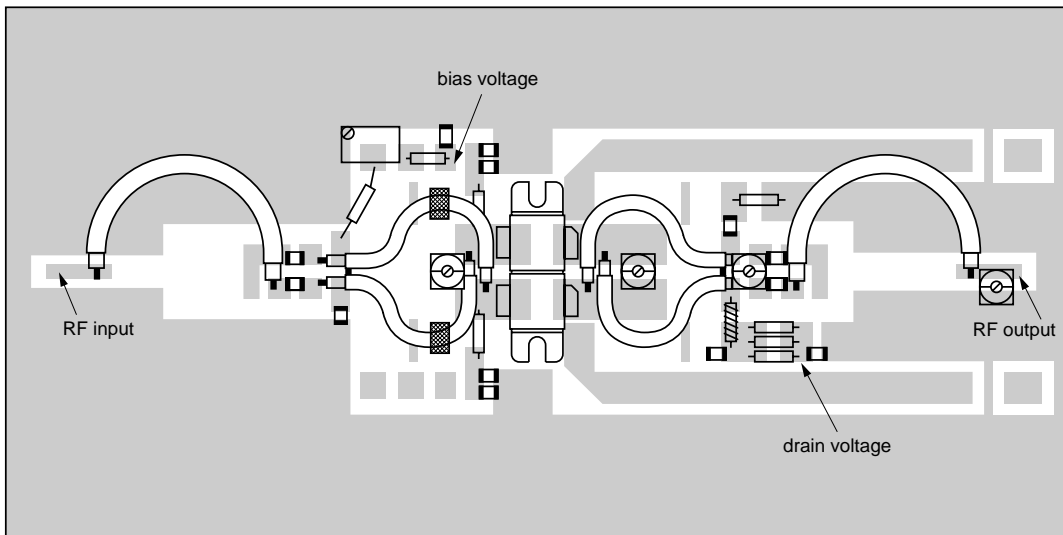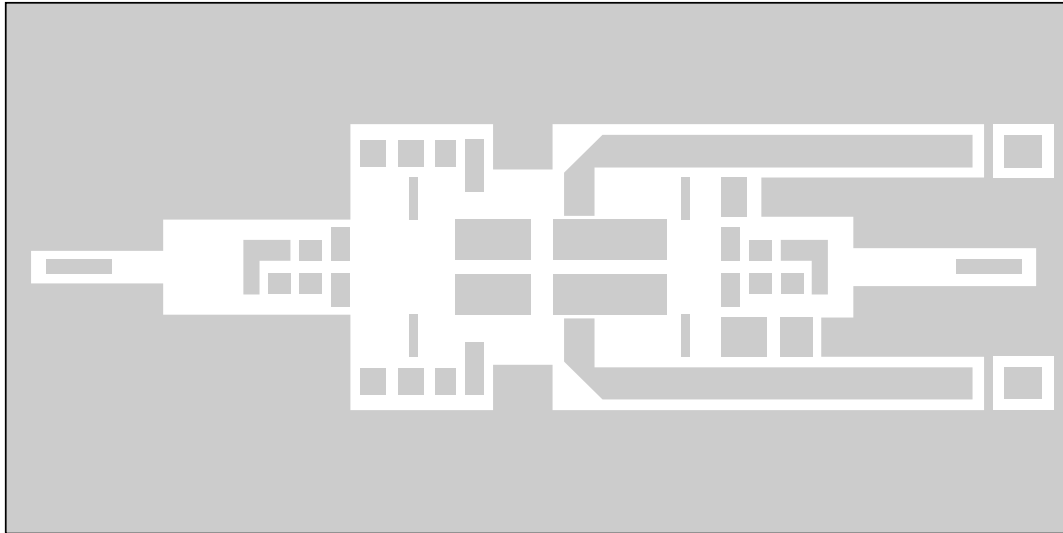

MGH789

Fig.6 Lay-out of one unit.

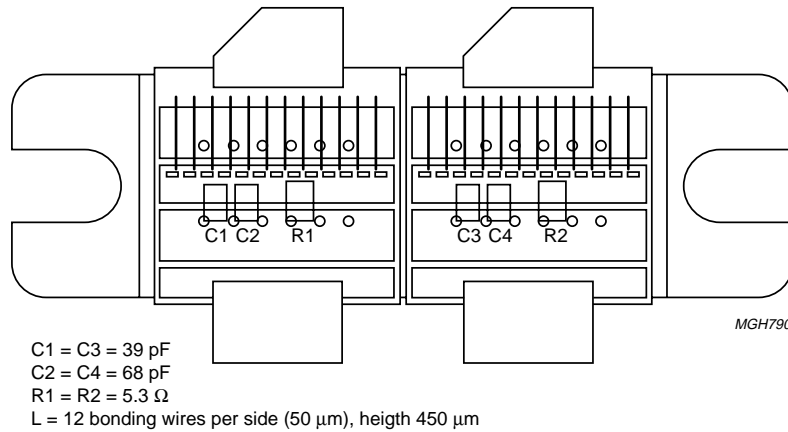


Fig.7 Lay-out of BLF548 dummyload.

By means of a RF-analyzer the predicted frequency response of the network can be reproduced in practice, while tuning C10 and C14 for optimum R1. This is presented in Fig.8. A comparison with the simulated networkresponse (Fig.3) shows a high amount of common behaviour.


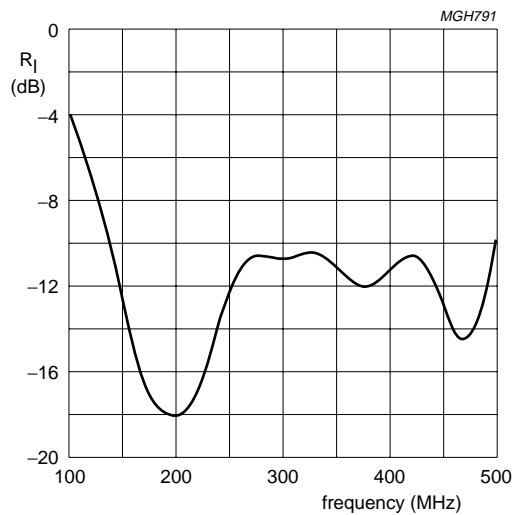


Fig.8 Measured network response of one unit after tuning C10 and C14.

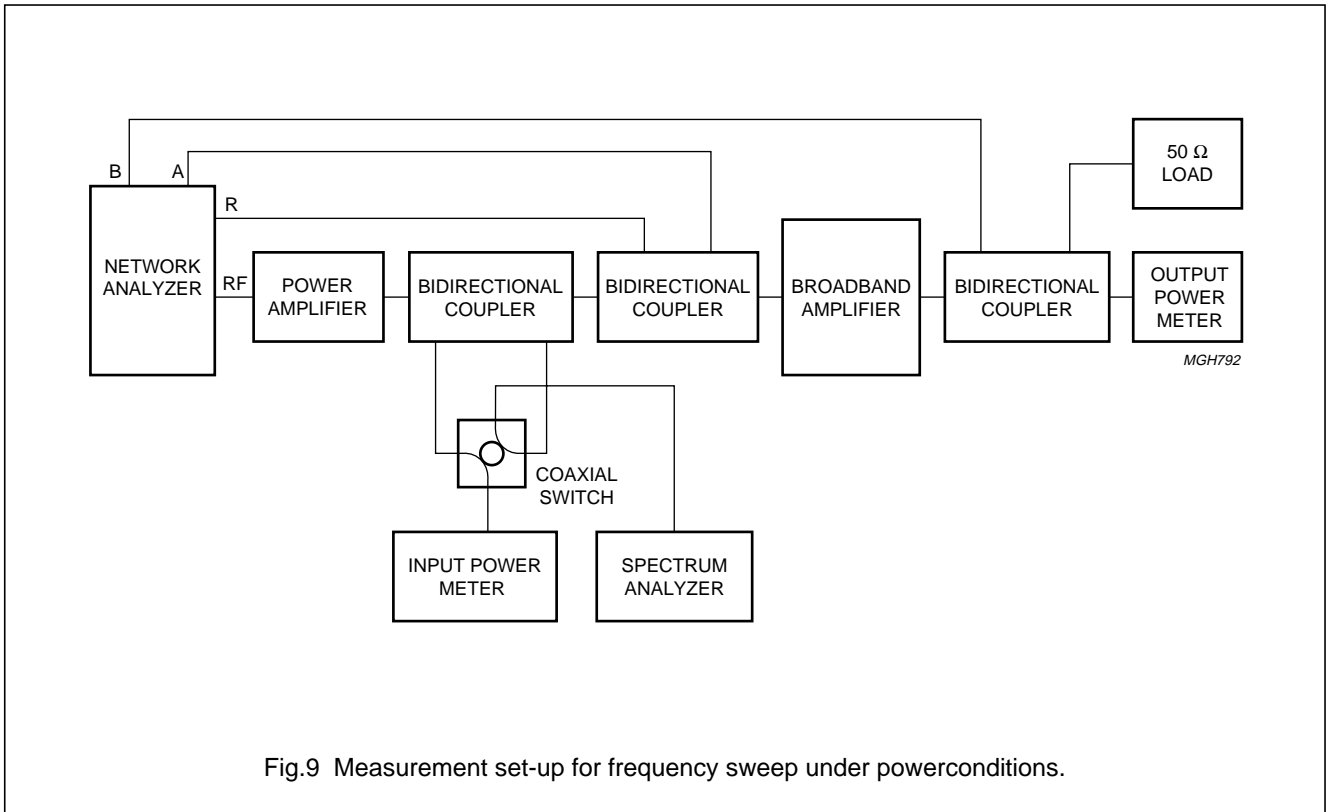
5.2 Testing the unit under RF conditions

After exchanging the dummyload for a BLF548, a frequencysweep under power conditions can be made with help of a network analyzer. The used measurement set-up is given in Fig.9.



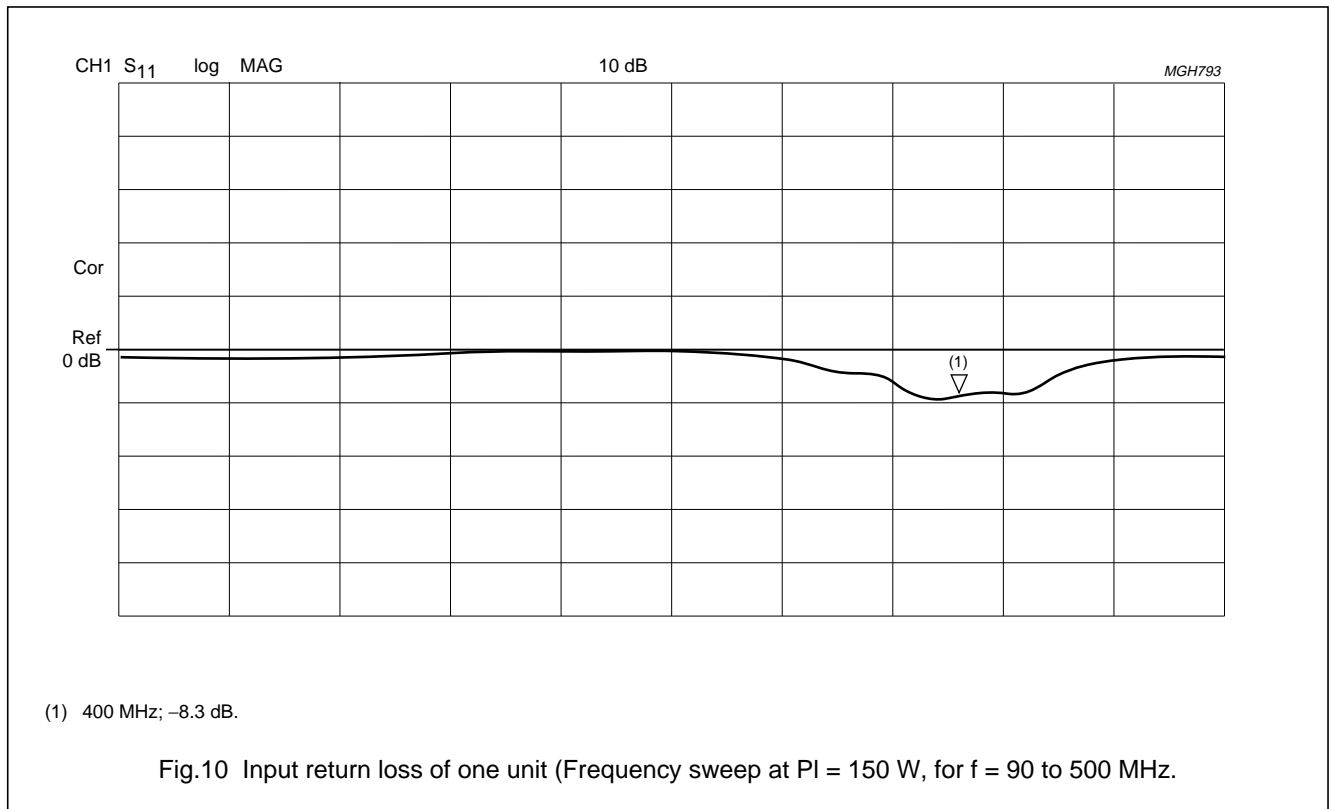
5.3 Tuning the unit's inputnetwork

After supplying both the bias- and drain voltages to the unit and adjusting the drain quiescent current with R2 to 320 mA (160 mA per side), the inputpower (Ps) is applied. Gainflatness is optimized while tuning C7. The unit's input returnloss is given in Fig.10. PI versus frequency is shown in Fig.11. A comparison with the simulated network response of the inputside (Fig.4) shows a high similarity. Gainflatness within 1 dB is achieved between 100 and 450 MHz.



100 – 450 MHz 250 W Power Amplifier with the BLF548 MOSFET

Application Note AN98021

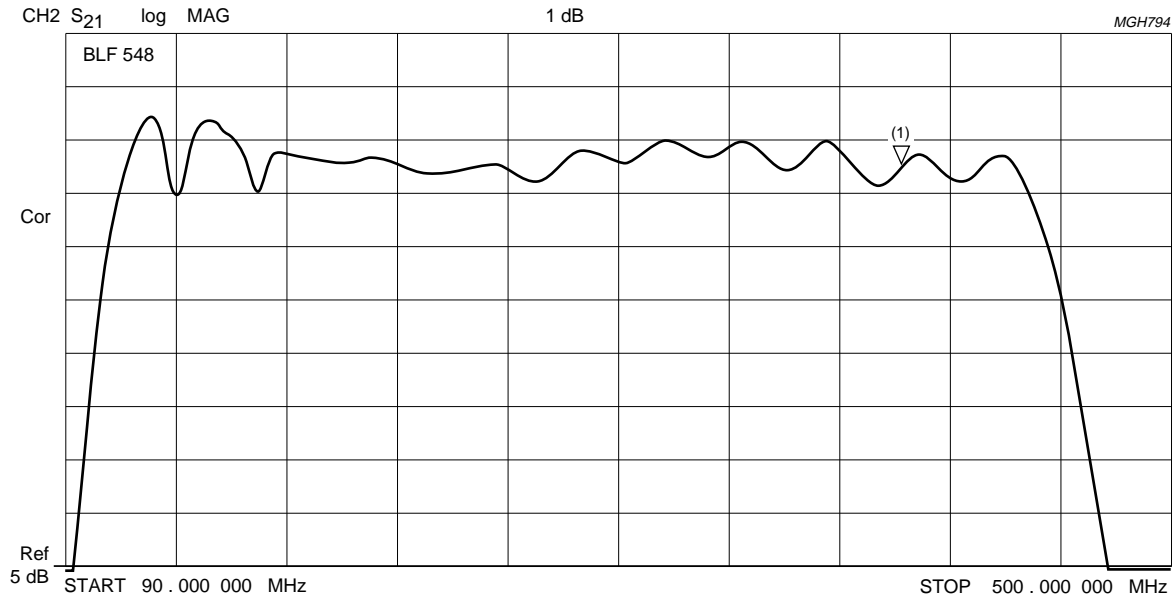



(1) 400 MHz; 12.526 dB.

Fig.11 Powergain of one unit (Frequency sweep at P_I = 150 W, for f = 90 to 500 MHz).

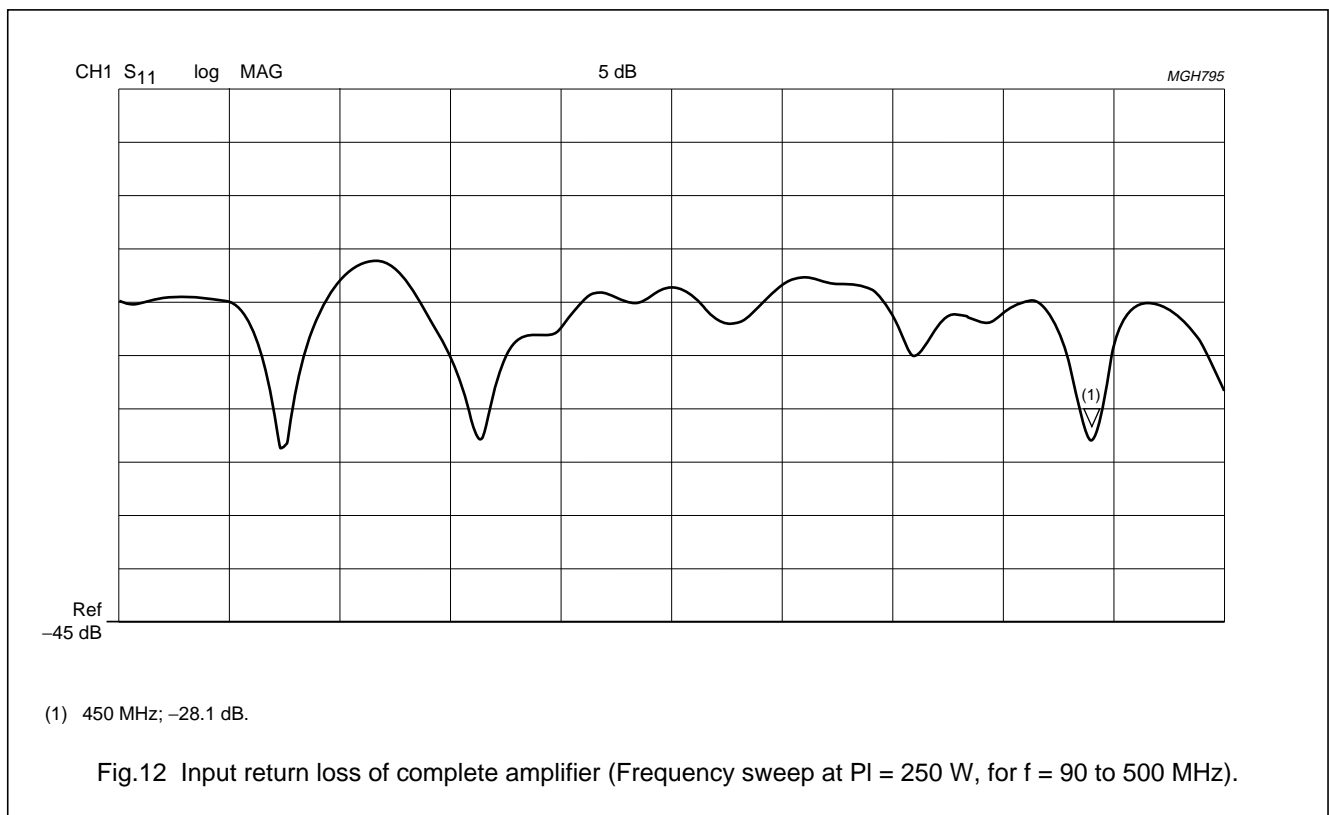5.4 Combining the units

After tuning the second unit similar as described above, the connection was made to the 90° hybrid couplers. The couplers do contain 4 ports, one at which the input signal is applied (1). The input is divided equally into two ports (3 and 4). Between ports 3 and 4 there is a voltage lag of 90°. Mismatch at ports 3 and 4 do not effect the VSWR of port 1, since port 2 is terminated with a 50 Ω load (KDI-PPT820-75-3 flange mounted). At the output side of the amplifier the units are combined in a similar way. Both input and output hybrids and 50 Ω loads are mounted in a Brass baseplate (dimensions; 200 × 160 × 10 mm), which also serves as a heatspreader for both BLF548 devices. The baseplate is connected to a heatsink which is cooled by means of forced air. Final results are given in Fig.12. (input return loss of the amplifier) and Fig.13 (the amplifier's powergain).



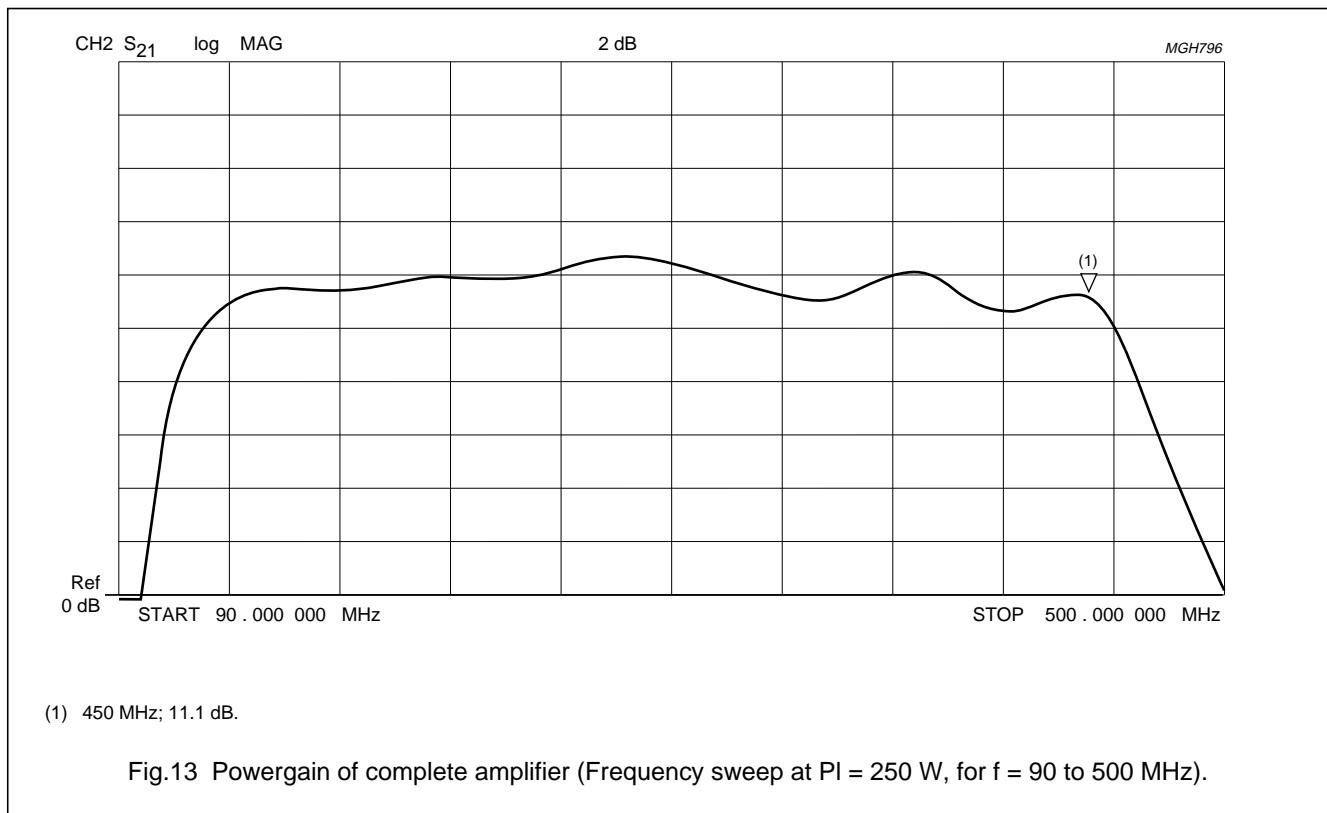

6 CONCLUSIONS

The described procedures shown in this paper, are a great help in designing high-power broadband amplifiers. The differences between theory and practice are relatively small.

The BLF548 is very well suited to perform in multi-octave broadband UHF-amplifiers; at a supply voltage of 28 V, between 100 and 450 MHz, 250 W of outputpower could be generated with a powergain of 11 dB (gainripple smaller than 1 dB). Drainefficiency is 45 to 55% throughout the band. The reduction of the second harmonic is more than 25 dB, with respect to the fundamental. The input returnloss is better than -12 dB.

7 REFERENCES

- Data Handbook SC08b, RF power MOS transistors – Philips Components
- Application Report Bipolar & MOS transmitting transistors – Philips Components
- A look inside those integrated two-chip amps – Joe Johnson – Microwaves feb. 1980
- Apply wideband techniques to balanced amplifiers – Lee B. Max – Microwaves apr. 1980
- Demystifying new generation silicon high power FETs – Steve McIntyre – Microwave Journal apr. 1984
- Anaren – Microwave components catalog no.17A.

100 – 450 MHz 250 W Power Amplifier
with the BLF548 MOSFET

Application Note
AN98021

8 APPENDIX A

DIM

FREQ MHz
RES OH
IND NH
CAP PF
LNG MM

VAR

C1 = 120 !c = 270
L2 = 74 !50
L3 = 53 !50
L10 = 9 !9
L11 = 0.350559 !0.5
R11 = 4.191123 !5.1
C11 = 64.2821 !75
4
L12 = 0.409981 !0.31
W1 = 6
L22 = 10
L33 = 66

CKT

RES 1 0 R = 50
DEFIP 1 REFIMP
S1PA 2 0 BLF548OU
DEF1P 2 BALI
IND 1 2 L^L11
RES 2 0 R^R11
SLC 2 0 L^L12; !to determine zload
C^C11
DEFIP 1 BAL3
SLC 1 0 L = 0.5
C = 4 !13.5
COAX 1 2 0 3 DI = 0.91; TAND = 0.0002;
DO = 2.98; RHO = 1
L^L3;
ER = 2.03
MSUB ER = 2.2; T = 0.035 RHO = 0.72;
H = 0.79 RGH = 1
SLC 2 4 L = 0.5; C^cl
SLC 3 5 L = 0.5; C^cl
COAX 4 6 0 8 DI = 1.63 DO = 2.95; L^L2
ER = 2.03;
TAND = 0.0002;
RHO = 1
COAX 5 8 0 6 DI = 1.63 DO = 2.95; L^L2;
ER = 2.03;
TAND = 0.0002;
RHO = 1
SLC 6 8 L = 0.5; IC = 41
C = 41
SLC 6 8 L = 0.7; IC = 0
C = 8
MLIN 919 w^w1;
1^122

MLIN 10 20 w^w1;
1^122
MBEND3 19 29 w^w1
MBEND3 20 30 w^w1
MLIN 29 0 w^w1;
1^133
MLIN 30 0 w^w1;
1^133
MCLIN 6 8 9 10 W = 8; !L = 13
S = 2.5;
L = 12
SLC 9 10 L = 0.5; !C = 5
C = 3
DEF3P 1 9 10 TRAFO !OUTPUT
NETWORK
BAL2 2 0
TRAFO 3 1 2 0
DEF2P 1 3 IMP2
BAL1 1 0
BAL1 2 0
TRAFO 3 1 2 0
DEFIP 3 IMP
FREQ
SWEEP 50 550 25
OUT
IMP RE(Z1)
IMP IM(Z1)
IMP DB(S11) GR1
IMP S11 SC2
!IMP VSWR1
BAL3 RE(Z1) !TO
DETERMIN
E
BAL3 IM(Z1) !ZLOAD
IMP2 DB(S12)
GRID
RANGE 50 550 50
GR1 -30 0 5
TERM
IMP2 BAL1 !50 Ω
REFIMP PORT1
OPT
RANGE 50 550
!IMP VSWR1 <
1.6
IMP MODEL
REFIMP

Note

- Slp file BLF5480U does contain data given in "Appendix C".

100 – 450 MHz 250 W Power Amplifier with the BLF548 MOSFET

Application Note AN98021

9 APPENDIX B

Input BLF548 application (300 W/28 V/500 MHz); input in 1P file fit between 100 – 500 MHz with 1 : 4 transformer ($Z_c = 10 \Omega$) to determine G_p and input VSWR Z_{IN} and G_p data derived from calculations, which represent the performance of the device after applying the output Network, given in "Appendix A" to IT.

Table 5

DIM				COAX	5 8 7 6	DI = 1.15; DO = 1.45; L^L2; ER = 2.03; TAND = 0.0002	RHO = 1
FREQ	MHZ			UNIT	7 0		
RES	OH			SLC	6 8	L = 0.5; C\0.103064 IC - 2.1	
IND	NH			MCLIN	6 8 9 10	W = 8; S = 2.5; L\3.05628 0	
CAP	PF			SLC	9 10	L = 0.5; C\0.923788; !c - 3.5	
LNG	MM			DEF3P	1 9 10	TRAFO	INPUT NETWORK
VAR				BALI	2 0		
C1\57.83880	!C = 27			TRAFO	3 5 4 0		
L2\64.28568	!L = 25			GPAF	4 2		
L3 = 55	!L = 25			GPAF	5 1		
R11 = 0.00020	!4.1			DEF2P	1 3	IMP2	!TO DETERMINE S11, S12
7							
C11 = 241.805	!65						
9							
L12 = 0.00004	!0.41						
8							
CKT							
RES	1 0	R = 50					
DEF1P	1	REFIMP	!50 Ω LOAD				
S1PA	2 0	BLF54812		FREQ			
DEF1P	2	BAL1	!BLF548's Z_{in}	SWEEP	100 500 25		
RES	1 2	R^R11		OUT			
SLC	2 0	L^L12; C^C11		IMP2 TE(Z2)			
DEF1P	1	BAL3		IMP2 IM(Z2)			
GAIN	1 2	A = 22.65; S = -4.79; F = 150	!Gp DATA DERIVED FROM	IMP2 DB(S22)	GR1	!S11 AT 50 Ω PORT	
GAIN	2 3	A = 0; S = 0.5; F = 350	!Table 3	IMP2 DB(S12)	GR1	!CALCULATED POWERGAIN	
GAIN	3 4	A = 0; S = 1.5; F = 400	!13 dB GAINCORRE CTION SINCE	IMP2 VSWR2			
DEF2P	1 3	GPAF	!2 SECTIONS ARE INVOLVED	GPAF DB(S21)	!BLF548's GP		
SLC	1 0	L = 0.5; C\0.016169 !2		GRID			
COAX	1 2 0 3	DI = 0.91; DO = 2.98	L^L3; ER = 2.03; TAND = 0.000 2; RHO = 1	RANGE	100 500 25		
MSUB		ER = 2.2; H = 0.79; T = 0.035; RHO = 0.72; RHG = 1		GRI	-20 20 5		
SLC	2 4	L = 0.5 C^cl		TERM			
SLC	3 5	L = 0.5 C^cl		IMP2 BAL1			
COAX	4 6 7 8	DI = 1.15; DO = 1.45; L^L2; ER = 2.03; TAND = 0.0002	RHO = 1	REFIMP			
				OPT			
				RANGE	150 550		
				IMP2	DB(S12) > 11		
				IMP2	DB(S12) < 12.4		
				Note			
				1. S1p file BLF548I2 does contain data given in Table 4. Format as shown in "Appendix C".			

100 – 450 MHz 250 W Power Amplifier
with the BLF548 MOSFET

Application Note
AN98021

10 APPENDIX C

Fit dummyloadmodel to calculated BLF548 Zoutput !Filename: E:\users\blf548ou.s1p
!reference: calculated data derived from transmod program;!Zload converted to Zoutput

					MOD	IM(Z1)			
DIM					MES	RE(Z1)			
FREQ	GHZ				MES	IM(Z1)			
RES	OH				OPT				
IND	NH				MOD	MES			
CAP	PF				MODEL				
LNG	MM								
CKT					Table 6				
MSUB	ER = 6.5	H = 1.02; T = 0.035 ; RHO = 1; RGH = 0			# GHz	RI	R 1		
					Z			! freq	R1 X1
					0.050	5.26	-0.86		
					0.075	5.04	-1.22		
IND	1 0	L = 0.168		!inductance to ground	0.100	4.73	-1.51		
					0.125	4.39	-1.73		
					0.150	4.04	-1.87		
RES	1 2	R = 5.280			0.175	3.70	-1.94		
					0.200	3.36	-1.95		
SLC	1 2	L = 0.3	C = 40		0.225	3.05	-1.92		
SLC	1 2	L = 0.3	C\65.8		0.250	2.76	-1.85		
CAP	2 0	C = 1			0.275	2.50	-1.75		
IND	2 3	L = 0.165		!bonding wires at drainside	0.300	2.27	-1.63		
					0.325	2.06	-1.50		
MLIN	3 4	W = 10.8	L = 1.6	!metallization of header	0.350	1.87	-1.35		
					0.375	1.71	-1.21		
DEF1p	4	MOD		!1-port of dummyload	0.400	1.56	-1.05		
					0.425	1.43	-0.90		
					0.450	1.31	-0.74		
S1PA	1 0	BLF5480 U.s1p		!calculated z-parameters of	0.475	1.21	-0.59		
					0.500	1.11	-0.43		
					0.525	1.03	-0.28		
					0.550	0.95	-0.13		
DEF1p	1	MES		!BLF548 output impedances					
FREQ					Note				
SWEEP	0.1	0.5	.050		1. Zload is derived from data given in Fig.3.				
OUT									
MOD	RE(Z1)								

Philips Semiconductors – a worldwide company

Argentina: see South America

Australia: 34 Waterloo Road, NORTH RYDE, NSW 2113,
Tel. +61 2 9805 4455, Fax. +61 2 9805 4466

Austria: Computerstr. 6, A-1101 WIEN, P.O. Box 213, Tel. +43 160 1010,
Fax. +43 160 101 1210

Belarus: Hotel Minsk Business Center, Bld. 3, r. 1211, Volodarski Str. 6,
220050 MINSK, Tel. +375 172 200 733, Fax. +375 172 200 773

Belgium: see The Netherlands

Brazil: see South America

Bulgaria: Philips Bulgaria Ltd., Energoproject, 15th floor,
51 James Bourchier Blvd., 1407 SOFIA,
Tel. +359 2 689 211, Fax. +359 2 689 102

Canada: PHILIPS SEMICONDUCTORS/COMPONENTS,
Tel. +1 800 234 7381

China/Hong Kong: 501 Hong Kong Industrial Technology Centre,
72 Tat Chee Avenue, Kowloon Tong, HONG KONG,
Tel. +852 2319 7888, Fax. +852 2319 7700

Colombia: see South America

Czech Republic: see Austria

Denmark: Prags Boulevard 80, PB 1919, DK-2300 COPENHAGEN S,
Tel. +45 32 88 2636, Fax. +45 31 57 0044

Finland: Sinikalliontie 3, FIN-02630 ESPOO,
Tel. +358 9 615800, Fax. +358 9 61580920

France: 51 Rue Carnot, BP317, 92156 SURESNES Cedex,
Tel. +33 1 40 99 6161, Fax. +33 1 40 99 6427

Germany: Hammerbrookstraße 69, D-20097 HAMBURG,
Tel. +49 40 23 53 60, Fax. +49 40 23 536 300

Greece: No. 15, 25th March Street, GR 17778 TAVROS/ATHENS,
Tel. +30 1 4894 339/239, Fax. +30 1 4814 240

Hungary: see Austria

India: Philips INDIA Ltd, Band Box Building, 2nd floor,
254-D, Dr. Annie Besant Road, Worli, MUMBAI 400 025,
Tel. +91 22 493 8541, Fax. +91 22 493 0966

Indonesia: see Singapore

Ireland: Newstead, Clonskeagh, DUBLIN 14,
Tel. +353 1 7640 000, Fax. +353 1 7640 200

Israel: RAPAC Electronics, 7 Kehilat Saloniki St, PO Box 18053,
TEL AVIV 61180, Tel. +972 3 645 0444, Fax. +972 3 649 1007

Italy: PHILIPS SEMICONDUCTORS, Piazza IV Novembre 3,
20124 MILANO, Tel. +39 2 6752 2531, Fax. +39 2 6752 2557

Japan: Philips Bldg 13-37, Kohnan 2-chome, Minato-ku, TOKYO 108,
Tel. +81 3 3740 5130, Fax. +81 3 3740 5077

Korea: Philips House, 260-199 Itaewon-dong, Yongsan-ku, SEOUL,
Tel. +82 2 709 1412, Fax. +82 2 709 1415

Malaysia: No. 76 Jalan Universiti, 46200 PETALING JAYA, SELANGOR,
Tel. +60 3 750 5214, Fax. +60 3 757 4880

Mexico: 5900 Gateway East, Suite 200, EL PASO, TEXAS 79905,
Tel. +9-5 800 234 7381

Middle East: see Italy

Netherlands: Postbus 90050, 5600 PB EINDHOVEN, Bldg. VB,
Tel. +31 40 27 82785, Fax. +31 40 27 88399

New Zealand: 2 Wagener Place, C.P.O. Box 1041, AUCKLAND,
Tel. +64 9 849 4160, Fax. +64 9 849 7811

Norway: Box 1, Manglerud 0612, OSLO,
Tel. +47 22 74 8000, Fax. +47 22 74 8341

Philippines: Philips Semiconductors Philippines Inc.,
106 Valero St. Salcedo Village, P.O. Box 2108 MCC, MAKATI,
Metro MANILA, Tel. +63 2 816 6380, Fax. +63 2 817 3474

Poland: Ul. Lukiska 10, PL 04-123 WARSZAWA,
Tel. +48 22 612 2831, Fax. +48 22 612 2327

Portugal: see Spain

Romania: see Italy

Russia: Philips Russia, Ul. Usatcheva 35A, 119048 MOSCOW,
Tel. +7 095 755 6918, Fax. +7 095 755 6919

Singapore: Lorong 1, Toa Payoh, SINGAPORE 1231,
Tel. +65 350 2538, Fax. +65 251 6500

Slovakia: see Austria

Slovenia: see Italy

South Africa: S.A. PHILIPS Pty Ltd., 195-215 Main Road Martindale,
2092 JOHANNESBURG, P.O. Box 7430 Johannesburg 2000,
Tel. +27 11 470 5911, Fax. +27 11 470 5494

South America: Al. Vicente Pinzon, 173, 6th floor,
04547-130 SÃO PAULO, SP, Brazil,
Tel. +55 11 821 2333, Fax. +55 11 821 2382

Spain: Balmes 22, 08007 BARCELONA,
Tel. +34 3 301 6312, Fax. +34 3 301 4107

Sweden: Kottbygatan 7, Akalla, S-16485 STOCKHOLM,
Tel. +46 8 632 2000, Fax. +46 8 632 2745

Switzerland: Allmendstrasse 140, CH-8027 ZÜRICH,
Tel. +41 1 488 2686, Fax. +41 1 488 3263

Taiwan: Philips Semiconductors, 6F, No. 96, Chien Kuo N. Rd., Sec. 1,
TAIPEI, Taiwan Tel. +886 2 2134 2865, Fax. +886 2 2134 2874

Thailand: PHILIPS ELECTRONICS (THAILAND) Ltd.,
209/2 Sanpavuth-Bangna Road Prakanong, BANGKOK 10260,
Tel. +66 2 745 4090, Fax. +66 2 398 0793

Turkey: Talatpasa Cad. No. 5, 80640 GÜLTEPE/ISTANBUL,
Tel. +90 212 279 2770, Fax. +90 212 282 6707

Ukraine: PHILIPS UKRAINE, 4 Patrice Lumumba str., Building B, Floor 7,
252042 KIEV, Tel. +380 44 264 2776, Fax. +380 44 268 0461

United Kingdom: Philips Semiconductors Ltd., 276 Bath Road, Hayes,
MIDDLESEX UB3 5BX, Tel. +44 181 730 5000, Fax. +44 181 754 8421

United States: 811 East Arques Avenue, SUNNYVALE, CA 94088-3409,
Tel. +1 800 234 7381

Uruguay: see South America

Vietnam: see Singapore

Yugoslavia: PHILIPS, Trg N. Pasica 5/v, 11000 BEOGRAD,
Tel. +381 11 625 344, Fax. +381 11 635 777

For all other countries apply to: Philips Semiconductors,
International Marketing & Sales Communications, Building BE-p, P.O. Box 218,
5600 MD EINDHOVEN, The Netherlands, Fax. +31 40 27 24825

Internet: <http://www.semiconductors.philips.com>

© Philips Electronics N.V. 1998

SCA57

All rights are reserved. Reproduction in whole or in part is prohibited without the prior written consent of the copyright owner.

The information presented in this document does not form part of any quotation or contract, is believed to be accurate and reliable and may be changed without notice. No liability will be accepted by the publisher for any consequence of its use. Publication thereof does not convey nor imply any license under patent- or other industrial or intellectual property rights.

Printed in The Netherlands

Date of release: 1998 Mar 23

Let's make things better.

**Philips
Semiconductors**



PHILIPS

SUNSTAR 商斯达实业集团是集研发、生产、工程、销售、代理经销、技术咨询、信息服务等为一体的高科技企业，是专业高科技电子产品生产厂家，是具有 10 多年历史的专业电子元器件供应商，是中国最早和最大的仓储式连锁规模经营大型综合电子零部件代理分销商之一，是一家专业代理和分销世界各大品牌 IC 芯片和电子元器件的连锁经营综合性国际公司，专业经营进口、国产名厂名牌电子元件，型号、种类齐全。在香港、北京、深圳、上海、西安、成都等全国主要电子市场设有直属分公司和产品展示展销窗口门市部专卖店及代理分销商，已在全国范围内建成强大统一的供货和代理分销网络。我们专业代理经销、开发生产电子元器件、集成电路、传感器、微波光电元器件、工控机/DOC/DOM 电子盘、专用电路、单片机开发、MCU/DSP/ARM/FPGA 软件硬件、二极管、三极管、模块等，是您可靠的一站式现货配套供应商、方案提供商、部件功能模块开发配套商。商斯达实业公司拥有庞大的资料库，有数位毕业于著名高校——有中国电子工业摇篮之称的西安电子科技大学（西军电）并长期从事国防尖端科技研究的高级工程师为您精挑细选、量身订做各种高科技电子元器件，并解决各种技术问题。

微波光电部专业代理经销高频、微波、光纤、光电元器件、组件、部件、模块、整机；电磁兼容元器件、材料、设备；微波 CAD、EDA 软件、开发测试仿真工具；微波、光纤仪器仪表。欢迎国外高科技微波、光纤厂商将优秀产品介绍到中国、共同开拓市场。长期大量现货专业批发高频、微波、卫星、光纤、电视、CATV 器件：晶振、VCO、连接器、PIN 开关、变容二极管、开关二极管、低噪晶体管、功率电阻及电容、放大器、功率管、MMIC、混频器、耦合器、功分器、振荡器、合成器、衰减器、滤波器、隔离器、环行器、移相器、调制解调器；光电子元件和组件：红外发射管、红外接收管、光电开关、光敏管、发光二极管和发光二极管组件、半导体激光二极管和激光器组件、光电探测器和光接收组件、光发射接收模块、光纤激光器和光放大器、光调制器、光开关、DWDM 用光发射和接收器件、用户接入系统光收发器件与模块、光纤连接器、光纤跳线/尾纤、光衰减器、光纤适配器、光隔离器、光耦合器、光环行器、光复用器/转换器；无线收发芯片和模组、蓝牙芯片和模组。

更多产品请看本公司产品专用销售网站：

商斯达中国传感器科技信息网：<http://www.sensor-ic.com/>

商斯达工控安防网：<http://www.pc-ps.net/>

商斯达电子元器件网：<http://www.sunstare.com/>

商斯达微波光电产品网：[HTTP://www.rfoe.net/](http://www.rfoe.net/)

商斯达消费电子产品网：<http://www.icasic.com/>

商斯达实业科技产品网：<http://www.sunstars.cn/> 微波元器件销售热线：

地址：深圳市福田区福华路福庆街鸿图大厦 1602 室

电话：0755-82884100 83397033 83396822 83398585

传真：0755-83376182 (0) 13823648918 MSN: SUNS8888@hotmail.com

邮编：518033 E-mail:szss20@163.com QQ: 195847376

深圳赛格展销部：深圳华强北路赛格电子市场 2583 号 电话：0755-83665529 25059422

技术支持：0755-83394033 13501568376

欢迎索取免费详细资料、设计指南和光盘；产品凡多，未能尽录，欢迎来电查询。

北京分公司：北京海淀区知春路 132 号中发电子大厦 3097 号

TEL: 010-81159046 82615020 13501189838 FAX: 010-62543996

上海分公司：上海市北京东路 668 号上海赛格电子市场 D125 号

TEL: 021-28311762 56703037 13701955389 FAX: 021-56703037

西安分公司：西安高新开发区 20 所(中国电子科技集团导航技术研究所)

西安劳动南路 88 号电子商城二楼 D23 号

TEL: 029-81022619 13072977981 FAX:029-88789382