



PHILIPS

Philips Semiconductors B.V.

Low cost DECT Power Amplifier PH97005

Preliminary Application Note
RNR-T45-97-M-0931

Author

L.C. Colussi

November 21, 1997

Discrete Semiconductors Nijmegen
Gerstweg 2, 6534 AE Nijmegen
The Netherlands

Keywords

PA, DECT, DPO, BFG425W, BFG21W

Abstract

Application of new 5th generation discrete bipolar RF transistors facilitates design of a low cost two-stage power amplifier for DECT systems, having a power gain of 26 dB and an overall efficiency better than 40%. The amplifier operates from a single supply voltage, includes bias circuitry for load power adjustment and on/off switching and is mounted on a bilayer pcb, requiring 10 x 20 mm. A description is given of the circuit design and the board layout, including measurement results.

INTRODUCTION

This note describes the application of two of the new 5th generation silicon bipolar RF transistors in SOT343R plastic SMD package in a two-stage power amplifier (PA), designed for use in DECT cordless telephone systems. These transistors, manufactured according to the new *double-poly* process, are characterised by their high transition frequency ($f_T > 20$ GHz) at low supply voltages, resulting in a superior power gain at microwave frequencies, usually a field dedicated to GaAs-devices. Two layers of polysilicon are used: one for contacting the base, yielding a low base resistance and one to form the emitter, resulting in a steep emitter dope profile and an effective emitter width of 0.5 μm . A buried N-layer (collector) is placed within a P-substrate, which is connected to the emitter package lead, which enables the die to be placed on the ground plane, reducing emitter inductance and thermal resistance. Figure 1 shows a cross section of a *double-poly* buried layer transistor.

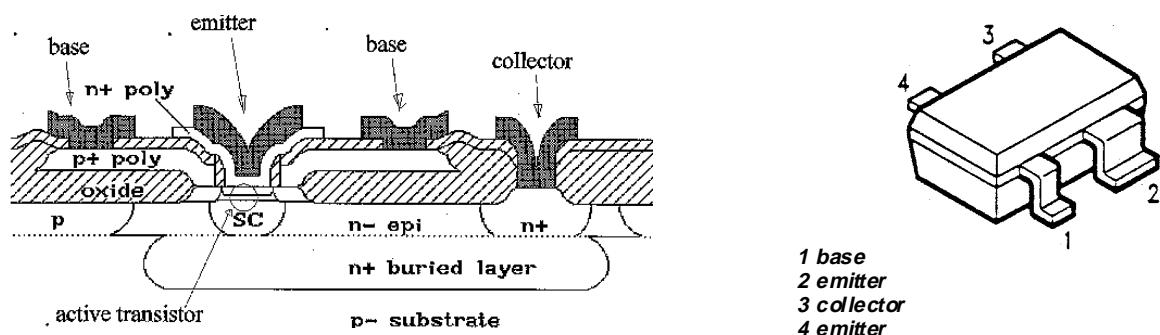


Figure 1: Cross section and package of the double-poly buried layer RF transistors.

With only two *double-poly* transistors a complete amplifier line-up can be realised, offering 26 dBm of output power with more than 26 dB power gain. The amplifier requires a single supply voltage of 3.6 V and typically has 44% efficiency. The biasing circuitry uses only one NPN transistor pair, which also performs load power adjustment and on/off switching functions. Thanks to the low component count and simple matching networks the entire amplifier (including bias part) only measures 10 x 20 mm.

As compared to a previous demonstration board, PH96060 (Preliminary Application Note RNR-T45-96-T-838) this one offers lower additional component count, but is less suitable for PHS application.

The main features of the PA are:

- low component count
- small size
- high efficiency
- single supply operation

CHARACTERISTICS

(unless otherwise specified the operating frequency is 1.89 GHz, the supply voltage is 3.6 V, the input power is 0 dBm and the period is 10 ms with a duty cycle of 1:8)

Parameter	Specification	Typical	Condition
General parameters			
Supply voltage (V_s)	$3.2 \leq 3.6 \leq 4.2$ V		
Control voltage (V_c)	on state: 3.6 V off state: 0 V		
Frequency range	1.88 - 1.92 GHz		
Type of operation	pulsed		duty cycle $\leq 50\%$
Source and load impedance	50Ω		
Power gain (G_p)	≥ 26 dB	26.3 dB	$P_o = 26$ dBm
Output power (P_o)	≥ 26 dBm	26.3 dBm	
Avg. supply current	11 mA		$P_o = 26$ dBm
Efficiency	$\geq 40\%$	44%	$P_o = 26$ dBm
Input VSWR	2 : 1		
Isolation (relative to input power)	≥ 50 dB	57 dB	$V_c = 0$ V
Spurious	≤ -60 dBc		$V_s = 3.2, 4.2$ V VSWR 6 : 1, all phases
Leakage current in off-state	≤ 10 μ A		$V_c = 0$ V
Harmonics: 2 nd 3 rd	≤ -30 dBm ≤ -30 dBm	-34 dBm -13 dBm	
Load mismatch:	No degradation		$P_o = 26$ dBm, $V_s \leq 4.5$ V VSWR 6 : 1, all phases
Printed circuit board	FR4 bilayer ($h=0.7$; $\epsilon_r=4.6$; $\tan\delta=0.02$)		
Dimensions	10 x 20 mm (including bias circuitry)		

Table 1: Characteristics of the DECT PA PH97005.

CIRCUIT DESCRIPTION

Figure 2 shows circuit diagram of the DECT PA including both RF transistors, matching circuits and biasing circuit. The appendix contains the part list of the demo board.

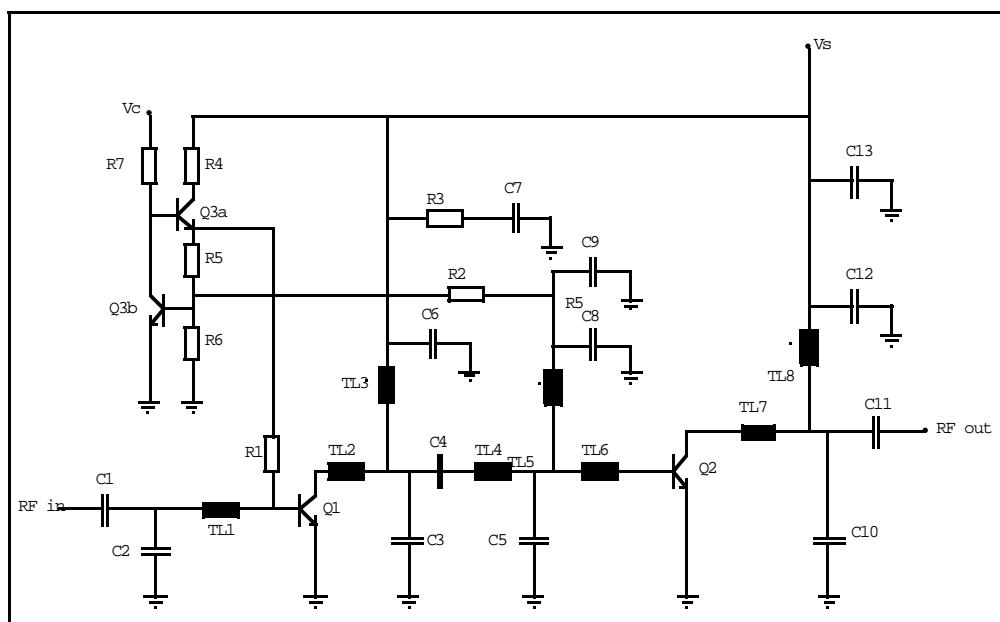


diagram of the DECT PA demo board PH97005.

Figure 2: Circuit

RF transistors

The RF chain of the PA consists of two transistor stages: a BFG425W (Q1) wideband transistor, operating in class A and a BFG21W (Q2), operating in class AB.

In accordance with the above settings the measured source and load impedances of both transistors are given in table 2.

Transistor	Source impedance (Z_s)	Load impedance (Z)
BFG425W ($V_{ce} = 3.6$ V; $I_c = 30$ mA; $f = 1.89$ GHz)	$12 + 0.7 j \Omega$	$52 + 102 j \Omega$
BFG21W ($V_{ce} = 3.6$ V; $P_o = 26$ dBm; $f = 1.89$ GHz)	$8 - 4.5 j \Omega$	$12 - 3.5 j \Omega$

Table 2 : Source and load impedances of the applied RF transistors.

Small signal S-parameter data for the BFG425W as well as large signal Spice parameters of both the BFG425W and the BFG21W are available on floppy disc.

The RF transistors have two emitters leads, which have to be carefully grounded to ensure stable operation and performance according to specification. Typically, the inductance of the vias has to be kept below 0.1 nH.

Impedance matching

The impedance matching part consists of three separate sections: the input, the interstage and the output matching networks. The purpose of these networks is to enable the RF transistors to give optimum performance with respect to power gain, output power and efficiency. Fortunately, the impedance levels of the applied *double-poly* transistors are not exceptionally high or low, so they're rather easy to match.

Decoupling is done by using capacitors C1, C4, C6, C8, C11 and C12, which are series resonant at 1.9 GHz. Capacitors C7 (with resistor R3) and C9 are used to suppress low frequency instability.

At the input side shunt capacitor C2 and series transmission line TL1 match the 50Ω source to the base of Q1. Base resistor R1 is used for biasing and has no effect on matching.

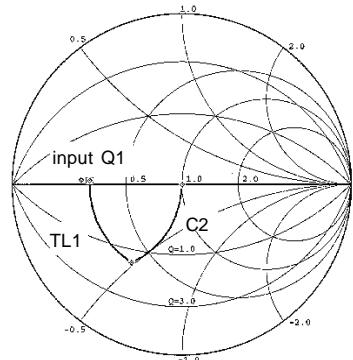


Fig. 3a: Input matching.

Between the collector of Q1 and the base of Q2 matching is done by series transmission line TL2, shunt capacitor C3 and series transmission lines TL4 and TL6. Both shunt capacitors C3 and C5 (partly) compensate the influence of bias stubs TL3 and TL5, which are both shorter than a quarter wavelength.

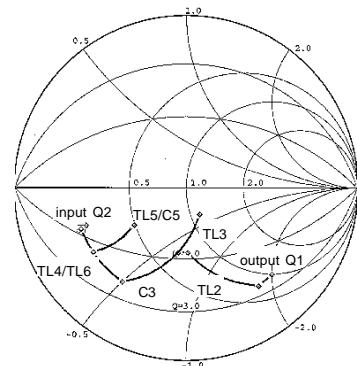


Fig. 3b: Interstage matching.

The output match is done by series transmission line TL7 and shunt capacitor C10. Again this capacitor also compensates the influence of bias stub TL6.

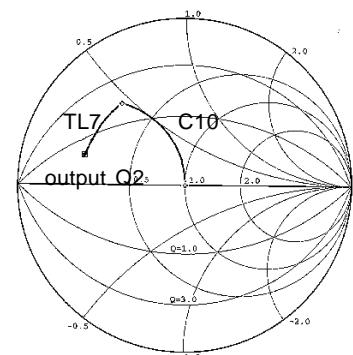


Fig. 3c: Output matching.

Biasing

The biasing part of the PA is centered around a dual NPN transistor, Q3 a and b. The circuit offers a temperature compensated bias voltage for both the first and the second RF stages. Unlike the previous demo board PH96060, the circuit is activated when V_c is high, which is beyond 2.4 V. The bias output voltage for the first stage is a little higher than for the second stage. Due to series resistor R1, the first stage is current driven and operates in class A. The second stage is driven by at the knee voltage (0.7 V) and operates in class AB. Series resistor R2 protects Q2 from thermal runaway.

The current design of the PA doesn't include any measures to reduce adjacent channel power due to switching transients. The slope of the RF pulse can be too steep and has to be relaxed to comply to the approval specification. This can be done by placing a capacitor at the base of Q3a. Experimental investigation has shown that a 10 nF capacitor approximately offers a 20 dB improvement of the adjacent channel power.

Recommendations for use

Figure 4 shows how the PA should be connected.

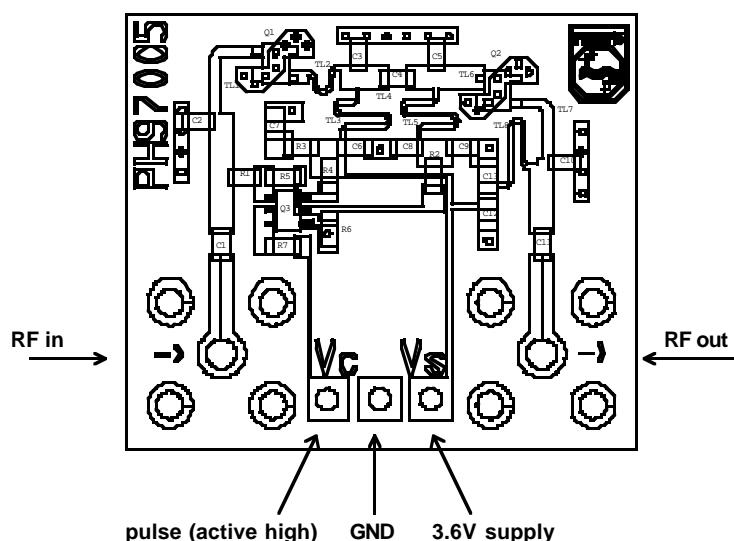


Figure 4: Schematic view of the PA connections.

In pulsed condition at nominal supply voltage and output power level, the load can be mismatched ($VSWR \leq 6 : 1$, all phases) without damage.

The PA can also be operated in CW, but only when the output is properly matched with 50Ω . When a mismatched load is applied when the amplifier is operated in CW, this will cause damage of the final stage.

BOARD LAYOUT

Figure 5 shows the layout of the PCB, which has the following properties:

type: FR4 bilayer (backside ground)

$h = 0.71 \text{ mm}$

$t = 35 \mu\text{m}$ (Cu cladding, not coated)

$\epsilon_r = 4.6$

$\tan\delta = 0.02$

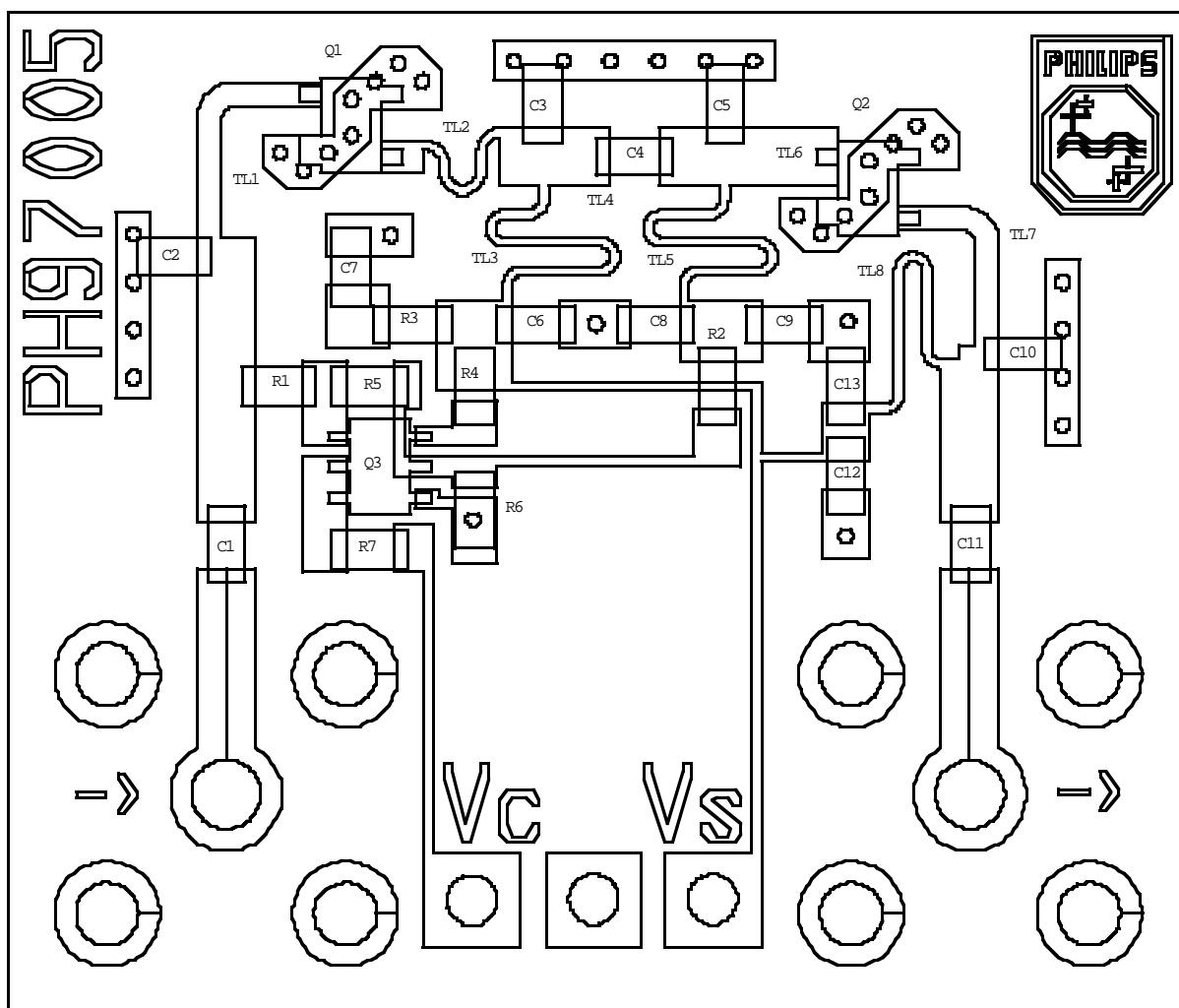


Figure 5: Layout of the DECT PA demo board.

All resistors and capacitors used are Philips 0603 SMD types. Appendix A contains the part list of the demo board. The position of components C2, C3, C5 and C10 is critical. The artwork file is available on floppy disc (DXF format).

MEASUREMENT RESULTS

Measurements under pulsed conditions, with a 10 ms period and a duty cycle of 1:8.

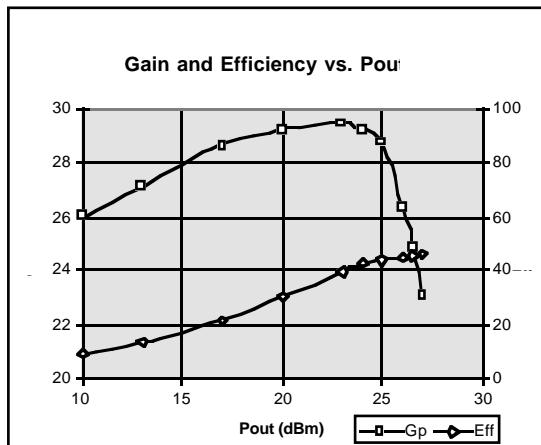


Figure 6a: $f = 1.89 \text{ GHz}$; $V_s = 3.6 \text{ V}$; $V_c = 3.6 \text{ V}$.

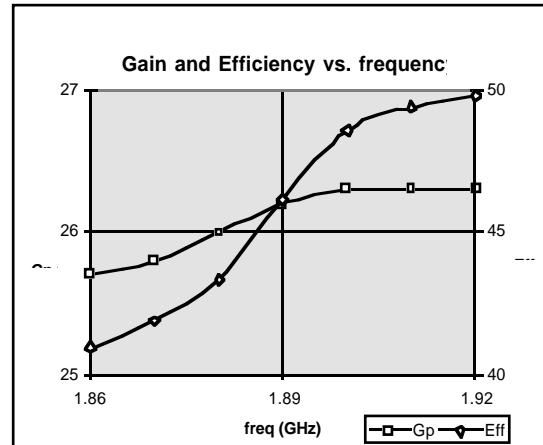


Figure 6b: $V_s = 3.6 \text{ V}$; $P_{in} = 0 \text{ dBm}$; $V_c = 3.6 \text{ V}$.

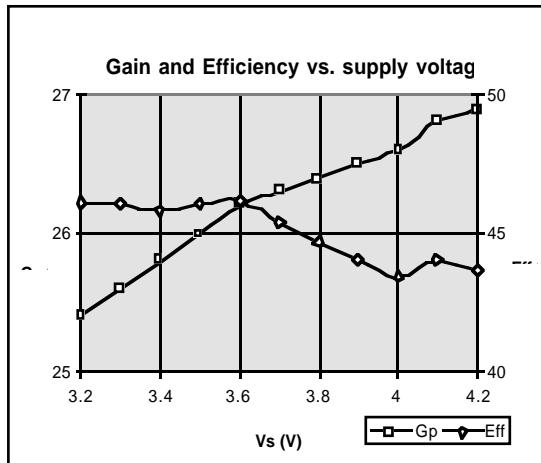


Figure 6c: $f = 1.89 \text{ GHz}$; $P_{in} = 0 \text{ dBm}$; $V_c = 3.6 \text{ V}$.
 0 dBm .

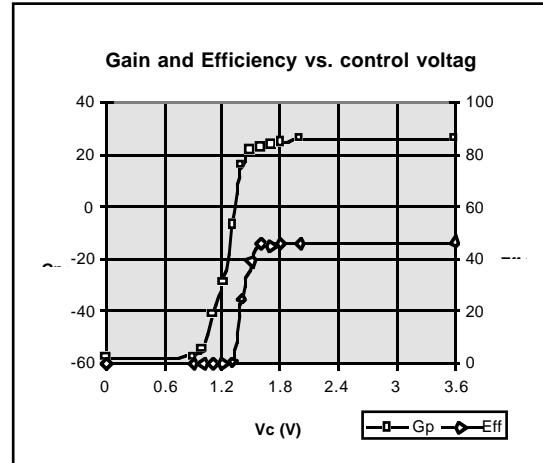


Figure 6d: $f = 1.89 \text{ GHz}$; $V_s = 3.6 \text{ V}$; $P_{in} = 0$

APPENDIX

Part list DECT PA demo board PH97005

Resistors

R1	560
R2	56
R3	10
R4	220
R5	82
R6	330
R7	1 K

C1	8.2p
C2	1.8p
C3	1.8p
C4	8.2p
C5	3.3p
C6	8.2p
C7	10n
C8	8.2p
C9	1n
C10	2.7p
C11	8.2p
C12	8.2p
C13	1n

Transmission lines

TL1	L = 6.5 mm W = 0.45 mm
TL2	L = 3.0 mm W = 0.15 mm
TL3	L = 7.5 mm W = 0.15 mm
TL4	L = 2.0 mm W = 1.15 mm
TL5	L = 7.5 mm W = 0.15 mm
TL6	L = 2.0 mm W = 1.15 mm
TL7	L = 5.0 mm W = 0.45 mm
TL8	L = 6.5 mm W = 0.15 mm

Transistors

Q1	BFG425W
Q2	BFG21W
Q3	PUMX1

Capacitors

SUNSTAR 商斯达实业集团是集研发、生产、工程、销售、代理经销、技术咨询、信息服务等为一体的高科技企业，是专业高科技电子产品生产厂家，是具有 10 多年历史的专业电子元器件供应商，是中国最早和最大的仓储式连锁规模经营大型综合电子零部件代理分销商之一，是一家专业代理和分销世界各大品牌 IC 芯片和电子元器件的连锁经营综合性国际公司，专业经营进口、国产名厂名牌电子元件，型号、种类齐全。在香港、北京、深圳、上海、西安、成都等全国主要电子市场设有直属分公司和产品展示展销窗口门市部专卖店及代理分销商，已在全国范围内建成强大统一的供货和代理分销网络。我们专业代理经销、开发生产电子元器件、集成电路、传感器、微波光电元器件、工控机/DOC/DOM 电子盘、专用电路、单片机开发、MCU/DSP/ARM/FPGA 软件硬件、二极管、三极管、模块等，是您可靠的一站式现货配套供应商、方案提供商、部件功能模块开发配套商。商斯达实业公司拥有庞大的资料库，有数位毕业于著名高校——有中国电子工业摇篮之称的西安电子科技大学（西军电）并长期从事国防尖端科技研究的高级工程师为您精挑细选、量身订做各种高科技电子元器件，并解决各种技术问题。

微波光电部专业代理经销高频、微波、光纤、光电元器件、组件、部件、模块、整机；电磁兼容元器件、材料、设备；微波 CAD、EDA 软件、开发测试仿真工具；微波、光纤仪器仪表。欢迎国外高科技微波、光纤厂商将优秀产品介绍到中国、共同开拓市场。长期大量现货专业批发高频、微波、卫星、光纤、电视、CATV 器件：晶振、VCO、连接器、PIN 开关、变容二极管、开关二极管、低噪晶体管、功率电阻及电容、放大器、功率管、MMIC、混频器、耦合器、功分器、振荡器、合成器、衰减器、滤波器、隔离器、环行器、移相器、调制解调器；光电子元器件和组件：红外发射管、红外接收管、光电开关、光敏管、发光二极管和发光二极管组件、半导体激光二极管和激光器组件、光电探测器和光接收组件、光发射接收模块、光纤激光器和光放大器、光调制器、光开关、DWDM 用光发射和接收器件、用户接入系统光光收发器件与模块、光纤连接器、光纤跳线/尾纤、光衰减器、光纤适配器、光隔离器、光耦合器、光环行器、光复用器/转换器；无线收发芯片和模组、蓝牙芯片和模组。

更多产品请看本公司产品专用销售网站：

商斯达中国传感器科技信息网：<http://www.sensor-ic.com/>

商斯达工控安防网：<http://www.pc-ps.net/>

商斯达电子元器件网：<http://www.sunstare.com/>

商斯达微波光电产品网：<HTTP://www.rfoe.net/>

商斯达消费电子产品网：<http://www.icasic.com/>

商斯达实业科技产品网：<http://www.sunstars.cn/> 微波元器件销售热线：

地址：深圳市福田区福华路福庆街鸿图大厦 1602 室

电话：0755-82884100 83397033 83396822 83398585

传真：0755-83376182 (0) 13823648918 MSN：SUNS8888@hotmail.com

邮编：518033 E-mail：szss20@163.com QQ：195847376

深圳赛格展销部：深圳华强北路赛格电子市场 2583 号 电话：0755-83665529 25059422

技术支持：0755-83394033 13501568376

欢迎索取免费详细资料、设计指南和光盘；产品凡多，未能尽录，欢迎来电查询。

北京分公司：北京海淀区知春路 132 号中发电子大厦 3097 号

TEL：010-81159046 82615020 13501189838 FAX：010-62543996

上海分公司：上海市北京东路 668 号上海赛格电子市场 D125 号

TEL：021-28311762 56703037 13701955389 FAX：021-56703037

西安分公司：西安高新区 20 所(中国电子科技集团导航技术研究所)

西安劳动南路 88 号电子商城二楼 D23 号

TEL：029-81022619 13072977981 FAX:029-88789382