

APPLICATION NOTE

**A linear amplifier (1.6 – 28 MHz) for
8 W PEP in class-A with the BLF175**

NCO8705

**A linear amplifier (1.6 – 28 MHz) for 8 W
PEP in class-A with the BLF175**

**Application Note
NCO8705**

CONTENTS

1	SUMMARY
2	INTRODUCTION
3	GENERAL CONSIDERATIONS
4	DESIGN OF THE AMPLIFIER
4.1	Circuit description
4.2	Design procedure
4.2.1	Powergain
4.2.2	Cut-off frequency
4.3	Calculation
4.4	Output matching
4.5	Input matching
5	AMPLIFIER ALIGNMENT
6	AMPLIFIER CONSTRUCTION
6.1	Construction notes
6.2	Heatsink
7	AMPLIFIER PERFORMANCE
7.1	General
7.2	Performance at constant output power
7.3	Performance at constant frequency
8	CONCLUSION
9	REFERENCE
9.1	CIRCUIT DIAGRAM OF THE WIDEBAND LINEAR AMPLIFIER

A linear amplifier (1.6 – 28 MHz) for 8 W PEP in class-A with the BLF175

Application Note
NCO8705

1 SUMMARY

In this report a description is given of a wideband linear amplifier intended for driver applications in SSB transmitters for the frequency range 1.6 to 28 MHz. It employs a MOS-transistor BLF175 suited for a supply voltage of 50 V. The transistor is adjusted in class-A with a quiescent drain current of 800 mA. The main properties at $P_o = 8$ W PEP are:

Powergain: 28.3 – 28.6 dB

IMD (d3): ≤ -41 dB

IMD (d5): ≤ -60 dB

Input return loss: ≤ -26 dB.

2 INTRODUCTION

The amplifier that will be discussed in this report concerns a wideband linear amplifier, designed for driver applications in SSB transmitters in the HF band. This design is based on the RF power MOS-transistor BLF175 which is primarily designed for communication purposes in the HF-band. This device can deliver 8 W PEP in class-A at an IMD (d3) < -40 dB, when operated from a supply voltage of 50 V. It is encapsulated in a SOT123 four-lead flange type with a ceramic cap.

3 GENERAL CONSIDERATIONS

One of the most important factors to be considered in the design of driver stages for SSB transmitters is intermodulation distortion. The major cause for intermodulation distortion is the non-linear transfer characteristic of the transistor. A generally accepted IM distortion figure is < -40 dB. To achieve this, driver stages must be operated in class-A. One of the properties of a class-A amplifier is its low efficiency, which for pre-drivers is of less importance.

The amplifier must have a flat gain response, within a few tenths of a dB. Its response should preferably be superior to that of the final amplifier of a SSB transmitter. The input return loss versus frequency must be low because, it will possibly form the load of a pre-driver.

4 DESIGN OF THE AMPLIFIER

4.1 Circuit description

Figure 1 shows the basic circuit of this broadband amplifier. Negative feedback combined with parallel input compensation has been applied to obtain flat gain and low input return loss.

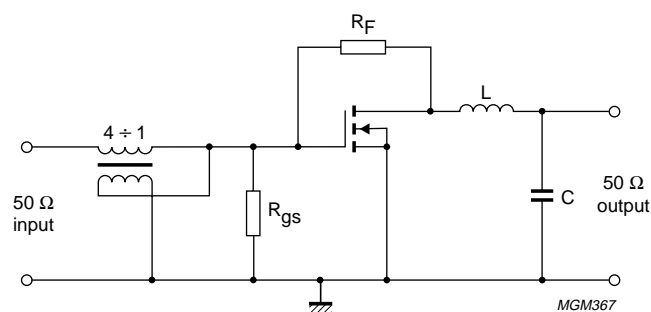


Fig.1 Basic circuit of the wideband amplifier.

A linear amplifier (1.6 – 28 MHz) for 8 W
PEP in class-A with the BLF175

Application Note
NCO8705

Matching of the input to 50 Ω is accomplished with a 4 ÷ 1 broadband transformer of the transmission line type. At the output side a LC-section compensates the output capacitance of the transistor for the frequency range of interest in order to provide the transistor with a constant resistive load.

4.2 Design procedure

The amplifier will be designed for a supply voltage of 50 V and a system impedance of 50 Ω.

First the DC-operating point must be determined. The most important factor that restricts the DC-current in MOS-transistors is the maximum allowable power dissipation in the transistor. For a maximum operating junction temperature of 200 °C and a maximum allowable heatsink temperature of 70 °C the maximum dissipation with $R_{thj-h} = 2.9 \text{ K/W}$ equals to 44.8 W. This corresponds with a drain current of 0.9 A at $V_{ds} = 50 \text{ V}$. In order to keep the dissipation within safe limits I_{ds} is set to 0.8 A.

Second the optimum load resistance is determined. For class-A amplifiers this is given by the relation:

$$R_L = \frac{V_{ds}}{I_{ds}} \tag{1}$$

In this case R_L equals to $\frac{50}{0.8} = 62.5 \text{ } \Omega$. In order to avoid an output transformer R_L is chosen to be 50 Ω.

Now the load resistance has been established, the input resistance can be determined. This resistance is formed by the input shunt resistance and that part of the feedback resistance reflected to the input. Several properties of this amplifier are determined by this resistance, viz.:

1. The power gain
2. The cut-off frequency.

In the next sections a brief analysis will be given of this amplifier in order to determine the input resistance and the powergain.

4.2.1 POWERGAIN

For class-A amplifiers small signal analysis produces sufficiently accurate results. The small-signal equivalent circuit of the amplifier is shown in Fig.2. All transistor package parasitics are neglected for this frequency range.

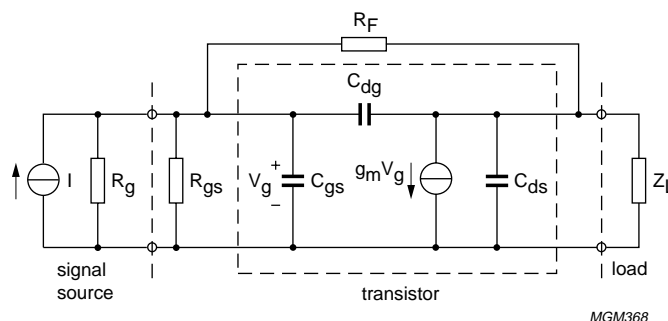


Fig.2 Small signal equivalent circuit of amplifier.

A linear amplifier (1.6 – 28 MHz) for 8 W
PEP in class-A with the BLF175

Application Note
NCO8705

The Y-parameters of the transistor with feedback resistor R_F and shunt resistor R_{gs} are:

$$Y_{11} = G_{gs} + G_F + j\omega(C_{gs} + C_{gd}) \tag{2}$$

$$Y_{12} = -j\omega C_{gd} - G_F \tag{3}$$

$$Y_{21} = g_m - G_F - j\omega C_{gd} \tag{4}$$

$$Y_{22} = G_F + j\omega(C_{ds} + C_{dg}) \tag{5}$$

The general expression for powergain of any linear amplifier is:

$$G_p = \frac{P_o}{P_i} = \frac{G_L |Y_{21}|^2}{|Y_{22} + Y_L|^2 \times \text{Re}(Y_{in})} \tag{6}$$

In which:

$$Y_{in} = Y_{11} - \frac{Y_{12} \times Y_{21}}{Y_{22} + Y_L} \tag{7}$$

The load admittance is:

$$Y_L = G_L - j\omega(C_{ds} + C_{dg}) \tag{8}$$

After substitution of equation (2) to (5) and (7), (8) into (6) we obtain:

$$G_p = \frac{G_L [(g_m - G_F)^2 + \omega^2 C_{gd}^2]}{(G_L + 2G_F) [G_{gs} (G_L + 2G_F) + G_L G + G_F^2 + \omega^2 C_{gd}^2]} \tag{9}$$

In which:

$$G = G_F \left(1 + \frac{g_m}{G_L} \right) \tag{10}$$

If G_F and ωC_{gd} are assumed very small with respect to G_L and G_m we get the simple expression:

$$G_p = \frac{g_m^2}{G_L (G_{gs} + G)} \tag{11}$$

4.2.2 CUT-OFF FREQUENCY

The cut-off frequency of this amplifier is dominated by the input circuit. The output circuit has a much higher cut-off frequency and is therefore not relevant. Figure 3 shows the unilaterised small-signal equivalent circuit of Fig.1.

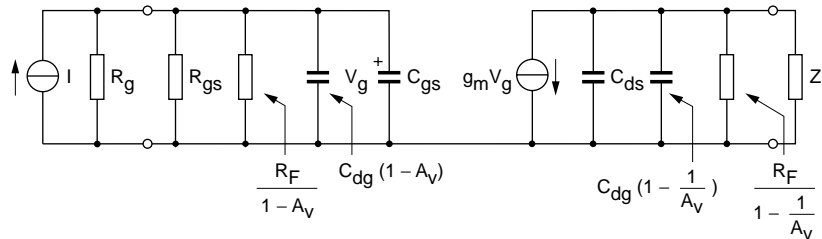


Fig.3 Unilaterised small-signal equivalent circuit.

A linear amplifier (1.6 – 28 MHz) for 8 W PEP in class-A with the BLF175

Application Note NCO8705

A_v is the voltage gain between drain and gate which is assumed to be a real number. The total input resistance is:

$$R_i = R_{gs} // \frac{R_F}{1 - A_v} \quad (12)$$

And the input capacitance is:

$$C_i = C_{gs} + C_{gd} (1 - A_v) \quad (13)$$

The 3 dB cut-off frequency of this RC-combination is given by:

$$f_c = \frac{1}{2\pi R_i C_i} \quad (14)$$

So, if C_i is known we can determine R_i for a certain bandwidth.

4.3 Calculation

Calculations are based on transistors from one batch of the BLF175. The mean values of the transistor parameters were taken. These are:

$$g_m = 1.5 \text{ S}; (V_{ds} = 10 \text{ V}; I_d = 1 \text{ A})$$

$$C_{gs} = 145.1 \text{ pF}$$

$$C_{ds} = 34.4 \text{ pF}; (V_{ds} = 50 \text{ V}; V_{gs} = 0 \text{ V}; f = 28 \text{ MHz})$$

$$C_{gd} = 3.42 \text{ pF}.$$

The transconductance (g_m) of this device is determined by a pulse measurement. Under normal operating conditions g_m will be lower due to the higher junction temperature. The reduction is approximately 25% for normal operating conditions. The effective transconductance is therefore:

$$g_{me} = 1.5 \times 0.75 = 1.1 \text{ S}$$

The capacitors C_{ds} and C_{gs} are voltage-dependent. Due to RF-excitation the effective capacitance in class-A will be 10% higher, so:

$$C_{ds_e} = 1.1 \times C_{ds} = 37.8 \text{ pF}$$

$$C_{gd_e} = 1.1 \times C_{gd} = 3.76 \text{ pF}$$

The voltage gain between drain and gate in Fig.1 can be calculated with:

$$A_v = -g_{me} \times R_L \quad (15)$$

For a load resistance of 50 Ω this amounts to:

$$A_v = -1.1 \times 50 = -55$$

According to eq. (13) the total input capacitance amounts to:

$$C_i = 145.1 + 3.76 \times (1 + 55) = 355.7 \text{ pF}$$

The total input resistance can now be determined with eq. (14). For $f = 28 \text{ MHz}$ this amounts to:

$$R_i \leq \frac{1}{2 \times \pi \times 28 \times 10^6 \times 355.7 \times 10^{-12}} = 16 \text{ } \Omega$$

For the ease of transformation a value of 12.5 Ω has been chosen. The cut-off frequency therefore increased to 35.8 MHz.

R_i consists of the parallel connection of R_{gs} and $R_F/(1-A_v)$ see Fig.3. First the feedback resistance R_F will be calculated. The only restriction that holds for the feedback resistance is the power dissipation in it. This must be kept low in order to

**A linear amplifier (1.6 – 28 MHz) for 8 W
PEP in class-A with the BLF175**

**Application Note
NCO8705**

prevent deterioration in IMD performance. The dissipation allowed, is set to ≈3% of the RMS output power. According to Fig.3 the total reflected feedback resistance to the output side is:

$$R'_F = \frac{R_F}{1 - \frac{1}{A_V}} \tag{16}$$

Because $A_V \gg 1$, $R'_F \approx R_F$ and amounts to:

$$R_F = 1500 \Omega$$

Now, R_{gs} can be calculated for $R_i = 12.5 \Omega$. With $R_F/(1 - A_V) = 26.8 \Omega$ we find for R_{gs} a value of 23.4 Ω . The closest practical value is 24 Ω .

The powergain in dB can be determined with eq. (9), and is calculated to be:

$$G_p = 10 \log (636.6) = 28.4 \text{ dB}$$

When the approximate equation is used (11) we get:

$$G_p = 10 \log (756.3) = 28.8 \text{ dB}$$

So, a good estimation is obtained when eq. (11) is used.

4.4 Output matching

The output impedance of the transistor can be represented by a parallel connection of a resistance and a capacitance. The resistance has a value of 50 Ω , see Section "Design procedure", and the capacitance is equal to $1.1 \times (C_{ds} + C_{dg}) = 41.6 \text{ pF}$ due to R_F -excitation. This output capacitance is compensated by a LC-section for the frequency range of interest in order to obtain a constant resistive load, see Fig.4.

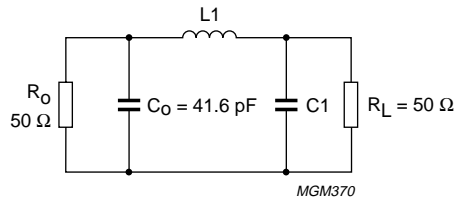


Fig.4 Output matching.

According to Ref. [1] the component values of L_1 and C_1 for a cut-off frequency of 28 MHz are:

$$L_1 = 189 \text{ nH and } C_1 = 41.6 \text{ pF with VSWR} = 1.05.$$

The output section contains two additional components, viz.:

1. A drain choke for biasing
2. A dc-blocking capacitor.

For RF-signals the drainchoke is connected in parallel with the output impedance, see Fig.5, and must therefore be large enough, in order to avoid performance degradation at the low end of the band. For the lowest frequency of interest (1.6 MHz) the choke inductance must be at least:

$$L_{ch} = \frac{4R_o}{2\pi f_{min}} \tag{17}$$

A linear amplifier (1.6 – 28 MHz) for 8 W PEP in class-A with the BLF175

Application Note NCO8705

In this case L_{ch} amounts to 20 μH . In practice this is obtained by winding 36 turns of enamelled copper-wire (0.7 mm) on a ferroxcube rod, grade 4B1, with a length of 30 mm and a diameter of 5 mm. Because of the open magnetic circuit saturation due to DC-current will hardly occur.

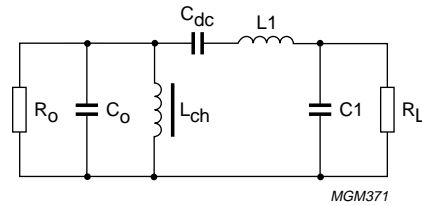


Fig.5 Output section.

The dc-blocking capacitor can be used to compensate the choke inductance for low frequencies. According to [1] this capacitor must be 8 nF for $f = 1.6$ MHz with $VSWR_{max} = 1.03$. In practice a chip capacitor was used of 10 nF.

The matching performance of the output section was verified with an impedance analyzer. The transistor was first replaced by a dummy transistor which consisted of a resistor of 50 Ω and a capacitor of 42 pF in a SOT123 header. The return loss was measured at the load connection. It appeared that the return loss improved when C_1 was replaced by a capacitor of 24 pF. This was due to parasitics introduced by the printed circuit board and the additional components like the drainchoke and the blocking capacitor. The return loss was better than -20 dB throughout the band.

4.5 Input matching

The input section is shown in Fig.6.

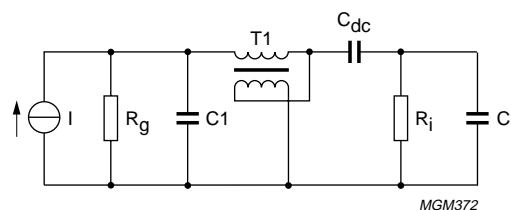


Fig.6 Input section.

A 4 : 1 broadband transformer is applied of the transmission line type. It utilizes a twisted-wire-pair transmission line wound on a toroidal core. The windings are uniformly distributed around the toroid. Figure 7 shows the electrical circuit diagram and constructional details of this transformer.

A linear amplifier (1.6 – 28 MHz) for 8 W PEP in class-A with the BLF175

Application Note NCO8705

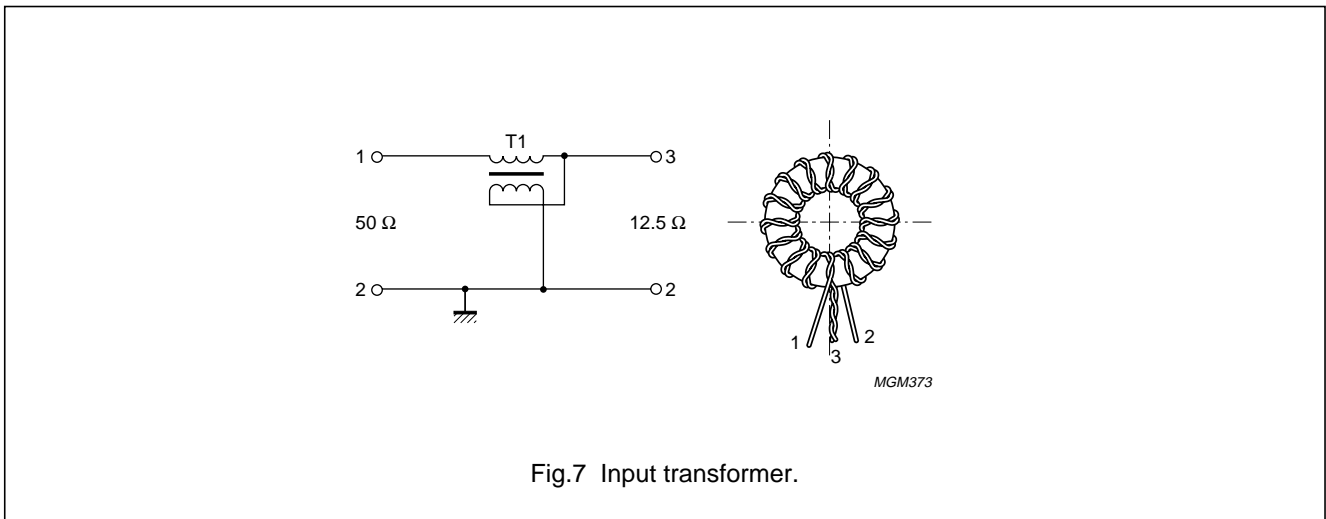


Fig.7 Input transformer.

The required characteristic impedance of the transmission line is:

$$Z_0 = \sqrt{R_g \times R_i}$$

For this case Z_0 equals to $\sqrt{50 \times 12.5} = 25 \Omega$. In practice Z_0 will deviate from the required value and compensation will be necessary to improve the broadband performance of the transistor. The characteristic impedance of 25Ω has been obtained by twisting two enamelled copper wires of 0.25 mm-bare diameter. The wire diameter with isolation included was 0.27 mm. Approximately 10 twists per cm were applied and the total wire length was 25 cm.

A ferroxcube toroid, grade 4C6, has been applied with dimensions (9 × 6 × 3) mm. Here the size is not primarily determined by the power handling capabilities, but the required number of turns needed to establish the parallel inductance between the transformer terminals. On the other hand this inductance must not be higher than necessary, because the broadband performance of the transformer will degrade if the transmission line becomes longer than $\lambda/8$. A good practical value is that given by equation (17). This means for the inductance at the 50 Ω side a value of 20 μH and for the 12.5 Ω side a value of 5 μH . The number of turns needed is that which is required to make 5 μH . According to the design information in ref. [2], 13 turns for this toroid were required to make 5 μH . From measurements it appeared to be too low. Therefore the number of turns had to be increased to 18. This is due to deviation in material properties which for smaller toroids is larger.

The dc-blocking capacitor compensates the parallel inductance of 5 μH . For 1.6 MHz, 31.8 nF is necessary according to ref. [1]. Three chip capacitors in parallel were used of 10 nF each.

High frequency compensation for deviation in Z_0 is accomplished by parallel capacitors between the transformer terminals. At the low ohmic side a part of C_i provides the required capacitance while at the high ohmic side C_1 provides this. Its value is determined by tuning a variable capacitor for optimum return loss at $f = 28 \text{ MHz}$ under nominal operating conditions. The required value was 3.9 pF.

5 AMPLIFIER ALIGNMENT

The amplifier was constructed according to the design procedure given in the previous chapter. Measurements were performed throughout the band at an output power of 8 W PEP. The results are given below.

Powergain = 27.5 – 28.6 dB

IMD(d3) ≤ -41 dB

IMD(d5) ≤ -60 dB

Input return loss ≤ -18.5 dB.

A linear amplifier (1.6 – 28 MHz) for 8 W PEP in class-A with the BLF175

Application Note NCO8705

The highest powergain occurred at $f = 1.6$ MHz. The total variation in gain of 1.1 dB was found to be relatively large. In order to improve this compensation measures were considered. There were two possibilities, viz.:

1. Parallel input compensation; an inductance in series with the input shunt resistance which increases the effective shunt resistance at high frequencies and hence the gain
2. Feedback compensation: an inductance in series with the feedback resistance which decreases the feedback at high frequencies and hence improves the gain.

The drawback of the latter is the relatively large inductance required for compensation, a few μH . The former is more elegant because of the low value of the required inductance. Calculation of the optimum inductance for maximally flat response is complicated. Therefore its value was determined in an empirical way. An inductance of 86 nH was found, which reduced the total variation to 0.3 dB for an average gain of 28.4 dB. An additional advantage of this compensation measure was the improvement of the input return loss, which became better than -26 dB.

6 AMPLIFIER CONSTRUCTION

6.1 Construction notes

The circuit diagram and component list are given in Fig.8 and Table 1. The circuit board of this amplifier design is made of two-sided copper clad epoxy fibreglass laminate with a thickness of 1/16 inch and a dielectric constant of 4.5. A full sized pattern of the printed circuit board is shown in Fig.9. The other side is fully metallized and used as ground plane. The ground planes on each side of the board are connected together by means of copper straps at the source leads and the N-connectors and the mounting screws. Figure 9 shows the component layout.

The unavoidable strip in the feedback path represents an inductance of 12 nH and a capacitance of 5.5 pF which can be neglected with respect to the feedback resistance. C4 is a dc-blocking capacitor and should have a low reactance for all frequencies. To prevent low frequency spurious oscillation, a network comprising C7 and R3 is applied. At low frequencies R3 serves as a series loss for choke L2 and thus avoids a high Q factor. C3 and C6 are small bypass capacitors for the carrier frequency. L3 needs to be as large as possible and still be able to handle the required current. C8 must provide a solid bypass at all frequencies including the very low ones.

6.2 Heatsink

The circuit board is attached to a solid brass plate, which is provided with a circular hole for cooling purposes. A water cooling system controls the heatsink temperature.

7 AMPLIFIER PERFORMANCE

7.1 General

Performance measurements were carried out under the following conditions:

Supply voltage: $V_{\text{dd}} = 50$ V

Quiescent drain current: $I_{\text{dq}} = 0.8$ A

Heatsink temperature: $T_{\text{hs}} = 25$ °C

The measuring frequency extends from 1.6 to 32 MHz. Two tones of equal amplitude were used with a frequency separation of 1 KHz. The distortion products were measured with respect to one of the two tones.

7.2 Performance at constant output power

The measurements were done at an output power of 8 W PEP. The results obtained are:

Powergain = 28.3 – 28.6 dB, see Fig.10

IMD (d3) = -41.4 – -47.4 dB, see Fig.11

IMD (d5) = ≤ -60 dB

Input return loss ≤ -26 dB, see Fig.12.

A linear amplifier (1.6 – 28 MHz) for 8 W PEP in class-A with the BLF175

Application Note
NCO8705

7.3 Performance at constant frequency

As shown in Fig.11 the worst third order IMD products occurs at the highest end of the band. Therefore, measurements versus output power were only carried out at $f = 28$ MHz. The results obtained are:

Powergain = 28.1 – 28.4 dB, see Fig.13;

IMD (d3) = –60 – –33.9 dB, see Fig.14 –40 dB is exceeded for $P_o \geq 9.5$ W PEP;

IMD (d5) \leq –58 dB;

Input return loss \leq –21.5 dB.

8 CONCLUSION

The design and construction of a wideband linear amplifier has been presented, with the MOS-transistor BLF175, for the frequency range 1.6 – 28 MHz. The transistor is adjusted in class-A and shows good linearity, IMD (d3) \leq –40 dB, up to an output power of 9.5 W. It is suited for driver applications in SSB transmitters.

9 REFERENCE

[1] H.Nielinger; "Optimale dimensionierung von Breitbandanpassungsnetzen"; NTZ 1968, Heft 2, pp. 88–91.

[2] Philips Data handbook; "Soft Ferrites"; Book MA01, 1996.

9.1 Circuit diagram of the wideband linear amplifier

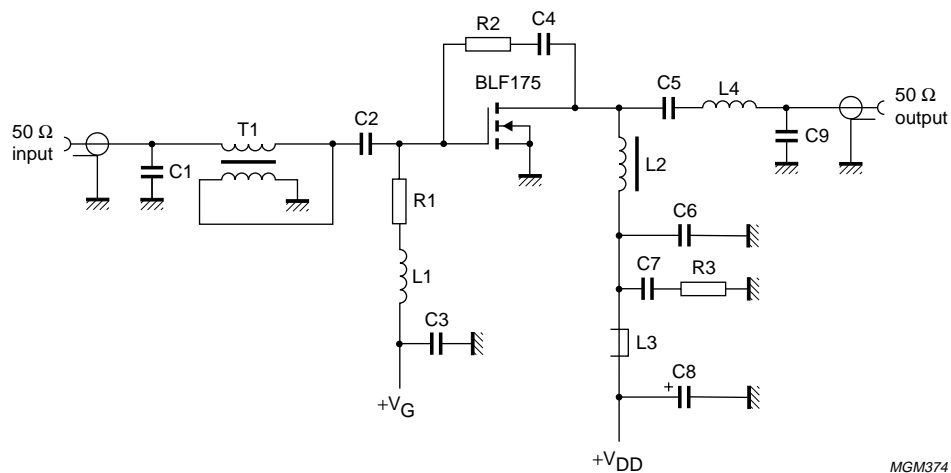


Fig.8 Circuit diagram of the wideband linear amplifier.

A linear amplifier (1.6 – 28 MHz) for 8 W PEP in class-A with the BLF175

Application Note NCO8705

Table 1 List of components



Capacitors	
C1 = 3.9 pF	multilayer ceramic chip capacitor; note 1
C2 = 3×10 nF	multilayer ceramic chip capacitor; (cat. nr. 2222 852 47103)
C3 = C4 = C6 = 100 nF	multilayer ceramic chip capacitor; (cat. nr. 2222 852 47104)
C5 = 10 nF	multilayer ceramic chip capacitor; (cat.nr. 2222 852 47103)
C7 = 3×100 nF	multilayer ceramic chip capacitor; (cat.nr. 2222 852 47104)
C8 = 10 μ F (63 V)	Aluminium electrolytic capacitor; (cat.nr. 2222 030 28109)
C9 = 24 pF	multilayer ceramic chip capacitor; note 1
Inductors	
L1 = 86 nH	4 turns enamelled Cu-wire (0.6 mm); int. dia. = 5.0 mm, length = 3.3 mm; leads 2×2.0 mm
L2 = 20 μ H	drain choke, 36 turns enamelled Cu-wire (0.7 mm) wound on a Ferroxcube rod grade 4B1, dimensions (5 \times 30) mm
L3 =	Ferroxcube RF choke, grade 3B (cat.nr. 4312 020 36640)
L4 = 189 nH	8 turns enamelled Cu-wire (1.0 mm); int.dia. = 5.0 mm, length = 9.5 mm; leads 2×3.0 mm
Resistor	
R1 = 24 Ω	metal film resistor; 0.4 W
R2 = 1500 Ω	metal film resistor; 0.4 W
R3 = 10 Ω	metal film resistor; 0.4 W
Transformer	
T1 – 4 : 1 transformer	18 turns of twisted pair of 0.25 mm enamelled Cu-wire (10 twists per cm) wound on a toroidal core grade 4C6, dimensions (9 \times 6 \times 3) mm. (cat.nr. 4322-020-97171)
Printed circuit board: double sided Cu-clad epoxy fibreglass laminate ($\epsilon_r = 4.5$), thickness 1/16 inch	

Note

1. American technical ceramics capacitor type 100B.

A linear amplifier (1.6 – 28 MHz) for 8 W PEP in class-A with the BLF175

Application Note NCO8705

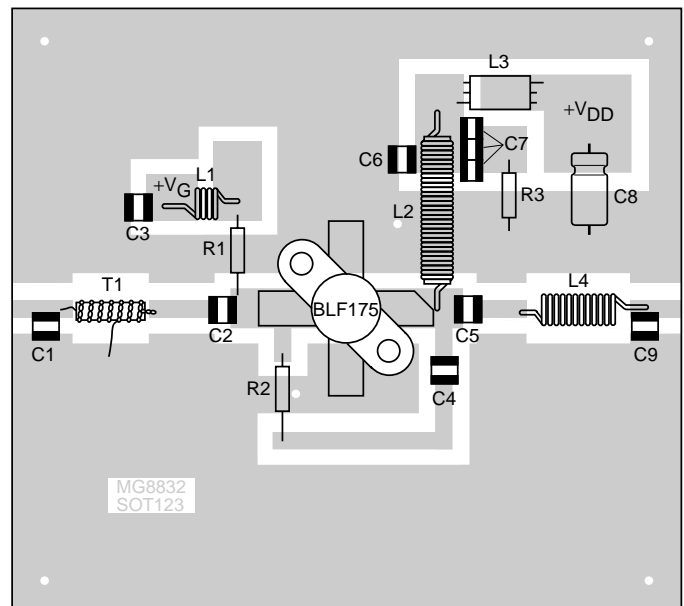
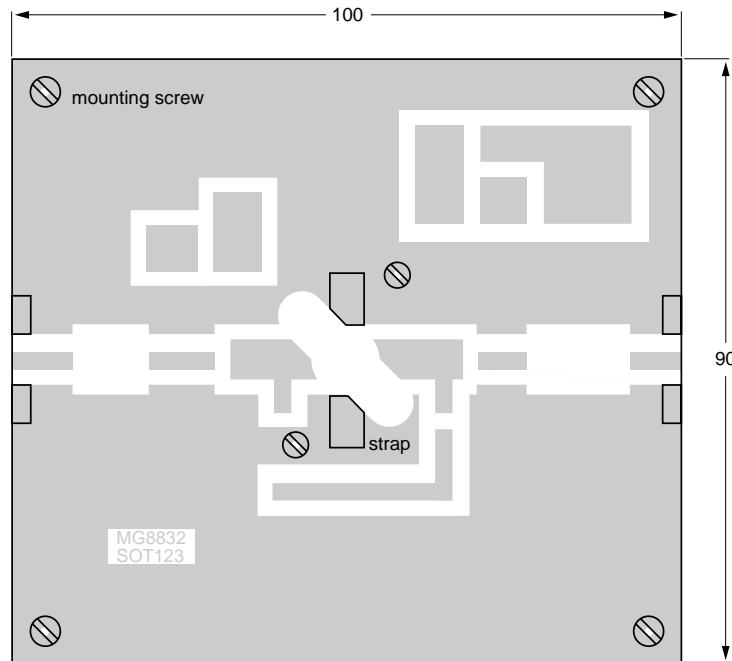


MGM375

Fig.9 Printed circuit board and component layout.


A linear amplifier (1.6 – 28 MHz) for 8 W
PEP in class-A with the BLF175

Application Note
NCO8705

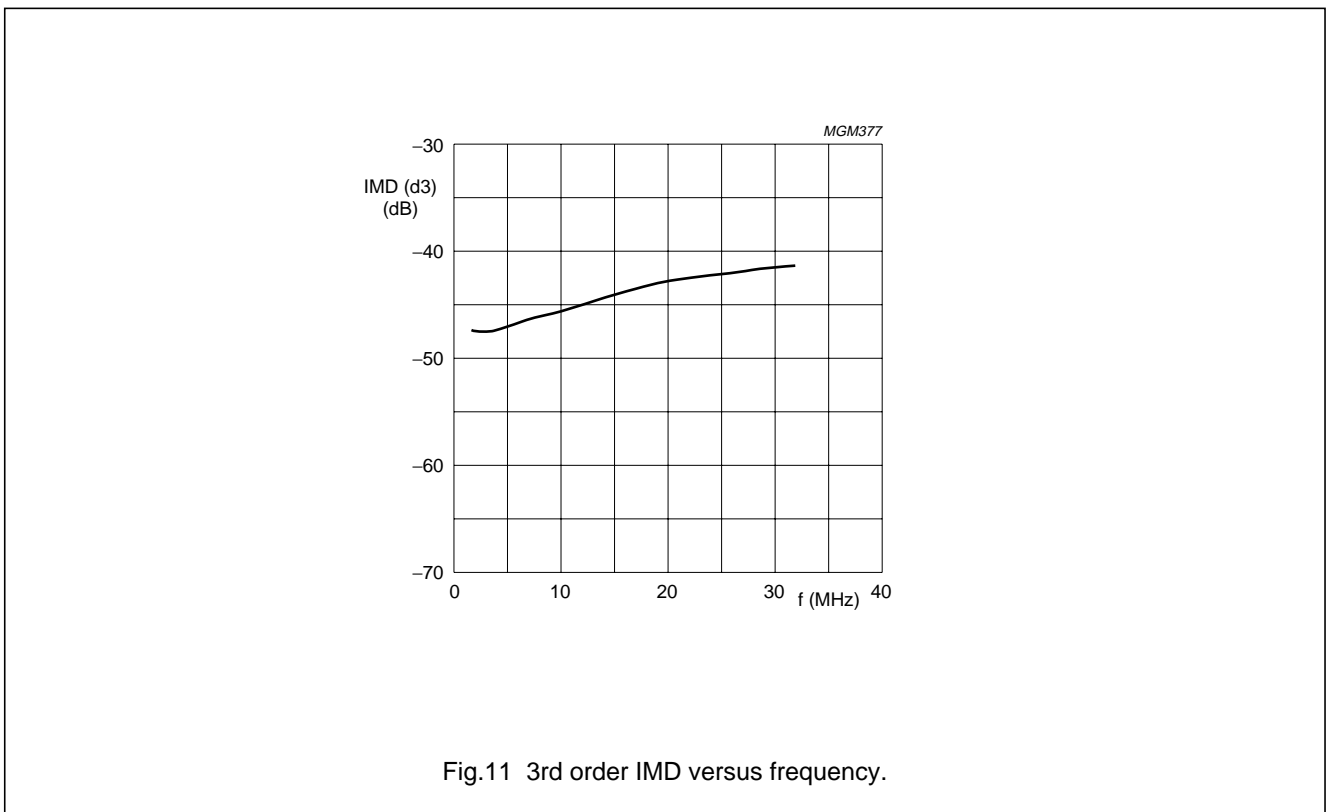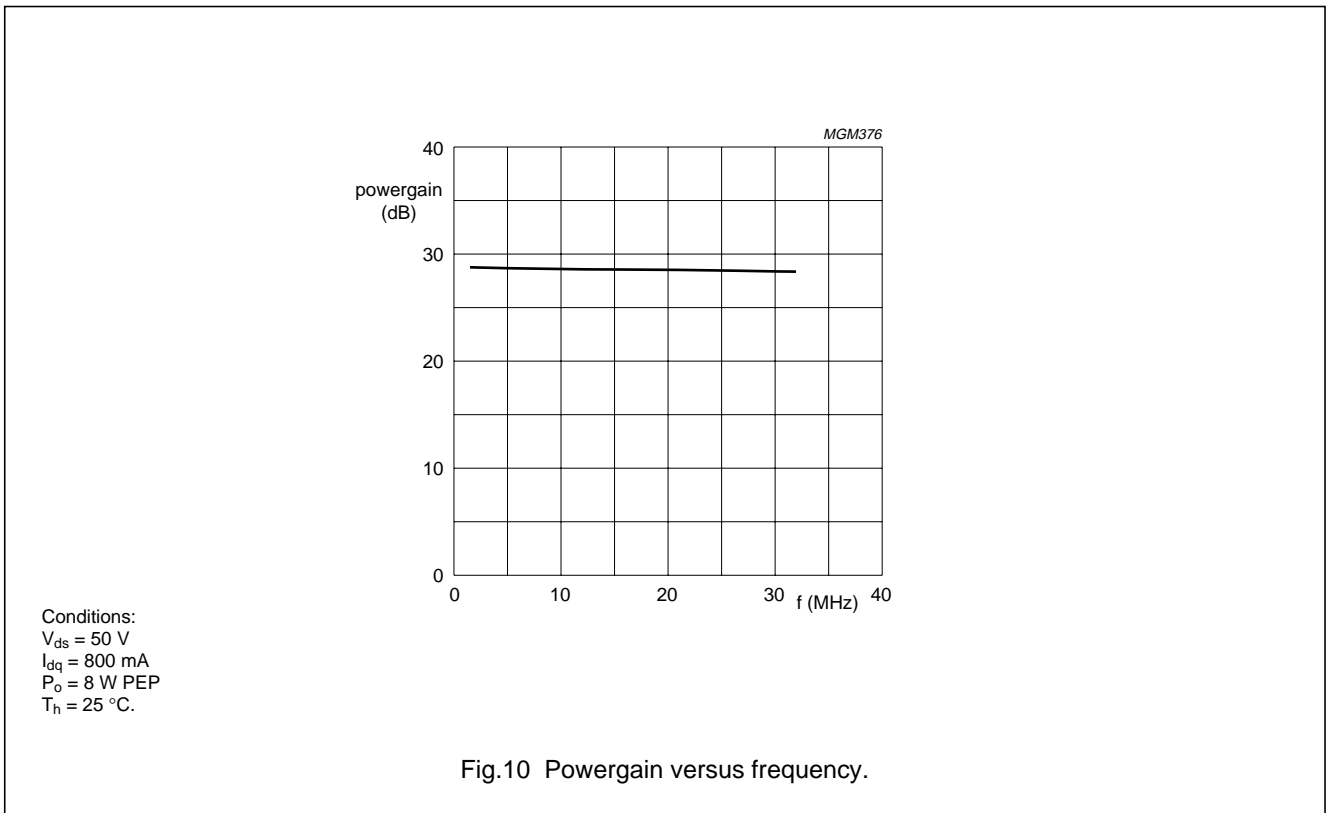

A linear amplifier (1.6 – 28 MHz) for 8 W
PEP in class-A with the BLF175

Application Note
NCO8705

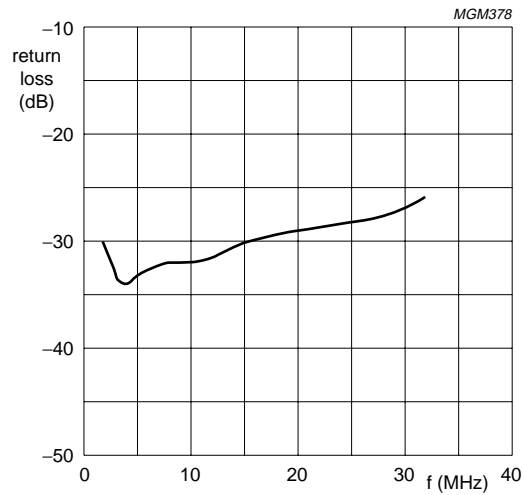

Conditions: $V_{ds} = 50$ V, $I_{dq} = 800$ mA, $P_o = 8$ W PEP, $T_h = 25$ °C
Tone separation = 1 kHz.

Fig.12 Input return loss versus frequency.


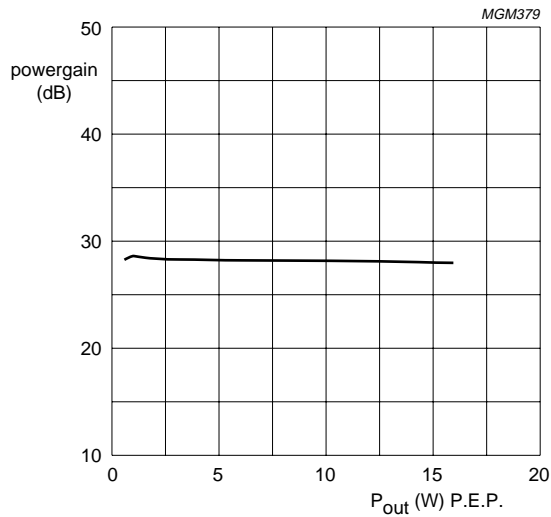


Fig.13 Powergain versus output power.

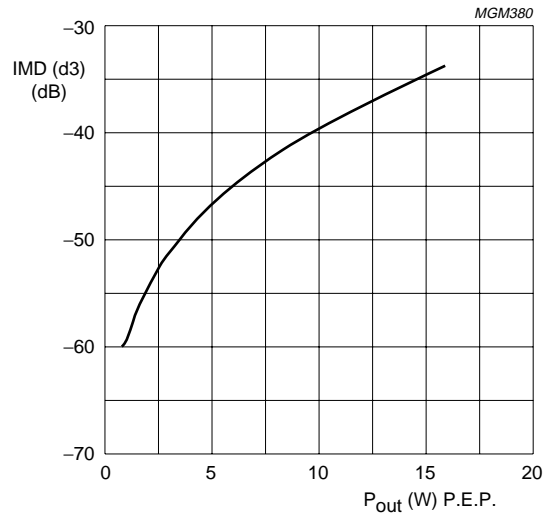

Conditions: $V_{ds} = 50 \text{ V}$, $I_{dq} = 800 \text{ mA}$, $T_h = 25 \text{ }^\circ\text{C}$, $f = 28 \text{ MHz}$ ($p-q = 1 \text{ kHz}$).

Fig.14 3th order IMD versus output power.

Philips Semiconductors – a worldwide company

Argentina: see South America

Australia: 34 Waterloo Road, NORTH RYDE, NSW 2113,
Tel. +61 2 9805 4455, Fax. +61 2 9805 4466

Austria: Computerstr. 6, A-1101 WIEN, P.O. Box 213, Tel. +43 160 1010,
Fax. +43 160 101 1210

Belarus: Hotel Minsk Business Center, Bld. 3, r. 1211, Volodarski Str. 6,
220050 MINSK, Tel. +375 172 200 733, Fax. +375 172 200 773

Belgium: see The Netherlands

Brazil: see South America

Bulgaria: Philips Bulgaria Ltd., Energoproject, 15th floor,
51 James Bourchier Blvd., 1407 SOFIA,
Tel. +359 2 689 211, Fax. +359 2 689 102

Canada: PHILIPS SEMICONDUCTORS/COMPONENTS,
Tel. +1 800 234 7381

China/Hong Kong: 501 Hong Kong Industrial Technology Centre,
72 Tat Chee Avenue, Kowloon Tong, HONG KONG,
Tel. +852 2319 7888, Fax. +852 2319 7700

Colombia: see South America

Czech Republic: see Austria

Denmark: Prags Boulevard 80, PB 1919, DK-2300 COPENHAGEN S,
Tel. +45 32 88 2636, Fax. +45 31 57 0044

Finland: Sinikalliontie 3, FIN-02630 ESPOO,
Tel. +358 9 615800, Fax. +358 9 61580920

France: 51 Rue Carnot, BP317, 92156 SURESNES Cedex,
Tel. +33 1 40 99 6161, Fax. +33 1 40 99 6427

Germany: Hammerbrookstraße 69, D-20097 HAMBURG,
Tel. +49 40 23 53 60, Fax. +49 40 23 536 300

Greece: No. 15, 25th March Street, GR 17778 TAVROS/ATHENS,
Tel. +30 1 4894 339/239, Fax. +30 1 4814 240

Hungary: see Austria

India: Philips INDIA Ltd, Band Box Building, 2nd floor,
254-D, Dr. Annie Besant Road, Worli, MUMBAI 400 025,
Tel. +91 22 493 8541, Fax. +91 22 493 0966

Indonesia: see Singapore

Ireland: Newstead, Clonskeagh, DUBLIN 14,
Tel. +353 1 7640 000, Fax. +353 1 7640 200

Israel: RAPAC Electronics, 7 Kehilat Saloniki St, PO Box 18053,
TEL AVIV 61180, Tel. +972 3 645 0444, Fax. +972 3 649 1007

Italy: PHILIPS SEMICONDUCTORS, Piazza IV Novembre 3,
20124 MILANO, Tel. +39 2 6752 2531, Fax. +39 2 6752 2557

Japan: Philips Bldg 13-37, Kohnan 2-chome, Minato-ku, TOKYO 108,
Tel. +81 3 3740 5130, Fax. +81 3 3740 5077

Korea: Philips House, 260-199 Itaewon-dong, Yongsan-ku, SEOUL,
Tel. +82 2 709 1412, Fax. +82 2 709 1415

Malaysia: No. 76 Jalan Universiti, 46200 PETALING JAYA, SELANGOR,
Tel. +60 3 750 5214, Fax. +60 3 757 4880

Mexico: 5900 Gateway East, Suite 200, EL PASO, TEXAS 79905,
Tel. +9-5 800 234 7381

Middle East: see Italy

Netherlands: Postbus 90050, 5600 PB EINDHOVEN, Bldg. VB,
Tel. +31 40 27 82785, Fax. +31 40 27 88399

New Zealand: 2 Wagener Place, C.P.O. Box 1041, AUCKLAND,
Tel. +64 9 849 4160, Fax. +64 9 849 7811

Norway: Box 1, Manglerud 0612, OSLO,
Tel. +47 22 74 8000, Fax. +47 22 74 8341

Philippines: Philips Semiconductors Philippines Inc.,
106 Valero St. Salcedo Village, P.O. Box 2108 MCC, MAKATI,
Metro MANILA, Tel. +63 2 816 6380, Fax. +63 2 817 3474

Poland: Ul. Lukiska 10, PL 04-123 WARSZAWA,
Tel. +48 22 612 2831, Fax. +48 22 612 2327

Portugal: see Spain

Romania: see Italy

Russia: Philips Russia, Ul. Usatcheva 35A, 119048 MOSCOW,
Tel. +7 095 755 6918, Fax. +7 095 755 6919

Singapore: Lorong 1, Toa Payoh, SINGAPORE 1231,
Tel. +65 350 2538, Fax. +65 251 6500

Slovakia: see Austria

Slovenia: see Italy

South Africa: S.A. PHILIPS Pty Ltd., 195-215 Main Road Martindale,
2092 JOHANNESBURG, P.O. Box 7430 Johannesburg 2000,
Tel. +27 11 470 5911, Fax. +27 11 470 5494

South America: Al. Vicente Pinzon, 173, 6th floor,
04547-130 SÃO PAULO, SP, Brazil,
Tel. +55 11 821 2333, Fax. +55 11 821 2382

Spain: Balmes 22, 08007 BARCELONA,
Tel. +34 3 301 6312, Fax. +34 3 301 4107

Sweden: Kottbygatan 7, Akalla, S-16485 STOCKHOLM,
Tel. +46 8 632 2000, Fax. +46 8 632 2745

Switzerland: Allmendstrasse 140, CH-8027 ZÜRICH,
Tel. +41 1 488 2686, Fax. +41 1 488 3263

Taiwan: Philips Semiconductors, 6F, No. 96, Chien Kuo N. Rd., Sec. 1,
TAIPEI, Taiwan Tel. +886 2 2134 2865, Fax. +886 2 2134 2874

Thailand: PHILIPS ELECTRONICS (THAILAND) Ltd.,
209/2 Sanpavuth-Bangna Road Prakanong, BANGKOK 10260,
Tel. +66 2 745 4090, Fax. +66 2 398 0793

Turkey: Talatpasa Cad. No. 5, 80640 GÜLTEPE/ISTANBUL,
Tel. +90 212 279 2770, Fax. +90 212 282 6707

Ukraine: PHILIPS UKRAINE, 4 Patrice Lumumba str., Building B, Floor 7,
252042 KIEV, Tel. +380 44 264 2776, Fax. +380 44 268 0461

United Kingdom: Philips Semiconductors Ltd., 276 Bath Road, Hayes,
MIDDLESEX UB3 5BX, Tel. +44 181 730 5000, Fax. +44 181 754 8421

United States: 811 East Arques Avenue, SUNNYVALE, CA 94088-3409,
Tel. +1 800 234 7381

Uruguay: see South America

Vietnam: see Singapore

Yugoslavia: PHILIPS, Trg N. Pasica 5/v, 11000 BEOGRAD,
Tel. +381 11 625 344, Fax. +381 11 635 777

For all other countries apply to: Philips Semiconductors,
International Marketing & Sales Communications, Building BE-p, P.O. Box 218,
5600 MD EINDHOVEN, The Netherlands, Fax. +31 40 27 24825

Internet: <http://www.semiconductors.philips.com>

© Philips Electronics N.V. 1998

SCA57

All rights are reserved. Reproduction in whole or in part is prohibited without the prior written consent of the copyright owner.

The information presented in this document does not form part of any quotation or contract, is believed to be accurate and reliable and may be changed without notice. No liability will be accepted by the publisher for any consequence of its use. Publication thereof does not convey nor imply any license under patent- or other industrial or intellectual property rights.

Printed in The Netherlands

Date of release: 1998 Mar 23

Let's make things better.

**Philips
Semiconductors**



PHILIPS

SUNSTAR 商斯达实业集团是集研发、生产、工程、销售、代理经销、技术咨询、信息服务等为一体的高科技企业，是专业高科技电子产品生产厂家，是具有 10 多年历史的专业电子元器件供应商，是中国最早和最大的仓储式连锁规模经营大型综合电子零部件代理分销商之一，是一家专业代理和分销世界各大品牌 IC 芯片和电子元器件的连锁经营综合性国际公司，专业经营进口、国产名厂名牌电子元件，型号、种类齐全。在香港、北京、深圳、上海、西安、成都等全国主要电子市场设有直属分公司和产品展示展销窗口门市部专卖店及代理分销商，已在全国范围内建成强大统一的供货和代理分销网络。我们专业代理经销、开发生产电子元器件、集成电路、传感器、微波光电元器件、工控机/DOC/DOM 电子盘、专用电路、单片机开发、MCU/DSP/ARM/FPGA 软件硬件、二极管、三极管、模块等，是您可靠的一站式现货配套供应商、方案提供商、部件功能模块开发配套商。商斯达实业公司拥有庞大的资料库，有数位毕业于著名高校——有中国电子工业摇篮之称的西安电子科技大学（西军电）并长期从事国防尖端科技研究的高级工程师为您精挑细选、量身订做各种高科技电子元器件，并解决各种技术问题。

微波光电部专业代理经销高频、微波、光纤、光电元器件、组件、部件、模块、整机；电磁兼容元器件、材料、设备；微波 CAD、EDA 软件、开发测试仿真工具；微波、光纤仪器仪表。欢迎国外高科技微波、光纤厂商将优秀产品介绍到中国、共同开拓市场。长期大量现货专业批发高频、微波、卫星、光纤、电视、CATV 器件：晶振、VCO、连接器、PIN 开关、变容二极管、开关二极管、低噪晶体管、功率电阻及电容、放大器、功率管、MMIC、混频器、耦合器、功分器、振荡器、合成器、衰减器、滤波器、隔离器、环行器、移相器、调制解调器；光电子元件和组件：红外发射管、红外接收管、光电开关、光敏管、发光二极管和发光二极管组件、半导体激光二极管和激光器组件、光电探测器和光接收组件、光发射接收模块、光纤激光器和光放大器、光调制器、光开关、DWDM 用光发射和接收器件、用户接入系统光收发器件与模块、光纤连接器、光纤跳线/尾纤、光衰减器、光纤适配器、光隔离器、光耦合器、光环行器、光复用器/转换器；无线收发芯片和模组、蓝牙芯片和模组。

更多产品请看本公司产品专用销售网站：

商斯达中国传感器科技信息网：<http://www.sensor-ic.com/>

商斯达工控安防网：<http://www.pc-ps.net/>

商斯达电子元器件网：<http://www.sunstare.com/>

商斯达微波光电产品网：[HTTP://www.rfoe.net/](http://www.rfoe.net/)

商斯达消费电子产品网：<http://www.icasic.com/>

商斯达实业科技产品网：<http://www.sunstars.cn/> 微波元器件销售热线：

地址：深圳市福田区福华路福庆街鸿图大厦 1602 室

电话：0755-82884100 83397033 83396822 83398585

传真：0755-83376182 (0) 13823648918 MSN: SUNS8888@hotmail.com

邮编：518033 E-mail:szss20@163.com QQ: 195847376

深圳赛格展销部：深圳华强北路赛格电子市场 2583 号 电话：0755-83665529 25059422

技术支持：0755-83394033 13501568376

欢迎索取免费详细资料、设计指南和光盘；产品凡多，未能尽录，欢迎来电查询。

北京分公司：北京海淀区知春路 132 号中发电子大厦 3097 号

TEL: 010-81159046 82615020 13501189838 FAX: 010-62543996

上海分公司：上海市北京东路 668 号上海赛格电子市场 D125 号

TEL: 021-28311762 56703037 13701955389 FAX: 021-56703037

西安分公司：西安高新开发区 20 所(中国电子科技集团导航技术研究所)

西安劳动南路 88 号电子商城二楼 D23 号

TEL: 029-81022619 13072977981 FAX:029-88789382