

DATA SHEET

Ideas for design Small-signal Field-effect Transistors

Product specification
Supersedes data of 1995 Apr 28
File under Discrete Semiconductors, SC07

1997 Oct 28

Small-signal Field-effect Transistors

Ideas for design

JFET CONSTANT-CURRENT SOURCES

The simplest JFET current source is shown in Fig.1. The JFET has been selected rather than a MOS-FET because it does not require gate bias (depletion mode). The current will be reasonably constant for a V_{DS} larger than several volts. However, because of I_{DSS} spread, the current is unpredictable. This can be seen, for example, with the 2N5484 which has a specified I_{DSS} of 1 to 5 mA. The circuit is attractive because of its simplicity. (Current regulator diodes are JFETs with the gate tied to the source, sorted according to current).

With a small variation this circuit gives an adjustable current source (see Fig.2). Resistor R back-biases the gate by $V = I_D \times R$, thus reducing I_D . The value of R can be calculated from the I_D/V_G characteristic for that particular JFET. This circuit makes it possible to set the current (must be less than I_{DSS}) as well as to make this current more predictable.

A JFET current source always shows some variation of output current with output voltage because of its finite output impedance, even if built with source resistor.

An improvement can be made by using a second JFET to hold the drain-source voltage of the current source constant (see Fig.3). The JFET Q2 has a larger I_{DSS} and is connected in series with the current source. It passes the (constant) drain current from Q1 through to the load, whilst holding the drain at Q1 at a fixed voltage; namely the gate-source voltage that makes Q2 operate at the same current as Q1. Q2 therefore shields Q1 from voltage swings at its output, and since Q1 is not subject to drain voltage variations, it provides constant current.

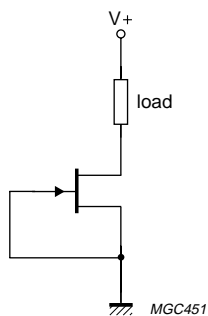


Fig.1 Simple JFET current source.

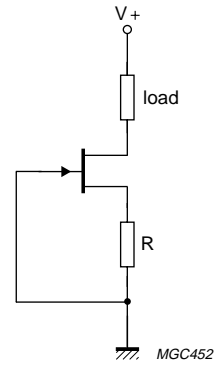


Fig.2 Adjustable JFET current source.

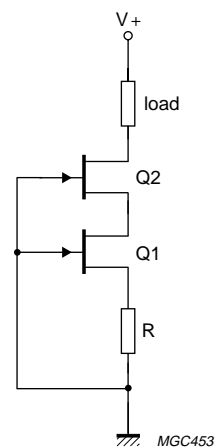


Fig.3 Adjustable JFET current source with high output impedance.

Small-signal Field-effect Transistors

Ideas for design

JFET SOURCE FOLLOWERS AND AMPLIFIERS

There are normally three major considerations to be taken into account when designing amplifiers: voltage gain, distortion and noise, and the importance of each of these depends on the application. This is also true for the type of circuit configuration used. There are three basic circuit configurations for JFETs:

- Common source configuration (CSC)
- Common gate configuration (CGC)
- Common drain configuration (CDC).

The choice of circuit configuration depends on the design requirements with respect to:

- Input impedance (high in CSC and CDC)
- Impedance matching to signal source and load
- Distortion (lowest in CGC).

Common-drain amplifiers, or source followers, and common-source amplifiers are analogous to emitter followers and common-emitter amplifiers in bipolar transistors. However, the absence of DC gate current makes it possible to realize very high input impedances. Such amplifiers are essential when dealing with the high-impedance signal sources encountered in measurement and instrumentation.

It is convenient to use a self-biasing scheme with a single gate-biasing resistor to ground.

Figure 4 shows a source follower, Fig.5 a common-source amplifier. The gate-biasing resistor can be quite large (at least 1 M Ω), because the gate leakage current is in the order of nA.

Matched FETs can be used to construct high input impedance front-end stages for bipolar differential amplifiers, op-amps and comparators.

There are many applications in which the signal source impedance is intrinsically high, e.g. capacitor microphones, pH probes, charged particle detectors, or microelectrode signals in biology and medicine. In these cases a FET input stage is ideal.

Within some circuits there are situations where the following stage must draw little or no current. Common examples are analog 'sample and hold' and 'peak detector' circuits, in which the level is stored in a capacitor and will 'droop' if the next amplifier draws significant input current. In all these applications the negligible input current of a FET is an important feature.

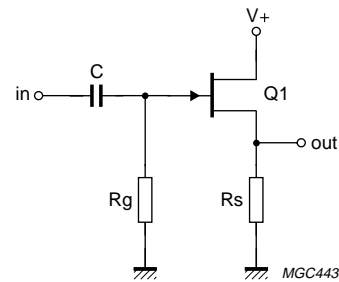


Fig.4 JFET source follower circuit.

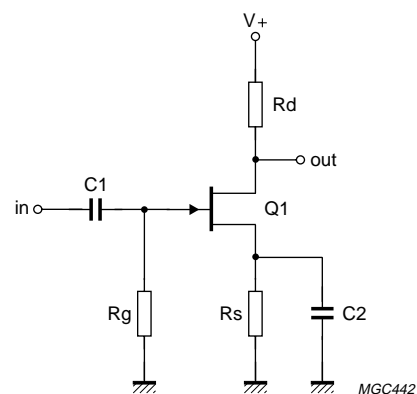


Fig.5 Common-source amplifier circuit.

Small-signal Field-effect Transistors

Ideas for design

JFET VOLTAGE CONTROLLED RESISTORS

Under certain biasing conditions, the on-resistance of the JFET is a function of the gate source voltage alone, so that the JFET will behave as an almost pure ohmic resistor.

Figure 6 shows the output characteristics of a PMBF4416 for relatively small positive and negative values of V_{DS} in the linear or triode region, where $V_{DS} < V_{GS} - V_{GSth}$. It can be seen that all characteristics pass through the origin (no offset) and are symmetrical and relatively linear. This means that the JFET can be used as a variable resistance in voltage controlled attenuators, analog multipliers, amplitude modulators, bandwidth controlled filters, automatic gain control circuits, and so on.

The channel resistance in the linear region is the inverse of the transconductance in the saturated region:
 $R_{DS} = 1/g_m$ at a given V_{GS} .

In the first quadrant, the boundaries are set by $V_{GS} = 0$ and $V_{GD} = -V_{GSth}$, in the third quadrant by $V_{GS} = -V_{GSth}$ and $V_{GD} = 0$.

In the first quadrant, as V_{DS} increases towards $V_{DSsat} = V_{GS} - V_{GSth}$, the value of R_{DSon} changes, causing distortion in voltage-controlled-resistor circuits. The same thing happens in the third quadrant, as the negative drain voltage exceeds the negative gate voltage and causes the gate-channel diode to start conducting.

This signal distortion must be as low as possible, while at the same time a large signal handling capability is desirable. The linearity can be improved by means of feedback from the drain to the gate (see Fig.7).

Now, part of the drain signal is applied to the gate. In the case of a positive V_{DS} signal, this reduces the gate voltage, increasing the drain current and pushing the bias line into the more linear part of the operating region.

When V_{DS} is negative, V_{GS} will go more negative, causing a reduction in drain current. This reduces the conduction of the gate channel diode, resulting in a more linear bias line.

The value of $R1$ and $R2$ should be equal, to maintain symmetry between the first and third quadrants.

Feedback is essential for a reasonably linear characteristic, and high values of I_{DSS} and V_{GSth} are preferred.

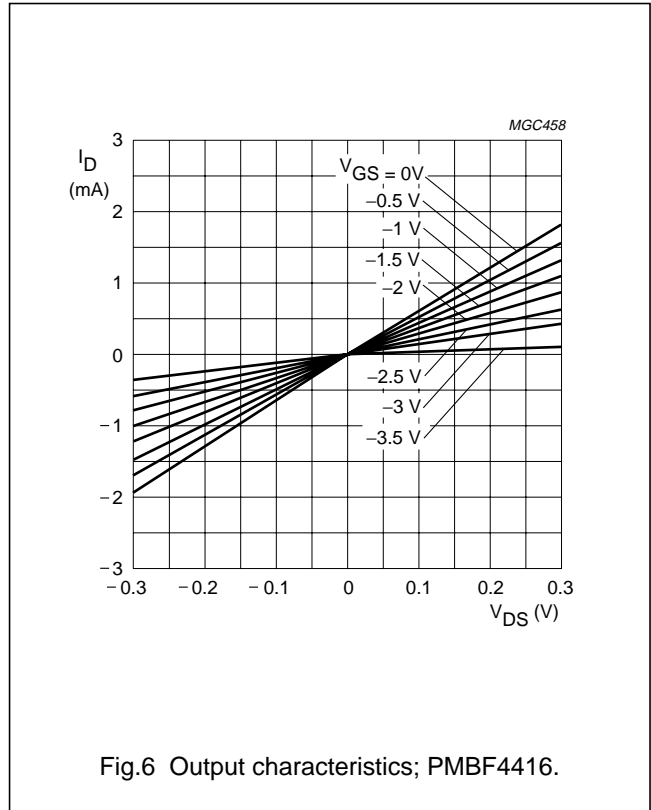


Fig.6 Output characteristics; PMBF4416.

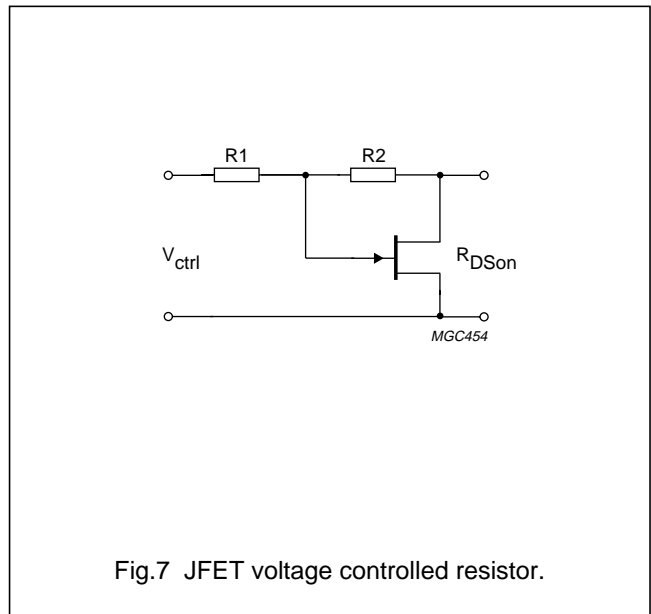


Fig.7 JFET voltage controlled resistor.

Small-signal Field-effect Transistors

Ideas for design

MOS-FET ANALOG SWITCHES

The combination of low on-resistance, extremely high off-resistance, low leakage current and low capacitance, makes FETs, particularly lateral MOS-FETs, ideal as voltage-controlled switching elements for analog signals.

Like mechanical switches, the FET switch is a bi-directional device; signals can go either way through it.

The circuit as shown in Fig.8 will switch signals in the -10 to $+10$ V range if the gate has been driven from -15 V (off) to $+15$ V (on); the body (back-gate) should then be tied to -15 V.

With any FET switch it is important to provide a load resistance in the 1 to 100 k Ω range in order to reduce capacitive feed-through of the input signal, that would otherwise occur during the off-state. If it is necessary to switch signals that may nearly reach the supply voltages, the simple N-channel switch shown in Fig.8 will not work, since the gate is not forward biased at the peak of the signal swing.

The solution is to use paralleled complementary MOS-FET switches (Fig.9). In this case the gate-drive is somewhat more complicated, since the N-channel FET needs to be positive biased with respect to the back-gate and the P-channel negative biased. This switch is also bidirectional; either terminal can be the input.

A useful application of FET analog switches is the 'multiplexer', a circuit that allows you to select any of several inputs, as specified by a control signal. The analog signal present on the selected input will be passed through to the output.

Because analog switches are bidirectional, an analog multiplexer is also a 'demultiplexer'; a signal can be fed into the output and will appear on the selected input.

Voltage-controlled analog switches form essential building blocks for op-amps, integrators, sample-and-hold circuits and peak detectors.

Another application is in switchable RC low-pass filters. A multiplexer is used to select one out of a series of resistors, or independent switches are used to select one or more resistors in parallel.

As stated before, a load resistor is necessary to reduce capacitive feed-through (cross-talk).

If a switch that has really low cross-talk performance is needed, the circuit shown in Fig.10 could be used. When switches Q1 and Q2 are off, Q3 is on and will prevent any capacitive feed-through.

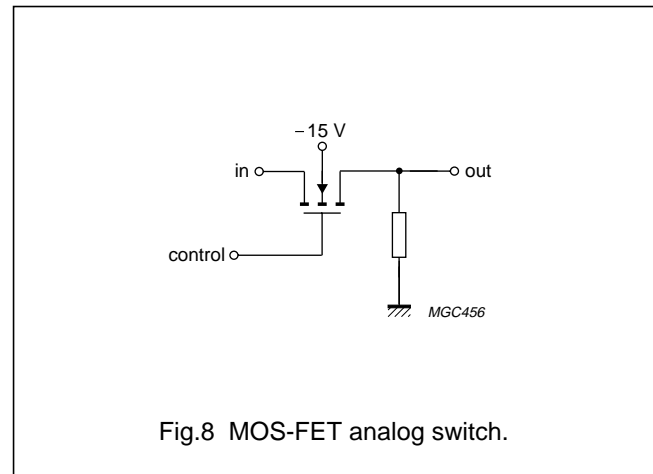


Fig.8 MOS-FET analog switch.

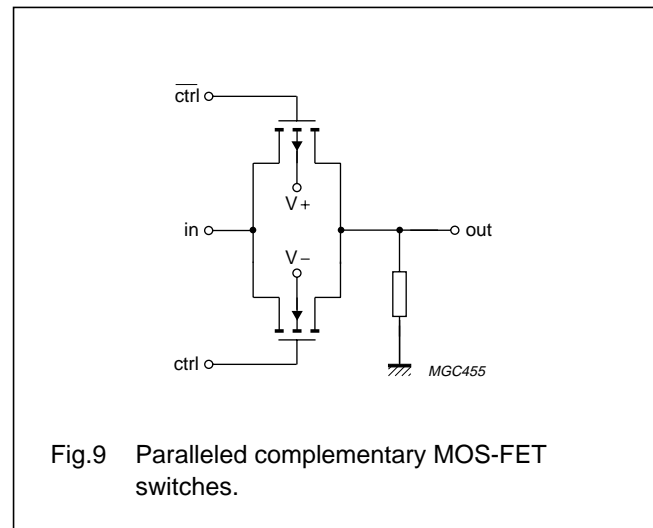


Fig.9 Paralleled complementary MOS-FET switches.

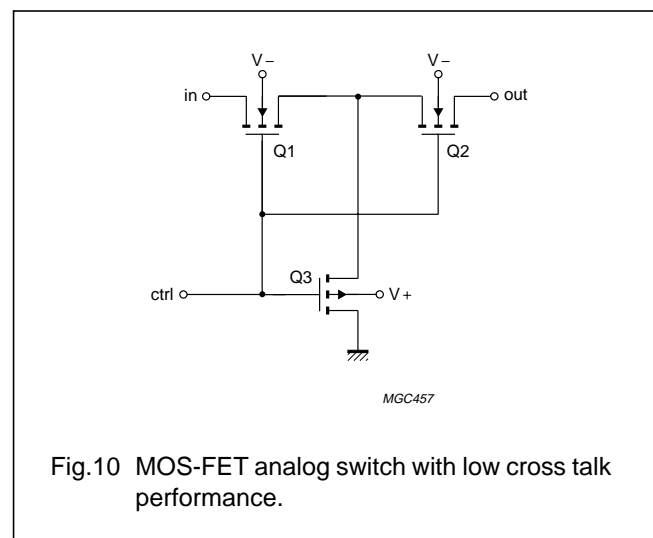


Fig.10 MOS-FET analog switch with low cross talk performance.

SUNSTAR 商斯达实业集团是集研发、生产、工程、销售、代理经销、技术咨询、信息服务等为一体的高科技企业，是专业高科技电子产品生产厂家，是具有 10 多年历史的专业电子元器件供应商，是中国最早和最大的仓储式连锁规模经营大型综合电子零部件代理分销商之一，是一家专业代理和分销世界各大品牌 IC 芯片和电子元器件的连锁经营综合性国际公司，专业经营进口、国产名厂名牌电子元件，型号、种类齐全。在香港、北京、深圳、上海、西安、成都等全国主要电子市场设有直属分公司和产品展示展销窗口门市部专卖店及代理分销商，已在全国范围内建成强大统一的供货和代理分销网络。我们专业代理经销、开发生产电子元器件、集成电路、传感器、微波光电元器件、工控机/DOC/DOM 电子盘、专用电路、单片机开发、MCU/DSP/ARM/FPGA 软件硬件、二极管、三极管、模块等，是您可靠的一站式现货配套供应商、方案提供商、部件功能模块开发配套商。商斯达实业公司拥有庞大的资料库，有数位毕业于著名高校——有中国电子工业摇篮之称的西安电子科技大学（西军电）并长期从事国防尖端科技研究的高级工程师为您精挑细选、量身订做各种高科技电子元器件，并解决各种技术问题。

微波光电部专业代理经销高频、微波、光纤、光电元器件、组件、部件、模块、整机；电磁兼容元器件、材料、设备；微波 CAD、EDA 软件、开发测试仿真工具；微波、光纤仪器仪表。欢迎国外高科技微波、光纤厂商将优秀产品介绍到中国、共同开拓市场。长期大量现货专业批发高频、微波、卫星、光纤、电视、CATV 器件：晶振、VCO、连接器、PIN 开关、变容二极管、开关二极管、低噪晶体管、功率电阻及电容、放大器、功率管、MMIC、混频器、耦合器、功分器、振荡器、合成器、衰减器、滤波器、隔离器、环行器、移相器、调制解调器；光电子元件和组件：红外发射管、红外接收管、光电开关、光敏管、发光二极管和发光二极管组件、半导体激光二极管和激光器组件、光电探测器和光接收组件、光发射接收模块、光纤激光器和光放大器、光调制器、光开关、DWDM 用光发射和接收器件、用户接入系统光收发器件与模块、光纤连接器、光纤跳线/尾纤、光衰减器、光纤适配器、光隔离器、光耦合器、光环行器、光复用器/转换器；无线收发芯片和模组、蓝牙芯片和模组。

更多产品请看本公司产品专用销售网站：

商斯达中国传感器科技信息网：<http://www.sensor-ic.com/>

商斯达工控安防网：<http://www.pc-ps.net/>

商斯达电子元器件网：<http://www.sunstare.com/>

商斯达微波光电产品网：[HTTP://www.rfoe.net/](http://www.rfoe.net/)

商斯达消费电子产品网：<http://www.icasic.com/>

商斯达实业科技产品网：<http://www.sunstars.cn/> 微波元器件销售热线：

地址：深圳市福田区福华路福庆街鸿图大厦 1602 室

电话：0755-82884100 83397033 83396822 83398585

传真：0755-83376182 (0) 13823648918 MSN: SUNS8888@hotmail.com

邮编：518033 E-mail:szss20@163.com QQ: 195847376

深圳赛格展销部：深圳华强北路赛格电子市场 2583 号 电话：0755-83665529 25059422

技术支持：0755-83394033 13501568376

欢迎索取免费详细资料、设计指南和光盘；产品凡多，未能尽录，欢迎来电查询。

北京分公司：北京海淀区知春路 132 号中发电子大厦 3097 号

TEL: 010-81159046 82615020 13501189838 FAX: 010-62543996

上海分公司：上海市北京东路 668 号上海赛格电子市场 D125 号

TEL: 021-28311762 56703037 13701955389 FAX: 021-56703037

西安分公司：西安高新开发区 20 所(中国电子科技集团导航技术研究所)

西安劳动南路 88 号电子商城二楼 D23 号

TEL: 029-81022619 13072977981 FAX:029-88789382