

**XEMICS**

---

**AN8000.03**  
***Application note***

---

**XE8851 DACs usage**

*For further information please contact*  
**XEMICS SA,**  
*Tel: +41 32 7205 511 Fax: +41 32 7205 770*  
[www.xemics.ch](http://www.xemics.ch)

---

## 1 Introduction

This application note concerns the XE8851R and XE8851M products.

## 2 Analog outputs

The PWM DACs available in all XE8000 products are described in the XE8000 series data book, TIMERS chapter.

The XE8851 has two additional digital to analog converters (DAC): a signal DAC able to pass a 4 KHz signal with 10 bits precision, and a bias DAC, able to output 10 mA to bias a resistive bridge sensor. Both are DACs formed from a generic DAC and an amplifier. This makes current and voltage drive possible and gives the user freedom to choose the preferred filtering scheme.

### 2.1 DAC Signal

#### 2.1.1 Application

The DAC signal block described in this document converts a digital signal into an analog output signal (voltage output or 4-20mA loop).

#### 2.1.2 Typical external components

External components are needed for the filtering of the generic DAC output. These external components depend on the characteristics the customer wants to obtain. Some application examples are shown in this document.

External resistors are required to fix the gain of the output amplifier. This gives the user freedom to set the output range of the block within certain limits.

In case the output signal is given through a 4-20mA loop, an external transistor is needed to generate the output current and some resistors to sense the current.

#### 2.1.3 Block diagram

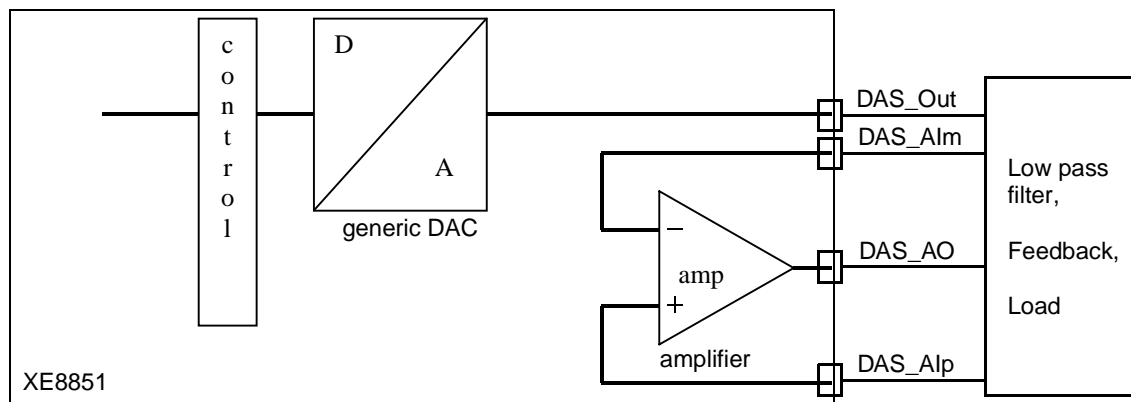


Figure 2.1: General block diagram

Figure 2.1 shows the general block diagram of the peripheral. It consists of a control block that manages all communication with the CPU, sets the configuration of the peripheral and implements the different test modes. The DAC converts the digital data in a PWM output signal. A completely independent amplifier is added. This allows the user to build a low impedance voltage output after the (external, probably passive) filter. It also allows building of a 4-20mA loop. (See amplifier section below for examples)

### 2.1.4 The generic DAC

The generic DAC block consists of two major parts: the noise shaper and the PWM modulator as shown in Figure 2.2.

 


Figure 2.2: The DAC signal structure

The DAC word width on input is 16 bit. If the word is narrower, 0's have to be added after the LSB to fill the 16 bits. To maintain maximum flexibility, the order of the noise shaper and the resolution of the PWM modulation are programmable by writing the codes **code\_lmax** and **ns\_order** to the configuration register. The possible noise shaper order is 0, 1 or 2. With noise shaper order 0, the generic DAC is a conventional PWM DAC. The possible PWM modulation resolution can be set between 4 and 11.

The purpose of the noise shaper is to increase the DAC resolution by changing the PWM input code such that the mean code is equal to the DAC input code. As an example, the PWM can directly generate codes h8000 and h8020, but not h8010, so if one wants to generate code h8010, the modulator will force PWM to issue alternatively code h8020 and code h8000. As the high frequencies have to be filtered out of the PWM signal, the increase in resolution is made at no extra cost. A first order noise shaper should be used with a first order filter, and a second order noise shaper needs a second order filter.

When using noise shaper, PWM period can be made smaller with same accuracy as without the noise shaper. This increases the system bandwidth accordingly, at the cost of some losses in linearity for full scale signals.

With a first order noise shaper, optimal filtering of the modulation is made with a first order filter, and so resolution is proportional to the number of samples. With a second order noise shaper, optimal filtering is made with a second order filter and so resolution is increasing much faster.

Filter corner frequency must be placed such that it rejects the fundamental frequency below the LSB (worst case is for the code having a duty cycle of 0.5, that is h8000) and that it averages a sufficient number of PWM codes.

One can define the following variables:

1. FC is the DAC main clock frequency
2. PWMresolution is the resolution reached by the PWM without the noise shaper
3. DACresolution is the resolution reached by the DAC
4. FPWM is the frequency associated with the period of the PWM
5. FF1 is the 1st order filter corner frequency required for suppressing the fundamental frequency of the PWM below the DAC resolution
6. FF2 is the 2nd order filter corner frequency required for suppressing the fundamental frequency of the PWM below the DAC resolution

One have the following relations:

1.  $FPWM = FC / 2^{PWMresolution}$
2.  $FF1 = FPWM / (DACresolution/2 - 1)$
3.  $FF2 = FPWM / ((DACresolution/2)^{0.5} - 1)$

**AN8000.03****Application Note**

Example for reaching 12 bits resolution with a 1 MHz clock and 4 bits on the PWM:

$$FPWM = 1 \text{ MHz} / 2^4 = 62.5 \text{ kHz}$$

$$FF1 = 62.5 \text{ kHz} / (2^{12} / 2 - 1) = 30 \text{ Hz}$$

$$FF2 = 62.5 \text{ kHz} / ((2^{12} / 2)^{0.5} - 1) = 1.4 \text{ kHz}$$

DACs and filter settings are resumed in Table 2.1

noise shaper order	PWM resolution in bits	DAC maximum resolution in bits	PWM sample output rate (1)	low passfilter type	filter corner frequency for maximum resolution (1)	filter corner frequency for 12 bits resolution (1)	filter corner frequency for 8 bits resolution (1)
0	4	4	62.5 kHz	1st order			
0	4	4	62.5 kHz	2nd order			
0	5	5	31 kHz	1st order			
0	11	11	500 Hz	1st order			3.8 Hz
0	11	11	500 Hz	2nd order			47 Hz
1	4	16	62.5 kHz	1st order		30 Hz	490 Hz
1	5	16	31 kHz	1st order		15 Hz	246 Hz
1	11	16	500 Hz	1st order		0.23 Hz	3.8 Hz
2	4	16	62.5 kHz	2nd order		1.4 kHz	6 kHz
2	5	16	31 kHz	2nd order		700 Hz	3 kHz
2	10	16	1 kHz	2nd order		22 Hz	95 Hz
2	11	16	500 Hz	2nd order		11 Hz	47 Hz

**Table 2.1: DAC settings examples**

**Note:** 1) For 1MHz main clock

### 2.1.5 The amplifier

The amplifier can be used in several configurations. Because of this, it is not connected internally. The first possibility is to use a normal voltage output. In this case, the amplifier is set as a normal inverting gain amplifier. It is not recommended to use the amplifier in unity gain configuration. The advantage of inverting the amplifier is that its common mode is fixed at a given voltage. This reduces the non-linearity. The matching between the external resistors setting the gain does not have to be very precise, since errors can be corrected by predistortion of the digital input code written to the A/D by the CPU. Figure 2.3 gives an application example for a voltage output configuration and a first order low pass filter at the PWM output.

 


Figure 2.3: Output configuration for a first order low pass filter and voltage output. DAS-Alp must be connected to a voltage source (like a resistive voltage divider between VDD and VSS).

A second possibility is a 4-20mA loop, not including the circuit consumption. In this case an external transistor is needed in order to deliver the required current. Figure 2.4 shows an example of such a configuration with again a first order low pass filter.

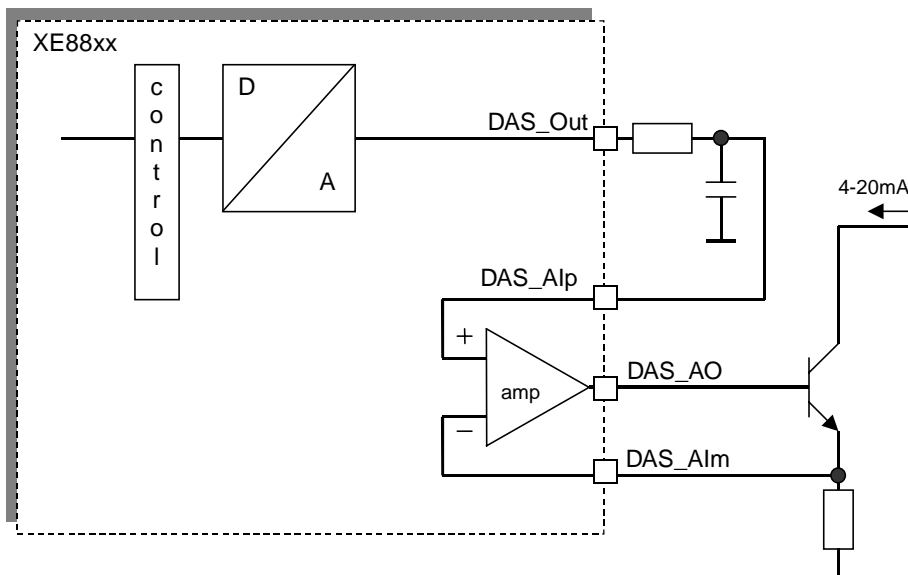


Figure 2.4: 4-20mA loop configuration without the circuit consumption (first order low pass)

Finally, a 4-20mA loop can be build including the consumption of the circuit. In this case the current consumption of the circuit itself has to be included in the sense resistor, while the sense voltage of the amplifier should stay within the supply voltages of the circuit. An example of such a circuit is given in Figure 2.5.

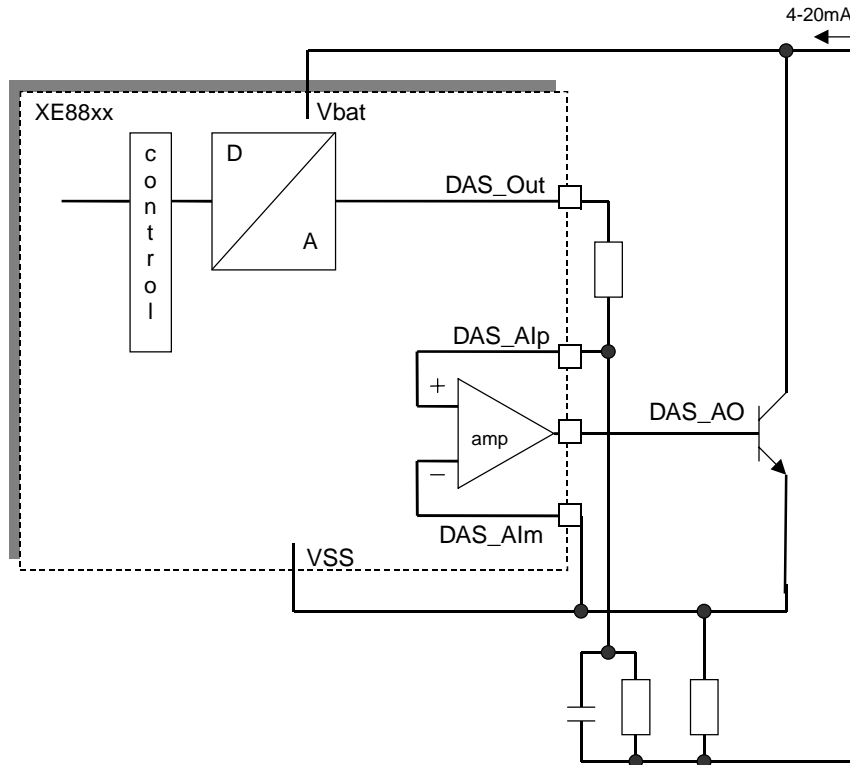


Figure 2.5: 4-20mA loop including the circuit (and bridge) current consumption (first order low pass)

In the case of a 2 wire current loop, the capacitive load of the output amplifier is much smaller than in the case of the voltage output configuration. However, the required bandwidth of the amplifier is higher since it has to be capable to react at all current consumption modifications of the circuit. Therefore, the amplifier bandwidth is made programmable.

sym	description	min	typ	max	unit	Comments
gain	gain at DC	80			dB	1
GBW0	gain bandwidth product	25			kHz	7
cl0	capacitive load			5	nF	7
GBW1	gain bandwidth product	250			kHz	8
cl1	capacitive load			200	pF	8
fm	phase margin	55			°	9
rl	resistive load	5			kohm	6
SR	slew rate	10			kV/s	5
CMR	common mode input range	vss-0.2		vdd-1.2	V	2
OR	output range	vss+0.2		vdd-0.2	V	
voff	offset			±5	mV	
CMRR	common mode rejection	60			dB	3
noise	integrated input noise			100	mVrms	
PSRR	power supply rejection ratio	20			dB	4
ibias	quiescent bias current		200	500	uA	
ioff	off current			1	uA	

Table 2.2: DAC signal amplifier performances

**Notes:** 1. For the minimal resistive load and the maximal capacitive load

**Application Note****AN8000.03**

- Notes:**
2. The amplifier common mode is vss in the 4-20mA loop (Figure 6).
  3. At DC
  4. At DC. Only a low rejection ratio is needed since the DAC output refers directly to the power supplies.
  5. For maximal load cl0, BW=0 and maximal resistive load rl
  6. Short circuit protection at ~5mA.
  7. GBW when the maximal load is cl0 and with the bit BW=0
  8. GBW when the maximal load is cl1 and with the bit BW=1
  9. In both cases BW=0 and BW=1 for the maximal capacitive load and the minimal resistive load.

**2.1.6 DAC signal registers**

register name	address (hex)	comments
RegDasInLsb	H0068	input code (LSB)
RegDasInMsb	H0069	input code (MSB)
RegDasCfg0	H006A	DAC settings
RegDasCfg1	H006B	

**Table 2.3: DAC signal registers**

bit	name	reset	rw	description
7-6	NsOrder	0 resetsystem	r w	modulator order
5-3	CodeImax	0 resetsystem	r w	PWM resolution
2-1	Enable	0 resetsystem	r w	DAC and buffer enable
0	Fin	0 resetsystem	r w	input frequency selection

**Table 2.4: RegDasCfg0**

bit	name	reset	rw	description
7-2	reserved	0 resetsystem	r w	
1	BW	0 resetsystem	r w	output bandwidth selection
0	Inv	0 resetsystem	r w	output polarity selection

**Table 2.5: RegDasCfg1**

The input data will have to be resynchronized with respect to the peripheral clock. To guarantee data integrity, the data will not be copied to the DAC while the interface signal cs is high and readwrite is low. In order to guarantee the synchronization of the MSB and LSB part of the input data, a validity flag will be reset when the CPU is writing into the LSB register and set again when the CPU is writing to the MSB register. The contents of the registers will not be copied to the DAC while the validity flag is reset. This means that the CPU always has to write the LSB register before writing the MSB register.

The different set-up words (set-up register definition in Table 2.4) are coded as indicated in the tables below.

ns_order(1:0)	Noise shaping order
00	0
01	1
1x	2

**Table 2.6: Noise shaping setting**

code_lmax	m (PWM resolution in bits)
000	4
001	5
010	6
011	7
100	8
101	9
110	10

**Table 2.7: PWM setting**

code_lmax	m (PWM resolution in bits)
111	11

**Table 2.7: PWM setting**

enable(1:0)	Peripheral status
00	DAC: switched off; Amplifier switched off
01	DAC: normal operation; Amplifier: switched off
10	DAC: switched off; Amplifier: normal operation
11	normal operation

**Table 2.8: DAC status**

The **Fin** bit allows the choice between two clock inputs that can be connected in two different places of the prescaler of the XE8000.

fin	used clock input	input clock frequency for RC at 1MHz
0	ckRC	1 MHz
1	ck500k	500 kHz

**Table 2.9: Clock setting**

Finally, the **inv** bit indicates if the PWM output pulse is active low or active high. This makes possible the use of the output amplifier in an inverting (e.g. in Figure 2.3) or not inverting configuration (e.g. in Figure 2.4).

inv	PWM pulse
0	active high
1	active low

**Table 2.10: PWM polarity**



## 2.2 DAC bias

### 2.2.1 Application

The DAC\_bias block described in this document converts a digital signal into an analog output signal in DC. It can be used to bias resistive sensors. In some cases it could also be used to do a rough offset calibration of a resistive bridge.

### 2.2.2 Typical external components

No other external devices are needed in case of voltage controlled bridge bias. An additional resistor is needed for current controlled bridge bias.

### 2.2.3 Block diagram

 


Figure 2.6: General block diagram

Figure 2.6 shows the general block diagram of the peripheral. It consists of a control block that manages all communication with the CPU, sets the configuration of the peripheral and implements the different test modes. The DAC converts the digital data in an analog output signal. An amplifier is added in order to be able to deliver large currents.

### 2.2.4 The DAC

The DAC convertor is a resistive divider connected between pads DAB\_R\_m and DAB\_R\_p.

sym	description	min	typ	max	unit	Comments
wda	number of input bits		8		bits	
tstep	step response			100	ms	1
range	DAC output range	DAB_R_m		DAB_R_p		2

Table 2.11: DAC performances

- Notes:**
- 1) Time to reach the final value within 5%.
  - 2) In most cases DAB\_R\_m will be connected to vss and DAB\_R\_p to vdd.

### 2.2.5 The amplifier

The amplifier can be used in several configurations for biasing a bridge in voltage or current. Application examples are given in the following figures. Figure 2.7 shows a configuration for the voltage biased bridge. Figure 2.8 shows a configuration for a current biased bridge.

sym	description	min	typ	max	unit	Comments
gain	gain at DC	60			dB	1
GBW	gain bandwidth product	100			Hz	1
fm	phase margin	60			°	1
rl	resistive load	300		100000	ohm	5,6
cl	capacitive load			1	nF	
CMR	common mode input range	vss		vdd	V	
OR	output range	vss+0.2		vdd-0.2	V	3,4
outp vr	outp pin voltage range	vss+2.3		vdd	V	
voff	offset			±10	mV	
noise	integrated input noise			100	uVrms	
isourc	max source current			10	mA	
PSRR	power supply rejection ratio	40			dB	2
ibias	quiescent bias current		2	5	uA	6
ioff	off current			1	uA	

Table 2.12: Amplifier performances

- Note:** 1) For all possible combinations of resistive load and capacitive load.
- Note:** 2) At DC.
- Note:** 3) For voltage controlled bias control. For current controlled operation the voltage drop on the pMOS output transistor has to be less than 200mV at maximum current.
- Note:** 4) Special analog output pads without series resistor will be needed in order to get the specification. Care has to be taken with the layout so that ESD and latchup specifications can be met.
- Note:** 5) Short circuit protection at ~80mA.
- Note:** 6) This amplifier must be loaded for correct operation. Ibias is without load current.

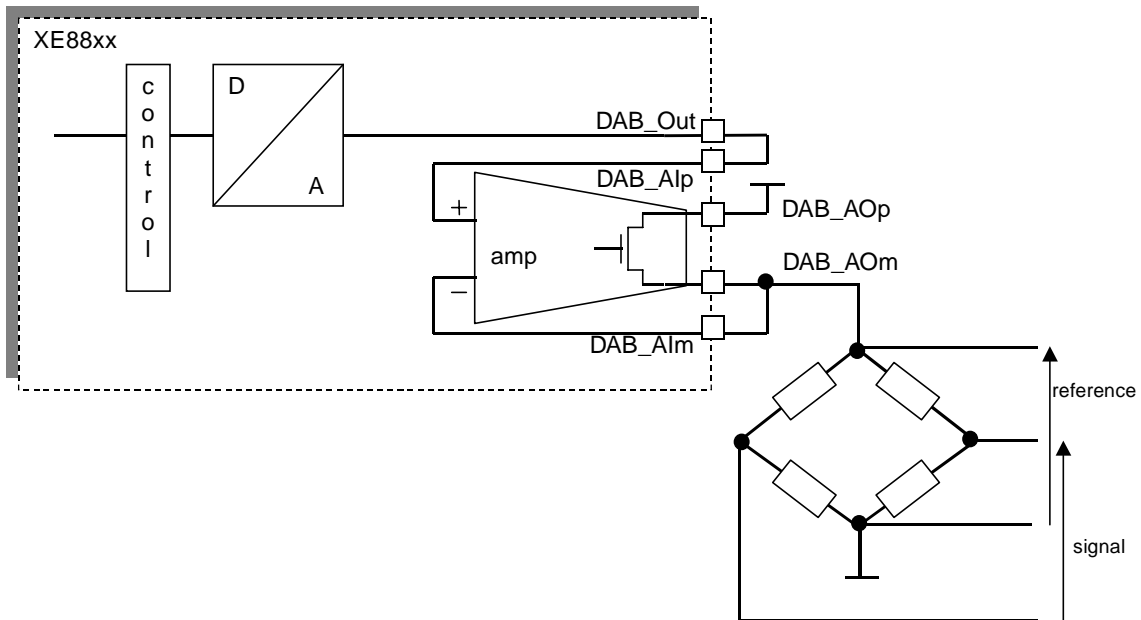


Figure 2.7: Voltage controlled bridge bias

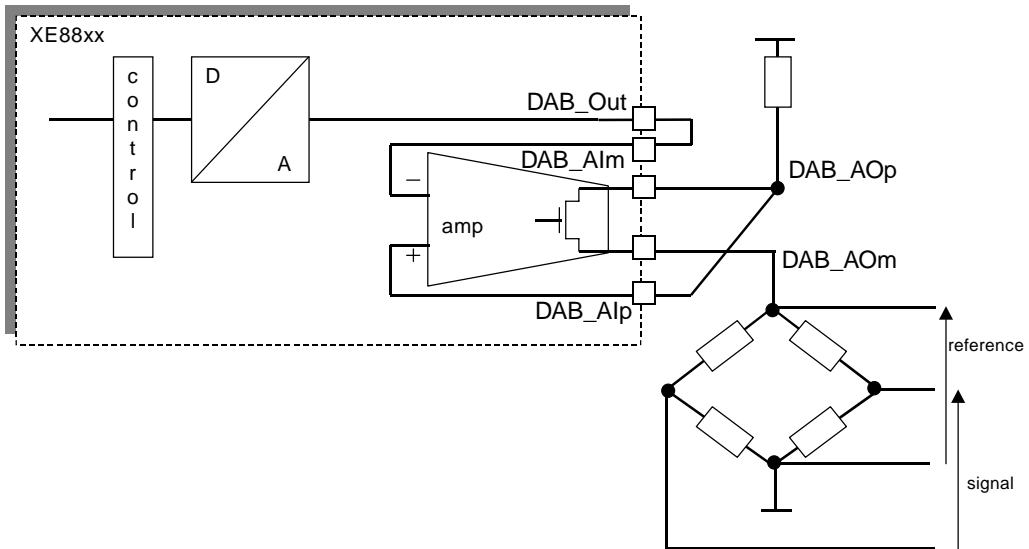


Figure 2.8: Current controlled bridge bias

### 2.2.6 DAC bias registers

register name	address (hex)	comments
RegDab1In	H006C	input code
RegDab1Cfg	H006D	DAC settings

Table 2.13: DAC bias registers

enable(1:0)	Peripheral status
00	DAC disabled, amplifier disabled
01	DAC: normal operation; Amplifier: switched off
10	DAC: switched off; Amplifier: normal operation
11	DAC: enabled; Amplifier: enabled

Table 2.14: RegDab1Cfg

Copyright XEMICS

All rights are reserved. Reproduction whole or in part is prohibited without the prior written consent of the copyright owner. The information presented in this document does not form part of any quotation or contract, is believed to be accurate and reliable and may be changed without notice. No liability will be accepted by the publisher for any consequence of its use. Publication thereof does not convey nor imply any license under patent- or other industrial or intellectual property rights.

Printed in Switzerland

Date of release 04-99

A904-043 - AN8000.03 Application Note: XE8851 DACs usage

SUNSTAR 商斯达实业集团是集研发、生产、工程、销售、代理经销、技术咨询、信息服务等为一体的高科技企业，是专业高科技电子产品生产厂家，是具有 10 多年历史的专业电子元器件供应商，是中国最早和最大的仓储式连锁规模经营大型综合电子零部件代理分销商之一，是一家专业代理和分销世界各大品牌 IC 芯片和电子元器件的连锁经营综合性国际公司，专业经营进口、国产名厂名牌电子元件，型号、种类齐全。在香港、北京、深圳、上海、西安、成都等全国主要电子市场设有直属分公司和产品展示展销窗口门市部专卖店及代理分销商，已在全国范围内建成强大统一的供货和代理分销网络。我们专业代理经销、开发生产电子元器件、集成电路、传感器、微波光电元器件、工控机/DOC/DOM 电子盘、专用电路、单片机开发、MCU/DSP/ARM/FPGA 软件硬件、二极管、三极管、模块等，是您可靠的一站式现货配套供应商、方案提供商、部件功能模块开发配套商。商斯达实业公司拥有庞大的资料库，有数位毕业于著名高校——有中国电子工业摇篮之称的西安电子科技大学（西军电）并长期从事国防尖端科技研究的高级工程师为您精挑细选、量身订做各种高科技电子元器件，并解决各种技术问题。

微波光电部专业代理经销高频、微波、光纤、光电元器件、组件、部件、模块、整机；电磁兼容元器件、材料、设备；微波 CAD、EDA 软件、开发测试仿真工具；微波、光纤仪器仪表。欢迎国外高科技微波、光纤厂商将优秀产品介绍到中国、共同开拓市场。长期大量现货专业批发高频、微波、卫星、光纤、电视、CATV 器件：晶振、VCO、连接器、PIN 开关、变容二极管、开关二极管、低噪晶体管、功率电阻及电容、放大器、功率管、MMIC、混频器、耦合器、功分器、振荡器、合成器、衰减器、滤波器、隔离器、环行器、移相器、调制解调器；光电子器件和组件：红外发射管、红外接收管、光电开关、光敏管、发光二极管和发光二极管组件、半导体激光二极管和激光器组件、光电探测器和光接收组件、光发射接收模块、光纤激光器和光放大器、光调制器、光开关、DWDM 用光发射和接收器件、用户接入系统光收发器件与模块、光纤连接器、光纤跳线/尾纤、光衰减器、光纤适配器、光隔离器、光耦合器、光环行器、光复用器/转换器；无线收发芯片和模组、蓝牙芯片和模组。

更多产品请看本公司产品专用销售网站：

商斯达微波光电产品网：[HTTP://www.rfoe.net/](http://www.rfoe.net/)

商斯达中国传感器科技信息网：<http://www.sensor-ic.com/>

商斯达工控安防网：<http://www.pc-ps.net/>

商斯达电子元器件网：<http://www.sunstare.com/>

商斯达消费电子产品网：<http://www.icasic.com/>

商斯达实业科技产品网：<http://www.sunstars.cn/> 射频微波光电元器件销售热线：

地址：深圳市福田区福华路福庆街鸿图大厦 1602 室

电话：0755-83396822 83397033 83398585 82884100

传真：0755-83376182 (0) 13823648918 MSN: SUNS8888@hotmail.com

邮编：518033 E-mail:szss20@163.com QQ: 195847376

深圳赛格展销部：深圳华强北路赛格电子市场 2583 号 电话：0755-83665529 25059422

技术支持：0755-83394033 13501568376

欢迎索取免费详细资料、设计指南和光盘；产品凡多，未能尽录，欢迎来电查询。

北京分公司：北京海淀区知春路 132 号中发电子大厦 3097 号

TEL: 010-81159046 82615020 13501189838 FAX: 010-62543996

上海分公司：上海市北京东路 668 号上海赛格电子市场 D125 号

TEL: 021-28311762 56703037 13701955389 FAX: 021-56703037

西安分公司：西安高新开发区 20 所(中国电子科技集团导航技术研究所)

西安劳动南路 88 号电子商城二楼 D23 号

TEL: 029-81022619 13072977981 FAX:029-88789382