

Application Note

Layout and Power Control for ARA05050 Rev 1

RELEVANT PRODUCTS

ARA05050

LAYOUT CONSIDERATIONS

There are two issues that must be taken into consideration when doing the PCB layout. The first is thermal management, and the second is RF related.

Thermal Layout Considerations

The ARA05050 will typically dissipate 0.9W, and as high as 1.2W. Since the interior of most set-top boxes and cable modems are typically at +70°C, consideration must be given to providing an adequate heat sink for the die to obtain the maximum MTF possible. To this end, the ARA05050 incorporates a heat slug in the bottom of the package, which provides a low thermal resistance path from the die to the outside of the package (See Figure 1). The typical thermal rise from the heat slug to the junction is 35°C/W; however, this is only half of the equation. Adequate heat sinking must be applied to the heat slug for good thermal dissipation. Providing a metalized pad with via holes to ground under the package will do this (see Figure 2). The part is then soldered to this pad during assembly. The recommended solder mask outline is shown in Figure 3.

RF Layout Considerations

The ARA05050 is an amplifier designed to drive a 75 Ohm load. Since this part connects the transmitter to the cable system, typically via a diplexer, at RF frequencies, the layout of the PCB will have an effect on the system performance. The first thing to consider in the RF layout are the connections to ground. These must be low impedance, and as short as possible. The best way to do this is to use a via hole 0.030 inches in diameter, located as close to the ground pin as possible, that connects to the ground plane (see Figure 2). Specifically, care should be given to the layout of the following connections (the traces leading from the following pins to their respective components should be as low in

impedance as is practical.):

Pins 5 & 19: the 20 ohm chip resistor should be as close as possible to the pins and the 1 uF capacitor should be kept close to the 20 ohm resistor.

Pins 6-9 & 20-23: the capacitors should be kept close to the pins.

Pin 11: the 1uF bypass capacitor should be kept close to the pin.

Pin 12: the bypass capacitor at this node should be reasonably close to the pin.

The path leading between pins 4–10, and the path between pins 18–24, should be kept as short as possible.

The bypass capacitors on the V_{DD} lines should be located as close as possible to the 10 uH inductors.

The traces leading to the RF input, and leading away from the RF output, should be 75 Ohms. Care should be taken to keep other traces, which may have clock signals on them, as far away as is practical to prevent unwanted coupling onto the signal line.

OUTPUT DISCONNECT SWITCH

For MCNS/DOCSIS applications an external switch to disconnect the output of the ARA05050 from the diplexer is required. This switch is needed due to the output noise requirement between bursts and the requirement that any shutdown transient not exceed 7mV. The switch shown in Figure 4 meets these conditions because it does not switch any current, or voltage, on the output line. The series FET (Q1) provides 35 dB of isolation, while the shunt FET (Q2) ensures that the diplexer remains terminated into a 75 Ohm impedance. Since the switch does not draw any current, it may be driven directly from a low power CMOS logic inverter; however, the control voltages must be +5V. When the switch is in the open state, it is good general practice

Layout and Power Control for ARA05050

to set the programmable attenuator to its maximum attenuation setting. This will increase the isolation between the cable modem output and upstream modulator, and provide the first stage amplifier with a 75 Ohm termination. The switching speed of the output disconnect switch is shown in Figure 5.

DEVICE SHUTDOWN

In some applications it may be desirable to shut the ARA05050 down for power saving. This can be done

by applying a negative voltage to pin 10 to shut down the input stage, and to pin 24 to shut down output stage (see Figure 6). Shutting down both amplifier stages will reduce the current drawn from the +5V supply to typically 10 mA. If only one stage is shutdown, it is recommended that the programmable attenuator be set to a minimum of 16 dB to provide a good impedance match to the remaining stage.

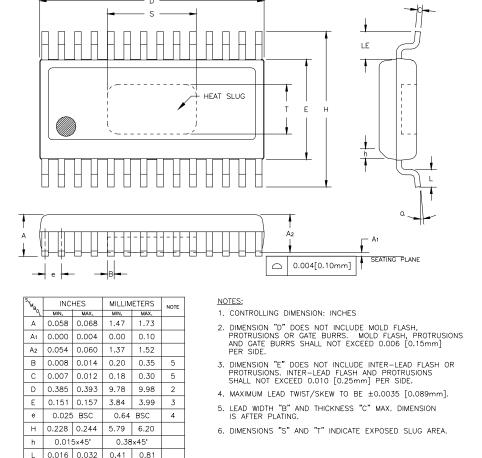


Figure 1: S12 Package Outline - 28 Pin SSOP with Heat Slug

LE 0.042

a l n

S 0.105

0.045

1.07

1 4 1

8

0.135


0.075

8.

3.43


1.91

6

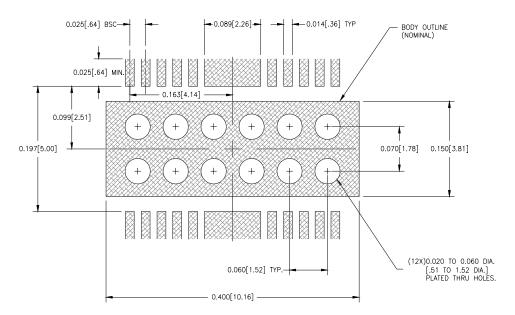

^{*} Dimensions are in Inches [Millimeters]

Figure 2: PC Board Layout

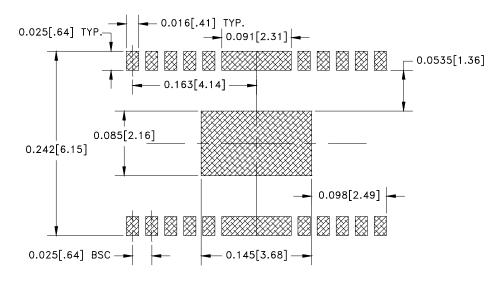

^{*} Dimensions are in Inches [Millimeters]

Figure 3: Solder Mask Outline



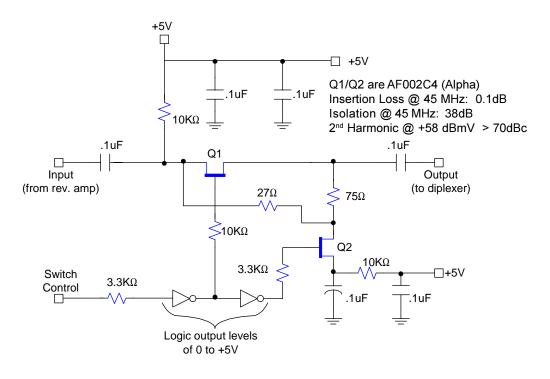


Figure 4: Output Switch

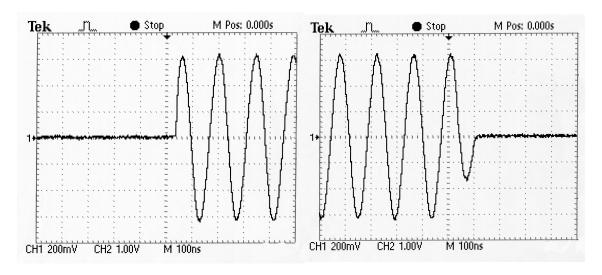


Figure 5: Switching Speed of Output Disconnect Switch

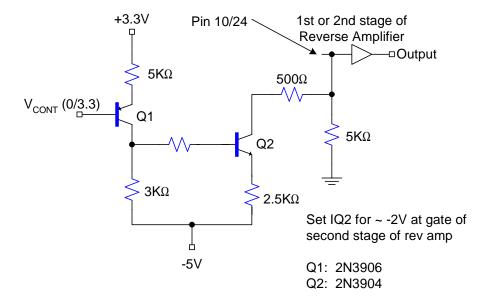


Figure 6: Negative Voltage Shutdown Circuit

Layout and Power Control for ARA05050

NOTES

NOTES





ANADIGICS, Inc.

141 Mount Bethel Road Warren, New Jersey 07059, U.S.A.

Tel: +1 (908) 668-5000 Fax: +1 (908) 668-5132

URL: http://www.anadigics.com E-mail: Mktg@anadigics.com

IMPORTANT NOTICE

ANADIGICS, Inc. reserves the right to make changes to its products or to discontinue any product at any time without notice. The product specifications contained in Advanced Product Information sheets and Preliminary Data Sheets are subject to change prior to a product's formal introduction. Information in Data Sheets have been carefully checked and are assumed to be reliable; however, ANADIGICS assumes no responsibilities for inaccuracies. ANADIGICS strongly urges customers to verify that the information they are using is current before placing orders.

WARNING

ANADIGICS products are not intended for use in life support appliances, devices or systems. Use of an ANADIGICS product in any such application without written consent is prohibited.



SUNSTAR 商斯达实业集团是集研发、生产、工程、销售、代理经销、技术咨询、信息服务等为一体的高科技企业,是专业高科技电子产品生产厂家,是具有 10 多年历史的专业电子元器件供应商,是中国最早和最大的仓储式连锁规模经营大型综合电子零部件代理分销商之一,是一家专业代理和分銷世界各大品牌 IC 芯片和電子元器件的连锁经营綜合性国际公司,专业经营进口、国产名厂名牌电子元件,型号、种类齐全。在香港、北京、深圳、上海、西安、成都等全国主要电子市场设有直属分公司和产品展示展销窗口门市部专卖店及代理分销商,已在全国范围内建成强大统一的供货和代理分销网络。 我们专业代理经销、开发生产电子元器件、集成电路、传感器、微波光电元器件、工控机/DOC/DOM 电子盘、专用电路、单片机开发、MCU/DSP/ARM/FPGA 软件硬件、二极管、三极管、模块等,是您可靠的一站式现货配套供应商、方案提供商、部件功能模块开发配套商。商斯达实业公司拥有庞大的资料库,有数位毕业于著名高校——有中国电子工业摇篮之称的西安电子科技大学(西军电)并长期从事国防尖端科技研究的高级工程师为您精挑细选、量身订做各种高科技电子元器件,并解决各种技术问题。

微波光电部专业代理经销高频、微波、光纤、光电元器件、组件、部件、模块、整机;电磁兼容元器件、材料、设备;微波 CAD、EDA 软件、开发测试仿真工具;微波、光纤仪器仪表。欢迎国外高科技微波、光纤厂商将优秀产品介绍到中国、共同开拓市场。长期大量现货专业批发高频、微波、卫星、光纤、电视、CATV 器件: 晶振、VCO、连接器、PIN 开关、变容二极管、开关二极管、低噪晶体管、功率电阻及电容、放大器、功率管、MMIC、混频器、耦合器、功分器、振荡器、合成器、衰减器、滤波器、隔离器、环行器、移相器、调制解调器;光电子元器件和组件:红外发射管、红外接收管、光电开关、光敏管、发光二极管和发光二极管组件、半导体激光二极管和激光器组件、光电探测器和光接收组件、光发射接收模块、光纤激光器和光放大器、光调制器、光开关、DWDM 用光发射和接收器件、用户接入系统光光收发器件与模块、光纤连接器、光纤跳线/尾纤、光衰减器、光纤适 配器、光隔离器、光耦合器、光环行器、光复用器/转换器;无线收发芯片和模组、蓝牙芯片和模组。

更多产品请看本公司产品专用销售网站:

商斯达中国传感器科技信息网: http://www.sensor-ic.com/

商斯达工控安防网: http://www.pc-ps.net/

商斯达电子元器件网: http://www.sunstare.com/

商斯达微波光电产品网:HTTP://www.rfoe.net/

商斯达消费电子产品网://www.icasic.com/

商斯达实业科技产品网://www.sunstars.cn/ 微波元器件销售热线:

地址:深圳市福田区福华路福庆街鸿图大厦 1602 室

电话: 0755-82884100 83397033 83396822 83398585

传真: 0755-83376182 (0) 13823648918 MSN: SUNS8888@hotmail.com

邮编: 518033 E-mail:szss20@163.com QQ: 195847376

深圳赛格展销部: 深圳华强北路赛格电子市场 2583 号 电话: 0755-83665529 25059422

技术支持: 0755-83394033 13501568376

欢迎索取免费详细资料、设计指南和光盘 : 产品凡多,未能尽录,欢迎来电查询。

北京分公司:北京海淀区知春路 132 号中发电子大厦 3097 号

TEL: 010-81159046 82615020 13501189838 FAX: 010-62543996

上海分公司: 上海市北京东路 668 号上海賽格电子市场 D125 号

TEL: 021-28311762 56703037 13701955389 FAX: 021-56703037

西安分公司: 西安高新开发区 20 所(中国电子科技集团导航技术研究所)

西安劳动南路 88 号电子商城二楼 D23 号

TEL: 029-81022619 13072977981 FAX:029-88789382