

# 950 to 2400 MHz IF Amplifier Using the INA-51063 and INA-54063


## Application Note 1139

### Introduction

IF Amplifiers for DBS applications generally require a high gain amplifier with moderate power output and less than a 5 dB noise figure. This application note describes a suitable amplifier using two integrated circuits. The first stage uses the Hewlett-Packard INA-51063 while the second stage is a Hewlett-Packard INA-54063. The INA-54063 also has an added feature of a positive gain slope which can be used to offset dielectric board losses. A positive gain slope can also be used to offset the customary high end roll-off the low noise amplifier (LNA).

### Circuit Design

The INA-51063 and INA-54063 mmics are designed for nominal  $50\ \Omega$  input and output impedance. The typical LNB has an IF port with a nominal  $75\ \Omega$  output impedance making it compatible with other set-top downconverter and CATV equipment. The INA-54063 is matched to  $75\ \Omega$  with an L network consisting of a shunt L, series L matching network. The matching network resembles a transformer that is tapped-up to make the impedance transformation. The lines can be meandered to fit the allotted space. The

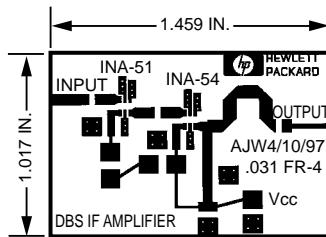

**Figure 1. Original Artwork for DBS IF Amplifier for ER = 4.8 and 0.031 inch thickness PCB**

artwork describing this amplifier is shown in Figure 1.


A schematic diagram and parts list are shown in Figure 2. The amplifier is designed to operate from a power supply voltage of 5 volts. Current draw for the INA-51063 is typically 12 mA and 29 mA for the INA-54063. The power

supply voltage for the INA-51063 is applied at a terminal separate from the output terminal. The INA-54063 requires power supply voltage at both the supply terminal and the RF output port. The output matching network doubles as a bias network.

A  $0.33\ \mu\text{H}$  RF choke is used to provide isolation in the bias circuits between the two stages. Without RFC1, there is potential for feedback in the bias decoupling networks which could result in oscillations.

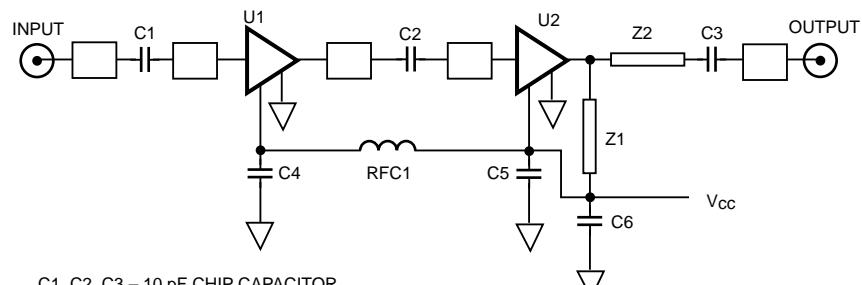
### Device Grounding

The grounding of the devices can greatly effect the performance of the amplifier. The original demo board artwork shown in Figure 1




C1, C2, C3 – 10 pF CHIP CAPACITOR  
 C4, C5, C6 – 1,000 pF CHIP CAPACITOR  
 RFC1 – 0.33  $\mu\text{H}$  RFC 9 (COILCRAFT 1008CS-331)  
 U1 – HEWLETT-PACKARD INA-51063 MMIC  
 U2 – HEWLETT-PACKARD INA-54063 MMIC  
 Z1, Z2 – MATCHING NETWORK


**Figure 2. Schematic Diagram of IF Amplifier**

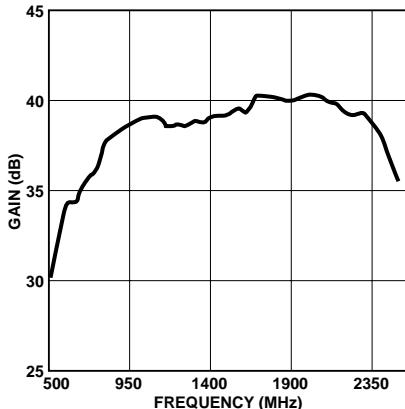

**Figure 3. Amplifier Gain vs. Frequency with Original Grounds**

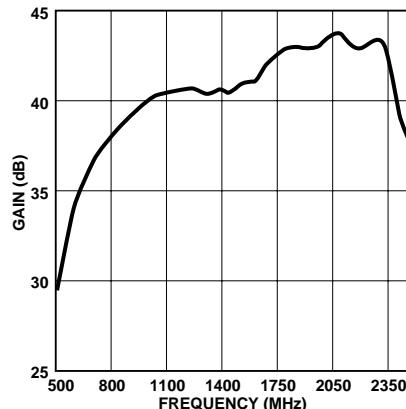

**Figure 4. Amplifier Gain vs. Frequency with Modified Grounds**

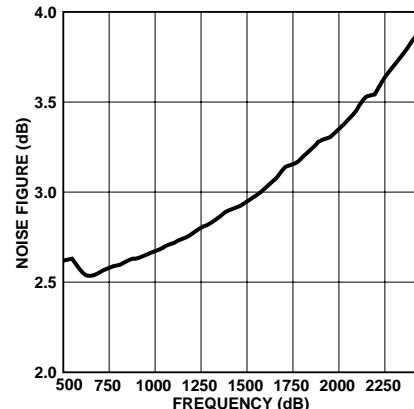


**Figure 5. Amplifier Noise Figure vs. Frequency**

used separate ground pads for each device ground lead. The swept gain plot with  $50\ \Omega$  source and load is shown in Figure 3.

The high-end gain seemed to roll-off at a lower frequency than expected. The INA-54063 data sheet suggests the use of separate ground pads as a way of reducing high end gain peaking. Since the two stage amplifier appeared to lack high-end gain, it was decided to fill in the ground pads on the top side of the board. Results were very good. The high end peaked up and the low end was improved slightly. No instabilities were noticed. A swept gain plot with  $50\ \Omega$  input and output loads is shown in Figure 4.

The revised artwork showing the connected ground pads is shown in Figure 6. Output VSWR with respect to  $75\ \Omega$  is less than 1.5:1 through 1450 MHz and less than 2.0:1 through 2.3 GHz. Typical P1 dB as measured in a  $50\ \Omega$  system was measured at +10 dBm at 1.45 GHz and +5 dBm at 950 MHz and +4.5 dBm at 2300 MHz. P1 dB should improve at 950 MHz when measured in a  $75\ \Omega$  system since that is where the best output match occurs. A plot of noise figure vs. frequency is shown in Figure 5.

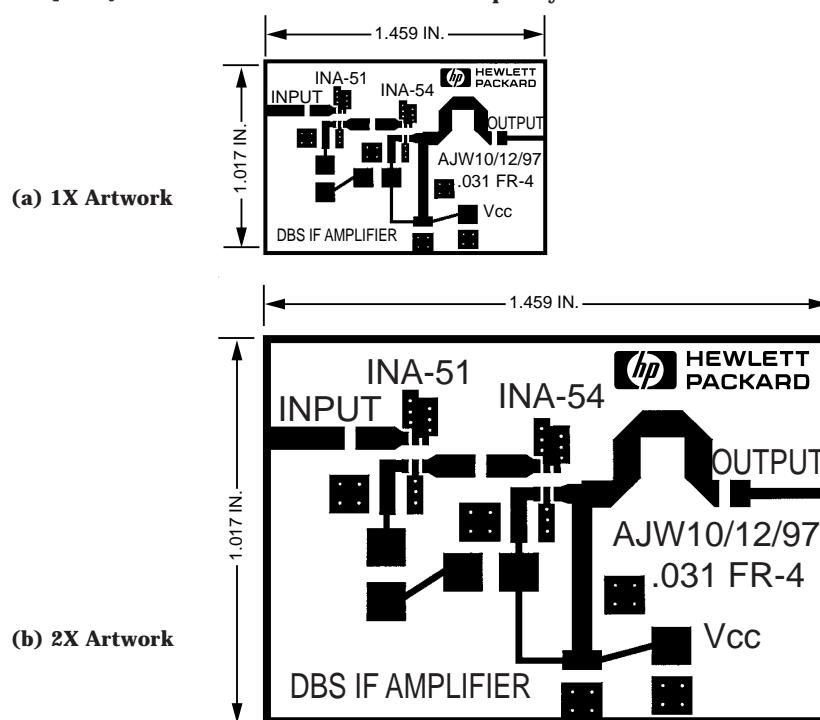

**Figure 6. Revised Artwork for DBS IF Amplifier for ER = 4.8 and 0.031 inch thickness PCB**

## Conclusion

The cascade of the INA-51063 and INA-54063 provides a simple low cost, high gain solution for both DBS and TVRO satellite systems.

The low noise figure coupled with good output compression point at 5 volts provides for a high dynamic range IF amplifier.

## [www.hp.com/go/rf](http://www.hp.com/go/rf)

For technical assistance or the location of your nearest Hewlett-Packard sales office, distributor or representative call:

**Americas/Canada:** 1-800-235-0312 or (408) 654-8675

**Far East/Australasia:** Call your local HP sales office.

**Japan:** (81 3) 3335-8152

**Europe:** Call your local HP sales office.

Data Subject to Change

Copyright © 1998 Hewlett-Packard Co.

Printed in U.S.A. 5966-3363E (7/98)

SUNSTAR 商斯达实业集团是集研发、生产、工程、销售、代理经销、技术咨询、信息服务等为一体的高科技企业，是专业高科技电子产品生产厂家，是具有 10 多年历史的专业电子元器件供应商，是中国最早和最大的仓储式连锁规模经营大型综合电子零部件代理分销商之一，是一家专业代理和分销世界各大品牌 IC 芯片和电子元器件的连锁经营综合性国际公司，专业经营进口、国产名厂名牌电子元件，型号、种类齐全。在香港、北京、深圳、上海、西安、成都等全国主要电子市场设有直属分公司和产品展示展销窗口门市部专卖店及代理分销商，已在全国范围内建成强大统一的供货和代理分销网络。我们专业代理经销、开发生产电子元器件、集成电路、传感器、微波光电元器件、工控机/DOC/DOM 电子盘、专用电路、单片机开发、MCU/DSP/ARM/FPGA 软件硬件、二极管、三极管、模块等，是您可靠的一站式现货配套供应商、方案提供商、部件功能模块开发配套商。商斯达实业公司拥有庞大的资料库，有数位毕业于著名高校——有中国电子工业摇篮之称的西安电子科技大学（西军电）并长期从事国防尖端科技研究的高级工程师为您精挑细选、量身订做各种高科技电子元器件，并解决各种技术问题。

微波光电部专业代理经销高频、微波、光纤、光电元器件、组件、部件、模块、整机；电磁兼容元器件、材料、设备；微波 CAD、EDA 软件、开发测试仿真工具；微波、光纤仪器仪表。欢迎国外高科技微波、光纤厂商将优秀产品介绍到中国、共同开拓市场。长期大量现货专业批发高频、微波、卫星、光纤、电视、CATV 器件：晶振、VCO、连接器、PIN 开关、变容二极管、开关二极管、低噪晶体管、功率电阻及电容、放大器、功率管、MMIC、混频器、耦合器、功分器、振荡器、合成器、衰减器、滤波器、隔离器、环行器、移相器、调制解调器；光电子元器件和组件：红外发射管、红外接收管、光电开关、光敏管、发光二极管和发光二极管组件、半导体激光二极管和激光器组件、光电探测器和光接收组件、光发射接收模块、光纤激光器和光放大器、光调制器、光开关、DWDM 用光发射和接收器件、用户接入系统光光收发器件与模块、光纤连接器、光纤跳线/尾纤、光衰减器、光纤适配器、光隔离器、光耦合器、光环行器、光复用器/转换器；无线收发芯片和模组、蓝牙芯片和模组。

更多产品请看本公司产品专用销售网站：

商斯达中国传感器科技信息网：<http://www.sensor-ic.com/>

商斯达工控安防网：<http://www.pc-ps.net/>

商斯达电子元器件网：<http://www.sunstare.com/>

商斯达微波光电产品网：<HTTP://www.rfoe.net/>

商斯达消费电子产品网：<http://www.icasic.com/>

商斯达实业科技产品网：<http://www.sunstars.cn/> 微波元器件销售热线：

地址：深圳市福田区福华路福庆街鸿图大厦 1602 室

电话：0755-82884100 83397033 83396822 83398585

传真：0755-83376182 (0) 13823648918 MSN：[SUNS8888@hotmail.com](mailto:SUNS8888@hotmail.com)

邮编：518033 E-mail：[szss20@163.com](mailto:szss20@163.com) QQ：195847376

深圳赛格展销部：深圳华强北路赛格电子市场 2583 号 电话：0755-83665529 25059422

技术支持：0755-83394033 13501568376

欢迎索取免费详细资料、设计指南和光盘；产品凡多，未能尽录，欢迎来电查询。

北京分公司：北京海淀区知春路 132 号中发电子大厦 3097 号

TEL：010-81159046 82615020 13501189838 FAX：010-62543996

上海分公司：上海市北京东路 668 号上海赛格电子市场 D125 号

TEL：021-28311762 56703037 13701955389 FAX：021-56703037

西安分公司：西安高新区 20 所(中国电子科技集团导航技术研究所)

西安劳动南路 88 号电子商城二楼 D23 号

TEL：029-81022619 13072977981 FAX:029-88789382