

Using the INA-12063 RFIC Amplifier for 2.4 GHz Applications

Application Note 1147

Introduction

The versatile INA-12063 RFIC amplifier provides an effective solution for many buffer, pre-driver, and multi-purpose gain stage requirements for applications in the 2.4 GHz frequency band. The INA-12063 is especially easy to use at this frequency, as illustrated in the RF schematic in Figure 1. This amplifier solution will be particularly useful for wireless data, RFID, WLAN, and HomeRF products.

One of the unique features of the INA-12063 is the user's ability to set the device current by means of an external resistor. For applications requiring minimal current drain, the INA-12063 operates satisfactorily with currents as low as 1 to 2 mA. For buffer and pre-driver stages, the device current can be increased to 8 mA to provide a 1 dB compressed output power of approximately +6 dBm. Although the nominal supply voltage for the INA-12063 is +3 volts, the device can operate over a voltage range of 1.5 to 5 volts.

Setting the Bias Current

The patented,[1] active bias regulation circuit is a 10:1 current mirror that forces the current in the RF section of the INA-12063 to be approximately 10 times the current supplied to the I_{bias} pin. Pin connections for the INA-12063 are shown in Figure 3. In normal use, a voltage between +1.5 and +5 volts is applied to both the V_d and V_c terminals of the INA-12063. The device current is then set by injecting a small control current into the I_{bias} pin that is approximately 1/10 of the desired device current. The simplest means of supplying the I_{bias} control current is to merely place a resistor, shown as R_{bias} in Figure 4, between the V_d and I_{bias} terminals. R_{bias} is sufficiently high that it simulates a current source. The value for R_{bias} is calculated as follows:

$$R_{bias} = 10 \left(\frac{V_d - 0.8}{I_c} \right) \quad (1)$$

where V_d is the device voltage (volts), I_c is the desired device current (amps), and R_{bias} is the value of the bias-determining resistor (ohms).

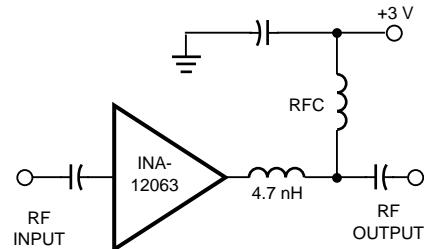


Figure 1. RF Schematic of 2.4 GHz Amplifier

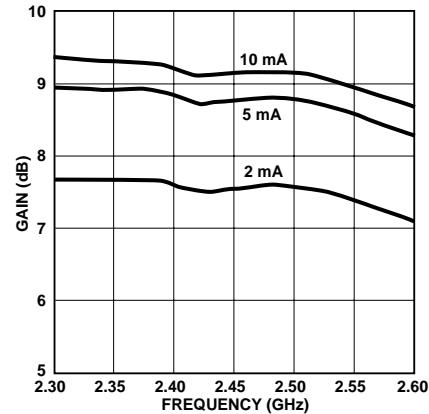


Figure 2. Gain of 2.4 GHz Circuit Using INA-12063

[1] U.S. Patent Number 5436595

2.4 GHz Design Example

An example circuit was designed to demonstrate the use of the INA-12063 for 2.4 GHz applications. The example amplifier was designed to operate from a power supply of +3 volts with a nominal device current of 5 mA.

The integrated series feedback in the INA-12063 provides a very good input match over the entire 2 to 3 GHz frequency range. The input match is typically under a VSWR of 2:1, improving to 1.3:1 at higher device currents. Therefore, the input to the INA-12063 may be used as is without the need for any impedance-matching circuitry.

The real part of the output impedance of the INA-12063 lies near 50 ohms at 2.4 GHz. The addition of a simple series inductor is all that is needed to achieve a very reasonable output match to 50 ohms. A CAD simulation using Hewlett-Packard's *Touchstone* program predicted the output of the INA-12063 could be matched by using a 4.5 nH series inductor. A 4.7 nH chip inductor was chosen as the nearest standard value to 4.5 nH.

The only other components required to complete the circuit are: DC blocking and bypass capacitors, a RF choke, and the current setting resistor, R_{bias} . The value for R_{bias} was calculated from Equation 1 above to be 4.4 k Ω for 3 volts and 5 mA. The nearest standard value of 4.7 k Ω will be used for this design. A value of 33 nH is used for the RFC and all capacitors are 56 pF. A schematic diagram of the complete circuit is shown in Figure 4.

A demonstration circuit for the INA-12063 was assembled on an "IAM-91-A" evaluation PCB. The IMA-91-A circuit board, originally designed for use with the IAM-91563 RFIC mixer, is readily adapted to accommodate the INA-12063. The unused circuit traces are cut away and an external wire is added to connect the supply voltage to the V_d terminal at Pin 4. The completed amplifier is shown in Figure 5.

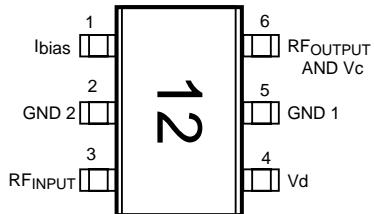


Figure 3. INA-12063 Pin Connections

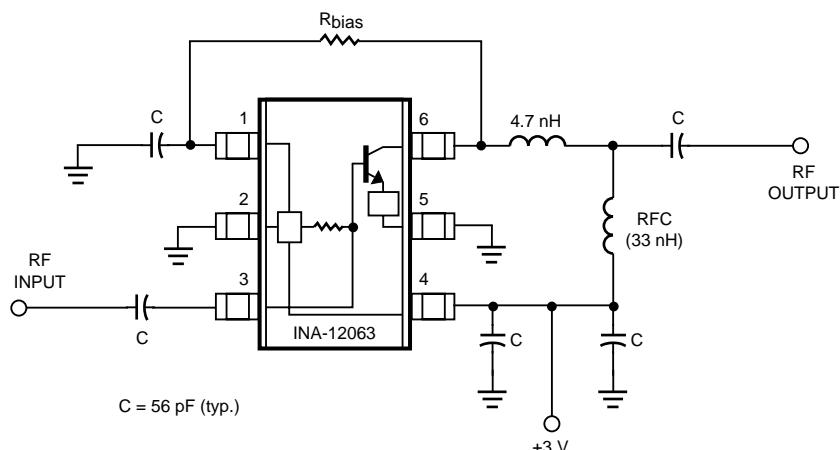


Figure 4. Complete Schematic of 2.4 GHz Amplifier

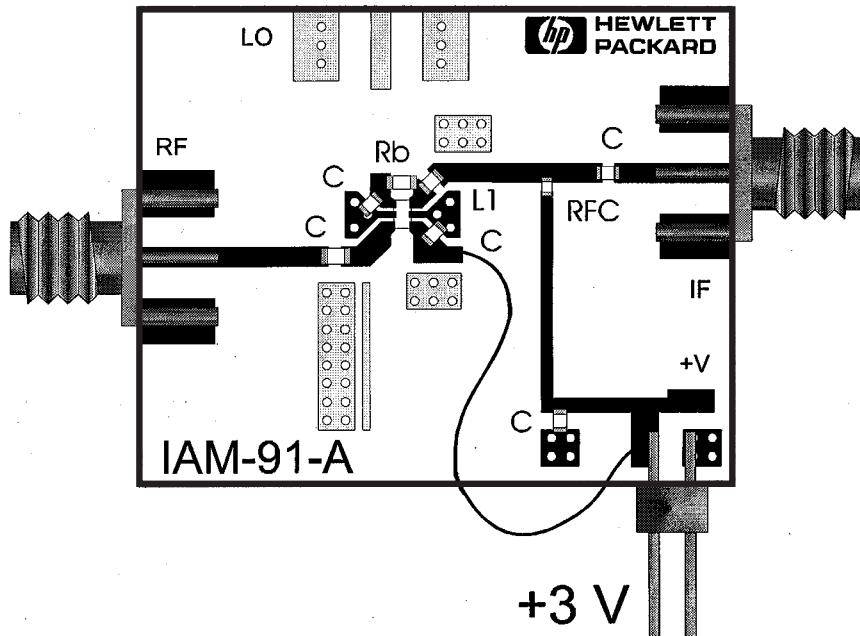


Figure 5. Example 2.4 GHz Circuit Using the HP INA-12063 RFIC Amplifier

Test Results

Actual measured gain of the completed amplifier from 2.3 to 2.6 GHz is shown in Figure 2 for three different device currents. The value of R_{bias} was changed to adjust the device current to 2, 5, and 10 mA.

Return loss for the RF input and output is plotted in Figure 6 from 2.0 to 3.0 GHz. These data are for a device current of 5 mA. The input and output VSWRs are both less than 1.6:1 over a 100 MHz bandwidth centered near 2.3 GHz. This result suggests the output match is tuned slightly low compared to the 2.4 GHz target frequency and is likely due to rounding up of the output matching inductor to a standard value.

Output power at 1 dB of gain compression was measured over a 1 to 10 mA decade of current and is plotted in Figure 7. The output power data was taken with fixed tuning, i.e., no re-tuning was done for different currents. The output power results show a point of diminishing return beyond a current of 8 mA where a maximum P_{1dB} of +6.5 dBm is obtained.

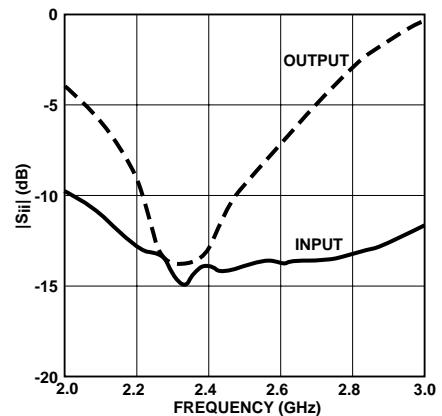


Figure 6. Input and Output Return Loss

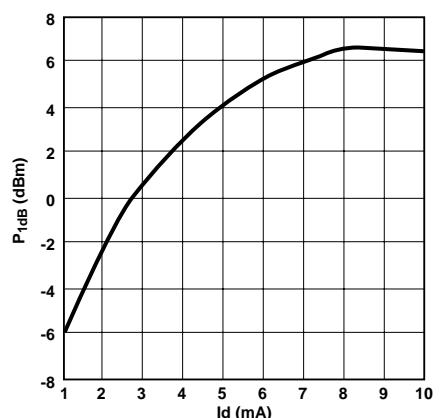


Figure 7. Output Power (P_{1dB}) vs. Device Current

The isolation (reverse gain) of the amplifier is shown in Figure 8 for a current of 5 mA. The isolation is fairly insensitive to current and varies only 1 dB over a 2 to 10 mA current range.

Noise figure for the example amplifier was measured as 3.4 dB at 2 mA, increasing to 3.8 dB at 10 mA of device current.

A measured plot of device current vs. R_{bias} is shown in Figure 9 for reference.

Refer to the Data Sheet for the INA-12063 RFIC for additional information.

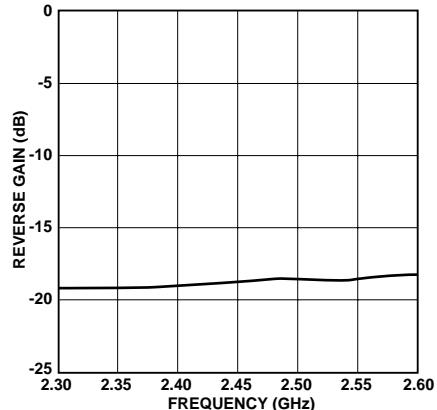


Figure 8. Amplifier Isolation vs. Frequency

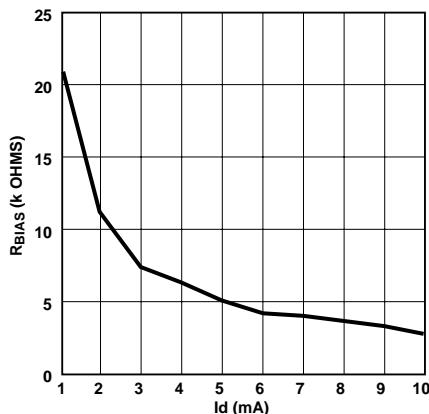


Figure 9. R_{bias} vs. I_d

www.hp.com/go/rf

For technical assistance or the location of your nearest Hewlett-Packard sales office, distributor or representative call:

Americas/Canada: 1-800-235-0312 or (408) 654-8675

Far East/Australasia: Call your local HP sales office.

Japan: (81 3) 3335-8152

Europe: Call your local HP sales office.

Data Subject to Change

Copyright © 1998 Hewlett-Packard Co.

Printed in U.S.A. 5968-0409E (7/98)

SUNSTAR 商斯达实业集团是集研发、生产、工程、销售、代理经销、技术咨询、信息服务等为一体的高科技企业，是专业高科技电子产品生产厂家，是具有 10 多年历史的专业电子元器件供应商，是中国最早和最大的仓储式连锁规模经营大型综合电子零部件代理分销商之一，是一家专业代理和分销世界各大品牌 IC 芯片和电子元器件的连锁经营综合性国际公司，专业经营进口、国产名厂名牌电子元件，型号、种类齐全。在香港、北京、深圳、上海、西安、成都等全国主要电子市场设有直属分公司和产品展示展销窗口门市部专卖店及代理分销商，已在全国范围内建成强大统一的供货和代理分销网络。我们专业代理经销、开发生产电子元器件、集成电路、传感器、微波光电元器件、工控机/DOC/DOM 电子盘、专用电路、单片机开发、MCU/DSP/ARM/FPGA 软件硬件、二极管、三极管、模块等，是您可靠的一站式现货配套供应商、方案提供商、部件功能模块开发配套商。商斯达实业公司拥有庞大的资料库，有数位毕业于著名高校——有中国电子工业摇篮之称的西安电子科技大学（西军电）并长期从事国防尖端科技研究的高级工程师为您精挑细选、量身订做各种高科技电子元器件，并解决各种技术问题。

微波光电部专业代理经销高频、微波、光纤、光电元器件、组件、部件、模块、整机；电磁兼容元器件、材料、设备；微波 CAD、EDA 软件、开发测试仿真工具；微波、光纤仪器仪表。欢迎国外高科技微波、光纤厂商将优秀产品介绍到中国、共同开拓市场。长期大量现货专业批发高频、微波、卫星、光纤、电视、CATV 器件：晶振、VCO、连接器、PIN 开关、变容二极管、开关二极管、低噪晶体管、功率电阻及电容、放大器、功率管、MMIC、混频器、耦合器、功分器、振荡器、合成器、衰减器、滤波器、隔离器、环行器、移相器、调制解调器；光电子元器件和组件：红外发射管、红外接收管、光电开关、光敏管、发光二极管和发光二极管组件、半导体激光二极管和激光器组件、光电探测器和光接收组件、光发射接收模块、光纤激光器和光放大器、光调制器、光开关、DWDM 用光发射和接收器件、用户接入系统光光收发器件与模块、光纤连接器、光纤跳线/尾纤、光衰减器、光纤适配器、光隔离器、光耦合器、光环行器、光复用器/转换器；无线收发芯片和模组、蓝牙芯片和模组。

更多产品请看本公司产品专用销售网站：

商斯达中国传感器科技信息网：<http://www.sensor-ic.com/>

商斯达工控安防网：<http://www.pc-ps.net/>

商斯达电子元器件网：<http://www.sunstare.com/>

商斯达微波光电产品网：<HTTP://www.rfoe.net/>

商斯达消费电子产品网：<http://www.icasic.com/>

商斯达实业科技产品网：<http://www.sunstars.cn/> 微波元器件销售热线：

地址：深圳市福田区福华路福庆街鸿图大厦 1602 室

电话：0755-82884100 83397033 83396822 83398585

传真：0755-83376182 (0) 13823648918 MSN：SUNS8888@hotmail.com

邮编：518033 E-mail：szss20@163.com QQ：195847376

深圳赛格展销部：深圳华强北路赛格电子市场 2583 号 电话：0755-83665529 25059422

技术支持：0755-83394033 13501568376

欢迎索取免费详细资料、设计指南和光盘；产品凡多，未能尽录，欢迎来电查询。

北京分公司：北京海淀区知春路 132 号中发电子大厦 3097 号

TEL：010-81159046 82615020 13501189838 FAX：010-62543996

上海分公司：上海市北京东路 668 号上海赛格电子市场 D125 号

TEL：021-28311762 56703037 13701955389 FAX：021-56703037

西安分公司：西安高新区 20 所(中国电子科技集团导航技术研究所)

西安劳动南路 88 号电子商城二楼 D23 号

TEL：029-81022619 13072977981 FAX:029-88789382