



HEWLETT  
PACKARD

## APPLICATION NOTE 970

# A 6 GHz Amplifier Using the HFET-1101 GaAs FET

### INTRODUCTION

The GaAs field effect transistor is establishing its performance superiority in most microwave low noise receiver designs. Even at frequencies as low as 1GHz the GaAs FET can be used with non-conventional stabilization circuitry<sup>1</sup>. The GaAs FET is a unique device with numerous applications, for example: amplifiers, oscillators; mixers; modulators; parametric-amplifier replacements; and RF switches.

The Hewlett-Packard HFET-1101 is a device designed for good noise, gain and power output characteristics when used as an amplifier. The purpose of this application note is to highlight some of the design tradeoffs when using a GaAs FET. The example is an amplifier for use in the 5.9 to 6.4 GHz telecommunications band. The amplifier's performance over this band is excellent, with a maximum noise figure of 3.3 dB, a minimum associated gain of 10.9 dB, a flatness of  $\pm 0.4$  dB and a 9.5 dBm minimum power output at 1dB gain compression. The maximum input and output SWR are 2.67:1 and 1.90:1 respectively.

### DESIGN TRADE-OFFS

The first choice facing a designer is biasing. In comparison to silicon bipolars, GaAs FETs require more current at a lower voltage, with the net result being about the same power dissipation. Power supply requirements should reflect this characteristic.

With any single stage amplifier design, there are three performance parameters that require different optimum bias settings.

They are:

1. Minimum noise figure  
 $V_{DS} = 3.5$  Volts,  $I_{DS} = 15\%$  loss
2. Linear power output  
 $V_{DS} = 4.0$  Volts,  $I_{DS} = 50\%$  loss
3. Maximum Gain  
 $V_{DS} = 4.0$  Volts,  $I_{DS} = 100\%$  loss

For the three critical bias settings above, the input and output matching data are available from the scattering<sup>(2)</sup>, noise<sup>(3)</sup>, power<sup>(3)</sup> and gain<sup>(4)</sup> parameters. The linear power bias point of  $V_{DS} = 4.0$  Volts and  $I_{DS} = 50\%$  loss provides a good compromise between minimum noise figure and maximum gain. At this bias point the scattering, noise,<sup>(2)</sup>

power and gain parameters can be measured by various known techniques<sup>(5)</sup>. Typical parameters at 6 GHz for the HFET-1101 are:

Scattering Parameters	Gain Parameters
$S_{11} = 0.641/-171.3^\circ$	$K = 1.504$
$S_{12} = 0.057/16.3^\circ$	$G_a (\max.) = 11.38$ dB
$S_{21} = 2.058/28.5^\circ$	$\Gamma_{MS} = 0.762/177.3^\circ$
$S_{22} = 0.572/-95.7^\circ$	$\Gamma_{ML} = 0.718/103.9^\circ$

Noise Parameters	Power Parameters @ $P_{TUNE} = 5$ dBm
$F_{MIN} = 2.9$ dB	$P_{1dB} = 15.5$ dBm
$R_n = 9.42$ ohms	$G_p = 8.2$ dB
$\Gamma_O = 0.542/141^\circ$	$\Gamma_{PS} = 0.729/166^\circ$
$\Gamma_L = 0.575/104.5^\circ$	$\Gamma_{PL} = 0.489/101^\circ$

Even at this compromise bias point, the input matching network has four performance trade-offs that can be juggled. They are: noise figure; available power gain; power output; and input SWR. Table I gives the conditions when the input impedance is chosen for, respectively: lowest noise figure; highest available power gain; and greatest linear power output.

TABLE I

Noise Figure	Gain	Power Output
$\Gamma_O = 0.542/141^\circ$	$\Gamma_{MS} = 0.762/177.3^\circ$	$\Gamma_{PS} = 0.729/166^\circ$
$\Gamma_L = 0.575/104.5^\circ$	$\Gamma_{ML} = 0.718/103.9^\circ$	$\Gamma_{PL} = 0.489/101^\circ$
$F_{MIN} = 2.90$ dB	$F = 4.44$ dB	$F = 3.69$ dB
$G_a = 9.33$ dB	$G_a (\max.) = 11.38$ dB	$G_p = 8.2$ dB
$P_{1dB} = 9.3$ dBm	$P_{1dB} = 13.4$ dBm	$P_{1dB} = 15.5$ dBm

When the input impedance is chosen for either lowest noise or maximum gain, the output is assumed to be conjugately matched. The noise figure and gain at the three conditions shown above are calculated from the parameters given, while the power output ( $P_{1dB}$ ) performance is experimentally measured.<sup>(3)(4)</sup>

The data for the power output was taken at an input drive level of 8.3 dBm. As we approach large signal conditions, i.e. 5 dBm or greater, it becomes difficult to predict compromises between noise, gain and input SWR. Since

noise and gain are small signal parameters and are not functions of input drive level it is possible to predict input SWR trends over a wide dynamic range.

Since most low noise receivers work in a small signal environment, the design engineer is typically concerned with compromising gain and input SWR for noise figure. To demonstrate this,  $\Gamma_0$  and  $\Gamma_{MS}$ , the source reflection coefficients for lowest noise figure and highest available gain are plotted on a Smith Chart in Figure 1.

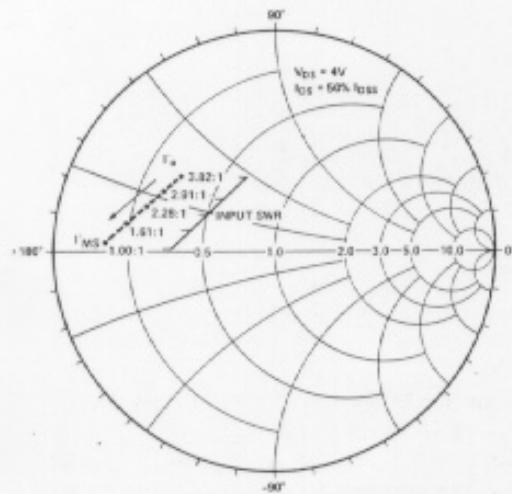


Figure 1. Source Reflection Coefficient Vs. Noise Figure.

Moving from  $\Gamma_0$  toward  $\Gamma_{MS}$  along a straight line, input SWR improves to 1.0:1 at  $\Gamma_{MS}$ , assuming the output to be conjugately matched. At the same time, noise figure and available gain are increasing. Table II shows corresponding values for noise, gain and input SWR.

TABLE II

$\Gamma_S$ Mag/Ang	$\Gamma_L$ Mag/Ang	N.F. [dB]	Ga [dB]	Input SWR	Output SWR
$\Gamma_0 = 0.542/141^\circ$	$0.575/104^\circ$	2.90	9.33	3.82:1	1.00:1
$0.572/152^\circ$	$0.601/105^\circ$	2.97	10.04	2.91:1	1.00:1
$0.614/160^\circ$	$0.627/106^\circ$	3.14	10.56	2.28:1	1.00:1
$0.678/169^\circ$	$0.667/105^\circ$	3.57	11.10	1.61:1	1.00:1
$\Gamma_{MS} = 0.762/177^\circ$	$0.718/104^\circ$	4.44	11.38	1.00:1	1.00:1

From Table II, a very good compromise input match condition is  $\Gamma_S = 0.614/160^\circ$  and the corresponding output conjugate match condition is  $\Gamma_L = 0.627/106^\circ$ . In comparison to the minimum noise match conditions the noise figure is increased by 0.24 dB but the associated gain is increased by 1.22 dB and the input, SWR is improved by 40% to 2.28:1. Of course, other compromises can also be chosen. For example, the optimum bias for noise figure may be chosen and the source impedance compromised between minimum noise figure and maximum gain at that bias. Values of noise figure and gain may be calculated and compared for each of these compromises.

With the choice of  $\Gamma_S$  and  $\Gamma_L$  discussed above, it is now possible to synthesize the input and output matching networks.

## INPUT MATCHING NETWORK

1. The impedance  $Z_S$ , corresponding to  $\Gamma_S = 0.614/160^\circ$  is:

$$Z_S = \frac{(1 - |\Gamma_S|^2) 50}{1 + |\Gamma_S|^2 - 2 |\Gamma_S| \cos \angle \Gamma_S} + j \frac{100 |\Gamma_S| \sin \angle \Gamma_S}{1 + |\Gamma_S|^2 - 2 |\Gamma_S| \cos \angle \Gamma_S}$$

$$Z_S = 12.31 + j8.30$$

$$2. Y_S = \frac{1}{Z_S} = 0.056 - j0.038$$


3. An open circuited stub looks like a shunt admittance  $Y = jY_0 \tan \beta l$ . Therefore, an open circuited stub that is three-eights wavelength long looks like a shunt inductor of admittance  $-jY_0$ . Hence:

$$Z_0 = \frac{1}{Y_0} = \frac{1}{I_m [Y_S]} = 26.55 \Omega$$

4. Since the driving source impedance is  $50\Omega$ , a quarter-wave transformer of characteristic impedance

$$Z'_0 = \sqrt{50 \left[ \frac{1}{R_e [Y_S]} \right]} = 29.92 \Omega$$

completes the input matching network.

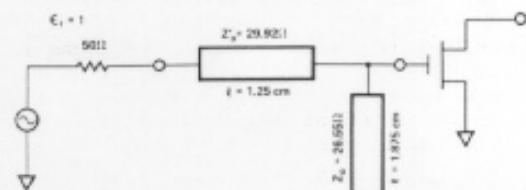

## OUTPUT MATCHING NETWORK

1. The impedance  $Z_L$ , corresponding to  $\Gamma_L = 0.627/106^\circ$  is:

$$Z_L = \frac{(1 - |\Gamma_L|^2) 50}{1 + |\Gamma_L|^2 - 2 |\Gamma_L| \cos \angle \Gamma_L} + j \frac{100 |\Gamma_L| \sin \angle \Gamma_L}{1 + |\Gamma_L|^2 - 2 |\Gamma_L| \cos \angle \Gamma_L}$$

$$Z_L = 17.45 + j34.66$$

$$2. Y_L = \frac{1}{Z_L} = 0.012 - j0.023$$


3. The output matching network is similar to the input matching network. An open circuited stub that is three-eights wavelength long looks like a shunt inductor of admittance  $-jY_0$ . Hence:

$$Z_0 = \frac{1}{Y_0} = \frac{1}{I_m [Y_L]} = 43.45 \Omega$$

4. Since the load impedance is  $50\Omega$ , a quarter-wave transformer of characteristic impedance:

$$Z'_0 = \sqrt{50 \left[ \frac{1}{R_e Y_L} \right]} = 65.69 \Omega$$

completes the output matching network.

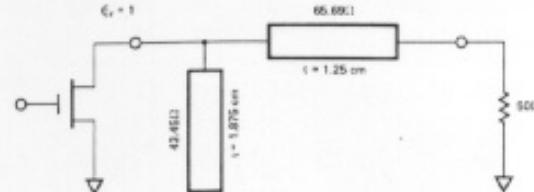

## PERFORMANCE

An amplifier was constructed using the design derived above. A comparison of the computer simulation with measured amplifier performance at 6 GHz is shown below.

Parameter	Measured Performance	Computer Simulation
Gain	11.50 dB	10.55 dB
Input SWR	2.67:1	2.28:1
Output SWR	1.90:1	1.00:1
Isolation	-23 dB	-20.60 dB
Noise Figure	3.27 dB	3.14 dB

The performance of the amplifier was measured over the 5.9 to 6.4 GHz band. Figures 2, 3, 4, 5, and 6 show the room temperature performance.

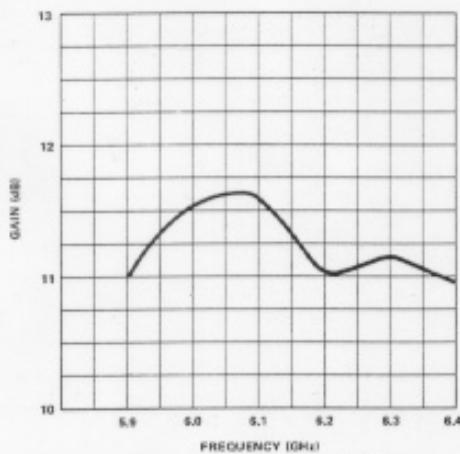


Figure 2. Gain Performance.

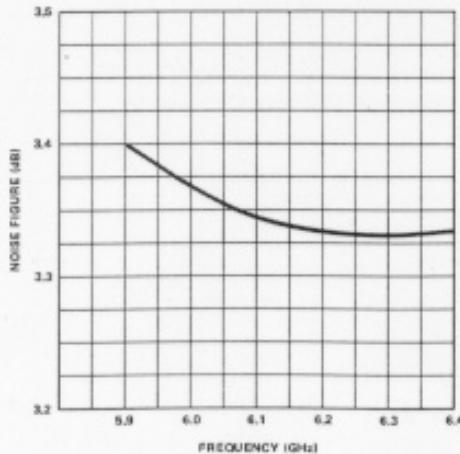


Figure 3. Noise Performance.

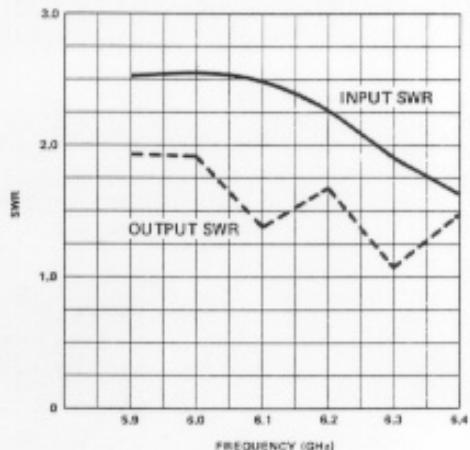


Figure 4. Input-Output SWR Performance.

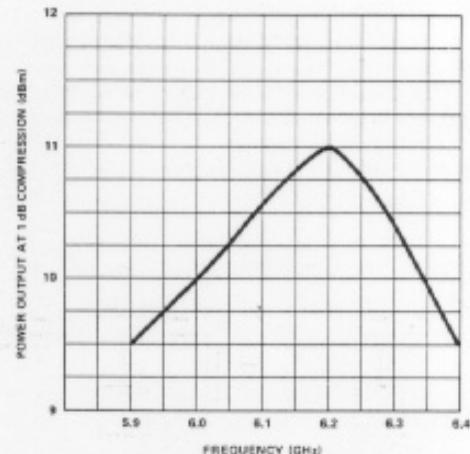


Figure 5. Power Output Performance.

**Isolation** — Isolation is better than -23 dB over the entire 5.9 to 6.4 GHz band.

**Phase Linearity** — Phase linearity is  $\pm 6^\circ$  over the entire 500 MHz bandwidth.

**AM to PM Conversion** — With an output power level of -13 dBm, the input power level is referenced. At this input reference level, the input power is varied  $\pm 10$  dB. Over the 5.9 to 6.4 GHz band, the average AM to PM conversion is  $0.055^\circ/\text{dB}$ .

**Third Order Intercepts** — With two fundamental signals injected into the input at 5.95 and 6.05 GHz, the output power level for each fundamental signal is set for 0 dBm. The third order intermodulation products are both 44 dB below the two fundamentals at the output. Therefore, the third order intercept point is +22 dBm.

The wideband gain performance is plotted on the following page.


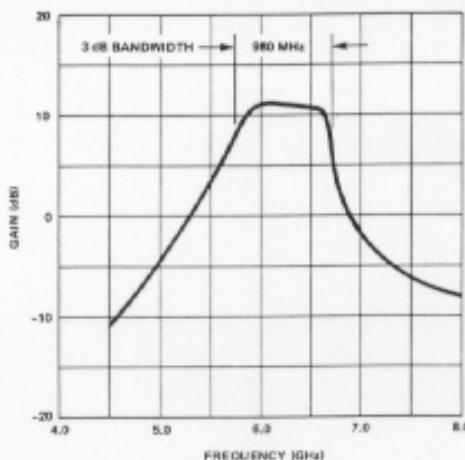


Figure 6. Wideband Gain Performance.
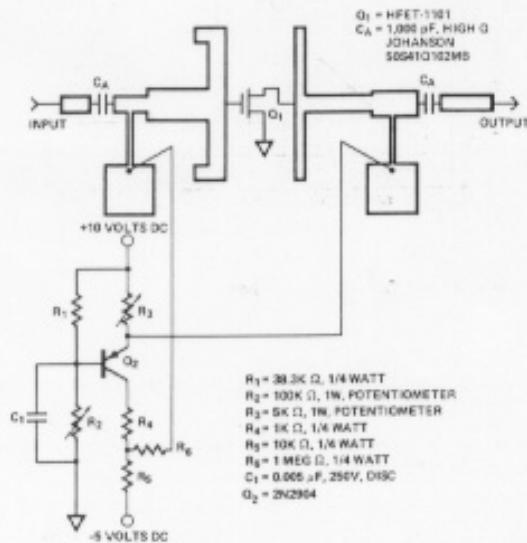
## CONSTRUCTION

The board material is 0.031" RT/Duroid 120-061 (D5880) (Manufactured by Roger Corp. in Chandler, AZ), with 1oz. copper clad on two sides. The relative dielectric constant ( $\epsilon_r$ ) is 2.23. Duroid was chosen because of its low loss tangent. The thickness of 0.031" was chosen so the source top cap could be soldered to the RF ground, thereby taking advantage of the low source inductance.




The quiescent point is controlled by  $R_2$  and  $R_3$ .  $R_2$  is adjusted to provide the proper  $V_{DS}$  and  $R_3$  is adjusted to supply the correct drain current ( $I_{DS}$ ).

## Schematic I Complete Amplifier

To minimize transition interactions the shunt stubs were balanced along the series transmission lines. The bias network is fed at the quarter-wavelength point of a half-wavelength open circuited stub.

Two different types of biasing networks were used with the same result. A schematic of the complete amplifier and biasing circuit can be seen in the diagram that follows. The differences between the biasing networks are:

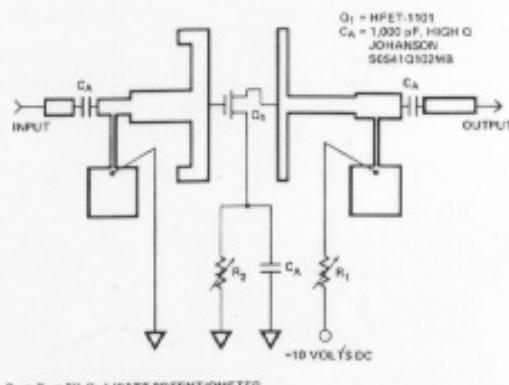1. Schematic I is an active network which requires a dual polarity supply with an active pulse recovery loop.
2. Schematic II is a self-biasing network which requires a very good source bypassing capacitor. It has a lower component count with a single supply requirement. It is, however, more subject to oscillations.



The quiescent point is controlled by  $R_1$  and  $R_2$ .  $R_1$  is adjusted to provide the proper  $V_{DS}$  and  $R_2$  is adjusted to supply the correct drain current ( $I_{DS}$ ).

## Schematic II Complete Amplifier

## REFERENCES

1. Hewlett-Packard E.M.A.C.C. '77 Technical Session Paper, "Low Noise Amplifier Design Techniques at 1.5 GHz" by Arthur Woo, Ottawa, May 3, 1977.
2. HFET-1101, Microwave GaAs FET, data sheet.
3. Hewlett-Packard Application Bulletin 19, "Noise and Power Parameters for the HFET-1101".
4. Hewlett-Packard Application Note 95-1, "S-Parameter Techniques for Faster, More Accurate Network Design", September 1968.
5. Hewlett-Packard Application Bulletin 10, "Transistor Noise Figure Measurements".

SUNSTAR 商斯达实业集团是集研发、生产、工程、销售、代理经销、技术咨询、信息服务等为一体的高科技企业，是专业高科技电子产品生产厂家，是具有 10 多年历史的专业电子元器件供应商，是中国最早和最大的仓储式连锁规模经营大型综合电子零部件代理分销商之一，是一家专业代理和分销世界各大品牌 IC 芯片和电子元器件的连锁经营综合性国际公司，专业经营进口、国产名厂名牌电子元件，型号、种类齐全。在香港、北京、深圳、上海、西安、成都等全国主要电子市场设有直属分公司和产品展示展销窗口门市部专卖店及代理分销商，已在全国范围内建成强大统一的供货和代理分销网络。我们专业代理经销、开发生产电子元器件、集成电路、传感器、微波光电元器件、工控机/DOC/DOM 电子盘、专用电路、单片机开发、MCU/DSP/ARM/FPGA 软件硬件、二极管、三极管、模块等，是您可靠的一站式现货配套供应商、方案提供商、部件功能模块开发配套商。商斯达实业公司拥有庞大的资料库，有数位毕业于著名高校——有中国电子工业摇篮之称的西安电子科技大学（西军电）并长期从事国防尖端科技研究的高级工程师为您精挑细选、量身订做各种高科技电子元器件，并解决各种技术问题。

微波光电部专业代理经销高频、微波、光纤、光电元器件、组件、部件、模块、整机；电磁兼容元器件、材料、设备；微波 CAD、EDA 软件、开发测试仿真工具；微波、光纤仪器仪表。欢迎国外高科技微波、光纤厂商将优秀产品介绍到中国、共同开拓市场。长期大量现货专业批发高频、微波、卫星、光纤、电视、CATV 器件：晶振、VCO、连接器、PIN 开关、变容二极管、开关二极管、低噪晶体管、功率电阻及电容、放大器、功率管、MMIC、混频器、耦合器、功分器、振荡器、合成器、衰减器、滤波器、隔离器、环行器、移相器、调制解调器；光电子元器件和组件：红外发射管、红外接收管、光电开关、光敏管、发光二极管和发光二极管组件、半导体激光二极管和激光器组件、光电探测器和光接收组件、光发射接收模块、光纤激光器和光放大器、光调制器、光开关、DWDM 用光发射和接收器件、用户接入系统光光收发器件与模块、光纤连接器、光纤跳线/尾纤、光衰减器、光纤适配器、光隔离器、光耦合器、光环行器、光复用器/转换器；无线收发芯片和模组、蓝牙芯片和模组。

更多产品请看本公司产品专用销售网站：

商斯达中国传感器科技信息网：<http://www.sensor-ic.com>

商斯达工控安防网：<http://www.pc-ps.net>

商斯达电子元器件网：<http://www.sunstare.com>

商斯达微波光电产品网：<HTTP://www.rfoe.net>

商斯达消费电子产品网：<http://www.icasic.com>

商斯达实业科技产品网：<http://www.sunstars.cn> 微波元器件销售热线：

地址：深圳市福田区福华路福庆街鸿图大厦 1602 室

电话：0755-82884100 83397033 83396822 83398585

传真：0755-83376182 (0) 13823648918 MSN：[SUNS8888@hotmail.com](mailto:SUNS8888@hotmail.com)

邮编：518033 E-mail：[szss20@163.com](mailto:szss20@163.com) QQ：195847376

深圳赛格展销部：深圳华强北路赛格电子市场 2583 号 电话：0755-83665529 25059422

技术支持：0755-83394033 13501568376

欢迎索取免费详细资料、设计指南和光盘；产品凡多，未能尽录，欢迎来电查询。

北京分公司：北京海淀区知春路 132 号中发电子大厦 3097 号

TEL：010-81159046 82615020 13501189838 FAX：010-62543996

上海分公司：上海市北京东路 668 号上海赛格电子市场 D125 号

TEL：021-28311762 56703037 13701955389 FAX：021-56703037

西安分公司：西安高新区 20 所(中国电子科技集团导航技术研究所)

西安劳动南路 88 号电子商城二楼 D23 号

TEL：029-81022619 13072977981 FAX:029-88789382