



# Ring Detection with the HCPL-3700 Optocoupler

## Application Note 1024

### Introduction

The field of telecommunications has reached the point where the efficient control of voice channels is essential. People in business are communicating to a larger extent over telephone, and they are requiring lower cost, easy, and quick access to phone lines. These requirements, coupled with the evolution of the modem, automatic phone answering equipment, and communication between computers over public lines, have resulted in the introduction of electronic control and private automatic branch ex-

change (PABX) systems. There must, however, be isolation between the sensitive, micro-processor-based, control circuitry and the higher voltage, transient-prone transmission line. Optocouplers, or optical isolators, are effective, reliable, and inexpensive devices for achieving this protection and isolation. An area where optocouplers can be used to great advantage is in the ring detection portion of the control circuitry, and that will be the emphasis of this report.

### The Nature of the Ring Signal

Ring detection is the first operation necessary in completing the connection between the central office and the individual telephone. Figure 1 illustrates a simplified version of this connection.

When a request to connect a particular line comes to the central office, the ring signal is transmitted on the tip and ring of the requested line until an off-hook condition is detected through the presence of a dc loop current. The

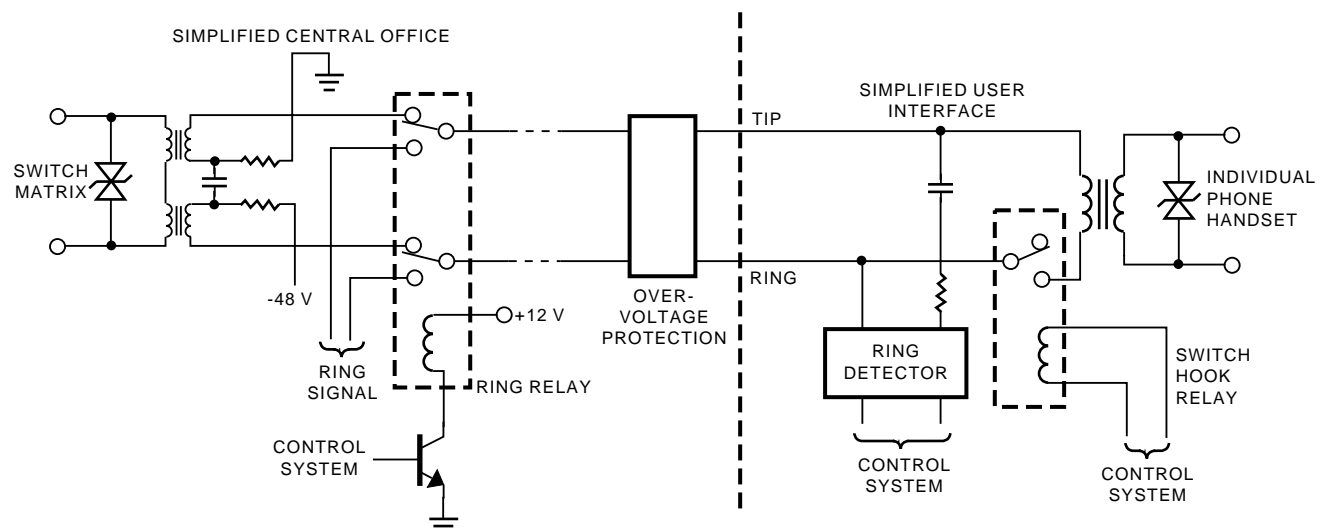


Figure 1. Simplified Central Office-to-User Interface

nature of this ring signal is addressed in the Federal Communications Commission's Part 68, in section 312 (On-hook Impedance Limitations). Essentially, the ringing signal is a sinusoidal wave of frequency ranging from 15.3 to 68.0 Hz. The amplitude of the ring signal, which is superimposed upon a dc voltage between tip and ring of -48 V, can vary from 40 to 150 VRMS. The ac impedance must be greater than 1600 Ω. Due to the fact that the central exchange detects an off-hook condition by the presence of a dc current, the dc impedance presented by the ring detection circuitry must be very high. Part 68 states that "the dc resistance between tip and ring conductors, and between each of the tip and ring conductors and earth ground shall be greater than 10 MΩ for dc voltages up to and including 100 V."

Regulations are slightly different in Europe, with voltage amplitudes varying from 30 VRMS to 100 VRMS at a nominal frequency of 25 Hz.

Therefore, the ring signal is obviously not logic compatible and cannot be interfaced directly to electronic circuitry. Furthermore, lightning-induced transients, in the form of a very high voltage, underdamped sinusoid, as well as other environmentally induced transients such as dial pulses from other extensions on the same line, must also be protected against. The ring detector must output a logic compatible signal in the presence of ring signal with amplitude anywhere within the U.S. or European regulations, and also discriminate between this signal and any transient that might be present on the transmission line.

### The HCPL-3700: Easy Threshold Detection and Filtering

The HCPL-3700 offers a complete, optimal solution to the ring detect problem with a minimal amount of external components needed. This optocoupler features a Zener diode full-wave bridge rectifier at the input, followed by a hysteresis buffer and constant current source to drive the LED. The LED is turned on or off at prescribed voltage and current thresholds. These thresholds can be adjusted by the insertion of a series impedance. The output stage of the optocoupler is a photodetector and a split-Darlington amplifier circuit. A schematic diagram of the HCPL-3700 is shown in Figure 2.

To turn the LED on, which results in an output low state, the positive threshold must be exceeded. The correct external impedance must be used to ensure that this switching occurs at the desired point, according to the following equation:

$$Z_{Ext} = \frac{V_{+(Min)} - V_{TH(Max)+}}{I_{TH(Max)+}} \quad (1)$$

where  $V_{TH(MAX)+}$  and  $I_{TH(MAX)+}$  are given in the data sheet and  $V_{+(MIN)}$  is the desired switching

point. (If detection of a ring signal of 40 VRMS minimum is desired, this value would be  $40 \times \sqrt{2} = 56.6$  V.)

To meet the requirement of presenting a very high dc impedance to the central office, it is advantageous to ac couple the ring signal. This is accomplished by using a series capacitor. This capacitor, in conjunction with series resistance, creates the impedance required to set the threshold of the HCPL-3700 and to meet the ac impedance requirement. The impedance is then approximated as shown in Equation (2).

$$Z_{Ext} \cong \left( R_{Ext}^2 + \left[ \frac{1}{2 \pi f_{Ring} C} \right]^2 \right)^{0.5} \quad (2)$$

If we choose a capacitor of 2.2 μF, and assume a minimum ringing frequency of 15 Hz and a minimum amplitude of 40 VRMS, then we can calculate a value for the external resistance using equations (1) and (2).

$$R_{Ext} = \left( \left[ \frac{V_{+(Min)} - V_{TH(Max)+}}{I_{TH(Max)+}} \right]^2 - \left( \frac{1}{2 \pi f_{Ring} C} \right)^2 \right)^{0.5}$$

$$R_{Ext} = 15700 \Omega \quad (3)$$

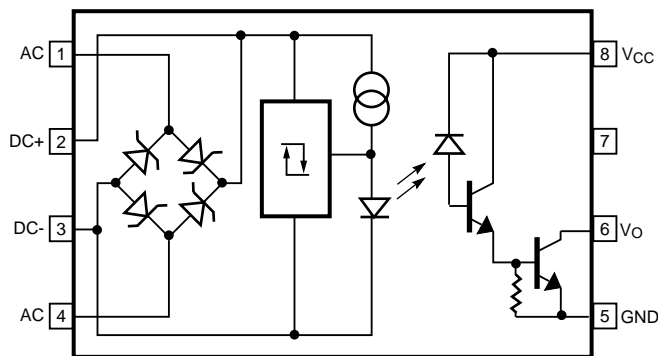


Figure 2. Schematic Diagram of HCPL-3700

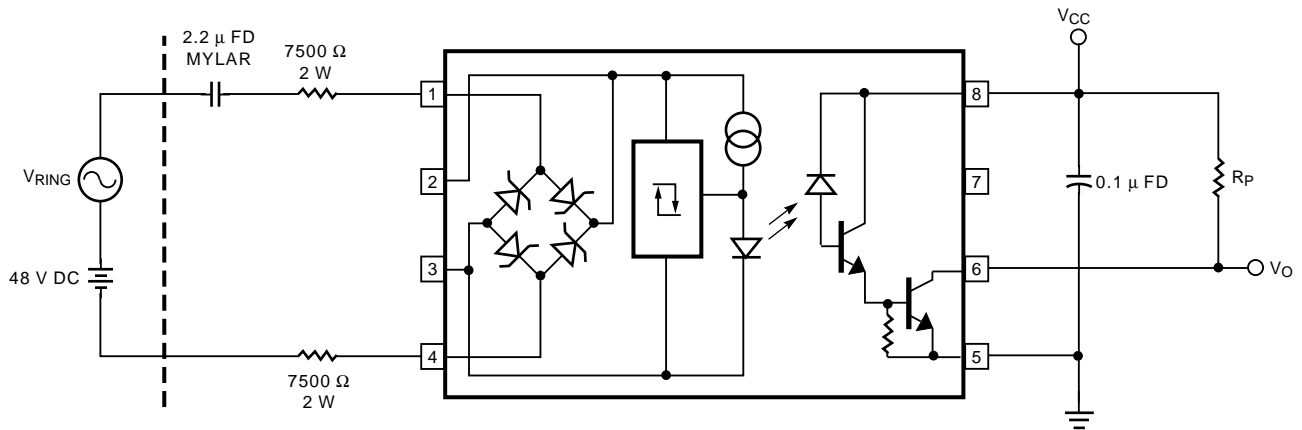


Figure 3. Equivalent Circuit for Detection of 40 VRMS Signal

The external resistance is then split up equally between the tip and the ring lines in order to provide a balanced line termination and transient suppression on both lines. Figure 3 shows the equivalent circuit using the results from equation (3).

The power dissipation required of the resistors must also be taken into account. The Zener diode bridge at the input of the HCPL-3700 clamps the voltage across the ac inputs at approximately 7 V. The amount of power that then must be dissipated by each of the two external resistors is shown in Equation (4):

$$P = [(V_{Ring(Max)} - 7) / 2]^2 / R \quad (4)$$

where R is  $R_{EXT}/2$ . If the peak amplitude of the ring signal is 150 VRMS, then each resistor must dissipate 1.4 watts. A 2-watt resistor will provide extra protection. At the level of current present in the circuit, there is no danger of exceeding the maximum current rating of the optocoupler.

The output signal is essentially a square wave of frequency twice that of the input signal. To obtain a signal that is at logic low throughout the duration of the ring signal some type of filtering is

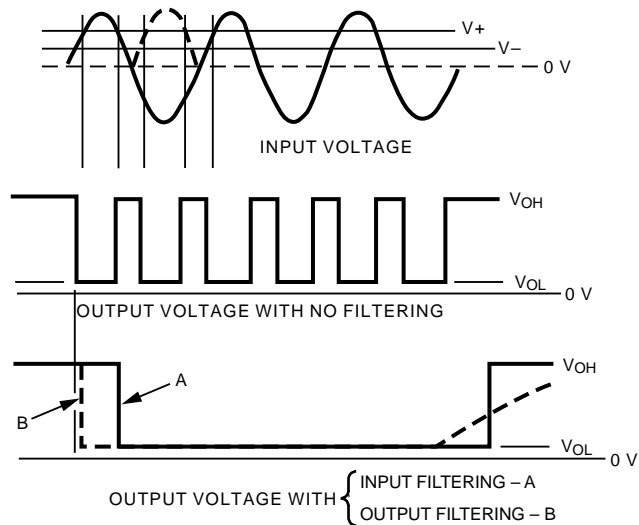


Figure 4. Waveforms for Input and Output Filtering

required. This filtering can either be done at the input or the output of the HCPL-3700. Figure 4 shows the waveforms that would be obtained with input or output filtering.

If filtering is done on the output, the result will be a signal that begins to respond very quickly to a change in the ring signal but has very slow transitions. A comparator with hysteresis would then be needed at the output to digitize the signal. If filtering were done at the input, the output would not respond as quickly to a change in the ring signal but the edges

would be much quicker. A comparator would not be needed. Since a slight delay in detection of the ring signal is generally tolerable, the input filtering technique is preferred. There is the added benefit of filtering, which follows from the fact that ring detection is slightly delayed. This benefit is that quick-edged transients with amplitudes in the range of the ring signal will not affect the output signal. The filter will eliminate them.

Input filtering is accomplished through the insertion of a capacitor across the dc inputs of the

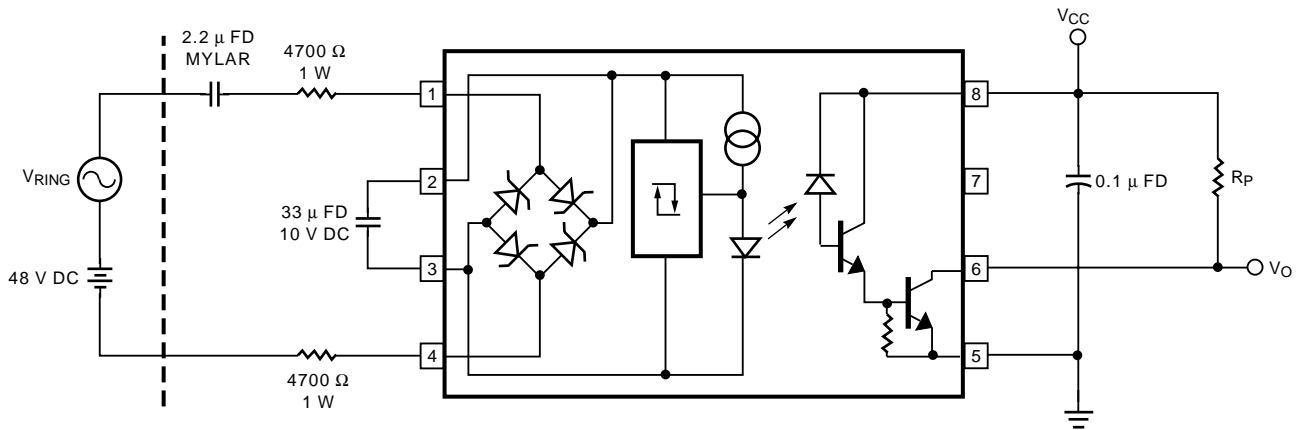


Figure 5. Equivalent Circuit with Input Filtering

optocoupler (pins 2 and 3). Because the frequency of the ring signal can go down as low as 15 Hz, this capacitor should be 33 μF. The voltage rating should be greater than 7 V, the clamping voltage of the Zener diode bridge rectifier. The introduction of this capacitor results in about a 30% reduction in the amplitude of the voltage detected by the optocoupler. This means that in order to maintain the desired effective threshold of operation, the external impedance must be lowered. Equation (1) given previously now becomes:

$$Z_{Ext} = \frac{[(V_{(Min)} (0.7) - V_{TH(Max)}) + I_{TH(Max)} + ]}{(5)}$$

Then, relating equations (2) and (5) we get the following equation which is similar to equation (3):

$$R_{Ext} = \frac{[(V_{(Min)} (0.7) - V_{TH(Max)}) + I_{TH(Max)} + ]^2 - (1/2 \pi f_{Ring} C)^2}{(6)}$$

Using the same values used previously, we obtain a value for  $R_{EXT}$  of 9845 Ω. The final equivalent circuit with filtering is then shown in Figure 5.

The power dissipation required of the resistors is reduced somewhat, to the point where 1 watt resistors could prove sufficient.

### The Agilent Technologies HCPL-3700 vs. Other Ring Detection Techniques

The HCPL-3700 optocoupler is a power-to-logic optocoupler which is very suitable for interfaces like ring detection where high voltage signals are monitored by sensitive electronics. It requires the least amount of external circuitry, and contains internal circuitry that allows for the most easily controllable switching point and higher reliability. Figure 6 illustrates another optocoupler design alternative which has “back-to-back” LED’s that transmit light to a single photodetector.

This type of optocoupler design has several disadvantages compared to the HCPL-3700. It is evident from the diagram of this optocoupler that input filtering is not possible. Input filtering with the HCPL-3700 is only possible because of the dc input, which allows for a capacitor to be added to integrate the already rectified signal. There is no way to integrate the ac signal after it is rectified at the input of the “back-to-back” optocoupler alternative. Therefore, in order to present a “clean,” digital signal to the following logic circuitry, output filtering must be done. This output filtering must include not only a capacitor but a comparator with hysteresis. Also, in looking at the data sheet the minimum guaranteed On-State RMS Input Current

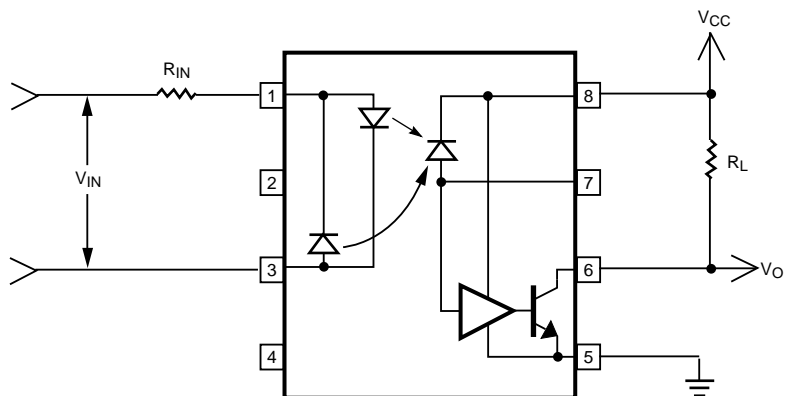


Figure 6. “Back-to-Back” Optocoupler

far exceeds the maximum guaranteed Off-State RMS Input Current. There is not a well defined threshold, which further amplifies the need for a comparator.

Another consideration, which affects reliability of the optocoupler and therefore reliability of the system, is the amount of forward current that the LED is subject to. Degradation in the light output of the LED due to high current levels reduces switching stability by raising the "effective" threshold over time. Each LED in the "back-to-back" optocoupler design experiences the full excursion of the half-wave rectified current signal. This means that, in order to ensure detection of a ring signal of the minimum amplitude specified by FCC Part 68, the circuit would have to be designed in such a way that the maximum current level experienced by the LEDs could be stressful and could lead to accelerated degradation. With the HCPL-3700, threshold detection is performed prior to the LED by the buffer (with hysteresis), and the LED is driven by a switched current source at low current levels. Degradation is therefore much lower.

More information on LED degradation can be found in the Agilent Technologies Application Note 1002, "Consideration of CTR Variations in Optically Coupled Isolator Designs."

There also exist integrated circuit packages specifically designed for ring detection applications. This family of ring detectors does not employ optical coupling and is less immune to transients than the HCPL-3700. An application report on this ring detector states that "when used in series with the proper resistor and capacitor, these devices will withstand 1500 V/200  $\mu$ s transients." This translates to 7.5 V/ $\mu$ s which, when compared to the HCPL-3700 values of -600 V/ $\mu$ s for Common Mode Transient Immunity at Logic Low Output and 4000 V/ $\mu$ s for CMTI at Logic High Output, is extremely low. To obtain an isolated ring detection circuit with this product, the application report recommends a single phototransistor optocoupler at the output. For the straightforward ring detection application, the HCPL-3700 is preferable for ease of design, number of external components required, isolation capabilities, and reliability.

## Summary

More and more aspects of the telecommunications industry are being automated, meaning that sensitive electronic devices are being interfaced with higher voltage, electrically-noisy circuitry. Ring detection is one area where this interface occurs. The sensitivity and expense of electronic equipment requires that this interface have high isolation capabilities, high performance capabilities, and a degree of versatility. Optical isolation with high performance optocouplers provides this.

For an integrated ring detection solution incorporating ease of design, a lower component count, and better predictability and reliability, the HCPL-3700 is optimal. The HCPL-3700 optocoupler contains a full-wave Zener diode bridge rectifier which, when combined with the correct input series impedance, provides a controllable, low-level current to an LED when a ring signal is present. With proper input filtering, consisting of a simple capacitor across the dc input, the output will be a digital, logic-compatible signal. A comparator is not required for interface to logic gates or microprocessors.



**Agilent Technologies**  
Innovating the HP Way

***www.semiconductor.agilent.com***

Data subject to change.

Copyright © 1999 Agilent Technologies, Inc.

5954-1006 (11/99)



SUNSTAR 商斯达实业集团是集研发、生产、工程、销售、代理经销、技术咨询、信息服务等为一体的高科技企业，是专业高科技电子产品生产厂家，是具有 10 多年历史的专业电子元器件供应商，是中国最早和最大的仓储式连锁规模经营大型综合电子零部件代理分销商之一，是一家专业代理和分销世界各大品牌 IC 芯片和电子元器件的连锁经营综合性国际公司，专业经营进口、国产名厂名牌电子元件，型号、种类齐全。在香港、北京、深圳、上海、西安、成都等全国主要电子市场设有直属分公司和产品展示展销窗口门市部专卖店及代理分销商，已在全国范围内建成强大统一的供货和代理分销网络。我们专业代理经销、开发生产电子元器件、集成电路、传感器、微波光电元器件、工控机/DOC/DOM 电子盘、专用电路、单片机开发、MCU/DSP/ARM/FPGA 软件硬件、二极管、三极管、模块等，是您可靠的一站式现货配套供应商、方案提供商、部件功能模块开发配套商。商斯达实业公司拥有庞大的资料库，有数位毕业于著名高校——有中国电子工业摇篮之称的西安电子科技大学（西军电）并长期从事国防尖端科技研究的高级工程师为您精挑细选、量身订做各种高科技电子元器件，并解决各种技术问题。

微波光电部专业代理经销高频、微波、光纤、光电元器件、组件、部件、模块、整机；电磁兼容元器件、材料、设备；微波 CAD、EDA 软件、开发测试仿真工具；微波、光纤仪器仪表。欢迎国外高科技微波、光纤厂商将优秀产品介绍到中国、共同开拓市场。长期大量现货专业批发高频、微波、卫星、光纤、电视、CATV 器件：晶振、VCO、连接器、PIN 开关、变容二极管、开关二极管、低噪晶体管、功率电阻及电容、放大器、功率管、MMIC、混频器、耦合器、功分器、振荡器、合成器、衰减器、滤波器、隔离器、环行器、移相器、调制解调器；光电子器件和组件：红外发射管、红外接收管、光电开关、光敏管、发光二极管和发光二极管组件、半导体激光二极管和激光器组件、光电探测器和光接收组件、光发射接收模块、光纤激光器和光放大器、光调制器、光开关、DWDM 用光发射和接收器件、用户接入系统光收发器件与模块、光纤连接器、光纤跳线/尾纤、光衰减器、光纤适配器、光隔离器、光耦合器、光环行器、光复用器/转换器；无线收发芯片和模组、蓝牙芯片和模组。

更多产品请看本公司产品专用销售网站：

商斯达微波光电产品网：[HTTP://www.rfoe.net/](http://www.rfoe.net/)

商斯达中国传感器科技信息网：<http://www.sensor-ic.com/>

商斯达工控安防网：<http://www.pc-ps.net/>

商斯达电子元器件网：<http://www.sunstare.com/>

商斯达消费电子产品网：<http://www.icasic.com/>

商斯达实业科技产品网：<http://www.sunstars.cn/> 射频微波光电元器件销售热线：

地址：深圳市福田区福华路福庆街鸿图大厦 1602 室

电话：0755-83396822 83397033 83398585 82884100

传真：0755-83376182 (0) 13823648918 MSN: SUNS8888@hotmail.com

邮编：518033 E-mail:szss20@163.com QQ: 195847376

深圳赛格展销部：深圳华强北路赛格电子市场 2583 号 电话：0755-83665529 25059422

技术支持：0755-83394033 13501568376

欢迎索取免费详细资料、设计指南和光盘；产品凡多，未能尽录，欢迎来电查询。

北京分公司：北京海淀区知春路 132 号中发电子大厦 3097 号

TEL: 010-81159046 82615020 13501189838 FAX: 010-62543996

上海分公司：上海市北京东路 668 号上海赛格电子市场 D125 号

TEL: 021-28311762 56703037 13701955389 FAX: 021-56703037

西安分公司：西安高新开发区 20 所(中国电子科技集团导航技术研究所)

西安劳动南路 88 号电子商城二楼 D23 号

TEL: 029-81022619 13072977981 FAX:029-88789382