



Linear Applications of Optocouplers

Application Note 951-2

Introduction

Optocouplers are useful in applications where analog or DC signals need to be transferred from one module to another in the presence of a large potential difference or induced noise between the ground or common points of these modules.

Potential applications are those in which large transformers, expensive instrumentation amplifiers or complicated A/D conversion schemes are used. Examples are: sensing circuits (thermocouples, transducers ...), patient monitoring equipment, power supply feedback, high voltage current monitoring, adaptive control systems, audio amplifiers and video amplifiers.

Agilent Technologies Optocouplers

Agilent's optocouplers have integrated photodetector/amplifiers with speed and linearity advantages over conventional photo-transistors. In a phototransistor, the photodetector is the collector-base junction so the capacitance impairs the collector rise time. Also, amplified photocurrent flows in the collector-base junction and modulates the photo-response,

thereby causing non-linearity. The photodetector in an Agilent optocoupler is a separately integrated diode so its photo-response is not affected by amplified photocurrent and its capacitance does not impair speed. Some linear isolation schemes employ digital conversion techniques (A/D-D/A, PWM, PCM, etc.) in which the higher speed of the integrated photodetector permits better linearity and bandwidth.

The 6N135/6N136 is recommended for single channel AC analog designs. The HCPL-2530/31 is recommended for dual channel DC linear designs. The 6N135/6 series or the 6N137 series are recommended for digital conversion schemes.

If the output transistor is biased in the active region, the current transfer relationship for the 6N135 series optocoupler can be represented as:

$$I_C = K \left(\frac{I_F}{I_F'} \right)^n$$

where I_C is the collector current; I_F is the input LED current; I_F' is the current at which K is measured; K is the collector

current when $I_F = I_F'$; and n is the slope of I_C vs. I_F on logarithmic coordinates.

The exponent n varies with I_F , but over some limited range of ΔI_F , n can be regarded as a constant. The current transfer relationship for an optoisolator will be linear only if n equals one.

For the 6N135 series optocoupler, n varies from approximately 2 at input currents less than 5 mA to approximately 1 at input currents greater than 16 mA. For AC coupled applications, reasonable linearity can be obtained with a single optocoupler. The optocoupler is biased at higher levels of input LED current where the ratio of incremental photodiode current to incremental LED current ($\delta I_D / \delta I_F$) is more nearly constant.

For better linearity and stability, servo or differential linearization techniques can be used.

The servo linearizer forces the input current of one optocoupler to track the input current of the second optocoupler by servo action. Thus, if $n_1 \cong n_2$ over the excursion range, the non-linearities will cancel and the

overall transfer function will be linear. In the differential linearizer, an input signal causes the input current of one optocoupler to increase by the same amount that input current of the second optocoupler is decreased. If $n_1 \cong n_2 \cong 2$, then a gain increment in the first optocoupler will be balanced by a gain decrement in the second optocoupler and the overall transfer function will be linear. With these techniques, matching of K will not effect the overall linearity of the circuit but will simplify circuit realization by reducing the required dynamic range of the zero and offset potentiometers.

Gain and offset stability over temperature is dependent on the stability of current sources, resistors, and the optocoupler. For the servo technique, changes of K over temperature will have only a small effect on overall gain and offset as long as the ratio of K_1 to K_2 remains constant. With the differential technique, changes of K over temperature will cause a change in gain of the circuit. Offset will remain stable as long as the ratio of K_1 to K_2 remains constant. In the AC circuit, since $(\delta I_D / \delta I_F)$ varies with temperature, the gain will also vary with temperature. A thermistor can be used in the output amplifiers of the Differential and AC circuits to compensate for this change in gain over temperature.

There are also several digital techniques to transmit an optocoupler analog signal. Optocouplers can be used to transmit a frequency- or pulse-width-modulated signal. In these applications, overall circuit bandwidth is determined by the required linearity as well as the propagation delay of the opto-

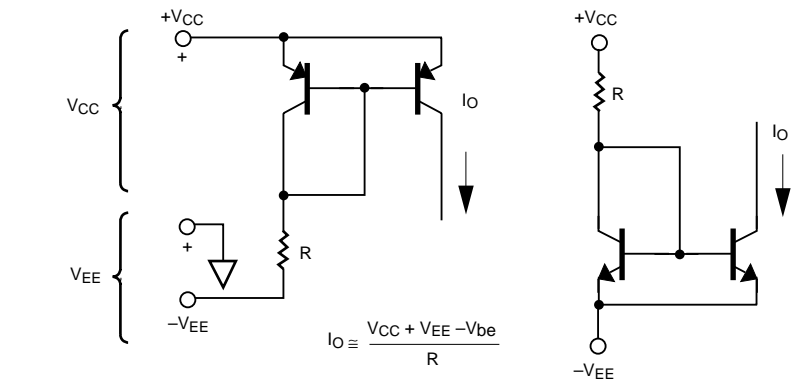


Figure 1.

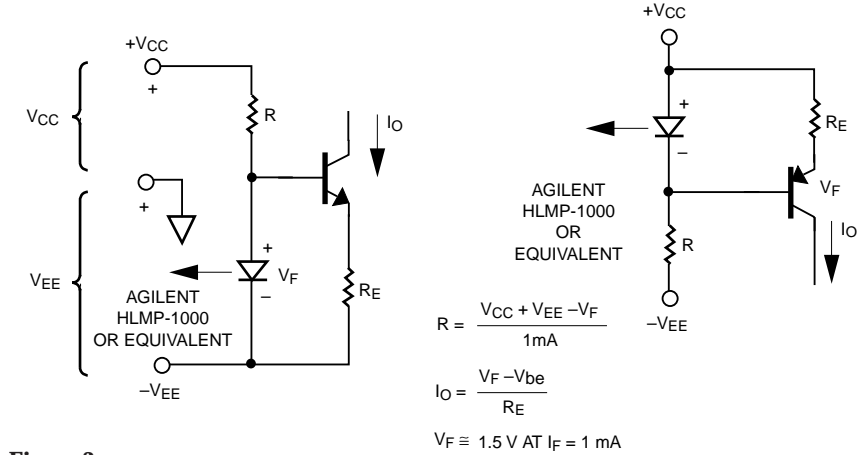


Figure 2.

coupler. The 6N137 series optocoupler features propagation delays typically less than 50 ns and the 6N135 series optocoupler features propagation typically less than 300 ns.

In several places the circuits shown call for a current source. They can be realized in several ways. If V_{CC} is stable, the current source can be a mirror type circuit as shown in Figure 1.

If V_{CC} is not stable, a simple current source such as the ones shown in Figure 2 can be realized with an LED as a voltage reference. The LED will approximately compensate the transistor over temperature since $\Delta V_{be} / \Delta T \cong \Delta V_F / \Delta T = -2 \text{ mV}/^\circ\text{C}$. See Figure 2.

$$R = \frac{V_{CC} + V_{EE} - V_F}{1\text{mA}}$$

$$I_O = \frac{V_F - V_{be}}{R_E}$$

$$V_F \cong 1.5 \text{ V AT } I_F = 1 \text{ mA}$$

Servo Isolation Amplifier

The servo amplifier shown in Figure 3 operates on the principle that two optocouplers will track each other if their gain changes by the same amount over some operating region. U_2 compares the outputs of each optocoupler and forces I_{F2} through D_2 to be equal to I_{F1} through D_1 . The constant current sources bias each I_F at 3 mA quiescent current. R_1 has been selected so that I_{F1} varies over the range of 2 mA to 4 mA as V_{IN} varies from -5 V to +5 V. R_1 can be adjusted to accommodate any desired range. With $V_{IN} = 0$, R_2 is adjusted so that $V_{OUT} = 0$. Then with V_{IN} at some value, R_4 can be adjusted for a gain of 1. Values for R_2 and R_4 have been picked for a worst case spread of optocoupler or current transfer ratios. The

transfer function of the servo amplifier is:

$$V_{OUT} = R_4 \left[(I_{F'2}) \left(\frac{K_1 R_2 (I_{CC1})^{n_1}}{K_2 R_3 (I_{F'1})^{n_1}} \right)^{1/n_2} \left(1 + \frac{V_{IN}}{R_1 I_{CC1}} \right)^{n_1/n_2} - I_{CC2} \right]$$

After zero adjustment, this transfer function reduces to:

$$V_{OUT} = R_4 I_{CC2} \left[(1 + x)^n - 1 \right]$$

Where $x = \frac{V_{IN}}{R_1 I_{CC1}}$, $n = \frac{n_1}{n_2}$

The non linearities in the transfer function where $n_1 \neq n_2$ can be written as shown below. For example, if $|x| \leq 0.35$, $n = 1.05$, then the linearity error is 1% of the desired signal.

$$\frac{\text{linearity error}}{\text{desired signal}} = \frac{(1 + x)^n - n x - 1}{n x}$$

Typical Performance for the Servo Linearized DC Amplifier:

- 1% linearity for 10 V p-p dynamic range
- Unity voltage gain
- 25 kHz bandwidth (limited by U_1 , U_2)
- Gain drift: $-0.03\%/^{\circ}\text{C}$
- Offset drift: $\pm 1 \text{ mV}/^{\circ}\text{C}$
- Common mode rejection: 46 dB at 1 kHz
- 500 V DC insulation (3000 V if two single couplers are used)

Differential Isolation Amplifier

The differential amplifier shown in Figure 4 operates on the principle that an operating region exists where a gain increment in one optocoupler can be approximately balanced by a gain decrement in the second optocoupler. As I_{F1} increases due to changes in V_{IN} , I_{F2} decreases by an equal amount. If $n_1 = n_2 = 2$, then the gain increment caused by increases in I_{F1} will be balanced by the gain decrement caused by decreases in I_{F2} . The constant current source

biases each I_F at 3 mA quiescent current. R_1 and R_2 are designed so that I_F varies over the range of 2 mA to 4 mA as V_{IN} varies from -5 V to +5 V. R_1 and R_2 can be adjusted to accommodate any desired dynamic range. U_3 and U_4 are used as a differential current amplifier:

$$V_{OUT} = R_5 [(R_3 / R_4) I_{C1} - I_{C2}]$$

R_3, R_4, R_5 have been picked for an amplifier with a gain of 1 for a worst case spread of coupler current transfer ratios. The transfer function of the differential amplifier is:

$$V_{OUT} = R_5 \left[\left(\frac{K_1 R_3}{R_4} \right) \left(\frac{I_{CC}}{2 I_{F'1}} \right)^{n_1} \left(1 + \frac{V_{IN}}{R I_{CC}} \right)^{n_1} - K_2 \left(\frac{I_{CC}}{2 I_{F'2}} \right)^{n_2} \left(1 - \frac{V_{IN}}{R I_{CC}} \right)^{n_2} \right]$$

if $R \equiv R_1 \equiv R_2$

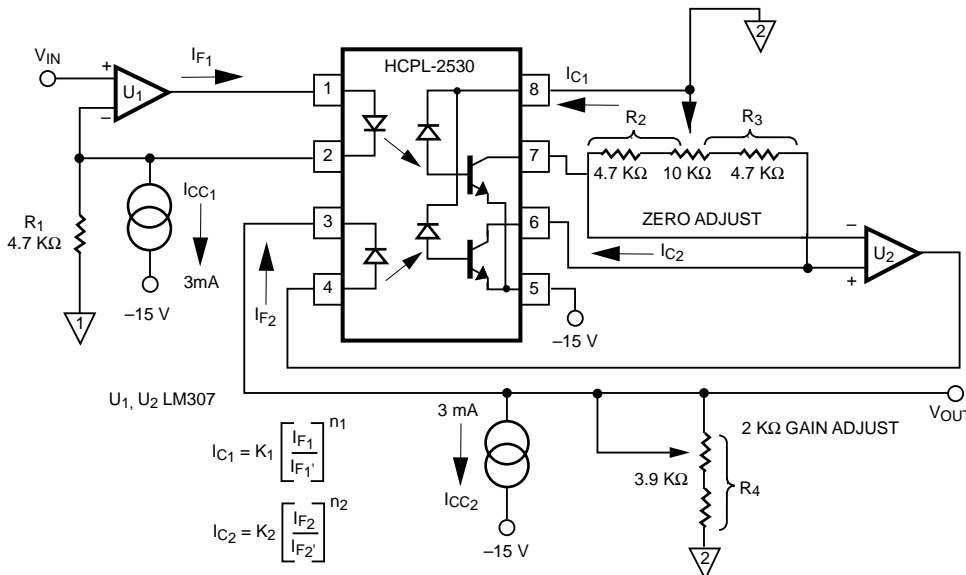


Figure 3. Servo Type DC Isolation Amplifier

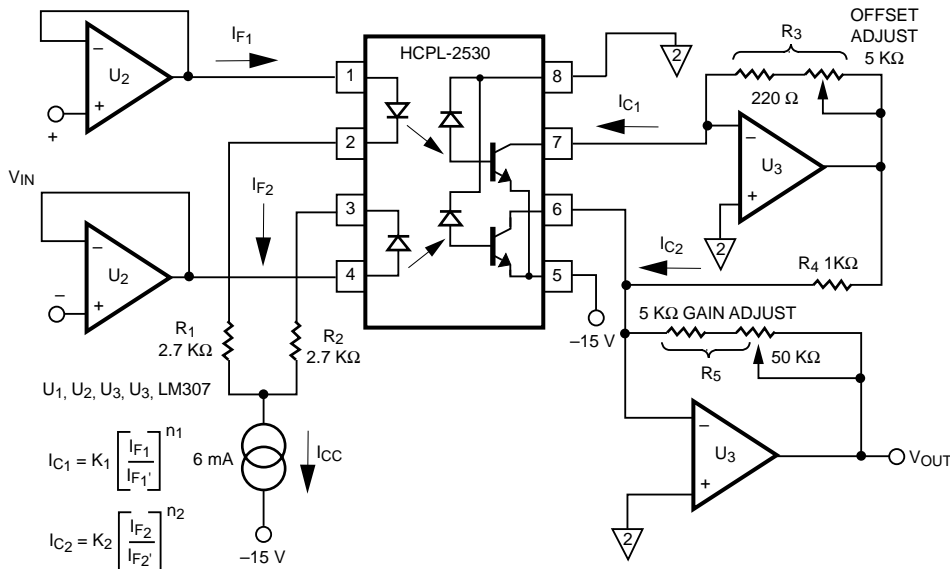


Figure 4. Differential Type DC Isolation Amplifier

After zero adjustment, this transfer function reduces to:

$$V_{OUT} = R_5 K' \left[\left(1 + \frac{V_{IN}}{R I_{CC}} \right)^{n_1} - \left(1 - \frac{V_{IN}}{R I_{CC}} \right)^{n_2} \right]$$

$$\text{Where } K' = \left(\frac{K_1 R_3}{R_4} \right) \left(\frac{I_{CC}}{2 I_{F'1}} \right)^{n_1} = K_2 \left(\frac{I_{CC}}{2 I_{F'2}} \right)^{n_2}$$

The non linearities in the transfer function when $n_1 \neq n_2 \neq 2$ can be written as shown below. For example, if $|x| \leq 0.35$, $n_1 = 1.9$, $n_2 = 1.8$, then the linearity error is 1.5% of the desired signal.

$\frac{\text{linearity error}}{\text{desired signal}} =$

$$\frac{(1+x)^{n_1} - (1-x)^{n_2} - (n_1 - n_2)x}{(n_1 + n_2)x}$$

where $x = \frac{V_{IN}}{R I_{CC}}$

Typical Performance of the Differential Linearized DC Amplifier:

- 3% linearity for 10 V p-p dynamic range
- Unity voltage gain
- 25 kHz bandwidth (limited by U1, U2, U3, U4)
- Gain drift: -0.4%/°C
- Offset drift: ±4 mV/°C
- Common mode rejection: 70 dB at 1 kHz
- 3000 V DC insulation

AC Coupled Amplifier

In an AC circuit, since there is no requirement for a DC reference, a single optocoupler can be utilized by biasing the optocoupler in a region of constant incremental CTR ($\delta I_D / \delta I_F$). An example of this type of circuit is shown in Figure 5. Q1 is biased by R1, R2 and R3 for a collector quiescent current of 20 mA. R3 is selected so that I_F varies from 15 mA to 25 mA for V_{IN} of 1 V p-p. Under these operating conditions, the 6N136 operates in a region of almost constant incremental CTR. Linearity can be improved at the expense of signal-to-noise ratio by reducing I_F excursions. This can be

accomplished by increasing R3, then adding a resistor from the collector of Q1 to ground to obtain the desired quiescent I_F of 20 mA. Q2 and Q3 form a cascade amplifier with feedback applied through R4 and R6. R6 is selected as V_{be}/I_3 with I3 selected for maximum gain bandwidth product of Q3. R7 is selected to allow maximum excursions of V_{OUT} without clipping. R5 provides DC bias to Q3. Closed loop gain ($\Delta V_{OUT}/\Delta V_{IN}$) can be adjusted with R4. The transfer function of the amplifier is:

$$\frac{V_{OUT}}{V_{IN}} \cong \left(\frac{\partial I_D}{\partial I_F} \right) \left(\frac{1}{R_3} \right) \left(\frac{R_4 R_7}{R_6} \right)$$

Typical Performance of the Wide Bandwidth AC Amplifier:

- 2% linearity over 1 V p-p dynamic range
- Unity voltage gain
- 10 MHz bandwidth
- Gain drift: -0.6%/°C
- Common mode rejection: 22 dB at 1 MHz
- 3000 V DC insulation

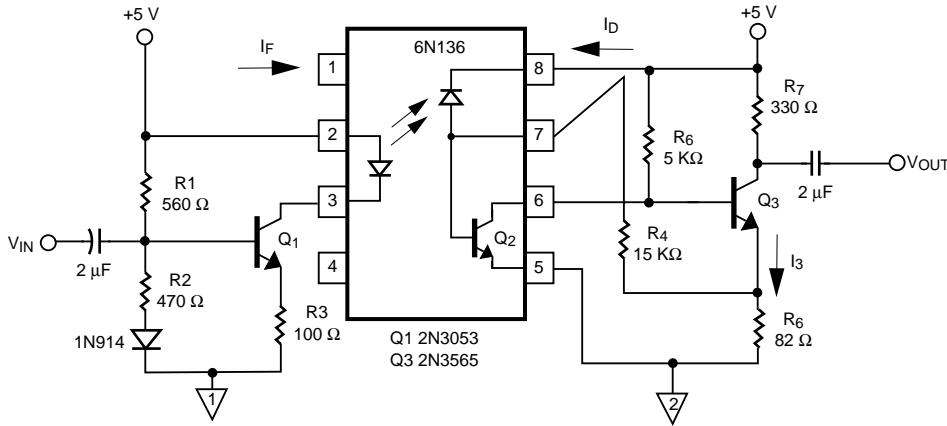


Figure 5. Wide Bandwidth AC Isolation Amplifier

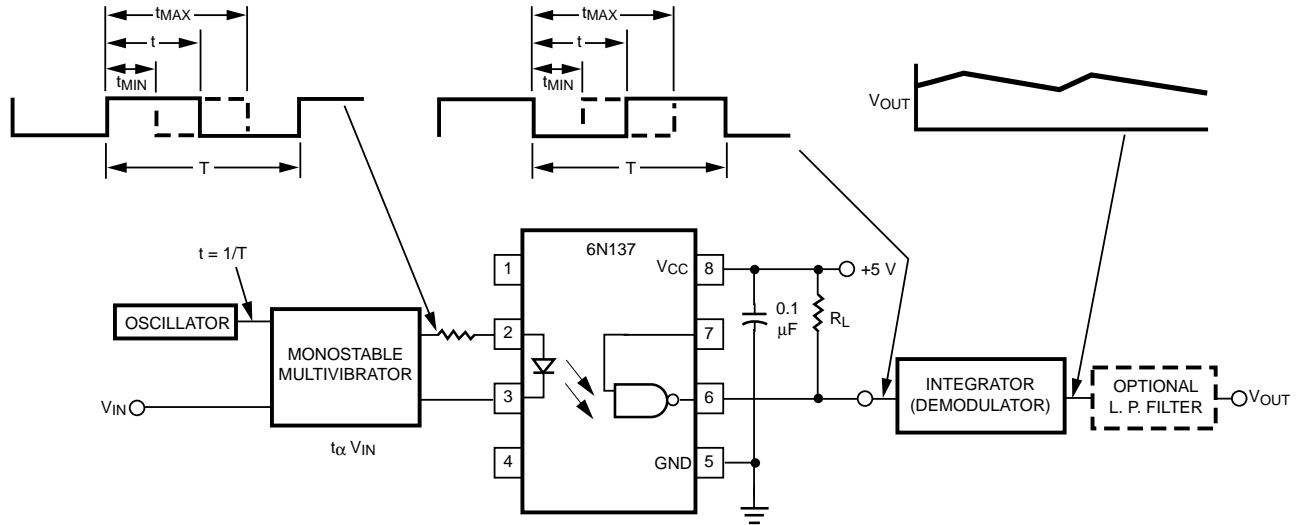


Figure 6. Pulse Width Modulation

Digital Isolation Techniques

Digital conversion techniques can be used to transfer an analog signal between two isolated systems. With these techniques, the analog signal is converted into some digital form and transmitted through the optocoupler. This digital information is then converted back to the analog signal at the output. Since the optocoupler is used only as a switch, the overall circuit linearity is primarily dependent on the accuracy by which the analog

signal can be converted into digital form and then back to the analog signal. However, the overall circuit bandwidth is limited by the propagation delays of the optocoupler.

Figure 6 shows a pulse width modulated scheme to isolate an analog signal. The oscillator operates at a fixed frequency, f , and the monostable multivibrator varies the duty factor of the oscillator proportional to the input signal, V_{IN} . The maximum frequency at which the oscillator can be operated is determined by

the required linearity of the circuit and the propagation delay of the optoisolators:

$$(t_{max} - t_{min}) (\text{required linearity}) \geq |t_{PLH} - t_{PHL}|$$

At the output, the pulse width modulated signal is then converted back to the original analog signal. This can be accomplished with an integrator circuit followed by a low pass filter or through some type of demodulator circuit that gives an output voltage proportional to the duty factor of the oscillator.



Figure 7 shows a voltage to frequency conversion scheme to isolate an analog signal. The voltage to frequency converter gives an output frequency proportional to V_{IN} . The maximum frequency that can be transmitted through the optocoupler is approximately:

$$f_{\max} \cong 1 / t,$$

where $t = t_{PLH}$ or t_{PHL} , whichever is larger.

At the output, the frequency is converted back into a voltage. The overall circuit linearity is dependent only on the linearity of the V-F and F-V converters.

Another scheme similar to voltage to frequency conversion is frequency modulation. A carrier frequency, f_o , is modulated by Δf such that $f_o \pm \Delta f$ is proportional to V_{IN} . Then at the output, V_{OUT} is reconstructed with a phase locked loop or similar circuit.

One further scheme to isolate an analog signal is to use A-D and D-A converters and transfer the binary or BCD information through

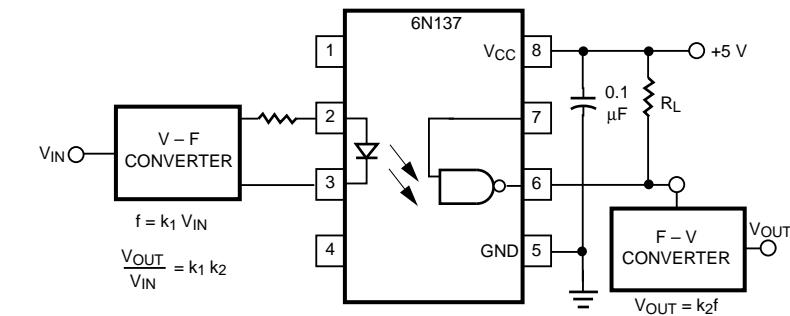


Figure 7. Voltage to Frequency Conversion

optocoupler. The information can be transmitted through the optocoupler in parallel or serial format depending on the outputs available from the A-D converter. If serial outputs are not available, the A-D outputs can be converted into serial form with a PISO shift register and transmitted through one high speed optocoupler. This scheme becomes economical especially where high resolution is required allowing several optocouplers to be replaced with one high speed optocoupler. Refer to Agilent Application Note 947 for further discussion of digital data transmission techniques.

SUNSTAR 商斯达实业集团是集研发、生产、工程、销售、代理经销、技术咨询、信息服务等为一体的高科技企业，是专业高科技电子产品生产厂家，是具有 10 多年历史的专业电子元器件供应商，是中国最早和最大的仓储式连锁规模经营大型综合电子零部件代理分销商之一，是一家专业代理和分销世界各大品牌 IC 芯片和电子元器件的连锁经营综合性国际公司，专业经营进口、国产名厂名牌电子元件，型号、种类齐全。在香港、北京、深圳、上海、西安、成都等全国主要电子市场设有直属分公司和产品展示展销窗口门市部专卖店及代理分销商，已在全国范围内建成强大统一的供货和代理分销网络。我们专业代理经销、开发生产电子元器件、集成电路、传感器、微波光电元器件、工控机/DOC/DOM 电子盘、专用电路、单片机开发、MCU/DSP/ARM/FPGA 软件硬件、二极管、三极管、模块等，是您可靠的一站式现货配套供应商、方案提供商、部件功能模块开发配套商。商斯达实业公司拥有庞大的资料库，有数位毕业于著名高校——有中国电子工业摇篮之称的西安电子科技大学（西军电）并长期从事国防尖端科技研究的高级工程师为您精挑细选、量身订做各种高科技电子元器件，并解决各种技术问题。

微波光电部专业代理经销高频、微波、光纤、光电元器件、组件、部件、模块、整机；电磁兼容元器件、材料、设备；微波 CAD、EDA 软件、开发测试仿真工具；微波、光纤仪器仪表。欢迎国外高科技微波、光纤厂商将优秀产品介绍到中国、共同开拓市场。长期大量现货专业批发高频、微波、卫星、光纤、电视、CATV 器件：晶振、VCO、连接器、PIN 开关、变容二极管、开关二极管、低噪晶体管、功率电阻及电容、放大器、功率管、MMIC、混频器、耦合器、功分器、振荡器、合成器、衰减器、滤波器、隔离器、环行器、移相器、调制解调器；光电子器件和组件：红外发射管、红外接收管、光电开关、光敏管、发光二极管和发光二极管组件、半导体激光二极管和激光器组件、光电探测器和光接收组件、光发射接收模块、光纤激光器和光放大器、光调制器、光开关、DWDM 用光发射和接收器件、用户接入系统光收发器件与模块、光纤连接器、光纤跳线/尾纤、光衰减器、光纤适配器、光隔离器、光耦合器、光环行器、光复用器/转换器；无线收发芯片和模组、蓝牙芯片和模组。

更多产品请看本公司产品专用销售网站：

商斯达微波光电产品网：[HTTP://www.rfoe.net/](http://www.rfoe.net/)

商斯达中国传感器科技信息网：<http://www.sensor-ic.com/>

商斯达工控安防网：<http://www.pc-ps.net/>

商斯达电子元器件网：<http://www.sunstare.com/>

商斯达消费电子产品网：<http://www.icasic.com/>

商斯达实业科技产品网：<http://www.sunstars.cn/> 射频微波光电元器件销售热线：

地址：深圳市福田区福华路福庆街鸿图大厦 1602 室

电话：0755-83396822 83397033 83398585 82884100

传真：0755-83376182 (0) 13823648918 MSN: SUNS8888@hotmail.com

邮编：518033 E-mail:szss20@163.com QQ: 195847376

深圳赛格展销部：深圳华强北路赛格电子市场 2583 号 电话：0755-83665529 25059422

技术支持：0755-83394033 13501568376

欢迎索取免费详细资料、设计指南和光盘；产品凡多，未能尽录，欢迎来电查询。

北京分公司：北京海淀区知春路 132 号中发电子大厦 3097 号

TEL: 010-81159046 82615020 13501189838 FAX: 010-62543996

上海分公司：上海市北京东路 668 号上海赛格电子市场 D125 号

TEL: 021-28311762 56703037 13701955389 FAX: 021-56703037

西安分公司：西安高新开发区 20 所(中国电子科技集团导航技术研究所)

西安劳动南路 88 号电子商城二楼 D23 号

TEL: 029-81022619 13072977981 FAX:029-88789382