

Agilent HCPL-8100/0810 In 7Vpp Isolated Powerline Communications Application Note 5087

Introduction

While 3.5Vpp output voltage of HCPL-8100/0810 line driver at full load is sufficient for most powerline communications, some applications such as AMR (Automated Meter Reading) call for higher carrier signal voltages. Class-122 of EN50065-1 regulation allows up to 7Vpp signal voltage at the powerline mains for carrier frequency between 95kHz and 148.5kHz. A simple method to

double (increase by 6dB) the output voltage yet without sacrificing the current driving capability exists – it is done through cascading 2 line drivers in series as shown in the above schematic drawing (Figure 1). For carrier frequencies <70kHz, more than 7Vpp powerline signal voltage is allowable under the same CENELEC Regulation. This is still achievable by increasing the turns-ratio of the signal transformer T1.

Detailed description of the configuration is given below:

A 3x gain is set for the first line driver (U1) assuming maximum input signal is 1.75Vpp. Vout1 will be 3.5Vpp. Due to inverting effect of HCPL-8100/0810, the output of U2 at Vout2 is also 3.5Vpp but at 180° out of phase with Vout1. The effective signal level will be 7Vpp across the primary winding of T1. For different input signal levels at Vin, Gain of U1 (R2/R1) stage can be adjusted to get 3.5Vpp at Vout1. But to achieve 180° matching effect between Vout1 and Vout2, gain of U2 (R4/R3) should always be fixed at unity.

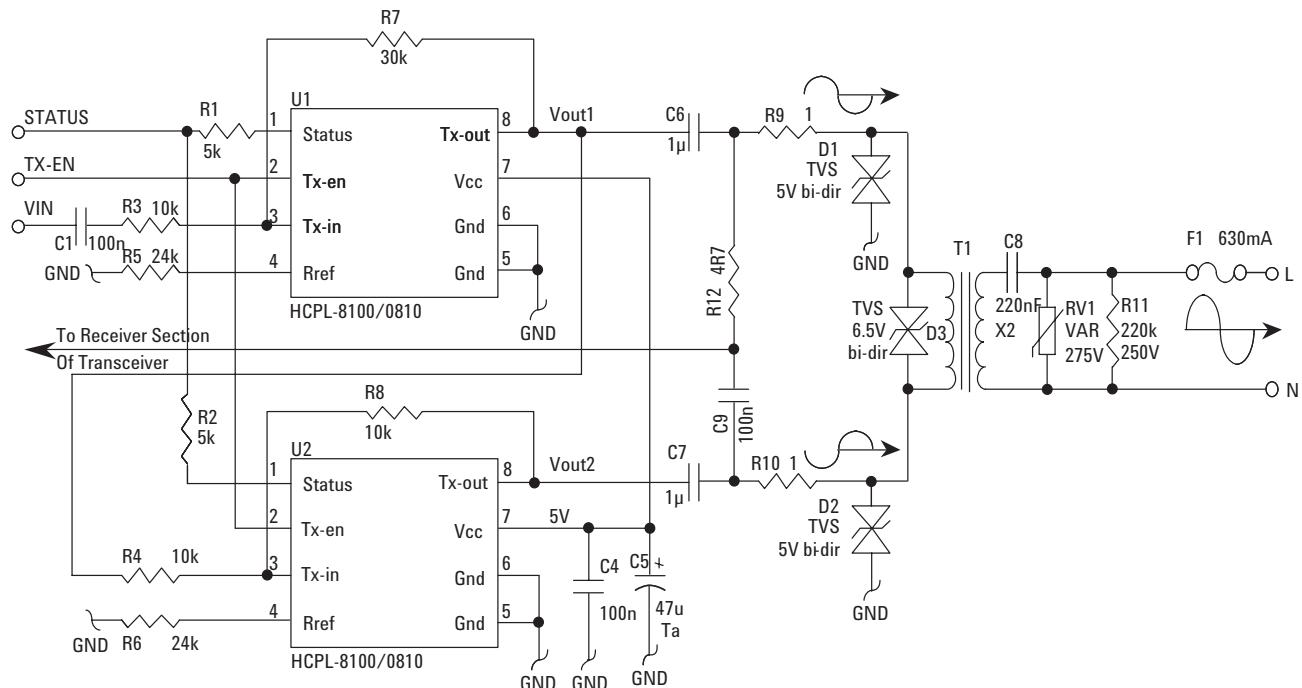


Figure 1. 7Vpp Applications Through Cascading 2 devices of HCPL-8100/0810 in Series



Agilent Technologies

External resistors R9 & R10 are recommended if the powerline impedance is lower than 7Ω in order to limit the output current within 1App.

Surge/transient protections are provided with RV1 MOV (275Vac rated Metal Oxide Varistor), D1/D2 TVS (5V rated bi-directional transient voltage suppressor) and D3 TVS (6.5V rated/bi-directional). Fuse is selected according to MOV's rating. 6.5V rated D3 TVS (with minimum breakdown voltage of 7.22V) across powerline terminals is sufficient as the full-load signal level is only 7Vpp. For powerline application, it should be able to withstand 4kV of transient/surge voltages according to EN50065-4-2 requirements. At such high transient/surge voltages, the terminal voltage of the D3 TVS will increase to a maximum voltage of 11V and the primary side voltage of T1 is protected at <11Vpp. Therefore, the maximum transient voltage experienced by both U1 & U2 devices is still within the acceptable 5.5V absolute maximum limit. No additional rail-rail diode protection is needed.

Powerline status such as short circuits or over-current will be available to the microcontroller through the STATUS pin. This pin acts as early warning system to prevent both U1 and U2 devices from catastrophic failures.

One important consideration before adopting the configuration as shown in Figure 1 is the phase delay of U2. If the phase delay displays by U2 is significant, the circuit will not work properly. It has been found from bench test that the standard phase delay

is only about 30ns at 400kHz carrier frequency. This is negligible for most of the applications.

The close loop response of the circuit is as shown in Figure 2. Thick line represents the close loop voltage gain while the thin line shows the frequency response of the open loop voltage gain. The close loop response is flat for a carrier frequency range of 9kHz ~ 400kHz, makes it suitable for both CENELEC EN50065 and FCC Part 15 requirements.

As expected, harmonics (HD2 & HD3) performance of the

configuration are still acceptable - both at -62dBc for 100kHz carrier frequency. Tested at 50Ω CISPR 16 load with 7Vpp signal & 5V supply.

Figure 3 shows the typical load curve of the circuit taken at 120kHz carrier signal with varying loads from 0Ω to 100Ω .

Characteristics of the above circuit configurations

Vout = 7Vpp;
 Iout = 1App maximum;
 Freq. range: 9kHz ~ 400kHz;
 U1 Gain: 3 (adjustable);
 U2 Gain: 1 (fixed);
 Phase Delay: 4.3° @ 400kHz;

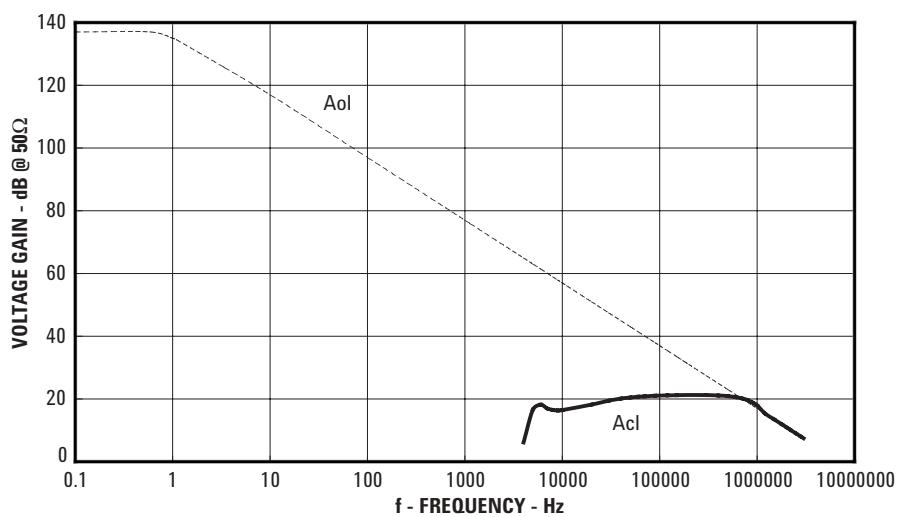


Figure 2. Close-loop Frequency Response of Figure 1

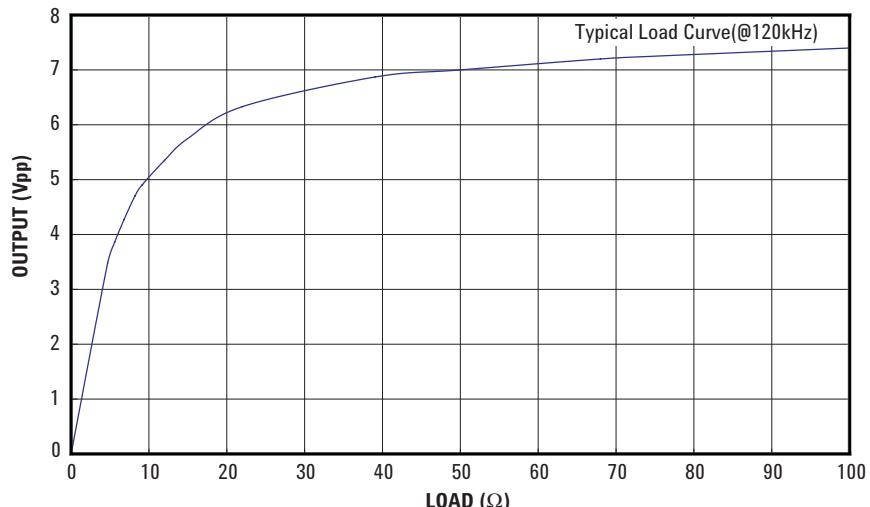


Figure 3. Typical Load Curve (0-100Ω)

**www.agilent.com/
semiconductors**

For product information and a complete list
of distributors, please go to our web site.

For technical assistance call:

Americas/Canada: +1 (800) 235-0312
or (408) 654-8675

Europe: +49 (0) 6441 92460

China: 10800 650 0017

Hong Kong: (+65) 6756 2394

India, Australia, New Zealand: (+65) 6755 1939

Japan: (+81 3) 3335-8152(Domestic/Inter-
national), or 0120-61-1280(Domestic Only)

Korea: (+65) 6755 1989

Singapore, Malaysia, Vietnam, Thailand,
Philippines, Indonesia: (+65) 6755 2044

Taiwan: (+65) 6755 1843

Data subject to change.

Copyright © 2004 Agilent Technologies, Inc.

September 16, 2004

5989-1573EN



Agilent Technologies

SUNSTAR 商斯达实业集团是集研发、生产、工程、销售、代理经销、技术咨询、信息服务等为一体的高科技企业，是专业高科技电子产品生产厂家，是具有 10 多年历史的专业电子元器件供应商，是中国最早和最大的仓储式连锁规模经营大型综合电子零部件代理分销商之一，是一家专业代理和分销世界各大品牌 IC 芯片和电子元器件的连锁经营综合性国际公司，专业经营进口、国产名厂名牌电子元件，型号、种类齐全。在香港、北京、深圳、上海、西安、成都等全国主要电子市场设有直属分公司和产品展示展销窗口门市部专卖店及代理分销商，已在全国范围内建成强大统一的供货和代理分销网络。我们专业代理经销、开发生产电子元器件、集成电路、传感器、微波光电元器件、工控机/DOC/DOM 电子盘、专用电路、单片机开发、MCU/DSP/ARM/FPGA 软件硬件、二极管、三极管、模块等，是您可靠的一站式现货配套供应商、方案提供商、部件功能模块开发配套商。商斯达实业公司拥有庞大的资料库，有数位毕业于著名高校——有中国电子工业摇篮之称的西安电子科技大学（西军电）并长期从事国防尖端科技研究的高级工程师为您精挑细选、量身订做各种高科技电子元器件，并解决各种技术问题。

微波光电部专业代理经销高频、微波、光纤、光电元器件、组件、部件、模块、整机；电磁兼容元器件、材料、设备；微波 CAD、EDA 软件、开发测试仿真工具；微波、光纤仪器仪表。欢迎国外高科技微波、光纤厂商将优秀产品介绍到中国、共同开拓市场。长期大量现货专业批发高频、微波、卫星、光纤、电视、CATV 器件：晶振、VCO、连接器、PIN 开关、变容二极管、开关二极管、低噪晶体管、功率电阻及电容、放大器、功率管、MMIC、混频器、耦合器、功分器、振荡器、合成器、衰减器、滤波器、隔离器、环行器、移相器、调制解调器；光电子元器件和组件：红外发射管、红外接收管、光电开关、光敏管、发光二极管和发光二极管组件、半导体激光二极管和激光器组件、光电探测器和光接收组件、光发射接收模块、光纤激光器和光放大器、光调制器、光开关、DWDM 用光发射和接收器件、用户接入系统光光收发器件与模块、光纤连接器、光纤跳线/尾纤、光衰减器、光纤适配器、光隔离器、光耦合器、光环行器、光复用器/转换器；无线收发芯片和模组、蓝牙芯片和模组。

更多产品请看本公司产品专用销售网站：

商斯达微波光电产品网：[HTTP://www.rfoe.net/](http://www.rfoe.net/)

商斯达中国传感器科技信息网：<http://www.sensor-ic.com/>

商斯达工控安防网：<http://www.pc-ps.net/>

商斯达电子元器件网：<http://www.sunstare.com/>

商斯达消费电子产品网：[//www.icasic.com/](http://www.icasic.com/)

商斯达实业科技产品网：[//www.sunstars.cn/](http://www.sunstars.cn/) 射频微波光电元器件销售热线：

地址：深圳市福田区福华路福庆街鸿图大厦 1602 室

电话：0755-83396822 83397033 83398585 82884100

传真：0755-83376182 (0) 13823648918 MSN：SUNS8888@hotmail.com

邮编：518033 E-mail：szss20@163.com QQ：195847376

深圳赛格展销部：深圳华强北路赛格电子市场 2583 号 电话：0755-83665529 25059422

技术支持：0755-83394033 13501568376

欢迎索取免费详细资料、设计指南和光盘；产品凡多，未能尽录，欢迎来电查询。

北京分公司：北京海淀区知春路 132 号中发电子大厦 3097 号

TEL：010-81159046 82615020 13501189838 FAX：010-62543996

上海分公司：上海市北京东路 668 号上海赛格电子市场 D125 号

TEL：021-28311762 56703037 13701955389 FAX：021-56703037

西安分公司：西安高新区 20 所(中国电子科技集团导航技术研究所)

西安劳动南路 88 号电子商城二楼 D23 号

TEL：029-81022619 13072977981 FAX:029-88789382