

900 MHz low noise amplifier demoboard

Application report

900 MHz LOW NOISE AMPLIFIER DEMOBOARD

Summary: The performance of wideband transistors, BFG505 (BFG520, BFR505, BFR520) is demonstrated in a 900 MHz Low Noise Amplifier in the frontend of a subscriber handset. (i.e. Cordless phone, cellular phone) The transistors, as evaluated in this application note, are available in the SOT23, SOT323 (SC70) and SOT143 (3 versions) packages.

General characteristics of demoboard with BFG505:

Supply	2.5-3.6 V, 2 mA	
Gain	typ. 11 dB	
Noise Figure	F<1.5 dB	includes losses
In/Out return loss	S11,S22<-10 dB	
PCB size	10 x 10 mm	active area
Components	BFG505 resistors capacitors coils	SOT143 Philips 0603/0805 Philips 0603 air wounded int. diam 1.5 mm wire 0.4 mm Cu
Stability	stable when terminated with 50 Ohm at all frequencies	

Introduction

Several AC-parameters are of importance when designing an RF low noise amplifier. The main goal is to improve system sensitivity. An optimally designed Low Noise Amp will be a trade off between noise and gain. Furthermore, when using 50 Ohm designed bandpass filters, a mismatch can result in extra losses. Obtaining 50 Ohm matching is also an important design aspect. Other AC-parameters include isolation to reduce Local Oscillator radiation and linearity. This contributes less to system performance, as it is determined mostly by the mixer. Other design requirements are a small size and very low power consumption.

Meeting all these requirements will always result in a design that is a trade off. Philips' fourth generation bipolar wideband transistors can meet the required specifications as they offer outstanding performance at 900 MHz.

Theory

A simplified formula valid for lower frequencies can learn us what match we should present to the input port of the bipolar transistor used in common emitter configuration to obtain minimum Noise Figure.

The optimal source impedance for minimum noise $R_{s\{opt\}}$ is given by:

$$R_{s\{opt\}} = \sqrt{[\beta/s*(1/s+2*r_b)]} \text{ Ohm}$$

while

$$s = qI_c/kT \text{ and } \beta = H_{FE}(DC)$$

This formula takes into account both shot noise and thermal noise.

One can see that a low bias current results in fairly high impedances. (for the BFR505 X-tal at 2 mA follows: $R_{s\{opt\}} = 270$ Ohm) For higher frequencies the optimum source impedances must be more inductive to be able to tune out internal device parasitics. The power match which gives optimum gain occurs for: $R_{s\{opt\}} = \beta/s + R_b$ (1.4 kOhm)

It is easily seen that for low currents both noise and gain match cannot be realised simultaneously.

The only way of obtaining noise and gain match simultaneously is applying a feedback. This can be done by a series emitter induction.

At 900 MHz, a few nH emitter induction can change the input impedance considerably and it will bring noise and gain match closer together at the cost of some gain (a few dB).

This makes a properly matched low noise design possible.

To show what trade-off can be reached figure 1 shows the results of Touchstone (R)* simulations based on the noise and gain parameters from the Touchstone Data diskette**.

Return losses at both input and output were below -10 dB.

As far as stability is concerned, it is impossible to design the amplifier to be unconditionally stable for both input and output for all source and load impedances at all frequencies. Some damping at frequencies outside the 900 MHz band could be necessary in some practical cases.

Negative feedback increases stability, positive feedback decreases stability.

Positive feedback can occur when the emitter is capacitively loaded. As far as possible, we should avoid this in an RF design.

* Touchstone is a registered trademark of Eesof

** Noise & s-parameter library surface mounted devices, available at your local Philips Sales office.

Practical circuit

The input and output match were realized with lumped elements since they give the smallest size at 900 MHz. (see fig. 2) Decoupling capacitors forming short circuit at 900 MHz are 27 pF. Power supply decoupling is done with a 1 nF capacitor. The coils could be replaced by PCB-track inductors or SMD inductors. Attention should be given to the value of the emitter induction which can be realized through a few mm track. A proper ground should be available. One should be carefull in choosing capacitance and inductance especially at the input since low Q elements give noise degradation. The high impedance match at the input is not easy to realize and is most sensitive to parameter spread of the passive components. The PCB design was optimized for minimum noise. Simulated component values for the different transistors can be found in figures 3-6. Results of measurements are shown in figures 7-9. Circuit layout can be seen in fig. 10. It was build on a 1 mm FR4 epoxy substrate. Theoretical component values may slightly differ from practical values due to layout parasitics.

Biassing considerations.

At 3V supply, stable biassing can be difficult. To reduce the effects of H_{FE} spread a decoupled emitter resistor is often necessary. This decouple capacitor increases the risk for instability. Another solution, requiring a low cost low frequency PNP transistor can be seen in fig.11. This solution gives H_{FE} independent biassing in grounded emitter configuration.

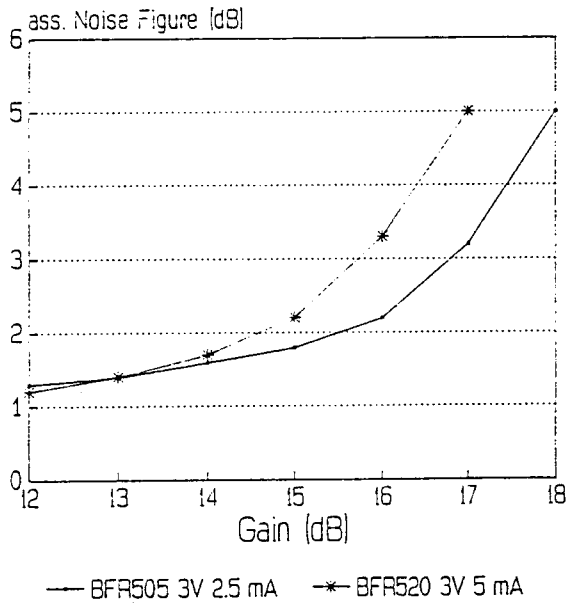


Fig. 1 Gain and associated Noise Figure

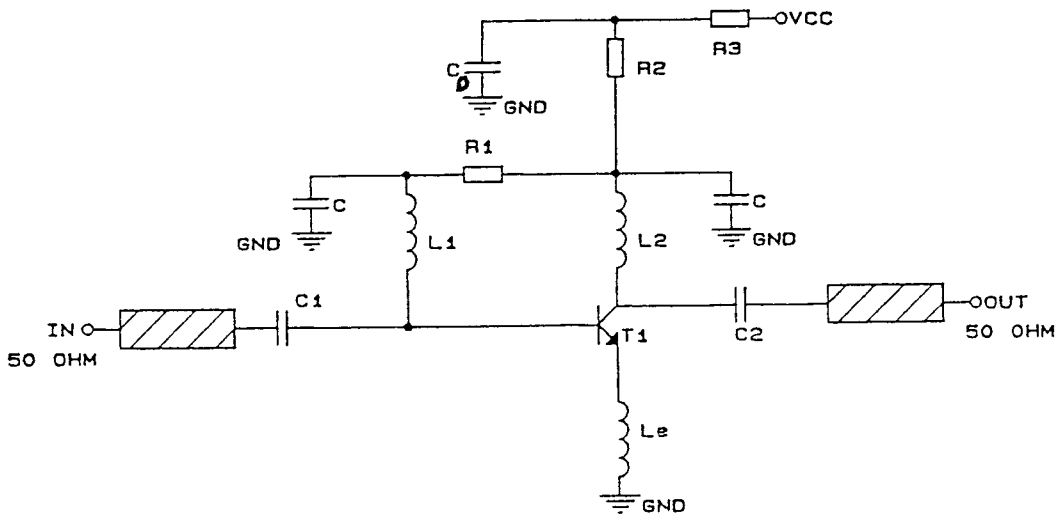


Fig 2. Schematic circuit diagram

900 MHz low noise amplifier demoboard

Application report

Fig 3. BFG505 3V 2.5 mA values of components

C1 pF	2.3	2.5	2.8	2.9	2.9	2.4	1.7
L1 nH	14	12.5	11	9.5	8.4	7.1	7.0
Le nH	3.9	3.0	2.3	1.9	1.6	1.6	2.0
C2 pF	2.2	2.2	2.1	1.9	1.7	1.2	0.8
L2 nH	14	13.4	13.3	13.0	13.0	14.7	17.7
G dB	12	13	14	15	16	17	18
NF dB	1.4	1.5	1.7	1.9	2.3	3.3	5.1

Fig 4. BFR505 3V 2.5 mA values of components

C1 pF	2.4	3.1	3.1	3.0	1.5		
L1 nH	12.5	11.5	9.5	7.5	8.2		
Le nH	2.8	2.0	1.6	1.5	1.6		
C2 pF	2.9	2.5	2.2	1.7	1.1		
L2 pF	13	12.7	11.5	11.9	12.1		
G dB	11	12	13	14	15		
NF dB	1.4	1.6	1.9	2.6	4.4		

Fig 5. BFR520 3V 5 mA value of components

C1 pF	5.7	7.2	8.5	9.5	10		
L1 nH	10.4	8.5	7	5.3	4		
Le nH	0.7	0.3	0.1	0.05	0.0		
C2 pF	3.6	3.2	2.7	2.0	1.4		
L2 nH	10.5	9.5	9.0	9.5	11.5		
G dB	12	13	14	15	16		
NF dB	1.3	1.5	1.8	2.3	3.5		

Fig 6. BFG520 3V 5 mA values of components

C1 pF	5.2	10	27	33	33		
L1 nH	13.7	20	12	8	5.9		
Le nH	2.2	1.0	0.7	0.5	0.4		
C2 pF	3.2	3.7	3.3	2.9	2.1		
L2 nH	13.3	11.3	9.3	8.7	9.1		
G dB	12	14	15	16	17		
NF dB	1.2	1.3	1.6	2.1	2.8		

900 MHz low noise amplifier demoboard

Application report


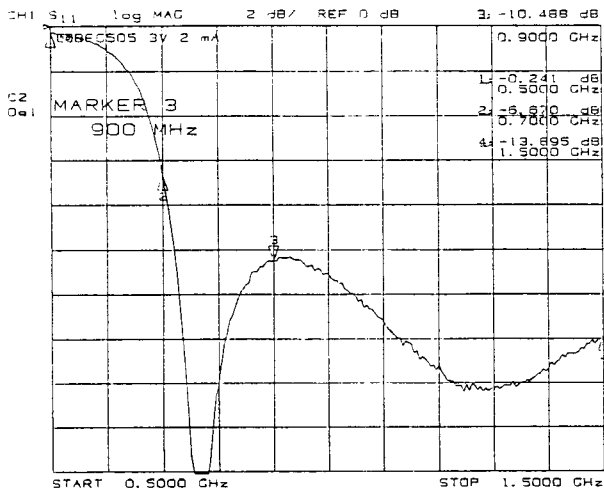
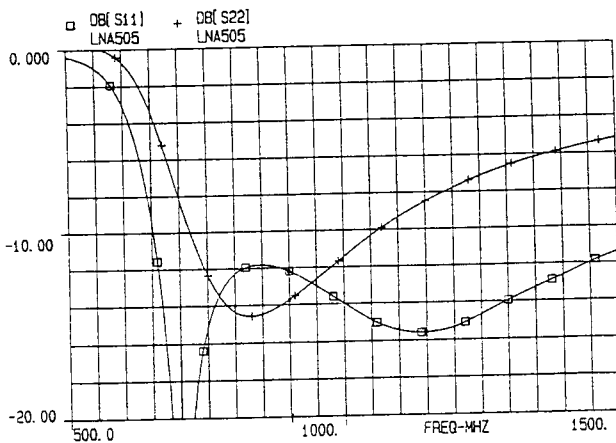


Fig 7. Measured and simulated in/out match.

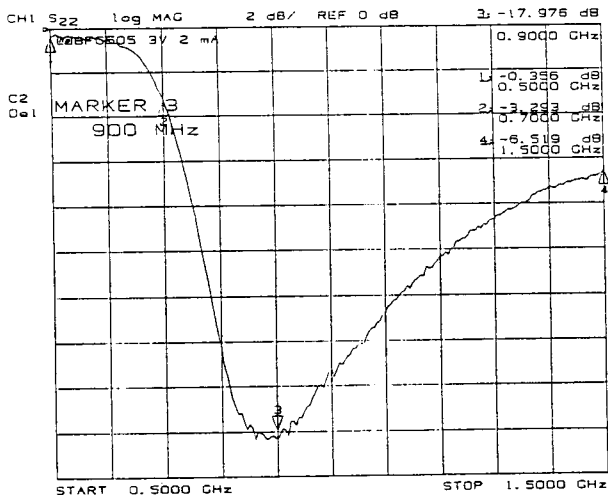

900 MHz low noise amplifier demoboard

Application report

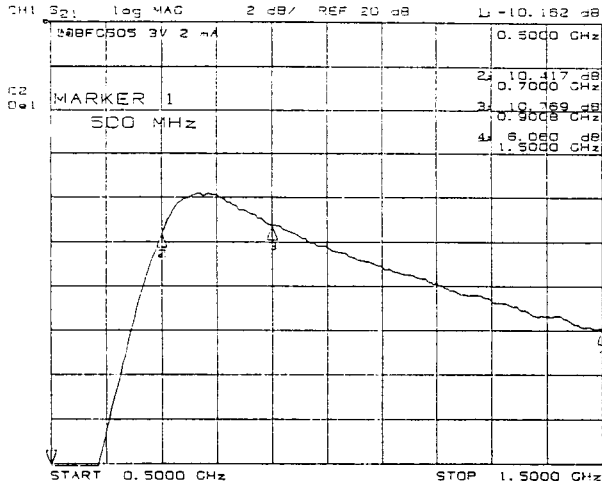


Fig.8 Measured and simulated gain.

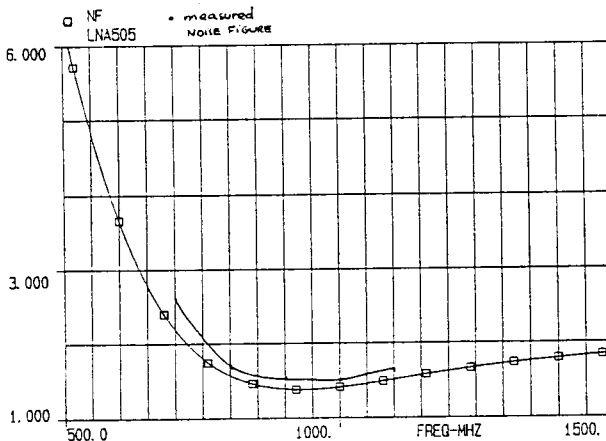
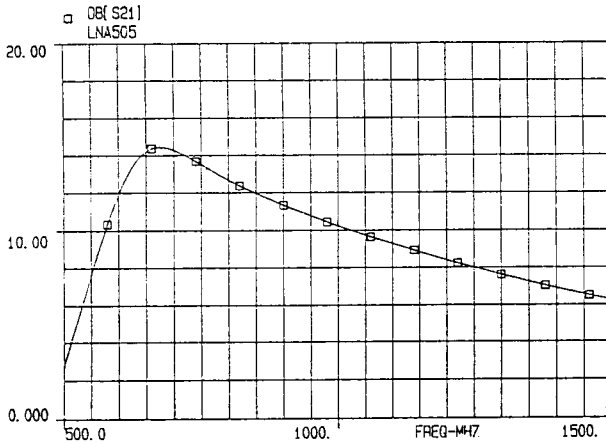


Fig.9 Measured and simulated Noise Figure

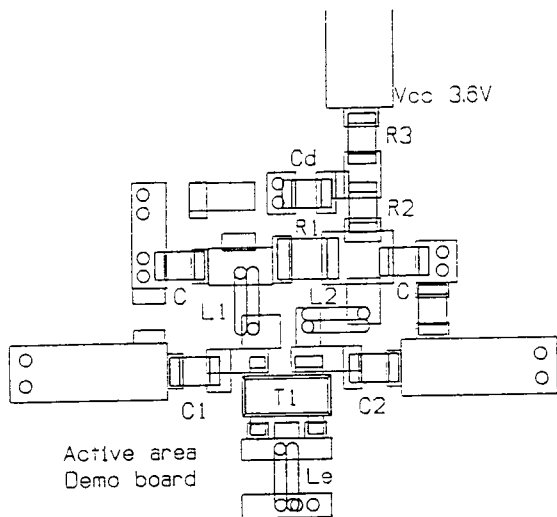


Fig. 10 Active Area Demoboard

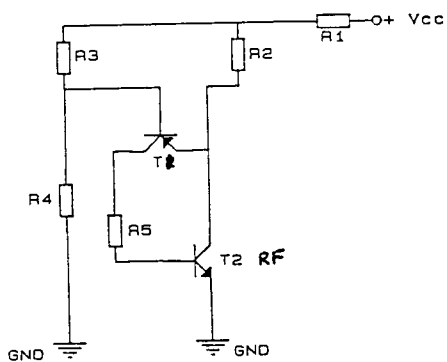


Fig. 11 schematic diagram biasing circuit

SUNSTAR 商斯达实业集团是集研发、生产、工程、销售、代理经销、技术咨询、信息服务等为一体的高科技企业，是专业高科技电子产品生产厂家，是具有 10 多年历史的专业电子元器件供应商，是中国最早和最大的仓储式连锁规模经营大型综合电子零部件代理分销商之一，是一家专业代理和分销世界各大品牌 IC 芯片和电子元器件的连锁经营综合性国际公司，专业经营进口、国产名厂名牌电子元件，型号、种类齐全。在香港、北京、深圳、上海、西安、成都等全国主要电子市场设有直属分公司和产品展示展销窗口门市部专卖店及代理分销商，已在全国范围内建成强大统一的供货和代理分销网络。我们专业代理经销、开发生产电子元器件、集成电路、传感器、微波光电元器件、工控机/DOC/DOM 电子盘、专用电路、单片机开发、MCU/DSP/ARM/FPGA 软件硬件、二极管、三极管、模块等，是您可靠的一站式现货配套供应商、方案提供商、部件功能模块开发配套商。商斯达实业公司拥有庞大的资料库，有数位毕业于著名高校——有中国电子工业摇篮之称的西安电子科技大学（西军电）并长期从事国防尖端科技研究的高级工程师为您精挑细选、量身订做各种高科技电子元器件，并解决各种技术问题。

微波光电部专业代理经销高频、微波、光纤、光电元器件、组件、部件、模块、整机；电磁兼容元器件、材料、设备；微波 CAD、EDA 软件、开发测试仿真工具；微波、光纤仪器仪表。欢迎国外高科技微波、光纤厂商将优秀产品介绍到中国、共同开拓市场。长期大量现货专业批发高频、微波、卫星、光纤、电视、CATV 器件：晶振、VCO、连接器、PIN 开关、变容二极管、开关二极管、低噪晶体管、功率电阻及电容、放大器、功率管、MMIC、混频器、耦合器、功分器、振荡器、合成器、衰减器、滤波器、隔离器、环行器、移相器、调制解调器；光电子元件和组件：红外发射管、红外接收管、光电开关、光敏管、发光二极管和发光二极管组件、半导体激光二极管和激光器组件、光电探测器和光接收组件、光发射接收模块、光纤激光器和光放大器、光调制器、光开关、DWDM 用光发射和接收器件、用户接入系统光收发器件与模块、光纤连接器、光纤跳线/尾纤、光衰减器、光纤适配器、光隔离器、光耦合器、光环行器、光复用器/转换器；无线收发芯片和模组、蓝牙芯片和模组。

更多产品请看本公司产品专用销售网站：

商斯达中国传感器科技信息网：<http://www.sensor-ic.com/>

商斯达工控安防网：<http://www.pc-ps.net/>

商斯达电子元器件网：<http://www.sunstare.com/>

商斯达微波光电产品网：[HTTP://www.rfoe.net/](http://www.rfoe.net/)

商斯达消费电子产品网：<http://www.icasic.com/>

商斯达实业科技产品网：<http://www.sunstars.cn/> 微波元器件销售热线：

地址：深圳市福田区福华路福庆街鸿图大厦 1602 室

电话：0755-82884100 83397033 83396822 83398585

传真：0755-83376182 (0) 13823648918 MSN: SUNS8888@hotmail.com

邮编：518033 E-mail:szss20@163.com QQ: 195847376

深圳赛格展销部：深圳华强北路赛格电子市场 2583 号 电话：0755-83665529 25059422

技术支持：0755-83394033 13501568376

欢迎索取免费详细资料、设计指南和光盘；产品凡多，未能尽录，欢迎来电查询。

北京分公司：北京海淀区知春路 132 号中发电子大厦 3097 号

TEL: 010-81159046 82615020 13501189838 FAX: 010-62543996

上海分公司：上海市北京东路 668 号上海赛格电子市场 D125 号

TEL: 021-28311762 56703037 13701955389 FAX: 021-56703037

西安分公司：西安高新开发区 20 所(中国电子科技集团导航技术研究所)

西安劳动南路 88 号电子商城二楼 D23 号

TEL: 029-81022619 13072977981 FAX:029-88789382