

TECHNICAL PUBLICATION

**Considerations on efficiency of
the RF power transistors in the
different classes of operation**

COE82101

**Considerations on efficiency of the RF power
transistors in the different classes of operation**

**Technical Publication
COE82101**

CONTENTS

1	SUMMARY
2	INTRODUCTION
3	CLASS-B OPERATION ($V_{BE} = 0$)
4	CLASS-C OPERATION
5	CLASS-D OPERATION
6	CLASS-E OPERATION
6.1	General considerations
6.2	Practical example
7	FINAL CONSIDERATIONS
8	REFERENCES

Considerations on efficiency of the RF power transistors in the different classes of operation

Technical Publication
COE82101

1 SUMMARY

In this report considerations are given concerning the obtainable collector efficiencies in the different classes of operation of R.F. power transistors. Also the frequency limitations are being considered.

As an example it can be mentioned that our 28 V transistors are able to operate in class-E with an efficiency of 85% up to frequencies of 60 to 70 MHz.

2 INTRODUCTION

Some times we receive questions on the possibilities to improve the efficiency of R.F. power amplifiers. Below some considerations will be given for the different classes of operation of nonlinear amplifiers.

3 CLASS-B OPERATION ($V_{BE} = 0$)

For most of our transmitting transistors we publish the collector efficiency as measured in a class-B common-emitter narrow-band test circuit. Typically this efficiency is 65 to 70%. This can be explained as follows:

- The current efficiency of a class-B amplifier is: $\pi/4 \times 100 = 78.5\%$
- The loss of the output matching network is approx. 5% because it is designed for a loaded Q-factor of 10 whilst the unloaded Q-factor is approx. 200
- The remaining losses are D.C. and R.F. losses in the built-in emitter and collector resistances of the transistor. The former is necessary for a good D.C. SOAR and the latter for a high reverse second breakdown energy giving the device sufficient ruggedness against load mismatch.

However from this situation there are deviations in both directions; e.g. the BLW89 has an efficiency of only 53%. This is caused by the tuning method of the narrow-band test circuit, because the circuit is tuned for maximum power gain. The corresponding load impedance of the transistor is sometimes strongly reactive. Phase angles of 40 to 45 ° can occur which means that the collector efficiency must be multiplied with the cosine of this angle. If a different aligning method was applied, e.g. with a more resistive dummy load, the same transistor would show a higher efficiency at the cost of some power gain.

The other extreme is formed by transistors like the BLW60 and BLY90 having efficiencies of approx. 80%. This happens only at relatively high operating frequencies where the power gain is only 4 to 5 dB. In such cases a substantial amount of the drive power is fed directly to the output circuit via the collector-base capacitance and the emitter lead inductance. This causes an artificially high collector efficiency. It is therefore better to compare transistors on the basis of oscillator efficiency being defined as:

$$\eta_0 = \frac{P_o - P_i}{V_{ce} \times I_c}$$

In addition to the considerations above there is a slow decrease of efficiency when the operating frequency comes in the neighbourhood of 50% of the f_T of the transistor. This is caused by the increased capacitive current through the transistors collector and emitter resistances.

4 CLASS-C OPERATION

The collector current efficiency can be improved by reduction of the angle of current flow. This is achieved by a negative base-emitter D.C. voltage, e.g. caused by an external base resistor which is effective for D.C.

We do not recommend this method because a bias voltage in excess of 300 mV in combination with the increased drive voltage may cause continuous breakdown of the base-emitter diode leading to degradation of this diode, i.e. higher leakage current and reduced h_{fe} .

On the other hand bias voltages below 300 mV are not very effective.

5 CLASS-D OPERATION

An excellent description of this type of operation is given in Ref.1. From this article some conclusions can be drawn:

- Push-pull operation is required with a very tight coupling between the two transistors. This can for instance be achieved by a complementary pair of transistors (NPN - PNP). However pairs showing sufficient equality of D.C. and R.F. properties are not available. As an alternative a matched pair of NPN-transistors can be used provided that a good combining transformer can be constructed which is only possible at frequencies up to appr. 30 MHz.
- The maximum frequency of operation is further restricted by the switching times of the transistors. For output powers above 10 W this is about 0.01 f_T . This means for our modern transistors with U.H.F. diffusions a maximum of 5 to 10 MHz.

6 CLASS-E OPERATION

6.1 General considerations

Design information on this class of operation can be found in Ref.2 through 5. The most important paper in this respect is Ref.4, section III B, pp. 731 to 732, equations 3.20 through 3.29. The basic circuit diagram is reproduced in Fig.1a en b. The reactance of RFC must be high compared with the load resistance. The series tuned circuit in Fig.1b. must have a sufficiently high loaded Q, e.g. greater than 5. After some re-arrangement of the above mentioned equations we find that:

$$R_L = \frac{2V_s^2}{P_o \times \left(1 + \frac{\pi^2}{4}\right)} = 0.5768 \times \frac{V_s^2}{P_o}$$

$$B = \omega_o C = \frac{2}{\pi \times \left(1 + \frac{\pi^2}{4}\right) R_L} = \frac{P_o}{\pi V_s^2}$$

$$X = \omega_o L = \frac{\pi}{8} \times \left(\frac{\pi^2}{2} - 2\right) R_L = \frac{\pi \left(\frac{\pi^2}{2} - 2\right) V_s^2}{4 \left(1 + \frac{\pi^2}{4}\right) P_o} = 0.6648 \frac{V_s^2}{P_o}$$

An ideal transistor (having zero saturation resistance) will then show a collector efficiency of 100%.

Further we know from Ref.4 that the collector peak voltage is 3.562 times the supply voltage and that the collector peak current is 2.862 times the collector D.C. current.

6.2 Practical example

To show the possibilities of class-E operation we choose the BLV 25 which is able to produce 175 W of output power at a supply voltage of 28 V up to a frequency of 108 MHz. In a 'normal' class-B amplifier this transistor shows an efficiency of 70 to 75%.

The guaranteed collector breakdown voltage of the BLV 25 is 65 V and the typical value 70 V. To prevent loss of efficiency by clipping of the collector voltage waveform we choose a supply voltage of 20 V.

The allowable collector peak current is 35 A. If we choose 30 A the drop of f_T is less than 20% compared with the point of maximum f_T .

Then the collector D.C. current becomes:

$$I_c = \frac{30}{2.862} = 10.5 \text{ A}$$

and the D.C. input power:

$$P_{dc} = 20 \times 10.5 = 210 \text{ W.}$$

Considerations on efficiency of the RF power transistors in the different classes of operation

Technical Publication
COE82101

The saturation resistance is appr. 0.1Ω and if we consider the collector current as a half sine wave the saturation loss can be approximated by:

$$P_{\text{sat}} = \frac{I_{\text{cp}}^2 \times R_{\text{sat}}}{4} = \frac{30^2 \times 0.1}{4} = 22.5 \text{ W}$$

So the transistor output power becomes:

$$P_0 = P_{\text{dc}} - P_{\text{sat}} = 210 - 22.5 = 187.5 \text{ W}$$

As mentioned earlier the loss of the output matching network is 5%, so the output power of the amplifier will then be:

$$P_0' = 0.95 \times P_0 = 0.95 \times 187.5 = 178 \text{ W}$$

This gives us a collector efficiency of:

$$\eta_c = \frac{P_0'}{P_{\text{dc}}} = \frac{178}{210} \times 100\% = 85\%$$

A question that still has to be answered is: up to what frequency can this performance be maintained? The answer can be found by inspection of the formula for B in the previous section. We must keep in mind that C in this formula is the total capacitance from collector to ground, i.e. the sum of the transistors effective collector capacitance and a possible external capacitor. If we reduce the latter to zero and rearrange the formula we will find the maximum frequency of operation:

$$f_{\text{max}} = \frac{P_0}{2\pi^2 C_c V_s^2}$$

C_c is the effective collector capacitance which is 344 pF at a collector voltage of 20 V, so:

$$f_{\text{max}} = 66 \text{ MHz.}$$

Unfortunately this is not sufficient to cover the F.M. broadcast band up to 108 MHz. However at least some of the advantage of class-E operation can be obtained by using the RFC to tune out the surplus of collector capacitance. In this way a collector efficiency of 80% is probably possible.

7 FINAL CONSIDERATIONS


An interesting question is whether the BLV25 is a good or a bad transistor for class-E operation. Examination of many Philips and competition 28 V transistors shows that it is a good average. f_{max} depends on the ratio P_0/C_c which does not spread so much.

A much greater improvement is obtained by the application of 12 V transistors. The quantity f_{max} rises then to the double value. However for a supply voltage of 12 V there are no transistors available with the output power of the BLV25.


If we would try to make such a device it would be a very impractical one, e.g. the optimum load resistance would be less than 0.5Ω and the power gain 3 dB less than that of the BLV25, i.e. 7 to 8 dB.

8 REFERENCES

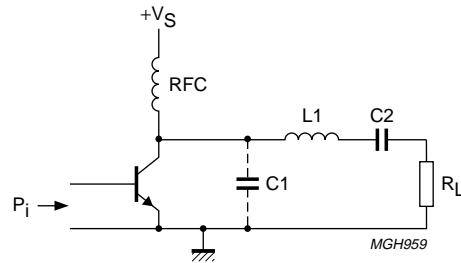1. W.J. Chudobiak and D.F. Page,
"Frequency and Power Limitations of Class-D Transistor Amplifiers",
I.E.E.E. Journal of Solid State Circuits, vol. SC-4, No. 1,
February 1969, pp. 25 to 37
2. N.O. Sokal and A.D. Sokal,
"Class E - A New Class of High-Efficiency Tuned Single-Ended Switching Power Amplifiers",
I.E.E.E. Journal of Solid State circuits, Vol. SC-10, No. 3,
June 1975, pp. 168 to 176.
3. N.O. Sokal,
"Class E can boost the efficiency",
Electronic Design, Sept. 27, 1977, pp. 96 to 102.
4. F.H. Raab,
"Idealized operation of the Class E Tuned Power Amplifier",
I.E.E.E. Trans. on Circuits and Systems, Vol. CAS-24, No. 12,
Dec. 1977, pp. 725 to 735.
5. F.H. Raab,
"Effects of Circuit Variations on the Class E Tuned Power Amplifier",
I.E.E.E. Journal of Solid-State circuits, Vol. SC-13, No. 2,
April 1978, pp. 239 to 247.



a.

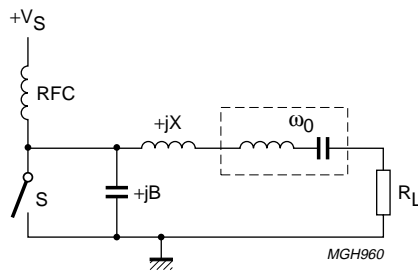

b.

Fig.1

Philips Semiconductors – a worldwide company

Argentina: see South America

Australia: 34 Waterloo Road, NORTH RYDE, NSW 2113,
Tel. +61 2 9805 4455, Fax. +61 2 9805 4466

Austria: Computerstr. 6, A-1101 WIEN, P.O. Box 213, Tel. +43 160 1010,
Fax. +43 160 101 1210

Belarus: Hotel Minsk Business Center, Bld. 3, r. 1211, Volodarski Str. 6,
220050 MINSK, Tel. +375 172 200 733, Fax. +375 172 200 773

Belgium: see The Netherlands

Brazil: see South America

Bulgaria: Philips Bulgaria Ltd., Energoproject, 15th floor,
51 James Bourchier Blvd., 1407 SOFIA,
Tel. +359 2 689 211, Fax. +359 2 689 102

Canada: PHILIPS SEMICONDUCTORS/COMPONENTS,
Tel. +1 800 234 7381

China/Hong Kong: 501 Hong Kong Industrial Technology Centre,
72 Tat Chee Avenue, Kowloon Tong, HONG KONG,
Tel. +852 2319 7888, Fax. +852 2319 7700

Colombia: see South America

Czech Republic: see Austria

Denmark: Prags Boulevard 80, PB 1919, DK-2300 COPENHAGEN S,
Tel. +45 32 88 2636, Fax. +45 31 57 0044

Finland: Sinikalliontie 3, FIN-02630 ESPOO,
Tel. +358 9 615800, Fax. +358 9 61580920

France: 51 Rue Carnot, BP317, 92156 SURESNES Cedex,
Tel. +33 1 40 99 6161, Fax. +33 1 40 99 6427

Germany: Hammerbrookstraße 69, D-20097 HAMBURG,
Tel. +49 40 23 53 60, Fax. +49 40 23 536 300

Greece: No. 15, 25th March Street, GR 17778 TAVROS/ATHENS,
Tel. +30 1 4894 339/239, Fax. +30 1 4814 240

Hungary: see Austria

India: Philips INDIA Ltd, Band Box Building, 2nd floor,
254-D, Dr. Annie Besant Road, Worli, MUMBAI 400 025,
Tel. +91 22 493 8541, Fax. +91 22 493 0966

Indonesia: see Singapore

Ireland: Newstead, Clonskeagh, DUBLIN 14,
Tel. +353 1 7640 000, Fax. +353 1 7640 200

Israel: RAPAC Electronics, 7 Kehilat Saloniki St, PO Box 18053,
TEL AVIV 61180, Tel. +972 3 645 0444, Fax. +972 3 649 1007

Italy: PHILIPS SEMICONDUCTORS, Piazza IV Novembre 3,
20124 MILANO, Tel. +39 2 6752 2531, Fax. +39 2 6752 2557

Japan: Philips Bldg 13-37, Kohnan 2-chome, Minato-ku, TOKYO 108,
Tel. +81 3 3740 5130, Fax. +81 3 3740 5077

Korea: Philips House, 260-199 Itaewon-dong, Yongsan-ku, SEOUL,
Tel. +82 2 709 1412, Fax. +82 2 709 1415

Malaysia: No. 76 Jalan Universiti, 46200 PETALING JAYA, SELANGOR,
Tel. +60 3 750 5214, Fax. +60 3 757 4880

Mexico: 5900 Gateway East, Suite 200, EL PASO, TEXAS 79905,
Tel. +9-5 800 234 7381

Middle East: see Italy

Netherlands: Postbus 90050, 5600 PB EINDHOVEN, Bldg. VB,
Tel. +31 40 27 82785, Fax. +31 40 27 88399

New Zealand: 2 Wagener Place, C.P.O. Box 1041, AUCKLAND,
Tel. +64 9 849 4160, Fax. +64 9 849 7811

Norway: Box 1, Manglerud 0612, OSLO,
Tel. +47 22 74 8000, Fax. +47 22 74 8341

Philippines: Philips Semiconductors Philippines Inc.,
106 Valero St. Salcedo Village, P.O. Box 2108 MCC, MAKATI,
Metro MANILA, Tel. +63 2 816 6380, Fax. +63 2 817 3474

Poland: Ul. Lukiska 10, PL 04-123 WARSZAWA,
Tel. +48 22 612 2831, Fax. +48 22 612 2327

Portugal: see Spain

Romania: see Italy

Russia: Philips Russia, Ul. Usatcheva 35A, 119048 MOSCOW,
Tel. +7 095 755 6918, Fax. +7 095 755 6919

Singapore: Lorong 1, Toa Payoh, SINGAPORE 1231,
Tel. +65 350 2538, Fax. +65 251 6500

Slovakia: see Austria

Slovenia: see Italy

South Africa: S.A. PHILIPS Pty Ltd., 195-215 Main Road Martindale,
2092 JOHANNESBURG, P.O. Box 7430 Johannesburg 2000,
Tel. +27 11 470 5911, Fax. +27 11 470 5494

South America: Al. Vicente Pinzon, 173, 6th floor,
04547-130 SÃO PAULO, SP, Brazil,
Tel. +55 11 821 2333, Fax. +55 11 821 2382

Spain: Balmes 22, 08007 BARCELONA,
Tel. +34 3 301 6312, Fax. +34 3 301 4107

Sweden: Kottbygatan 7, Akalla, S-16485 STOCKHOLM,
Tel. +46 8 632 2000, Fax. +46 8 632 2745

Switzerland: Allmendstrasse 140, CH-8027 ZÜRICH,
Tel. +41 1 488 2686, Fax. +41 1 488 3263

Taiwan: Philips Semiconductors, 6F, No. 96, Chien Kuo N. Rd., Sec. 1,
TAIPEI, Taiwan Tel. +886 2 2134 2865, Fax. +886 2 2134 2874

Thailand: PHILIPS ELECTRONICS (THAILAND) Ltd.,
209/2 Sanpavuth-Bangna Road Prakanong, BANGKOK 10260,
Tel. +66 2 745 4090, Fax. +66 2 398 0793

Turkey: Talatpasa Cad. No. 5, 80640 GÜLTEPE/ISTANBUL,
Tel. +90 212 279 2770, Fax. +90 212 282 6707

Ukraine: PHILIPS UKRAINE, 4 Patrice Lumumba str., Building B, Floor 7,
252042 KIEV, Tel. +380 44 264 2776, Fax. +380 44 268 0461

United Kingdom: Philips Semiconductors Ltd., 276 Bath Road, Hayes,
MIDDLESEX UB3 5BX, Tel. +44 181 730 5000, Fax. +44 181 754 8421

United States: 811 East Arques Avenue, SUNNYVALE, CA 94088-3409,
Tel. +1 800 234 7381

Uruguay: see South America

Vietnam: see Singapore

Yugoslavia: PHILIPS, Trg N. Pasica 5/v, 11000 BEOGRAD,
Tel. +381 11 625 344, Fax. +381 11 635 777

For all other countries apply to: Philips Semiconductors,
International Marketing & Sales Communications, Building BE-p, P.O. Box 218,
5600 MD EINDHOVEN, The Netherlands, Fax. +31 40 27 24825

Internet: <http://www.semiconductors.philips.com>

© Philips Electronics N.V. 1998

SCA57

All rights are reserved. Reproduction in whole or in part is prohibited without the prior written consent of the copyright owner.

The information presented in this document does not form part of any quotation or contract, is believed to be accurate and reliable and may be changed without notice. No liability will be accepted by the publisher for any consequence of its use. Publication thereof does not convey nor imply any license under patent- or other industrial or intellectual property rights.

Printed in The Netherlands

Date of release: 1998 Mar 23

Let's make things better.

**Philips
Semiconductors**



PHILIPS

SUNSTAR 商斯达实业集团是集研发、生产、工程、销售、代理经销、技术咨询、信息服务等为一体的高科技企业，是专业高科技电子产品生产厂家，是具有 10 多年历史的专业电子元器件供应商，是中国最早和最大的仓储式连锁规模经营大型综合电子零部件代理分销商之一，是一家专业代理和分销世界各大品牌 IC 芯片和电子元器件的连锁经营综合性国际公司，专业经营进口、国产名厂名牌电子元件，型号、种类齐全。在香港、北京、深圳、上海、西安、成都等全国主要电子市场设有直属分公司和产品展示展销窗口门市部专卖店及代理分销商，已在全国范围内建成强大统一的供货和代理分销网络。我们专业代理经销、开发生产电子元器件、集成电路、传感器、微波光电元器件、工控机/DOC/DOM 电子盘、专用电路、单片机开发、MCU/DSP/ARM/FPGA 软件硬件、二极管、三极管、模块等，是您可靠的一站式现货配套供应商、方案提供商、部件功能模块开发配套商。商斯达实业公司拥有庞大的资料库，有数位毕业于著名高校——有中国电子工业摇篮之称的西安电子科技大学（西军电）并长期从事国防尖端科技研究的高级工程师为您精挑细选、量身订做各种高科技电子元器件，并解决各种技术问题。

微波光电部专业代理经销高频、微波、光纤、光电元器件、组件、部件、模块、整机；电磁兼容元器件、材料、设备；微波 CAD、EDA 软件、开发测试仿真工具；微波、光纤仪器仪表。欢迎国外高科技微波、光纤厂商将优秀产品介绍到中国、共同开拓市场。长期大量现货专业批发高频、微波、卫星、光纤、电视、CATV 器件：晶振、VCO、连接器、PIN 开关、变容二极管、开关二极管、低噪晶体管、功率电阻及电容、放大器、功率管、MMIC、混频器、耦合器、功分器、振荡器、合成器、衰减器、滤波器、隔离器、环行器、移相器、调制解调器；光电子器件和组件：红外发射管、红外接收管、光电开关、光敏管、发光二极管和发光二极管组件、半导体激光二极管和激光器组件、光电探测器和光接收组件、光发射接收模块、光纤激光器和光放大器、光调制器、光开关、DWDM 用光发射和接收器件、用户接入系统光收发器件与模块、光纤连接器、光纤跳线/尾纤、光衰减器、光纤适配器、光隔离器、光耦合器、光环行器、光复用器/转换器；无线收发芯片和模组、蓝牙芯片和模组。

更多产品请看本公司产品专用销售网站：

商斯达中国传感器科技信息网：<http://www.sensor-ic.com/>

商斯达工控安防网：<http://www.pc-ps.net/>

商斯达电子元器件网：<http://www.sunstare.com/>

商斯达微波光电产品网：[HTTP://www.rfoe.net/](http://www.rfoe.net/)

商斯达消费电子产品网：<http://www.icasic.com/>

商斯达实业科技产品网：<http://www.sunstars.cn/> 微波元器件销售热线：

地址：深圳市福田区福华路福庆街鸿图大厦 1602 室

电话：0755-82884100 83397033 83396822 83398585

传真：0755-83376182 (0) 13823648918 MSN: SUNS8888@hotmail.com

邮编：518033 E-mail:szss20@163.com QQ: 195847376

深圳赛格展销部：深圳华强北路赛格电子市场 2583 号 电话：0755-83665529 25059422

技术支持：0755-83394033 13501568376

欢迎索取免费详细资料、设计指南和光盘；产品凡多，未能尽录，欢迎来电查询。

北京分公司：北京海淀区知春路 132 号中发电子大厦 3097 号

TEL: 010-81159046 82615020 13501189838 FAX: 010-62543996

上海分公司：上海市北京东路 668 号上海赛格电子市场 D125 号

TEL: 021-28311762 56703037 13701955389 FAX: 021-56703037

西安分公司：西安高新开发区 20 所(中国电子科技集团导航技术研究所)

西安劳动南路 88 号电子商城二楼 D23 号

TEL: 029-81022619 13072977981 FAX:029-88789382