

APPLICATION NOTE

**Design of H.F. Wideband Power
Transformers; Part II**

ECO7213

CONTENTS

1	SUMMARY
2	INTRODUCTION
3	L.F. LIMITATIONS OF CONVENTIONAL TRANSFORMERS
4	H.F. LIMITATION OF CONVENTIONAL TRANSFORMERS
5	H.F. COMPENSATION OF CONVENTIONAL TRANSFORMERS
6	A PRACTICAL EXAMPLE
7	REFERENCES

1 SUMMARY

In part I of this report (ECO6907) the transmission line transformer has been discussed extensively. In this second part attention has been paid to the conventional transformer as a wideband matching element in e.g. S.S.B. transmitters. The main problem in these transformers is stray-inductance. Some H.F. compensation methods are discussed and a design example is given.

2 INTRODUCTION

Report ECO6907 (Ref. 1) has been devoted entirely to the design of transmission line transformers. This type of transformer has undoubtedly the advantage of the largest possible bandwidth. However it has also some drawbacks:

1. The impedance transformation ratio is restricted to $(n : m)^2$ in which n and m are small integers
2. They are difficult to construct when a number of windings must be combined.

Therefore it is certainly worthwhile to consider the possibility of applying a conventional transformer if the abovementioned problems arise.

3 L.F. LIMITATIONS OF CONVENTIONAL TRANSFORMERS

These limitations are the same as for transmission line transformers, viz. parallel inductance and maximum flux density. They have been described in the abovementioned reports including compensation methods for the parallel inductance.

4 H.F. LIMITATION OF CONVENTIONAL TRANSFORMERS

The most important property that limits the H.F. performance of a conventional transformer is the well-known stray-inductance. The equivalent circuit of the transformer for this frequency region is shown in Fig.1.

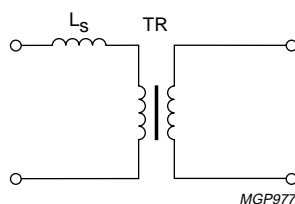


Fig.1

L_s is the stray-inductance and TR an ideal transformer. An easy way of measuring L_s is to measure the reactance between the primary terminals when the secondary is short-circuited. This can be done e.g. with the H.P. Vector Impedance meter. The most accurate result is obtained when the measurement is made at the highest frequency of operation and on the high-ohmic winding.

It is obvious that L_s must be kept as small as possible to avoid degradation of the H.F. performance of the transformer. For this end the following measures are recommended:

1. The windings must be as close to the core and to each other as possible
2. Each winding must be divided equally around the whole periphery of the core
3. Each winding must cover the core as much as possible.

Some practical steps that can be taken are:

1. The use of copper foil for the low-ohmic winding; this can be in direct contact with the core as the resistivity of the ferrite is very high. For better covering of the core two windings can be connected in parallel in such a way that one winding is wound in between the other one; the isolation material required in this case must be very thin.
2. For the high-ohmic winding enamelled copper wire can be used. An appreciable reduction of L_s can be obtained by parallel connection of two or more wires.

5 H.F. COMPENSATION OF CONVENTIONAL TRANSFORMERS

In Ref. 2 some forms of compensation have been described. They are compared in Table 1.

Table 1

NUMBER OF COMPENSATION ELEMENTS	0	1	2
Maximum X/R	0.18	0.44	1.09

Table 1 is based on a maximum input V.S.W.R. of 1.2. The quantity X/R is the reactance of the stray-inductance (referred to the primary) divided by the nominal input resistance of the transformer. Compensation with one element is possible either by connecting a capacitor in parallel with the primary winding, or by connecting a capacitor in parallel with the secondary winding.

Compensation with two elements is carried out by connecting capacitors in parallel with both primary and secondary windings. This method has already been applied several times. A short description will be given with reference to Fig.2.

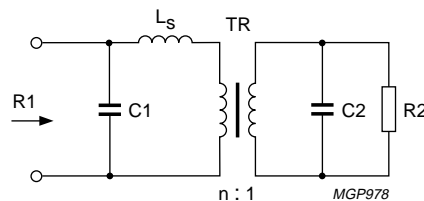


Fig.2

TR is an ideal transformer with a voltage transformation ratio of $n : 1$ ($n > 1$) and L_s is the stray-inductance (referred to the primary). R_1 is the nominal input resistance:

$$R_1 = n^2 \times R_2$$

First we determine the normalized stray-inductance:

$$L_{sn} = \frac{\omega_{max} \times L_s}{R_1}, \text{ in which } \omega_{max} \text{ must be equal to or higher than } 2\pi \text{ times the maximum frequency to be handled.}$$

With the aid of Fig.5 we find the maximum input V.S.W.R (S) and the normalized correction capacitance (C_{1n}). Then C1 and C2 can be calculated:

$$C_1 = \frac{C_{1n}}{\omega_{max} \times R_1} \text{ and } C2 = n^2 \times C_1$$

A practical problem that can arise is that the capacitor across the low-ohmic winding must have such a high value that it approaches series resonance with its own lead inductance. In that case a sufficiently large number of smaller capacitors must be connected in parallel.

The practical limit to which the above described compensation system can be used is appr.:

$$L_{sn} = 1$$

If the stray-inductance is larger a more complicated compensation system is required. The above described system is based on a 3-element Chebyshev low-pass filter, but this can be extended to a 5-element network, which means that for the compensation 4 elements are required. This situation is depicted Fig.3.

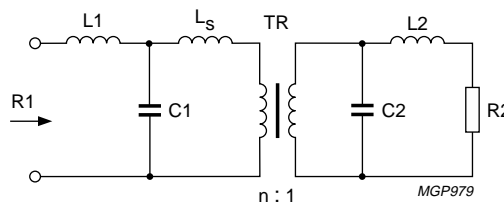


Fig.3

Two inductors (L1 and L2) have been added. The normalized elements versus the maximum input V.S.W.R. (S) have been given in Fig.6 (this graph and that of Fig.5 have been made with the aid of a computer program which is based on the design formulae for Chebyshev low-pass filters as can be found e.g. in Ref. 3.). From this graph it can be seen that L_{sn} may be as high as 1.77 for $S_{max} = 1.2$. A good practical limit is: $L_{sn} = 1.6$

The procedure for calculating the compensation elements is very similar to the previous case. We start again with

determination of the normalized stray-inductance:
$$L_{sn} = \frac{\omega_{max} \times L_s}{R_1}$$

With the aid of Fig.6 we find the maximum value of S and the normalized values of the correction elements C_{1n} and L_{1n} .

Now C_1 and L_1 can be calculated:
$$C_1 = \frac{C_{1n}}{\omega_{max} \times R_1} \text{ and } L_1 = \frac{L_{1n} \times R_1}{\omega_{max}}$$

At the secondary side the correction components become:

$$C_2 = n^2 \times C_1 \text{ and } L_2 = \frac{L_1}{n^2}$$

In general L_2 is so small that the tracks on the p.c. board can perform this function.

6 A PRACTICAL EXAMPLE

For a low voltage S.S.B. amplifier a transformer was required with the following specification:

Frequency range: 1.6 – 28 MHz

Power handling: 52 W

Load impedance: 100 Ω

Input impedance: 4.6 Ω

The most suitable Ferroxcube material for this frequency range is 4C6. From the power handling point of view a toroid core will be chosen with the dimensions: $23 \times 14 \times 7 \text{ mm}^3$, catalog nr. 4322 020 91070. The parallel reactance at 1.6 MHz measured at the secondary side must be +j400 Ω (see Ref. 1), corresponding with an inductance of 40 μH . The required number of turns is then:

$$n_{\text{sec}} = \sqrt{\frac{L \times l}{\mu_0 \times \mu_r \times A}}$$

in which $\frac{A}{l} = 0.5525 \text{ mm}$ for this core and $\mu_r = 120$ for 4C6 material, so:

$$n_{\text{sec}} = 21.9$$

A logical choice would be $n_{\text{sec}} = 22$. The voltage transformation ratio is $\sqrt{\frac{100}{4.6}} = 4.66$, by which the primary number of

turns must be: $\frac{22}{4.66} = 4.7$

We choose: $n_{\text{pr}} = 5$.

The required transformation ratio can be approached better if the secondary number of turns is modified from 22 to 23.

Now the secondary parallel inductance becomes 44 μH and the impedance transformation ratio $\left(\frac{23}{5}\right)^2 = 21.1$ by which the input impedance will be 4.74 Ω being appr. 3% higher than the required value.

L.F. compensation of the parallel inductance can be carried out by means of a single capacitor in series with the secondary (see Ref. 1):

$$C_L = \frac{L_{\text{psec}}}{R_{\text{sec}}^2} = \frac{44 \times 10^{-6}}{100^2} = 4400 \text{ pF}$$

A standard value of 4700 pF has been chosen.

The maximum voltage across the secondary winding is: $V_{\text{sec}} = \sqrt{2R_{\text{sec}} \times P} = \sqrt{2 \times 100 \times 52} = 102 \text{ V}$

Now the maximum flux density can be calculated:

$$B_{\max} = \frac{V_{\text{sec}}}{\omega_{\min} \times A \times n_{\text{sec}}}$$

in which $A = 31.5 \text{ mm}^2$ for this core, so: $B_{\max} = \frac{102}{2\pi \times 1.6 \times 10^6 \times 31.5 \times 10^{-6} \times 23} = 140 \text{ gauss at } 1.6 \text{ MHz}$

This gives a core loss of appr. 1% or 0.5 W.

To keep the stray-inductance low the transformer has been wound as follows:

- The primary consists of the parallel connection of two windings each having 5 turns of 4 mm wide copper foil. Each winding has been equally divided around the periphery of the core; one winding was wound in between the other one. Between these two windings a thin layer of isolation material was used.
- The secondary consists of the parallel connection of two windings each having 23 turns of 0.45 mm enamelled copper wire. The method of winding was the same as for the primary.

The stray-inductance measured at the secondary side was $0.67 \mu\text{H}$. To make the correction less critical we choose a maximum frequency of 35 MHz instead of the specified 28 MHz. The normalized stray-inductance becomes then:

$$L_{\text{sn}} = \frac{2\pi \times 35 \times 10^6 \times 0.67 \times 10^{-6}}{100} = 1.47$$

From Fig.6 we find:

$$S_{\max} = 1.064$$

$$C_{1n} = 1.24$$

$$L_{1n} = 0.66$$

In this case the index 1 applies to the secondary and index 2 to the primary. The compensation elements become:

$$C_1 = \frac{1.24}{2\pi \times 35 \times 10^6 \times 100} = 56.4 \text{ pF}$$

$$L_1 = \frac{0.66 \times 100}{2\pi \times 35 \times 10^6} = 0.3 \mu\text{H}$$

$$C_2 = 21.1 \times 56.4 = 1190 \text{ pF}$$

$$L_2 = 0.3/21.1 = 0.0142 \mu\text{H}$$

For C_1 a standard value of 56 pF was chosen. C_2 consisted of the parallel connection of 330 pF and $3 \times 270 \text{ pF}$ being 1140 pF in total; the slightly lower value was chosen because of the series inductance of the capacitors. L_2 was formed by the tracks on the p.c. board.

The first measurements on the compensated transformer showed a too high V.S.W.R. at 28 MHz together with a capacitive behaviour of the impedance from which we got the impression that it was over-compensated. This appeared to be due to the capacitance between the primary and the secondary winding. Therefore we reduced the values of the compensation elements by 10 to 20%. The new values are:

$$C_1 = 47 \text{ pF}$$

$$L_1 = 0.27 \mu\text{H}$$

$$C_2 = 980 \text{ pF (parallel connection of } 2 \times 270 \text{ pF and } 2 \times 220 \text{ pF)}$$

$$L_2 \approx 2 \times 6 \text{ nH (tracks on p.c. board)}$$

The complete situation is depicted in Fig.4. The load impedance Z_L consisted of the parallel connection of 2 resistors of 15 Ω , 1 resistor of 12 Ω and a capacitor of 120 pF. The latter was added to compensate the series inductance of the resistors.

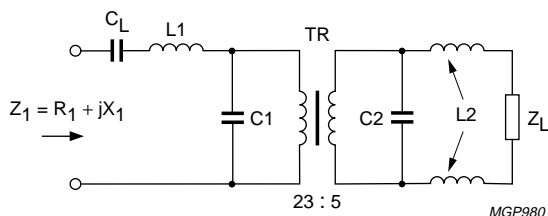


Fig.4

The results of the measurements have been summarized in Table 2.

Table 2

f (MHz)	R1 (Ω)	X1 (Ω)	V.S.W.R. (-)
1.6	98	-1.87	1.03
3.5	100.5	-2.1	1.02
7.0	98.3	-5.84	1.06
14	89.9	-4.41	1.12
20	87.4	+1.24	1.14
28	100	+7.18	1.07

It can be seen from Table 2 that the maximum input V.S.W.R has been reduced to 1.14. Without H.F. compensation this V.S.W.R. would have been appr. 3 at 28 MHz.

7 REFERENCES

1. A.H. Hilbers; "On the Design of H.F. Wideband Power Transformers", C.A.B. report nr. ECO6907, March 14, 1969.
2. H. Nielinger; "Optimale Dimensionierung von Breitbandanpassungsnetzwerken", N.T.Z. 1968, Heft 2, pp. 88 to 91.
3. S.B. Cohn; "Direct-Coupled-Resonator Filters", Proc. IRE, February 1957, pp 187 to 196.

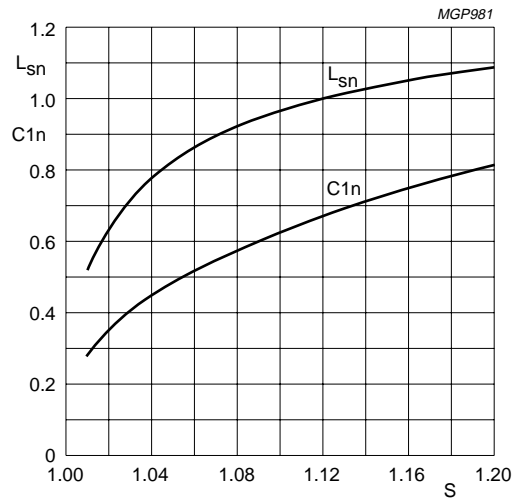


Fig.5

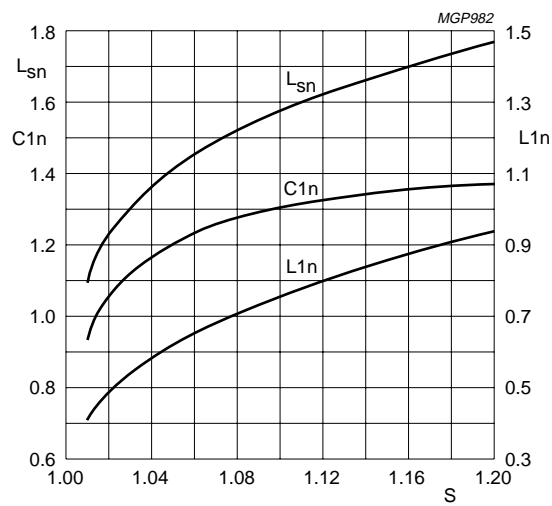


Fig.6

Philips Semiconductors – a worldwide company

Argentina: see South America

Australia: 34 Waterloo Road, NORTH RYDE, NSW 2113,
Tel. +61 2 9805 4455, Fax. +61 2 9805 4466

Austria: Computerstr. 6, A-1101 WIEN, P.O. Box 213, Tel. +43 160 1010,
Fax. +43 160 101 1210

Belarus: Hotel Minsk Business Center, Bld. 3, r. 1211, Volodarski Str. 6,
220050 MINSK, Tel. +375 172 200 733, Fax. +375 172 200 773

Belgium: see The Netherlands

Brazil: see South America

Bulgaria: Philips Bulgaria Ltd., Energoproject, 15th floor,
51 James Bourchier Blvd., 1407 SOFIA,
Tel. +359 2 689 211, Fax. +359 2 689 102

Canada: PHILIPS SEMICONDUCTORS/COMPONENTS,
Tel. +1 800 234 7381

China/Hong Kong: 501 Hong Kong Industrial Technology Centre,
72 Tat Chee Avenue, Kowloon Tong, HONG KONG,
Tel. +852 2319 7888, Fax. +852 2319 7700

Colombia: see South America

Czech Republic: see Austria

Denmark: Prags Boulevard 80, PB 1919, DK-2300 COPENHAGEN S,
Tel. +45 32 88 2636, Fax. +45 31 57 0044

Finland: Sinikalliontie 3, FIN-02630 ESPOO,
Tel. +358 9 615800, Fax. +358 9 61580920

France: 51 Rue Carnot, BP317, 92156 SURESNES Cedex,
Tel. +33 1 40 99 6161, Fax. +33 1 40 99 6427

Germany: Hammerbrookstraße 69, D-20097 HAMBURG,
Tel. +49 40 23 53 60, Fax. +49 40 23 536 300

Greece: No. 15, 25th March Street, GR 17778 TAVROS/ATHENS,
Tel. +30 1 4894 339/239, Fax. +30 1 4814 240

Hungary: see Austria

India: Philips INDIA Ltd, Band Box Building, 2nd floor,
254-D, Dr. Annie Besant Road, Worli, MUMBAI 400 025,
Tel. +91 22 493 8541, Fax. +91 22 493 0966

Indonesia: see Singapore

Ireland: Newstead, Clonskeagh, DUBLIN 14,
Tel. +353 1 7640 000, Fax. +353 1 7640 200

Israel: RAPAC Electronics, 7 Kehilat Saloniki St, PO Box 18053,
TEL AVIV 61180, Tel. +972 3 645 0444, Fax. +972 3 649 1007

Italy: PHILIPS SEMICONDUCTORS, Piazza IV Novembre 3,
20124 MILANO, Tel. +39 2 6752 2531, Fax. +39 2 6752 2557

Japan: Philips Bldg 13-37, Kohnan 2-chome, Minato-ku, TOKYO 108,
Tel. +81 3 3740 5130, Fax. +81 3 3740 5077

Korea: Philips House, 260-199 Itaewon-dong, Yongsan-ku, SEOUL,
Tel. +82 2 709 1412, Fax. +82 2 709 1415

Malaysia: No. 76 Jalan Universiti, 46200 PETALING JAYA, SELANGOR,
Tel. +60 3 750 5214, Fax. +60 3 757 4880

Mexico: 5900 Gateway East, Suite 200, EL PASO, TEXAS 79905,
Tel. +9-5 800 234 7381

Middle East: see Italy

Netherlands: Postbus 90050, 5600 PB EINDHOVEN, Bldg. VB,
Tel. +31 40 27 82785, Fax. +31 40 27 88399

New Zealand: 2 Wagener Place, C.P.O. Box 1041, AUCKLAND,
Tel. +64 9 849 4160, Fax. +64 9 849 7811

Norway: Box 1, Manglerud 0612, OSLO,
Tel. +47 22 74 8000, Fax. +47 22 74 8341

Philippines: Philips Semiconductors Philippines Inc.,
106 Valero St. Salcedo Village, P.O. Box 2108 MCC, MAKATI,
Metro MANILA, Tel. +63 2 816 6380, Fax. +63 2 817 3474

Poland: Ul. Lukiska 10, PL 04-123 WARSZAWA,
Tel. +48 22 612 2831, Fax. +48 22 612 2327

Portugal: see Spain

Romania: see Italy

Russia: Philips Russia, Ul. Usatcheva 35A, 119048 MOSCOW,
Tel. +7 095 755 6918, Fax. +7 095 755 6919

Singapore: Lorong 1, Toa Payoh, SINGAPORE 1231,
Tel. +65 350 2538, Fax. +65 251 6500

Slovakia: see Austria

Slovenia: see Italy

South Africa: S.A. PHILIPS Pty Ltd., 195-215 Main Road Martindale,
2092 JOHANNESBURG, P.O. Box 7430 Johannesburg 2000,
Tel. +27 11 470 5911, Fax. +27 11 470 5494

South America: Al. Vicente Pinzon, 173, 6th floor,
04547-130 SÃO PAULO, SP, Brazil,
Tel. +55 11 821 2333, Fax. +55 11 821 2382

Spain: Balmes 22, 08007 BARCELONA,
Tel. +34 3 301 6312, Fax. +34 3 301 4107

Sweden: Kottbygatan 7, Akalla, S-16485 STOCKHOLM,
Tel. +46 8 632 2000, Fax. +46 8 632 2745

Switzerland: Allmendstrasse 140, CH-8027 ZÜRICH,
Tel. +41 1 488 2686, Fax. +41 1 488 3263

Taiwan: Philips Semiconductors, 6F, No. 96, Chien Kuo N. Rd., Sec. 1,
TAIPEI, Taiwan Tel. +886 2 2134 2865, Fax. +886 2 2134 2874

Thailand: PHILIPS ELECTRONICS (THAILAND) Ltd.,
209/2 Sanpavuth-Bangna Road Prakanong, BANGKOK 10260,
Tel. +66 2 745 4090, Fax. +66 2 398 0793

Turkey: Talatpasa Cad. No. 5, 80640 GÜLTEPE/ISTANBUL,
Tel. +90 212 279 2770, Fax. +90 212 282 6707

Ukraine: PHILIPS UKRAINE, 4 Patrice Lumumba str., Building B, Floor 7,
252042 KIEV, Tel. +380 44 264 2776, Fax. +380 44 268 0461

United Kingdom: Philips Semiconductors Ltd., 276 Bath Road, Hayes,
MIDDLESEX UB3 5BX, Tel. +44 181 730 5000, Fax. +44 181 754 8421

United States: 811 East Arques Avenue, SUNNYVALE, CA 94088-3409,
Tel. +1 800 234 7381

Uruguay: see South America

Vietnam: see Singapore

Yugoslavia: PHILIPS, Trg N. Pasica 5/v, 11000 BEOGRAD,
Tel. +381 11 625 344, Fax. +381 11 635 777

For all other countries apply to: Philips Semiconductors,
International Marketing & Sales Communications, Building BE-p, P.O. Box 218,
5600 MD EINDHOVEN, The Netherlands, Fax. +31 40 27 24825

Internet: <http://www.semiconductors.philips.com>

© Philips Electronics N.V. 1998

SCA57

All rights are reserved. Reproduction in whole or in part is prohibited without the prior written consent of the copyright owner.

The information presented in this document does not form part of any quotation or contract, is believed to be accurate and reliable and may be changed without notice. No liability will be accepted by the publisher for any consequence of its use. Publication thereof does not convey nor imply any license under patent- or other industrial or intellectual property rights.

Printed in The Netherlands

Date of release: 1998 Mar 23

Let's make things better.

Philips
Semiconductors



PHILIPS

SUNSTAR 商斯达实业集团是集研发、生产、工程、销售、代理经销、技术咨询、信息服务等为一体的高科技企业，是专业高科技电子产品生产厂家，是具有 10 多年历史的专业电子元器件供应商，是中国最早和最大的仓储式连锁规模经营大型综合电子零部件代理分销商之一，是一家专业代理和分销世界各大品牌 IC 芯片和电子元器件的连锁经营综合性国际公司，专业经营进口、国产名厂名牌电子元件，型号、种类齐全。在香港、北京、深圳、上海、西安、成都等全国主要电子市场设有直属分公司和产品展示展销窗口门市部专卖店及代理分销商，已在全国范围内建成强大统一的供货和代理分销网络。我们专业代理经销、开发生产电子元器件、集成电路、传感器、微波光电元器件、工控机/DOC/DOM 电子盘、专用电路、单片机开发、MCU/DSP/ARM/FPGA 软件硬件、二极管、三极管、模块等，是您可靠的一站式现货配套供应商、方案提供商、部件功能模块开发配套商。商斯达实业公司拥有庞大的资料库，有数位毕业于著名高校——有中国电子工业摇篮之称的西安电子科技大学（西军电）并长期从事国防尖端科技研究的高级工程师为您精挑细选、量身订做各种高科技电子元器件，并解决各种技术问题。

微波光电部专业代理经销高频、微波、光纤、光电元器件、组件、部件、模块、整机；电磁兼容元器件、材料、设备；微波 CAD、EDA 软件、开发测试仿真工具；微波、光纤仪器仪表。欢迎国外高科技微波、光纤厂商将优秀产品介绍到中国、共同开拓市场。长期大量现货专业批发高频、微波、卫星、光纤、电视、CATV 器件：晶振、VCO、连接器、PIN 开关、变容二极管、开关二极管、低噪晶体管、功率电阻及电容、放大器、功率管、MMIC、混频器、耦合器、功分器、振荡器、合成器、衰减器、滤波器、隔离器、环行器、移相器、调制解调器；光电子元件和组件：红外发射管、红外接收管、光电开关、光敏管、发光二极管和发光二极管组件、半导体激光二极管和激光器组件、光电探测器和光接收组件、光发射接收模块、光纤激光器和光放大器、光调制器、光开关、DWDM 用光发射和接收器件、用户接入系统光收发器件与模块、光纤连接器、光纤跳线/尾纤、光衰减器、光纤适配器、光隔离器、光耦合器、光环行器、光复用器/转换器；无线收发芯片和模组、蓝牙芯片和模组。

更多产品请看本公司产品专用销售网站：

商斯达中国传感器科技信息网：<http://www.sensor-ic.com/>

商斯达工控安防网：<http://www.pc-ps.net/>

商斯达电子元器件网：<http://www.sunstare.com/>

商斯达微波光电产品网：[HTTP://www.rfoe.net/](http://www.rfoe.net/)

商斯达消费电子产品网：<http://www.icasic.com/>

商斯达实业科技产品网：<http://www.sunstars.cn/> 微波元器件销售热线：

地址：深圳市福田区福华路福庆街鸿图大厦 1602 室

电话：0755-82884100 83397033 83396822 83398585

传真：0755-83376182 (0) 13823648918 MSN: SUNS8888@hotmail.com

邮编：518033 E-mail:szss20@163.com QQ: 195847376

深圳赛格展销部：深圳华强北路赛格电子市场 2583 号 电话：0755-83665529 25059422

技术支持：0755-83394033 13501568376

欢迎索取免费详细资料、设计指南和光盘；产品凡多，未能尽录，欢迎来电查询。

北京分公司：北京海淀区知春路 132 号中发电子大厦 3097 号

TEL: 010-81159046 82615020 13501189838 FAX: 010-62543996

上海分公司：上海市北京东路 668 号上海赛格电子市场 D125 号

TEL: 021-28311762 56703037 13701955389 FAX: 021-56703037

西安分公司：西安高新开发区 20 所(中国电子科技集团导航技术研究所)

西安劳动南路 88 号电子商城二楼 D23 号

TEL: 029-81022619 13072977981 FAX:029-88789382