



**PHILIPS**

Philips Semiconductors

---

## **Application Note**

# ***Ultra Low Noise Amplifiers for 900 and 2000 MHz with High IP3***

**by Korné Vennema  
Philips Semiconductors  
Slatersville, RI**

**December 1996  
#KV96-157**

This application note describes four Low Noise Amplifier designs with the BFG410W and the BFG425W, two devices from Philips Semiconductors' fifth generation wideband technology. The amplifier designs include measurement results and pcb layouts. The following designs are included:


- a) 900 Mhz LNA with BFG410W
- b) 2 GHz LNA with BFG410W
- c) 900 Mhz LNA with BFG425W
- d) 2 Ghz LNA with BFG425W

## Introduction

Today's wireless applications require Low Noise Amplifiers with a high third order intercept point (IP3) and a low noise figure (NF) at the same time. This is particularly interesting for 1900 MHz CDMA receiver front ends. This report describes four ultra low noise amplifiers for 900 MHz and 1900 MHz wireless applications, using Philips Semiconductors' fifth generation wideband technology. Philips' fifth generation die technology uses a double polysilicon process with a buried layer which results in transition frequencies ( $f_T$ ) higher than 20 GHz, gains in excess of 20 dB and Noise Figures as low as 1.2 dB. The amplifiers are designed for use at 2 Volt collector emitter voltage. A separate paragraph describes ways to improve IP3 in a LNA.


## The fifth generation

Philips' fifth generation double poly silicon wideband technology (see figure 1) uses a steep emitter doped profile resulting in transition frequencies over 20 GHz, and with poly base contacts a low base resistance is obtained. Via the buried layer, the collector contact is brought out at the top of the die.

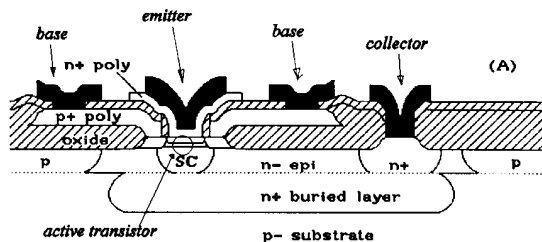

**Figure 1: Double polysilicon buried transistor**

The substrate is connected directly to the emitter package lead, resulting in improved thermal performance (see figure 2).

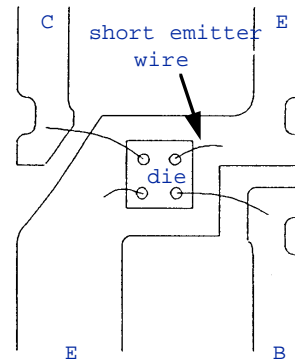

**Figure 2: Short emitter bonding wires reduce emitter inductance, which results in high gain. Heat flows through two emitter leads which lowers thermal resistance. Overall: Improved RF and thermal performance**


## The types of the fifth generation

The table below shows the three new types that use the fifth generation die technology.

Type	$I_E^{\wedge}$ (mA)	$f_T$ (GHz)	MSG (dB)	NF (dB)
			$f=2\text{GHz}$	$f=2\text{GHz}$
BFG403W	3	17	22	1.5
BFG410W	10	22	23	1.3
BFG425W	25	24	21	1.3


## IP3, using bypassing to improve it

Third order intercept point is usually determined by using a two tone test, i.e. two equal carriers with a small offset in frequency. Due to transistor non-linearities, these two carriers generate distortion products, both in-band and out of band (see figure 3). The product  $f_2-f_1$  is a low frequency product that is generated, which can modulate

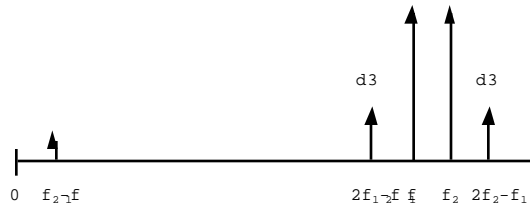

**Figure 3: Two tone test and generated intermodulation distortion products.  $f_2-f_1$  is the low frequency product**


the base-emitter and collector-emitter voltages of a transistor used in an amplifier. This results in a fluctuating bias (base) voltage and supply (collector) voltage. For good linearity, a constant base and collector voltage are required. Lowering the collector voltage causes an amplifier to saturate earlier, thus decreasing linearity for a certain power level. The base voltage sets the quiescent current for the device, and thus the linearity (see also figure 4) . A fluctuating base voltage would change the linearity of the amplifier. Therefore it is important to apply proper bypassing at both collector and base.

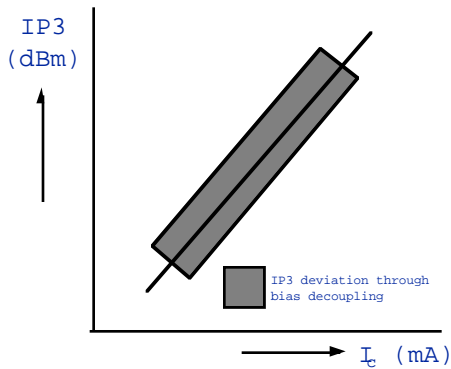

**Figure 4: IP3 in a Low Noise Amplifier is related to the collector current and also collector emitter voltage. As a rule of thumb for bipolar technology:  $IP_{3out} = 10 \log (V_{ce} * I_c * 5E3)$  in dBm**

Figure 5 shows the typical circuit diagram for a bipolar LNA. C is the bypassing capacitor for the working

frequency, i.e. either 900 or 1900 MHz. Adding additional bypassing by means

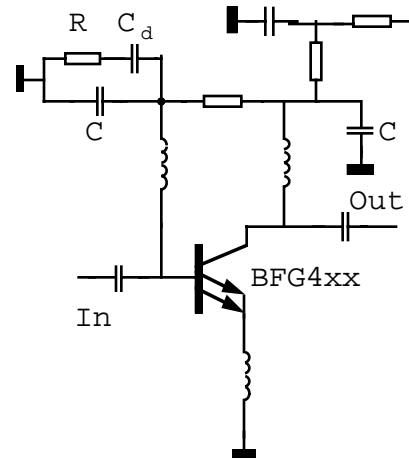

**Figure 5: Typical circuit diagram for a LNA.  $C_d$  is the additional bypassing for low frequencies. R is added to prevent low frequency instabilities. C is a short for the working frequency (27 pF at 900 MHz and 5.6 pF at 1900 MHz)**

of  $C_d$  improves the IP3 considerably. An improvement of 6 - 10 dB in IP3 can be expected. As a rule of thumb, the impedance of  $C_d$  should be smaller than 25 percent of the input impedance of the transistor at a particular carrier spacing. In case of a BFG520 (fourth generation wideband transistor) the following calculation is valid:

$$Z_{in} (25kHz) \approx h_{fe} / g_m = 120 / (40 * 0.0065) \approx 450 \Omega$$

$$C_d < 0.25 * 450 \approx 100 \Omega$$

At 25 kHz, the capacitor value equals:

$$C_d = 1 / (2 * \pi * f * 100) \approx 63 \text{ nF}$$


63 nF is the minimum recommended value. It is obvious that a higher capacitor value does a better job. Space constraints often don't allow the use of electrolytic (or even better tantalum) capacitors. In most cases, a 100 nF or 220 nF capacitor is sufficient. So far only base bypassing has been discussed. Similar effects can be

expected when collector bypassing is also applied; however, the effects are less dramatic.

**a) 900 MHz LNA with BFG410W**

This section describes a 900 MHz LNA with the BFG410W. The performance can be summarized as follows:

- $V_{ce}=2V, I_c=2mA, V_{SUP}\approx 3.3V$
- freq. = 900MHz
- $|S_{21}|^2 = 14 \text{ dB}$
- $|S_{12}|^2 = -26 \text{ dB}$
- NF = 1.4 dB
- $VSWR_i = 1 : 1.9$
- $VSWR_o = 1 : 2.3$
- $IP3_{in} = -9 \text{ dBm} (\Delta f=100 \text{ kHz})$

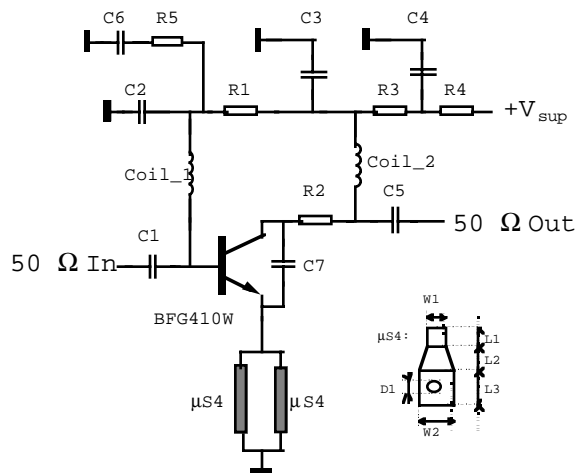

**Figure 6: Schematic diagram 900 MHz LNA with BFG410W.**

Input and output matching is realized with a LC combination. Additional emitter inductance on both emitter leads is used to improve the matching. All resistors and capacitors are 0603 or 0805 Philips SMD components. Coils are Coilcraft 0805. Board material is FR4.


Comp.:	Value:	Comment:
R1*	47 kΩ	Bias.

R2*	120 Ω	Better RF-stability ( $K>1$ ).
R3*	22 Ω	RF-block.
R4*	560 Ω	Cancelling $H_{FE}$ -spread.
R5**	100 Ω	To improve $IP3$ -performance
C1*	2.2 pF	Input match.
C2*	27 pF	900MHz short.
C3*	27 pF	900MHz short.
C4*	1 nF	RF-short
C5*	1.5 pF	Output match.
C6**	100 nF	To improve $IP3$ -performance
C7*	0.47 pF	Better RF-stability ( $K>1$ ).
Coil_1	12 nH	Input match.
Coil_2	15 nH	Output match.
μS4	next table	μ-stripline + via
Board FR4: $\epsilon_r=4.6, h=0.5 \text{ mm}, t=35 \mu\text{m}$		
* 0603 Philips		
** 0805 Philips		
Coils: 0805CS Coilcraft		

**μS4 Emitter inductance (μ-stripline + via):**

L1	2.0mm	μ-stripline $Z_0 \sim 48\Omega$ (PCB: $\epsilon_r \sim 4.6, H=0.5\text{mm}$ )
L2	1.0mm	
L3	1.0mm	
W1	0.5mm	Emitter inductance: μ-stripline
W2	1.0mm	
D1	0.4mm	via-hde

**Table 1: 900 MHz LNA with BFG410W, List of components.**

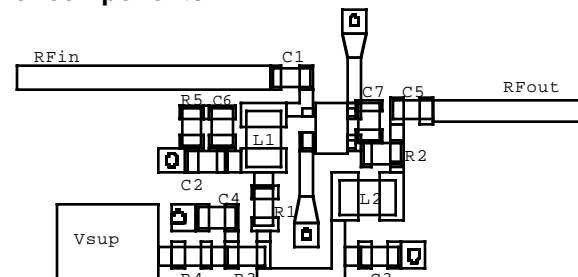

**Figure 7: PCB-layout 900 MHz LNA with BFG410W.**

### b) 2 GHz LNA with BFG410W

This paragraph describes a 2 GHz LNA with the BFG410W. The performance can be summarized as follows:

$$V_{ce}=2V, I_c=2mA, V_{SUP}\approx 3.3V$$

freq. = 2 GHz

$$|S_{21}|^2 = 14.3 \text{ dB}$$

$$|S_{12}|^2 = -30 \text{ dB}$$

NF = 1.7 dB

$$VSWR_i = 1 : 2.1$$

$$VSWR_o = 1 : 2.1$$

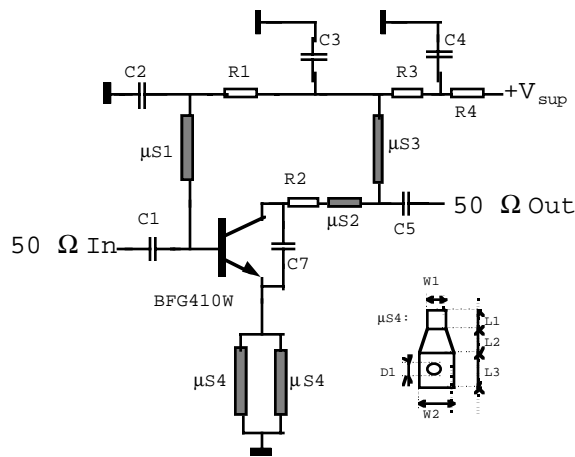


Figure 8: Schematic diagram 2 GHz LNA with BFG410W.

Input and output matching is realized with a microstrip-C combination. Additional emitter inductance on both emitter leads is used to improve the matching to 50 Ω. All resistors and capacitors are 0603 Philips SMD components. Coils are Coilcraft 0805. Board material is FR4.

Please note that this amplifier is not optimized for noise and IP3 (extra bypassing is missing)

R1	47 KΩ	Bias.
R2	10 Ω	Better RF-stability (K>1).
R3	22 Ω	RF-block.
R4	560 Ω	Cancelling H <sub>FE</sub> -spread.
C1	1 pF	Input match.
C2	5.6 pF	2GHz short.
C3	5.6 pF	2GHz short.
C4	1 nF	RF-short
C5	3.3 pF	Output match.
C7	0.47 pF	Better RF-stability (K>1).
μs1	W=0.25mm	μ-stripline Z <sub>0</sub> ~95Ω
μs2	W=0.25mm	μ-stripline Z <sub>0</sub> ~95Ω
μs3	W=0.25mm	μ-stripline Z <sub>0</sub> ~95Ω
μs4	(next table)	μ-stripline + via
BoardFR4: ε <sub>r</sub> =4.6, h=0.5 mm, t=35 μm		
All resistors and capacitors 0603 Philips		

μS4 Emitter inductance (μ-stripline + via):

L1	2.0mm	μ-stripline Z <sub>0</sub> ~48Ω
L2	1.0mm	
L3	1.0mm	
W1	0.5mm	Emitter inductance: μ-stripline
W2	1.0mm	
D1	0.4mm	via-hde

Table 2: 2 GHz LNA with BFG410W, List of components.

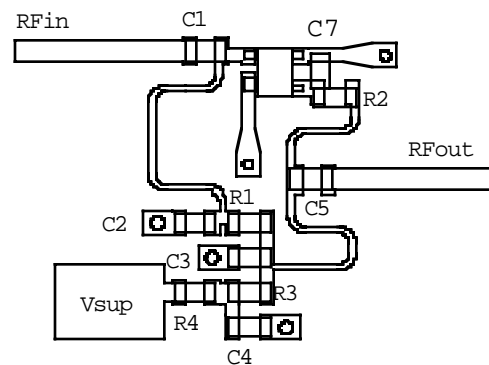


Figure 9: PCB-layout 2 GHz LNA with BFG410W.

### c) 900 MHz LNA with BFG425W

Comp	Value:	Comment:
------	--------	----------

This section describes a 900 MHz LNA with the BFG425W. The performance can be summarized as follows:

$V_{ce}=2V, I_c=10mA, V_{SUP}\approx 3.7V$   
 freq. = 900MHz  
 $|S_{21}|^2 = 17.3 \text{ dB}$   
 NF = 1.7 dB  
 $VSWR_i = 1 : 2.5$   
 $VSWR_o = 1 : 1.8$   
 $IP3_{in} = +3 \text{ dBm} (\Delta f=200 \text{ kHz})$

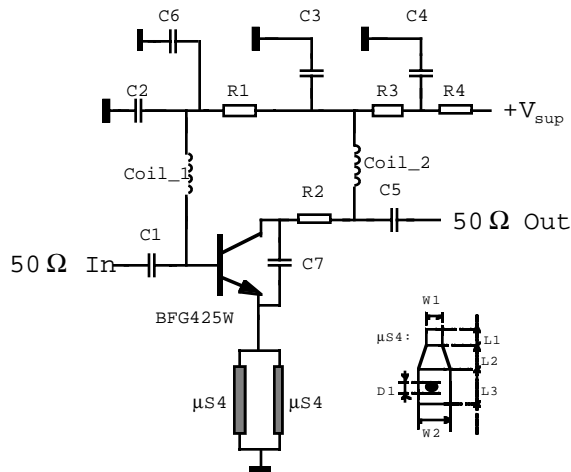


Figure 10: Schematic diagram 900 MHz LNA with BFG425W.

Comp	Value	Purpose, comment
R1*	8.2 kΩ	Bias (coll.-base)
R2*	10 Ω	better S22 and stability
R3*	22 Ω	RF blocking
R4*	150 Ω	cancelling hFE spread
C1*	8.2 pF	Input match (input to base)
C2*	27 pF	900 MHz short (L1 to ground)
C3*	27 pF	900 MHz short (L2 to ground)
C4**	100 nF	RF decoupling collector bias
C5*	22 pF	Output match
C6**	100 nF	To improve IP3
C7*	3.3 pF	Output match, stability
Coil_1	22 nH	Input match (base-bias)
Coil_2	12 nH	Output match (collector-bias)
μS4	next table	μ-stripline Emitter-inductance

Board FR4:  $\epsilon_r=4.6, h=0.5 \text{ mm}, t=35\mu\text{m}$   
 \* = 0603 Philips  
 \*\* = 0805 Philips  
 Coils: 0805CS Coilcraft

μS4 Emitter inductance of μ-stripline and via-hole

Name	Dimension	Description
L1	2.5mm	length μ-stripline; $Z_0 \sim 48\Omega$
L2	1.0mm	length interconnect stripline and via-hole area
L3	1.0mm	length via-hole area

W1	0.5mm	width μ-stripline
W2	1.0mm	width via-hole area
D1	0.4mm	diameter of via-hole

Table 3: 900 MHz LNA with BFG425W, List of components.

Input and output matching is realized with a microstrip-C combination. Additional emitter inductance on both emitter leads is used to improve the matching to 50 Ω. All resistors and capacitors are 0603 or 0805 Philips SMD components. Coils are Coilcraft 0805. Board material is FR4.

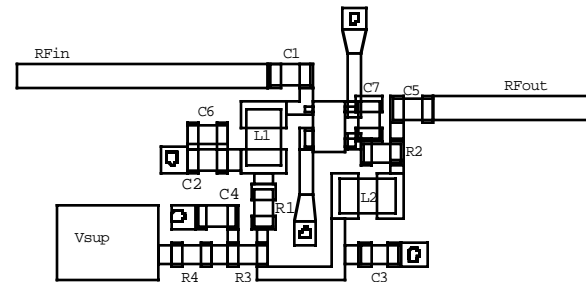


Figure 11: PCB-layout 900 MHz LNA with BFG425W.

### d) 2 GHz LNA with BFG425W

This section describes a 2 GHz LNA with the BFG425W. The performance, for different collector currents can be summarized as follows:

$I_C$ [mA]	$ S_{21} ^2$ [dB]	IP3_A [dBm]	IP3_B [dBm]	NF [dB]
$V_{CE} \sim 2.5V$	2GHz	input	input	2 GHz
2	14.4	-10.9	-2.3	1.5
3	15.9	-3.4	-0.4	1.7
5	16.3	-0.9	1.8	1.8
6	16.6	1.0	2.6	1.9
8	16.9	3.9	5.6	2.1
10	17.1	6.5	6.7	2.3

Table 4: Performance summary 2 GHz LNA with BFG425W

Input and Output VSWR is in all cases better than 1 : 2. IP3\_A is the third order intercept *without* R5 and C6. IP3\_B is the third order intercept *with* R5 and C6. It can be noticed that the IP3 improvement becomes less effective when the collector current increases.

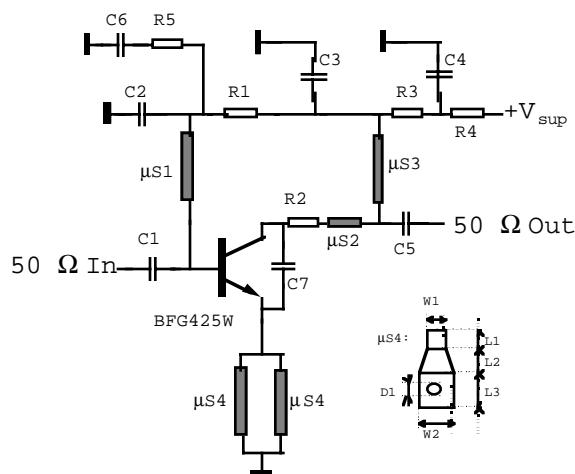


Figure 12: Schematic diagram 2 GHz LNA with BFG425W.

Comp	Value:	Comment:
R1*	15 K $\Omega$	Bias.
R2*	0 $\Omega$	Omitted.
R3*	22 $\Omega$	RF-block.
R4*	82 $\Omega$	Cancelling H <sub>FE</sub> -spread.
R5**	100 $\Omega$	To improve IP3-performance
C1*	4.7 pF	Input match.
C2*	5.6 pF	2GHz short.
C3*	5.6 pF	2GHz short.
C4*	1 nF	RF-short
C5*	2.7 pF	Output match.
C6**	100 nH	To improve IP3-performance
$\mu$ s1	8.9 x 0.25mm	$\mu$ -stripline $Z_0 \sim 95\Omega$
$\mu$ s2	3.9 x 0.25mm	$\mu$ -stripline $Z_0 \sim 95\Omega$
$\mu$ s3	6.6 x 0.25mm	$\mu$ -stripline $Z_0 \sim 95\Omega$
$\mu$ s4	(next table)	$\mu$ -stripline + via

BoardFR4:  $\epsilon_r=4.6, h=0.5$  mm,  $t=35$   $\mu$ m  
 \* 0603 Philips  
 \*\* 0805 Philips

$\mu$ S4 Emitter induction ( $\mu$ -stripline + via):

L1	1.0mm	$\mu$ -stripline $Z_0 \sim 48\Omega$
L2	1.0mm	
L3	1.0mm	
W1	0.5mm	Emitter inductance $\mu$ -stripline
W2	1.0mm	
D1	0.4mm	via-hde

Table 5: 2 GHz LNA with BFG425W, List of components.

Input and output matching is realized with a microstrip-C combination. Additional emitter inductance on both emitter leads is used to improve the matching to 50  $\Omega$ . All resistors and capacitors are 0603 or 0805 Philips SMD components. Coils are Coilcraft 0805. Board material is FR4.

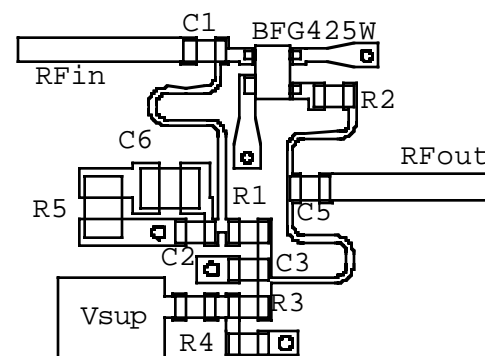


Figure 13: PCB-layout 2 GHz LNA with BFG425W.

### CONCLUSION

High performance small size LNAs, with a low supply voltage and current can be made with the new Philips BFG400W series double polysilicon transistors. IP3 can be optimized with extra components, and/or by increasing  $I_C$ . Increasing voltage also improves the IP3 point.

The LNAs presented in this brief application note are not the most optimized designs, nor are shown all possible circuit configurations by any means . They only show some possible LNA-designs with the BFG400W series double polysilicon transistors.



SUNSTAR 商斯达实业集团是集研发、生产、工程、销售、代理经销、技术咨询、信息服务等为一体的高科技企业，是专业高科技电子产品生产厂家，是具有 10 多年历史的专业电子元器件供应商，是中国最早和最大的仓储式连锁规模经营大型综合电子零部件代理分销商之一，是一家专业代理和分销世界各大品牌 IC 芯片和电子元器件的连锁经营综合性国际公司，专业经营进口、国产名厂名牌电子元件，型号、种类齐全。在香港、北京、深圳、上海、西安、成都等全国主要电子市场设有直属分公司和产品展示展销窗口门市部专卖店及代理分销商，已在全国范围内建成强大统一的供货和代理分销网络。我们专业代理经销、开发生产电子元器件、集成电路、传感器、微波光电元器件、工控机/DOC/DOM 电子盘、专用电路、单片机开发、MCU/DSP/ARM/FPGA 软件硬件、二极管、三极管、模块等，是您可靠的一站式现货配套供应商、方案提供商、部件功能模块开发配套商。商斯达实业公司拥有庞大的资料库，有数位毕业于著名高校——有中国电子工业摇篮之称的西安电子科技大学（西军电）并长期从事国防尖端科技研究的高级工程师为您精挑细选、量身订做各种高科技电子元器件，并解决各种技术问题。

微波光电部专业代理经销高频、微波、光纤、光电元器件、组件、部件、模块、整机；电磁兼容元器件、材料、设备；微波 CAD、EDA 软件、开发测试仿真工具；微波、光纤仪器仪表。欢迎国外高科技微波、光纤厂商将优秀产品介绍到中国、共同开拓市场。长期大量现货专业批发高频、微波、卫星、光纤、电视、CATV 器件：晶振、VCO、连接器、PIN 开关、变容二极管、开关二极管、低噪晶体管、功率电阻及电容、放大器、功率管、MMIC、混频器、耦合器、功分器、振荡器、合成器、衰减器、滤波器、隔离器、环行器、移相器、调制解调器；光电子元件和组件：红外发射管、红外接收管、光电开关、光敏管、发光二极管和发光二极管组件、半导体激光二极管和激光器组件、光电探测器和光接收组件、光发射接收模块、光纤激光器和光放大器、光调制器、光开关、DWDM 用光发射和接收器件、用户接入系统光收发器件与模块、光纤连接器、光纤跳线/尾纤、光衰减器、光纤适配器、光隔离器、光耦合器、光环行器、光复用器/转换器；无线收发芯片和模组、蓝牙芯片和模组。

更多产品请看本公司产品专用销售网站：

商斯达中国传感器科技信息网：<http://www.sensor-ic.com/>

商斯达工控安防网：<http://www.pc-ps.net/>

商斯达电子元器件网：<http://www.sunstare.com/>

商斯达微波光电产品网：[HTTP://www.rfoe.net/](http://www.rfoe.net/)

商斯达消费电子产品网：<http://www.icasic.com/>

商斯达实业科技产品网：<http://www.sunstars.cn/> 微波元器件销售热线：

地址：深圳市福田区福华路福庆街鸿图大厦 1602 室

电话：0755-82884100 83397033 83396822 83398585

传真：0755-83376182 (0) 13823648918 MSN: SUNS8888@hotmail.com

邮编：518033 E-mail:[szss20@163.com](mailto:szss20@163.com) QQ: 195847376

深圳赛格展销部：深圳华强北路赛格电子市场 2583 号 电话：0755-83665529 25059422

技术支持：0755-83394033 13501568376

欢迎索取免费详细资料、设计指南和光盘；产品凡多，未能尽录，欢迎来电查询。

北京分公司：北京海淀区知春路 132 号中发电子大厦 3097 号

TEL: 010-81159046 82615020 13501189838 FAX: 010-62543996

上海分公司：上海市北京东路 668 号上海赛格电子市场 D125 号

TEL: 021-28311762 56703037 13701955389 FAX: 021-56703037

西安分公司：西安高新开发区 20 所(中国电子科技集团导航技术研究所)

西安劳动南路 88 号电子商城二楼 D23 号

TEL: 029-81022619 13072977981 FAX:029-88789382