

APPLICATION NOTE

The BLF246 as an H.F.-S.S.B. amplifier

NCO8801

The BLF246 as an H.F.-S.S.B. amplifier

Application Note
NCO8801

CONTENTS

- 1 SUMMARY
- 2 INTRODUCTION
- 3 NARROW BAND TEST AT 28 MHz
- 4 WIDEBAND OPERATION
- 5 ACKNOWLEDGEMENT

1 SUMMARY

This report gives information on the BLF246 as a linear amplifier at 28 MHz for S.S.B. signals.

Typically the device produces an output power of 80 W P.E.P. at an I.M. distortion of -34 dB.
At a supply voltage of 28 V the power gain is 20 dB and the 2-tone efficiency 40%.

For the design of wideband amplifiers in the range of 1.5 – 30 MHz additional information is presented showing that the power gain drops to appr. 19 dB with a variation of ± 0.4 dB.

2 INTRODUCTION

The BLF246 is an R.F. power MOS-transistor in SOT121 package specified at a frequency of 108 MHz and a supply voltage of 28 V for an output power of 80 W C.W.

During the development period this device has also been tested in a class-AB amplifier at 28 MHz to investigate its behaviour as a linear amplifier for possible application in the H.F. band (1.5 – 30 MHz) with S.S.B. modulation.
In that case the 3rd and 5th order intermodulation products are of special interest.

3 NARROW BAND TEST AT 28 MHz

The R.F. circuit used for this purpose is depicted in Fig.1. The optimum drain quiescent current for linear operation of this device in class-AB is 0.6 A.

This is achieved with a V_{gs} which is appr. 0.48 V higher than the specified $V_{gs(th)}$.

The output circuit has been aligned with a dummy load consisting of the parallel connection of a 3.5Ω resistor and a 400 pF capacitor. This results in a load seen by the transistor of appr. 3.3Ω with a negligible reactive part.

The capacitors C9 and C10 are used to reduce the second harmonic voltage at the drain.

In a wideband amplifier this is not necessary because the same effect is obtained by other means like a centre-tapped drain choke in a push-pull amplifier.

The input circuit is aligned for minimum reflection at 50% of the maximum output power.

The gate-source damping resistors R1 and R2 are needed for 2 reasons:

1. Stability i.e. to prevent oscillation when the output circuit is detuned
2. Low intermodulation distortion. In general it can be said that I.M. distortion is improved by lowering the value of these resistors. Of course they will influence the power gain of the amplifier.

The average performance of the BLF246 in this amplifier is shown in Figs 2, 3, 4 and 5.

At an output power of 80 W P.E.P. the average performance is:

$$G_p = 20 \text{ dB}$$

$$\text{Eff.} = 40\% \text{ (2-tone)}$$

$$d_3 = -34 \text{ dB}$$

$$d_5 = -42 \text{ dB.}$$

The distortion products have been measured with respect to one tone.

It must be mentioned that the information given here is typical i.e. it is not guaranteed by measurements on individual transistors.

4 WIDEBAND OPERATION

For operation in the H.F. range (1.5 – 30 MHz) it will be necessary to reduce the value of R_{gs} from 18Ω as used in the narrow band amplifier down to 12Ω to obtain a more constant power gain over the band and to achieve a smaller variation in the input impedance to allow an easier matching to a driver stage or a 50Ω source.

The BLF246 as an H.F.-S.S.B. amplifier

Application Note
NCO8801

Table 2 shows the results of a computer calculation on this basis. It appears that the power gain is reduced by appr. 1 dB while the gain variation is then ± 0.4 dB.

The optimum load impedance is still appr. 3.3Ω with a negligible reactive part.

It must be mentioned that the figures given for power gain and input impedance include already the effects of an R_{GS} of 12Ω .

As mentioned earlier the lowering of R_{GS} has a positive effect on the intermodulation behaviour.

For the design of a suitable wideband input matching network one is referred to application report nr. NCO8703.

5 ACKNOWLEDGEMENT

The 28 MHz amplifier described in this report was designed and constructed by Mr. G. Lukkassen of our laboratory. He also made the various measurements.

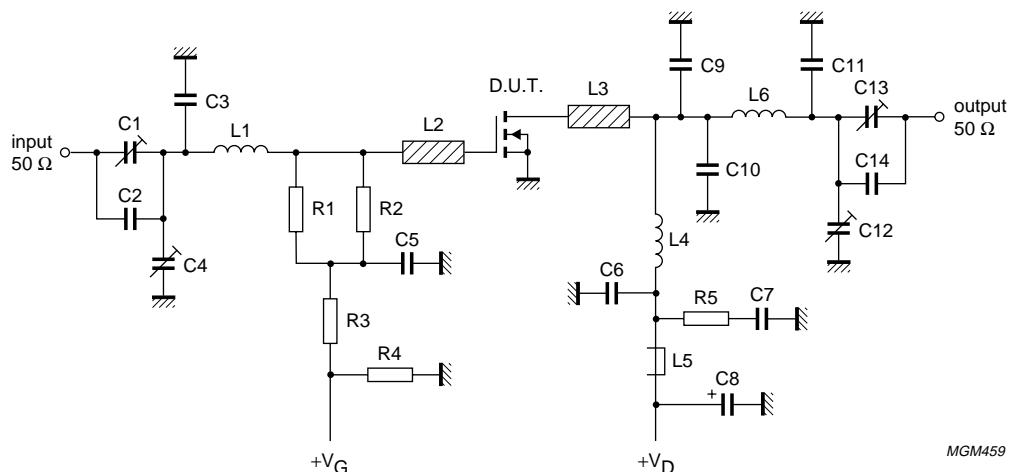


Fig.1 BLF246 Testcircuit at 28 MHz.

The BLF246 as an H.F.-S.S.B. amplifier


Application Note
NCO8801**Table 1** PC-board: double Cu-clad, 1.6 mm PTFE fibre-glas dielectric ($\epsilon_r = 2.2$)

C1 = C4	6 to 80 pF	film dielectric trimmer (cat.nr. 2222 809 07013)
C2	62 pF	multilayer ceramic chip capacitor; note 1
C3	150 pF	multilayer ceramic chip capacitor; note 1
C5 = C6	100 nF	multilayer ceramic chip capacitor (cat.nr. 2222 852 47104)
C7	3 × 100 nF	multilayer ceramic chip capacitor (cat.nr. 2222 852 47104)
C8	2.2 µF	electrolytic capacitor
C9 = C10 = C14	75 pF	multilayer ceramic chip capacitor; note 1
C11	100 pF	multilayer ceramic chip capacitor; note 1
C12 = C13	7 to 100 pF	film dielectric trimmer (cat.nr. 2222 809 07015)
L1	184 nH	6 turns enamelled Cu-wire (0.7 mm), int.dia: 6 mm
L2 = L3	41.1 Ω	stripline (10 × 6 mm)
L4	278 nH	7 turns enamelled Cu-wire (1.5 mm), int.dia: 8 mm
L5		Ferroxcube h.f. coke, grade 3B (cat.nr. 4312 020 36642)
L6	131 nH	4 turns enamelled Cu-wire (1.5 mm), int.dia: 8 mm
R1 = R2	34.8 Ω	metal film resistor (cat.nr. 2322 153 53489)
R3	1 kΩ	metal film resistor (cat.nr. 2322 151 71002)
R4	1 MΩ	metal film resistor (cat.nr. 2322 151 71005)
R5	10 Ω	metal film resistor (cat.nr. 2322 153 51009)

Note


1. American Technical Ceramics type 100B or capacitor of same quality.

The BLF246 as an H.F.-S.S.B. amplifier

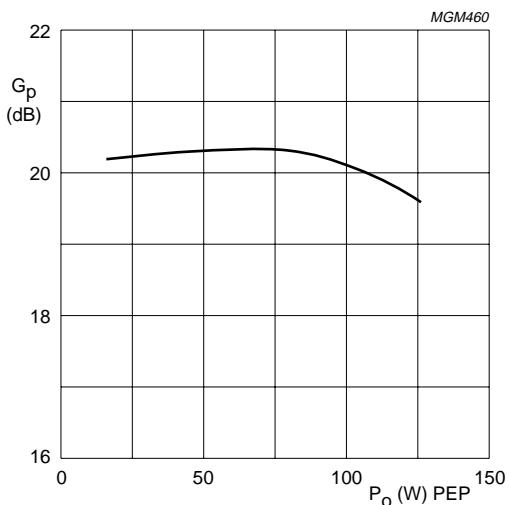Application Note
NCO8801**Conditions**

$f = 28 \text{ MHz}$ $I_{dQ} = 0.6 \text{ A}$ $T_h = 25^\circ\text{C}$
 $V_{ds} = 28 \text{ V}$ $R_{gs} = 18 \Omega$ $R_{th \text{ mb-h}} = 0.2 \text{ K/W}$


Fig.2 Power gain versus output power.

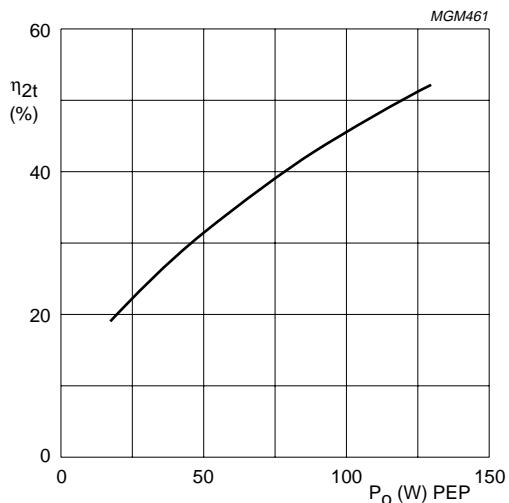**Conditions**

$f = 28 \text{ MHz}$ $I_{dQ} = 0.6 \text{ A}$ $T_h = 25^\circ\text{C}$
 $V_{ds} = 28 \text{ V}$ $R_{gs} = 18 \Omega$ $R_{th \text{ mb-h}} = 0.2 \text{ K/W}$


Fig.3 2-tone efficiency versus output power.

The BLF246 as an H.F.-S.S.B. amplifier

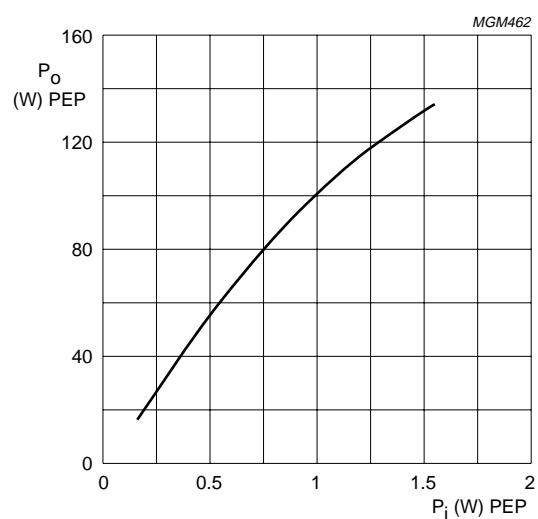Application Note
NCO8801**Conditions**

$f = 28 \text{ MHz}$ $I_{dQ} = 0.6 \text{ A}$ $\text{Th} = 25^\circ\text{C}$
 $V_{ds} = 28 \text{ V}$ $R_{gs} = 18 \Omega$ $R_{th mb-h} = 0.2 \text{ K/W}$

Fig.4 Output power versus drive power.

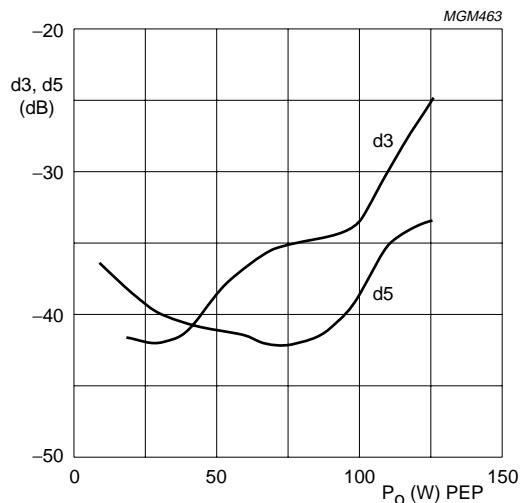**Conditions**

$f = 28 \text{ MHz}$ $I_{dQ} = 0.6 \text{ A}$ $\text{Th} = 25^\circ\text{C}$
 $V_{ds} = 28 \text{ V}$ $R_{gs} = 18 \Omega$ $R_{th mb-h} = 0.2 \text{ K/W}$

Fig.5 Intermodulation distortion versus output power.

The BLF246 as an H.F.-S.S.B. amplifier

Application Note
NCO8801**Table 2** Power gain, input and load impedance versus frequency; $I_{dQ} = 0.6 \text{ A}$; $R_{GS} = 12 \Omega$

BLF246	$V_{DS} = 28 \text{ V}$	$P_O = 80 \text{ W P.E.P.}$	Class-AB
f	G	Inp.Imp.	Load Imp.
MHz	dB	Ω	Ω
1.5	19.57	$11.97 - j0.51$	$3.34 + j0.01$
5.0	19.54	$11.71 - j1.67$	$3.34 + j0.02$
10.0	19.47	$10.92 - j3.06$	$3.33 + j0.04$
15.0	19.35	$9.86 - j4.03$	$3.32 + j0.07$
20.0	19.20	$8.75 - j4.59$	$3.31 + j0.09$
25.0	19.00	$7.72 - j4.84$	$3.30 + j0.11$
30.0	18.77	$6.83 - j4.86$	$3.28 + j0.13$

Philips Semiconductors – a worldwide company

Argentina: see South America

Australia: 34 Waterloo Road, NORTH RYDE, NSW 2113,
Tel. +61 2 9805 4455, Fax. +61 2 9805 4466

Austria: Computerstr. 6, A-1101 WIEN, P.O. Box 213, Tel. +43 1 60 1010,
Fax. +43 1 60 101 1210

Belarus: Hotel Minsk Business Center, Bld. 3, r. 1211, Volodarski Str. 6,
220050 MINSK, Tel. +375 172 200 733, Fax. +375 172 200 773

Belgium: see The Netherlands

Brazil: see South America

Bulgaria: Philips Bulgaria Ltd., Energoproject, 15th floor,
51 James Bourchier Blvd., 1407 SOFIA,
Tel. +359 2 689 211, Fax. +359 2 689 102

Canada: PHILIPS SEMICONDUCTORS/COMPONENTS,
Tel. +1 800 234 7381

China/Hong Kong: 501 Hong Kong Industrial Technology Centre,
72 Tat Chee Avenue, Kowloon Tong, HONG KONG,
Tel. +852 2319 7888, Fax. +852 2319 7700

Colombia: see South America

Czech Republic: see Austria

Denmark: Prags Boulevard 80, PB 1919, DK-2300 COPENHAGEN S,
Tel. +45 32 88 2636, Fax. +45 31 57 0044

Finland: Sinikalliontie 3, FIN-02630 ESPOO,
Tel. +358 9 615800, Fax. +358 9 61580920

France: 51 Rue Carnot, BP317, 92156 SURESNES Cedex,
Tel. +33 1 40 99 6161, Fax. +33 1 40 99 6427

Germany: Hammerbrookstraße 69, D-20097 HAMBURG,
Tel. +49 40 23 53 60, Fax. +49 40 23 536 300

Greece: No. 15, 25th March Street, GR 17778 TAVROS/ATHENS,
Tel. +30 1 4894 339/239, Fax. +30 1 4814 240

Hungary: see Austria

India: Philips INDIA Ltd, Band Box Building, 2nd floor,
254-D, Dr. Annie Besant Road, Worli, MUMBAI 400 025,
Tel. +91 22 493 8541, Fax. +91 22 493 0966

Indonesia: see Singapore

Ireland: Newstead, Clonskeagh, DUBLIN 14,
Tel. +353 1 7640 000, Fax. +353 1 7640 200

Israel: RAPAC Electronics, 7 Kehilat Saloniki St, PO Box 18053,
TEL AVIV 61180, Tel. +972 3 645 0444, Fax. +972 3 649 1007

Italy: PHILIPS SEMICONDUCTORS, Piazza IV Novembre 3,
20124 MILANO, Tel. +39 2 6752 2531, Fax. +39 2 6752 2557

Japan: Philips Bldg 13-37, Kohnan 2-chome, Minato-ku, TOKYO 108,
Tel. +81 3 3740 5130, Fax. +81 3 3740 5077

Korea: Philips House, 260-199 Itaewon-dong, Yongsan-ku, SEOUL,
Tel. +82 2 709 1412, Fax. +82 2 709 1415

Malaysia: No. 76 Jalan Universiti, 46200 PETALING JAYA, SELANGOR,
Tel. +60 3 750 5214, Fax. +60 3 757 4880

Mexico: 5900 Gateway East, Suite 200, EL PASO, TEXAS 79905,
Tel. +9-5 800 234 7381

Middle East: see Italy

Netherlands: Postbus 90050, 5600 PB EINDHOVEN, Bldg. VB,
Tel. +31 40 27 82785, Fax. +31 40 27 88399

New Zealand: 2 Wagener Place, C.P.O. Box 1041, AUCKLAND,
Tel. +64 9 849 4160, Fax. +64 9 849 7811

Norway: Box 1, Manglerud 0612, OSLO,
Tel. +47 22 74 8000, Fax. +47 22 74 8341

Philippines: Philips Semiconductors Philippines Inc.,
106 Valero St. Salcedo Village, P.O. Box 2108 MCC, MAKATI,
Metro MANILA, Tel. +63 2 816 6380, Fax. +63 2 817 3474

Poland: Ul. Lukiska 10, PL 04-123 WARSZAWA,
Tel. +48 22 612 2831, Fax. +48 22 612 2327

Portugal: see Spain

Romania: see Italy

Russia: Philips Russia, Ul. Usatcheva 35A, 119048 MOSCOW,
Tel. +7 095 755 6918, Fax. +7 095 755 6919

Singapore: Lorong 1, Toa Payoh, SINGAPORE 1231,
Tel. +65 350 2538, Fax. +65 251 6500

Slovakia: see Austria

Slovenia: see Italy

South Africa: S.A. PHILIPS Pty Ltd., 195-215 Main Road Martindale,
2092 JOHANNESBURG, P.O. Box 7430 Johannesburg 2000,
Tel. +27 11 470 5911, Fax. +27 11 470 5494

South America: Al. Vicente Pinzon, 173, 6th floor,
04547-130 SÃO PAULO, SP, Brazil,
Tel. +55 11 821 2333, Fax. +55 11 821 2382

Spain: Balmes 22, 08007 BARCELONA,
Tel. +34 3 301 6312, Fax. +34 3 301 4107

Sweden: Kottbygatan 7, Akalla, S-16485 STOCKHOLM,
Tel. +46 8 632 2000, Fax. +46 8 632 2745

Switzerland: Allmendstrasse 140, CH-8027 ZÜRICH,
Tel. +41 1 488 2686, Fax. +41 1 488 3263

Taiwan: Philips Semiconductors, 6F, No. 96, Chien Kuo N. Rd., Sec. 1,
TAIPEI, Taiwan Tel. +886 2 2134 2865, Fax. +886 2 2134 2874

Thailand: PHILIPS ELECTRONICS (THAILAND) Ltd.,
209/2 Sanpavut-Bangna Road Prakanong, BANGKOK 10260,
Tel. +66 2 745 4090, Fax. +66 2 398 0793

Turkey: Talatpasa Cad. No. 5, 80640 GÜLTEPE/İSTANBUL,
Tel. +90 212 279 2770, Fax. +90 212 282 6707

Ukraine: PHILIPS UKRAINE, 4 Patrice Lumumba str., Building B, Floor 7,
252042 KIEV, Tel. +380 44 264 2776, Fax. +380 44 268 0461

United Kingdom: Philips Semiconductors Ltd., 276 Bath Road, Hayes,
MIDDLESEX UB3 5BX, Tel. +44 181 730 5000, Fax. +44 181 754 8421

United States: 811 East Arques Avenue, SUNNYVALE, CA 94088-3409,
Tel. +1 800 234 7381

Uruguay: see South America

Vietnam: see Singapore

Yugoslavia: PHILIPS, Trg N. Pasica 5/v, 11000 BEOGRAD,
Tel. +381 11 625 344, Fax. +381 11 635 777

Internet: <http://www.semiconductors.philips.com>

For all other countries apply to: Philips Semiconductors,
International Marketing & Sales Communications, Building BE-p, P.O. Box 218,
5600 MD EINDHOVEN, The Netherlands, Fax. +31 40 27 24825

© Philips Electronics N.V. 1998

SCA57

All rights are reserved. Reproduction in whole or in part is prohibited without the prior written consent of the copyright owner.

The information presented in this document does not form part of any quotation or contract, is believed to be accurate and reliable and may be changed without notice. No liability will be accepted by the publisher for any consequence of its use. Publication thereof does not convey nor imply any license under patent- or other industrial or intellectual property rights.

Printed in The Netherlands

Date of release: 1998 Mar 23

Let's make things better.

Philips
Semiconductors



PHILIPS

SUNSTAR 商斯达实业集团是集研发、生产、工程、销售、代理经销、技术咨询、信息服务等为一体的高科技企业，是专业高科技电子产品生产厂家，是具有 10 多年历史的专业电子元器件供应商，是中国最早和最大的仓储式连锁规模经营大型综合电子零部件代理分销商之一，是一家专业代理和分销世界各大品牌 IC 芯片和电子元器件的连锁经营综合性国际公司，专业经营进口、国产名厂名牌电子元件，型号、种类齐全。在香港、北京、深圳、上海、西安、成都等全国主要电子市场设有直属分公司和产品展示展销窗口门市部专卖店及代理分销商，已在全国范围内建成强大统一的供货和代理分销网络。我们专业代理经销、开发生产电子元器件、集成电路、传感器、微波光电元器件、工控机/DOC/DOM 电子盘、专用电路、单片机开发、MCU/DSP/ARM/FPGA 软件硬件、二极管、三极管、模块等，是您可靠的一站式现货配套供应商、方案提供商、部件功能模块开发配套商。商斯达实业公司拥有庞大的资料库，有数位毕业于著名高校——有中国电子工业摇篮之称的西安电子科技大学（西军电）并长期从事国防尖端科技研究的高级工程师为您精挑细选、量身订做各种高科技电子元器件，并解决各种技术问题。

微波光电部专业代理经销高频、微波、光纤、光电元器件、组件、部件、模块、整机；电磁兼容元器件、材料、设备；微波 CAD、EDA 软件、开发测试仿真工具；微波、光纤仪器仪表。欢迎国外高科技微波、光纤厂商将优秀产品介绍到中国、共同开拓市场。长期大量现货专业批发高频、微波、卫星、光纤、电视、CATV 器件：晶振、VCO、连接器、PIN 开关、变容二极管、开关二极管、低噪晶体管、功率电阻及电容、放大器、功率管、MMIC、混频器、耦合器、功分器、振荡器、合成器、衰减器、滤波器、隔离器、环行器、移相器、调制解调器；光电子元器件和组件：红外发射管、红外接收管、光电开关、光敏管、发光二极管和发光二极管组件、半导体激光二极管和激光器组件、光电探测器和光接收组件、光发射接收模块、光纤激光器和光放大器、光调制器、光开关、DWDM 用光发射和接收器件、用户接入系统光光收发器件与模块、光纤连接器、光纤跳线/尾纤、光衰减器、光纤适配器、光隔离器、光耦合器、光环行器、光复用器/转换器；无线收发芯片和模组、蓝牙芯片和模组。

更多产品请看本公司产品专用销售网站：

商斯达中国传感器科技信息网：<http://www.sensor-ic.com/>

商斯达工控安防网：<http://www.pc-ps.net/>

商斯达电子元器件网：<http://www.sunstare.com/>

商斯达微波光电产品网：<HTTP://www.rfoe.net/>

商斯达消费电子产品网：<http://www.icasic.com/>

商斯达实业科技产品网：<http://www.sunstars.cn/> 微波元器件销售热线：

地址：深圳市福田区福华路福庆街鸿图大厦 1602 室

电话：0755-82884100 83397033 83396822 83398585

传真：0755-83376182 (0) 13823648918 MSN：SUNS8888@hotmail.com

邮编：518033 E-mail：szss20@163.com QQ：195847376

深圳赛格展销部：深圳华强北路赛格电子市场 2583 号 电话：0755-83665529 25059422

技术支持：0755-83394033 13501568376

欢迎索取免费详细资料、设计指南和光盘；产品凡多，未能尽录，欢迎来电查询。

北京分公司：北京海淀区知春路 132 号中发电子大厦 3097 号

TEL：010-81159046 82615020 13501189838 FAX：010-62543996

上海分公司：上海市北京东路 668 号上海赛格电子市场 D125 号

TEL：021-28311762 56703037 13701955389 FAX：021-56703037

西安分公司：西安高新区 20 所(中国电子科技集团导航技术研究所)

西安劳动南路 88 号电子商城二楼 D23 号

TEL：029-81022619 13072977981 FAX:029-88789382